


THE No 1 UK MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

# **EPE** EVERYDAY PRACTICAL ELECTRONICS

www.epemag.com
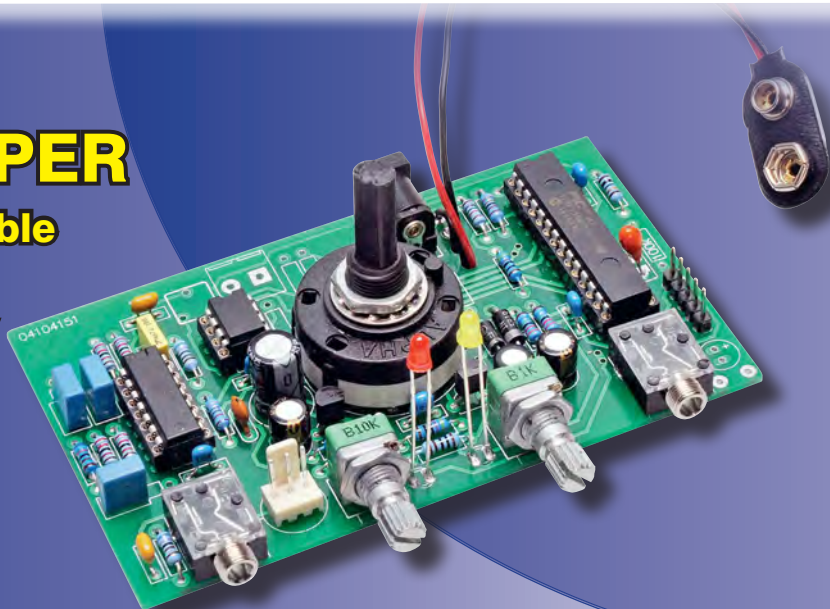
## **INFRASOUND SNOOPER**

- Convert infrasonic sound to audible
- 'Hear' sound from 1-20Hz
- Assess amplitude and frequency




## **AUDIO SIGNAL INJECTOR AND TRACER**

Perfect for troubleshooting AM radio and audio circuits

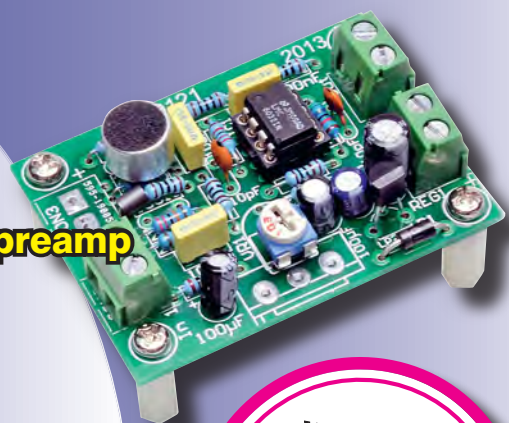
## **CHAMPION PREAMP**

Fantastic, general-purpose stereo or dual-channel preamp



## **TEACH-IN 2016 INTRODUCING THE ARDUINO**

Part 5: 1-Wire interface

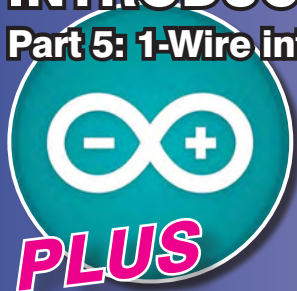

**INTERFACE, NET WORK, PIC n' MIX, COOL BEANS,  
CIRCUIT SURGERY, TECHNO TALK, AUDIO OUT &  
ELECTRONIC BUILDING BLOCKS**

WIN ONE  
OF THREE  
MICROCHIP  
PICKIT 3 Debug  
Express Kits

JUNE 2016 £4.40



# Increase Energy Efficiency and Lower System Cost

With Microchip's Off-Line LED Drivers with True DC Output Current



Microchip is driving innovation and efficiency in LED applications with its powerful HV9805 IC. If you need to simplify your LED lighting design while improving performance and lowering overall system cost, Microchip has a solution for you. This high power factor IC offers high-efficiency through two simple stages.



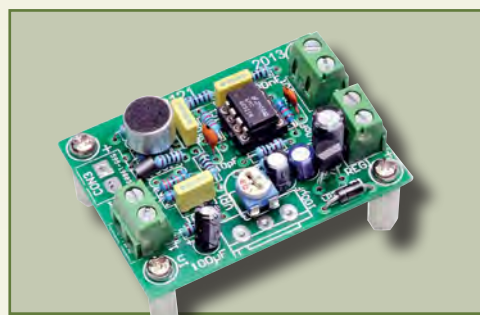
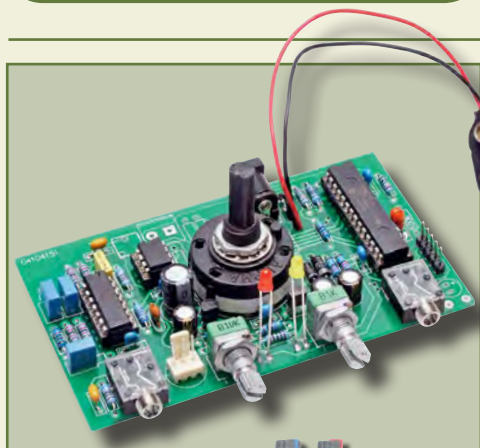
## Benefits

- ▶ True DC Light
- ▶ Excellent LED utilization
- ▶ Excellent driving efficiency
- ▶ System cost advantages



[www.microchip.com/lighting](http://www.microchip.com/lighting)





## Teach-In 2016

Exploring the  
Arduino  
Part 5: 1-Wire Interface



© Wimborne Publishing Ltd 2016. Copyright in all drawings, photographs and articles published in *EVERYDAY PRACTICAL ELECTRONICS* is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our July 2016 issue will be published on Thursday 2 June 2016, see page 80 for details.

Everyday Practical Electronics, June 2016

## Projects and Circuits

- THE BAD VIBES INFRASOUND SNOOPER** 12  
by Nicholas Vinen  
Listen to low frequency vibrations from wind turbines, elephants and crocodiles
- AUDIO SIGNAL INJECTOR AND TRACER** 22  
by John Clarke  
Ideal for troubleshooting AM radio and audio circuits
- CHAMPION PREAMP** 32  
by Leo Simpson  
Great performance from a tiny, low-cost, stereo/dual-channel circuit

## Series and Features

- TECHNO TALK** by Mark Nelson 11  
Proof at last!
- TEACH-IN 2016 – EXPLORING THE ARDUINO** 36  
by Mike and Richard Tooley  
Part 5: 1-Wire interface
- WYSIWYG – ALAN SUGAR AUTOBIOGRAPHY REVIEW** 44  
by Alan Winstanley
- NET WORK** by Alan Winstanley 48  
It's a cardboard world... VR headsets... Board's eye view... Set up and use  
Follow the arrows... 21st century radio
- INTERFACE** by Robert Penfold 51  
Raspberry Pi 3
- PIC n' MIX** by Mike O'Keeffe 55  
PICs and the PICkit 3: A beginner's guide – Part 1
- CIRCUIT SURGERY** by Ian Bell 58  
State machines – Part 1
- AUDIO OUT** by Jake Rothman 62  
Super-simple retro amp-speaker combo – Part 1
- MAX'S COOL BEANS** by Max The Magnificent 70  
Pull up a rock... Welcome to the pleasure dome... Lords of chaos!...  
Quest for fire... GLOW, SPARK and DARK modes
- ELECTRONIC BUILDING BLOCKS** by Julian Edgar 76  
USB Boost Charger

## Regulars and Services

- SUBSCRIBE TO EPE** and save money 4
- EDITORIAL** 7  
Now is the time to learn about PICs... Troubleshooting... *EPE's* got talent!
- NEWS** – Barry Fox highlights technology's leading edge 8  
Plus everyday news from the world of electronics
- MICROCHIP READER OFFER** 21  
*EPE* Exclusive – Win one of three Microchip PICkit 3 Debug Express Kits
- EPE BACK ISSUES** 46
- NEW – ELECTRONICS TEACH-IN 7 BOOK** 47
- EPE BACK ISSUES CD-ROM** 54
- DIRECT BOOK SERVICE** 67  
A wide range of technical books available by mail order, plus more CD-ROMs
- CD-ROMS FOR ELECTRONICS** 73  
A wide range of CD-ROMs for hobbyists, students and engineers
- EPE PCB SERVICE** 78  
PCBs for *EPE* projects
- ADVERTISERS INDEX** 79
- NEXT MONTH!** – Highlights of next month's *EPE* 80

## PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

### Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) £9.95  
18Vdc Power supply (661.121) £25.95  
Leads: Parallel (LDC136) £3.95 / Serial (LDC441) £3.95 / USB (LDC644) £2.95

### USB & Serial Port PIC Programmer



USB or Serial connection.  
Header cable for ICSP.  
Free Windows software.  
See website for PICs supported. ZIF Socket & USB lead extra. 16-18Vdc.

Kit Order Code: 3149EKT - £49.95

Assembled Order Code: AS3149E - £64.95

Assembled with ZIF socket Order Code: AS3149EZIF - £74.95

### USB PIC Programmer and Tutor Board

This tutorial project board is all you need to take your first steps into Microchip PIC programming using a PIC16F882 (included). Later you can use it for more advanced programming. It programs all the devices a Microchip PICKIT2<sup>®</sup> can! You can use the free Microchip tools for the PICKIT2<sup>™</sup> and the MPLAB<sup>®</sup> IDE environment.  
Order Code: EDU10 - £55.96



### ATMEL 89xxx Programmer

Uses serial port and any standard terminal comms program. 4 LED's display the status. ZIF sockets not included. 16Vdc.

Kit Order Code: 3123KT - £28.95

Assembled Order Code: AS3123 - £39.95



### Introduction to PIC Programming

Go from complete beginner to burning a PIC and writing code in no time! Includes 49 page step-by-step PDF Tutorial Manual + Programming Hardware (with LED test section) + Windows Software (Program, Read, Verify & Erase) + a rewritable PIC16F84A. 4 detailed examples provided for you to learn from. PC parallel port. 12Vdc.

Kit Order Code: 3081KT - £16.95

Assembled Order Code: AS3081 - £24.95



### PIC Programmer Board

Low cost PIC programmer board supporting a wide range of Microchip<sup>®</sup> PIC<sup>™</sup> microcontrollers. Serial port. Free Windows software.  
Kit Order Code: K8076 - £29.94



### PIC Programmer & Experimenter Board

PIC Programmer & Experimenter Board with test buttons and LED indicators to carry out educational experiments such as the supplied programming examples. Includes a 16F627 Flash Microcontroller that can be reprogrammed up to 1000 times. Software to compile and program your source code is included. Supply: 12-15Vdc.

Kit Order Code: K8048 - £23.94

Assembled Order Code: VM111 - £39.12



## Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. 12Vdc PSU for all units: Order Code 660.446UK £11.52

### USB Experiment Interface Board

5 digital input channels and 8 digital output channels plus two analogue inputs and two analogue outputs with 8 bit resolution.

Kit Order Code: K8055N - £25.19

Assembled Order Code: VM110N - £40.20



### 2-Channel High Current UHF RC Set

State-of-the-art high security. 2 channel. Momentary or latching relay output rated to switch up to 240Vac @ 10 Amps. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 3 indicator LEDs. Rx: PCB 88x60mm, supply 9-15Vdc.

Kit Order Code: 8157KT - £49.95

Assembled Order Code: AS8157 - £54.95



### Computer Temperature Data Logger



Serial port 4-channel temperature logger. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 45x45mm. Powered by PC. Includes one DS1820 sensor.

Kit Order Code: 3145KT - £19.95

Assembled Order Code: AS3145 - £26.95

Additional DS1820 Sensors - £4.95 each

### Remote Control Via GSM Mobile Phone

Place next to a mobile phone (not included). Allows toggle or auto-timer control of 3A mains rated output relay from any location



### 4-Ch DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, **Rings** to Answer, Auto Hang-up and Lockout. Includes plastic case. 130 x 110 x 30mm. Power: 12Vdc.

Kit Order Code: 3140KT - £79.95

Assembled Order Code: AS3140 - £94.95



### 8-Ch Serial Port Isolated I/O Relay Module

Computer controlled 8 channel relay board. 5A mains rated relay outputs and 4 opto-isolated digital inputs (for monitoring switch states, etc). Useful in a variety of control and sensing applications. Programmed via serial port (use our new Windows interface, terminal emulator or batch files). Serial cable can be up to 35m long. Includes plastic case 130x100x30mm. Power: 12Vdc/500mA.

Kit Order Code: 3108KT - £74.95

Assembled Order Code: AS3108 - £89.95



### Infrared RC 12-Channel Relay Board



Control 12 onboard relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112 x 122mm. Supply: 12Vdc/0.5A

Kit Order Code: 3142KT - £64.95

Assembled Order Code: AS3142 - £74.95

### Audio DTMF Decoder and Display



Detect DTMF tones from tape recorders, receivers, two-way radios, etc using the built-in mic or direct from the phone line. Characters are displayed on a

16 character display as they are received and up to 32 numbers can be displayed by scrolling the display. All data written to the LCD is also sent to a serial output for connection to a computer. Supply: 9-12V DC (Order Code PSU375). Main PCB: 55x95mm.

Kit Order Code: 3153KT - £37.95

Assembled Order Code: AS3153 - £49.95

### 3x5Amp RGB LED Controller with RS232

3 independent high power channels. Preprogrammed or user-editable light sequences. Standalone option and 2-wire serial interface for microcontroller or PC communication with simple command set. Suitable for common anode RGB LED strips, LEDs and incandescent bulbs. 56 x 39 x 20mm. 12A total max. Supply: 12Vdc.

Kit Order Code: 8191KT - £29.95

Assembled Order Code: AS8191 - £39.95



**Most items are available in kit form (KT suffix) or pre-assembled and ready for use (AS prefix).**



## Hot New Products!

Here are a few of the most recent products added to our range. See website or join our email Newsletter for all the latest news.

### 4-Channel Serial Port Temperature Monitor & Controller Relay Board

4 channel computer serial port temperature monitor and relay controller. Four inputs for Dallas DS18S20 or DS18B20 digital thermometer sensors (£3.95 each). Four 5A rated relay outputs are independent of sensor channels allowing flexibility to setup the linkage in any way you choose. Simple text string commands for reading temperature and relay control via RS232 using a comms program like Windows HyperTerminal or our free Windows application.  
**Kit Order Code: 3190KT - £84.95**  
**Assembled Order Code: AS3190 - £99.95**



### 40 Second Message Recorder

Feature packed non-volatile 40 second multi-message sound recorder module using a high quality Winbond sound recorder IC. Standalone operation using just six onboard buttons or use onboard SPI interface. Record using built-in microphone or external line in. 8-24Vdc powered. Change a resistor for different recording duration/sound quality. Sampling frequency 4-12 kHz. (120 second version also available)  
**Kit Order Code: 3188KT - £29.95**  
**Assembled Order Code: AS3188 - £37.95**



### Bipolar Stepper Motor Chopper Driver

Get better performance from your stepper motors with this dual full bridge motor driver based on SGS Thompson chips L297 & L298. Motor current for each phase set using on-board potentiometer. Rated to handle motor winding currents up to 2 Amps per phase. Operates on 9-36Vdc supply voltage. Provides all basic motor controls including full or half stepping of bipolar steppers and direction control. Allows multiple driver synchronisation. Perfect for desktop CNC applications.  
**Kit Order Code: 3187KT - £39.95**  
**Assembled Order Code: AS3187 - £49.95**



### Video Signal Cleaner

Digitally cleans the video signal and removes unwanted distortion in video signal. In addition it stabilises picture quality and luminance fluctuations. You will also benefit from improved picture quality on LCD monitors or projectors.  
**Kit Order Code: K8036 - £24.70**  
**Assembled Order Code: VM106 - £36.53**



## Motor Speed Controllers

Here are just a few of our controller and driver modules for AC, DC, Unipolar/Bipolar stepper motors and servo motors. See website for full details.

### DC Motor Speed Controller (100V/7.5A)

Control the speed of almost any common DC motor rated up to 100V/7.5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 5-15Vdc. Box supplied. Dimensions (mm): 60Wx100Lx60H.  
**Kit Order Code: 3067KT - £19.95**  
**Assembled Order Code: AS3067 - £27.95**



### Bidirectional DC Motor Speed Controller

Control the speed of most common DC motors (rated up to 32Vdc/10A) in both the forward and reverse direction. The range of control is from fully OFF to fully ON in both directions. The direction and speed are controlled using a single potentiometer. Screw terminal block for connections.  
**Kit Order Code: 3166v2KT - £23.95**  
**Assembled Order Code: AS3166v2 - £33.95**



### Computer Controlled / Standalone Unipolar Stepper Motor Driver

Drives any 5-35Vdc 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps. Provides speed and direction control. Operates in stand-alone or PC-controlled mode for CNC use. Connect up to six 3179 driver boards to a single parallel port. Board supply: 9Vdc. PCB: 80x50mm.  
**Kit Order Code: 3179KT - £17.95**  
**Assembled Order Code: AS3179 - £24.95**



### Computer Controlled Bi-Polar Stepper Motor Driver

Drive any 5-50Vdc, 5 Amp bi-polar stepper motor using externally supplied 5V levels for STEP and DIRECTION control. Opto-isolated inputs make it ideal for CNC applications using a PC running suitable software. Board supply: 8-30Vdc. PCB: 75x85mm.  
**Kit Order Code: 3158KT - £24.95**  
**Assembled Order Code: AS3158 - £34.95**



### AC Motor Speed Controller (600W)

Reliable and simple to install project that allows you to adjust the speed of an electric drill or 230V AC single phase induction motor rated up to 600 Watts. Simply turn the potentiometer to adjust the motors RPM. PCB: 48x65mm. Not suitable for use with brushless AC motors.  
**Kit Order Code: 1074KT - £15.95**  
**Assembled Order Code: AS1074 - £23.95**



**See website for lots more DC, AC and stepper motor drivers!**



**QUASAR**  
electronics  
The Electronic Kit Specialists Since 1993

**Credit Card Sales**  
**01279 467 799**

## Electronic Project Labs

Great introduction to the world of electronics. Ideal gift for budding electronics expert!

### 130-in-1 Electronic Project Lab

Get started on the road to a great hobby or career in electronics. Contains all the parts and instructions to assemble 130 educational and fun experiments and circuits. Build a radio, AM broadcast station, electronic organ, kitchen timer, logic circuits and more. Built-in speaker, 7-segment LED display, two integrated circuits and rotary controls. Manual has individual circuit explanations, schematic and connection diagrams. Requires 6 x AA batteries (not included). Suitable for age 14+.  
**Order Code EPL130 - £55.95**  
**Also available: 30-in-1 £24.95, 50-in-1 £33.95, 75-in-1 £45.95, 200-in-1 £65.95, 300-in-1 £89.95, 500-in-1 £199.95**



## Tools & Test Equipment

We stock an extensive range of soldering tools, test equipment, power supplies, inverters & much more - please visit website to see our full range of products.

### Advanced Personal Scope 2 x 240MS/s

Features 2 input channels - high contrast LCD with white backlight - full auto set-up for volt/div and time/div - recorder roll mode, up to 170h per screen - trigger mode: run - normal - once - roll ... - adjustable trigger level and slope and much more.  
**Order Code: APS230 - £374.95-£249.95**



### Handheld Personal Scope with USB

Designed by electronics enthusiasts for electronics enthusiasts! Powerful, compact and USB connectivity, this sums up the features of this oscilloscope. 40 MHz sampling rate, 12 MHz analog bandwidth, 0.1 mV sensitivity, 5mV to 20V/div in 12 steps, 50ns to 1 hour/div time base in 34 steps, ultra fast full auto set up option, adjustable trigger level, X and Y position signal shift, DVM readout and more...  
**Order Code: HPS50 - £289.95-£203.95**  
**See website for more super deals!**



[www.quasarelectronics.co.uk](http://www.quasarelectronics.co.uk)

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads



## UK readers you can **SAVE 81p** on every issue of *EPE*

How would you like to pay £3.59 instead of £4.40 for your copy of *EPE*?



Well you can – just take out a one year subscription and save **81p** an issue, or **£9.80** over the year. You can even save £1.08 an issue if you subscribe for two years – a total saving of **£26.10**

Overseas rates also represent exceptional value

You also:

- Avoid any cover price increase for the duration of your subscription
- Get your magazine delivered to your door each month
- Ensure your copy, even if the newsagents sell out

Order by phone, or fax with a credit card, or by post with a cheque or postal order, or buy online from [www.epemag.com](http://www.epemag.com) (go to the Online Shop).

## SUBSCRIPTION PRICES

Subscriptions for delivery direct to any address in the UK: 6 months £23.50, 12 months £43.00, two years £79.50; Europe Airmail: 6 months £28.00, 12 months £52.00, 24 months £99.00; Rest Of The World Airmail: 6 months £37.00, 12 months £70.00, 24 months £135.00.

Cheques or bank drafts (in **£ sterling only**) payable to *Everyday Practical Electronics* and sent to EPE Subs. Dept., Wimborne Publishing Ltd., 113 Lynwood Drive, Merley, Wimborne, Dorset, BH21 1UU. Tel: 01202 880299. Fax: 01202 843233. Email: [subs@wimborne.co.uk](mailto:subs@wimborne.co.uk). Also via the Web at: [www.epemag.com](http://www.epemag.com).

Subscriptions start with the next available issue. We accept MasterCard, Maestro or Visa. (For past issues see the Back Issues page.)

## ONLINE SUBSCRIPTIONS

Online subscriptions, for reading the magazine via the Internet, £19.99 for one year, visit [www.epemag.com](http://www.epemag.com) for more details.

## SUBSCRIPTION ORDER FORM

- ☐ 6 Months: UK £23.50, Europe £28.00 (Airmail), Rest Of The World £37.00 (Airmail)
- ☐ 1 Year: UK £43.00, Europe £52.00 (Airmail), Rest Of The World £70.00 (Airmail)
- ☐ 2 Years: UK £79.50, Europe £99.00 (Airmail), Rest Of The World £135.00 (Airmail)

To: Everyday Practical Electronics,  
Wimborne Publishing Ltd., 113 Lynwood Drive, Merley,  
Wimborne, Dorset BH21 1UU  
Tel: 01202 880299 Fax: 01202 843233  
E-mail: [subs@epemag.wimborne.co.uk](mailto:subs@epemag.wimborne.co.uk)

I enclose payment of £ ..... (cheque/PO in £ sterling only), payable to *Everyday Practical Electronics*

☐ Please charge my Visa/Mastercard/Maestro

My card number is: .....  
Please print clearly, and check that you have the number correct

Signature .....

Card Security Code ..... Valid From Date.....  
(The last 3 digits on or just under the signature strip)

Card Ex. Date .....Maestro Issue No. ....

Name .....

Address .....

Post code ..... Tel. ....


Subscriptions can only start with the next available issue.





# P955H PIC Training Circuit

by Peter Brunning

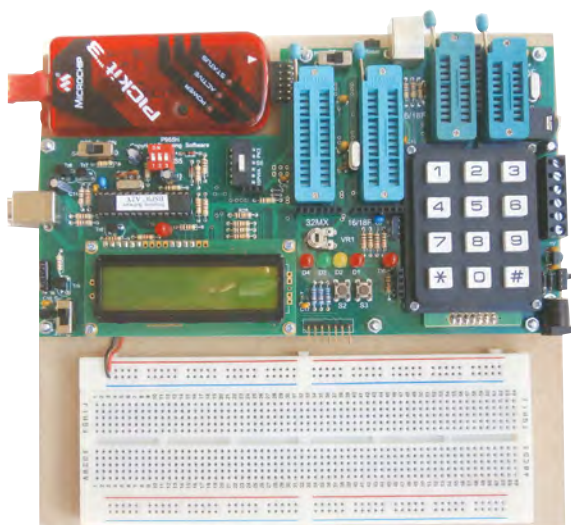

When you start learning about programming PICs you need a simple easy to use system. The Microchip system MPLAB + PICkit3 is great when you know what you are doing but for beginners its extensive complexity is a daunting prospect. So you need a simple easy to use system to get started then when you get up to speed you may want to use the Microchip system. The P955H training circuit has an onboard PIC programmer which is simple and straightforward to use. The P955H also has provision to plug on a PICkit3 so changing over when you are ready is no problem. The P955H has four ZIF sockets to accommodate the various PIC sizes and types. Just fit a PIC in the appropriate ZIF socket and your experimental circuit is wired with four LEDs, two push buttons, two line 16 character display, keypad, serial link to your PC, and four 5 amp open drain outputs.

## The Brunning Software P955H PIC Training Course

We start by learning to use a relatively simple 8 bit PIC microcontroller. We make our connections directly to the input and output pins of the chip and we have full control of the internal facilities of the chip. We work at the grass roots level.

The first book starts by assuming you know nothing about PICs but instead of wading into the theory we jump straight in with four easy experiments. Then having gained some experience we study the basic principles of PIC programming., learn about the 8 bit timer, how to drive the alphanumeric liquid crystal display, create a real time clock, experiment with the watchdog timer, sleep mode, beeps and music. Then there are two projects to work through. In the space of 24 experiments two project and 56 exercises we work through from absolute beginner to experienced engineer level using the latest 8 bit PICs (16F and 18F).


The second book introduces the C programming language for 8 bit PICs in very simple terms. The third book Experimenting with Serial Communications teaches Visual C# programming for the PC so that we can create PC programmes to control PIC circuits.

In the fourth book we learn to programme 32 bit MX PICs using fundamental C instructions. Flash the LEDs, study the 16 bit and 32 bit timers, and write text to the LCD. This is all quite straightforward as most of the code is the same as already used with the 8 bit PICs. Then life gets more complex as we delve into serial communications with the final task being to create an audio oscilloscope with advanced triggering and adjustable scan rate.

The complete P955H training course is £254 including P955H training circuit, 4 books (240 x 170mm 1200 pages total), 6 PIC microcontrollers, PIC assembler and programme text on CD, 2 USB to PC leads, pack of components, and carriage to a UK address. (To programme 32 bit PICs you will need to plug on a PICkit3 which you need to buy from Microchip, Farnell or RS for £38).

Prices start from £159 for the P955H training circuit with books 1 and 2 (240 x 170mm 624 pages total), 2 PIC microcontrollers, PIC assembler and programme text on CD, USB to PC lead, and carriage to UK address. (PICkit3 not needed for this option). You can buy books 3 and 4, USB PIC, 32 bit PIC and components kit as required later. See website for details.

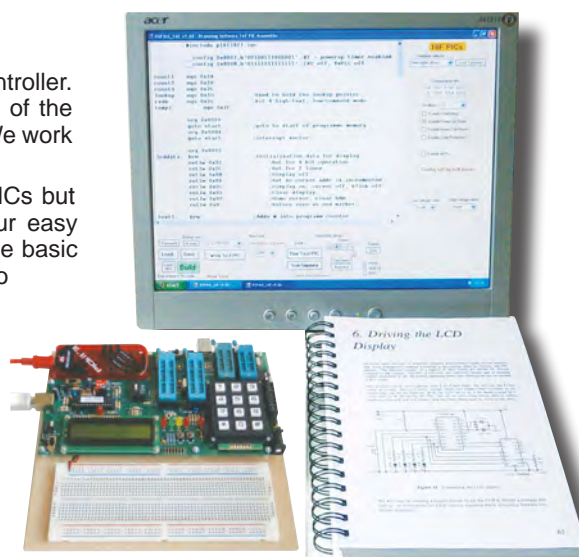Web site:- [www.brunningsoftware.co.uk](http://www.brunningsoftware.co.uk)



Mail order address:

**Brunning Software**

138 The Street, Little Clacton, Clacton-on-sea,  
Essex, CO16 9LS. Tel 01255 862308

### Arduino Starter Kit

Genuine Arduino Starter kit which comprises of a 170 page instruction manual, Arduino UNO Board, Breadboard, components & more.

The kit walks you through the Arduino programming and basic electronics in a hands on way. You will be able to build 15 projects using the components supplied. They allow you to control the physical world through different kinds of sensors and actuators. Once you have mastered this knowledge, you will have the ability and circuits to create something beautiful, and make someone smile with what you invent. So build, hack and share!

The Arduino Starter kit is the ideal partner for anyone following the Teach-In 2016 which started in the February 2016 issue of EPE Everyday Practical Electronics.

This Starter kit is supplied with a Wood base, USB & Interconnect leads, Electric motor, Piezo sounder, Movement and Temperature sensors, Switches, LCD, Breadboard & Servo motor. The kit also includes over 100 electronic components:- Diodes, Transistors, Capacitors, h-Bridge, Resistors, LED's, Switches and Trimmers. Quote: EPEARDSK

**£69.90**  
Inc Delivery & VAT



**Great for**  
**Teach-In 2016**  
Exploring the  
Arduino



### Official Arduino Dealer

**Genuine Arduino UNO R3**  
from **£18.98+p&p**



**Wide range of Boards, Shields & Accessories**

### HPS140i Oscilloscope

The HPS140i Oscilloscope packs a lot of power in a tiny box. Now you can really take a powerful oscilloscope everywhere. These features make the HPS140 indispensable to the professional user, service centres and even to the hobbyist. Supplied with a probe.



- \* 40Mhz real time sample rate
- \* Full auto range option
- \* Hold & store function
- \* Operates up to 6 hours on one charge
- \* Scope Lead and Charger Supplied

Quote: EPEHPS

**£99.60**  
Inc Delivery & VAT



### HPG1 Function Generator

A complete pocket function generator. Now you can take test signals on the move, 3 waveforms can be selected. Set the output voltage or frequency and select signal waveform using the on the screen menu. A powerful sweep function is also included.

- \* Frequency range: 1Hz to 1,000,000Hz
- \* Frequency steps: 1Hz, 10Hz, 100Hz, 1kHz and 10kHz
- \* Sine, square and triangle wave forms
- \* Runs on NiMH rechargeable battery pack (included)
- \* BNC Lead and Charger Included.

Quote: EPEHPG



**£87.60**  
Inc Delivery & VAT

### 2.4GHz Frequency Counter

0.01Hz to 2.4GHz  
8 Digit LED Display  
Gate Time: 100ms to 10s  
2 Channel Operating mode  
Power Supply: 110-220Vac 5W  
Quote: EPE24G



**£81.00**  
Inc Delivery & VAT



### 30V 5A Programmable PSU

Dual LED (Voltage & Current) Displays  
Course & Fine Voltage /Current Adjustment  
Voltage or Current Limiting.

- \* 5 Memories
- \* PC Link via USB or RS232
- \* Output:  
0-30Vdc  
0-5A

Quote: EPEPSU



**£99.90**  
Inc Delivery & VAT


### Build your own Oscilloscope

A new self assembly kit, ideal for education and way to visualise signals. Features: Markers, Frequency, dB, True RMS readouts  
Timebase range:

- 10µs-500ms/division (15 steps)
- Input sensitivity:  
100mV-5V/division (6 steps)
- Max Input voltage: 30Vpp
- Max Sample Rate:  
1ms/s repetitive signal,  
100ks/s real time signal
- Dim: 80 x 115 x 40mm

Quote: EPESCOPE

**£49.99**  
Inc Delivery & VAT

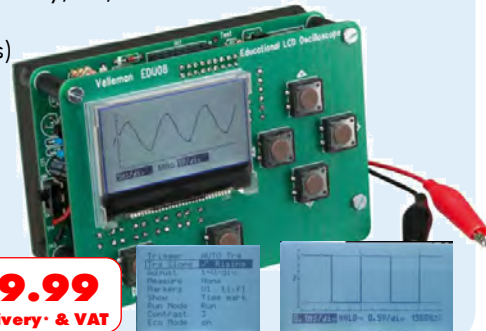



**Editorial Offices:**

EVERYDAY PRACTICAL ELECTRONICS  
EDITORIAL Wimborne Publishing Ltd., 113 Lynwood  
Drive, Merley, Wimborne, Dorset, BH21 1UU  
**Phone:** 01202 880299. **Fax:** 01202 843233.  
**Email:** fay.kearn@wimborne.co.uk  
**Website:** www.epemag.com

See notes on **Readers' Technical Enquiries** below  
— we regret technical enquiries cannot be answered  
over the telephone.

**Advertisement Offices:**

Everyday Practical Electronics Advertisements  
113 Lynwood Drive, Merley, Wimborne, Dorset,  
BH21 1UU  
**Phone:** 01202 880299 **Fax:** 01202 843233  
**Email:** stewart.kearn@wimborne.co.uk

**Editor:** MATT PULZER  
**Subscriptions:** MARILYN GOLDBERG  
**General Manager:** FAY KEARN  
**Graphic Design:** RYAN HAWKINS  
**Editorial/Admin:** 01202 880299  
**Advertising and  
Business Manager:** STEWART KEARN  
01202 880299  
**On-line Editor:** ALAN WINSTANLEY

**Publisher:** MIKE KENWARD

**READERS' TECHNICAL ENQUIRIES**

**Email:** fay.kearn@wimborne.co.uk

We are unable to offer any advice on the use, purchase,  
repair or modification of commercial equipment or the  
incorporation or modification of designs published  
in the magazine. We regret that we cannot provide  
data or answer queries on articles or projects that are  
more than five years' old. Letters requiring a personal  
reply must be accompanied by a stamped self-  
addressed envelope or a self-addressed envelope and  
international reply coupons. We are not able to answer  
technical queries on the phone.

**PROJECTS AND CIRCUITS**

All reasonable precautions are taken to ensure that  
the advice and data given to readers is reliable. We  
cannot, however, guarantee it and we cannot accept  
legal responsibility for it.

A number of projects and circuits published in  
EPE employ voltages that can be lethal. You should  
not build, test, modify or renovate any item of mains-  
powered equipment unless you fully understand the  
safety aspects involved and you use an RCD adaptor.

**COMPONENT SUPPLIES**

We do not supply electronic components or kits for  
building the projects featured, these can be supplied  
by advertisers.

We advise readers to check that all parts are still  
available before commencing any project in a back-  
dated issue.

**ADVERTISEMENTS**

Although the proprietors and staff of EVERYDAY  
PRACTICAL ELECTRONICS take reasonable  
precautions to protect the interests of readers by  
ensuring as far as practicable that advertisements are  
bona fide, the magazine and its publishers cannot give  
any undertakings in respect of statements or claims  
made by advertisers, whether these advertisements  
are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances  
will the magazine accept liability for non-receipt of  
goods ordered, or for late delivery, or for faults in  
manufacture.

**TRANSMITTERS/BUGS/TELEPHONE  
EQUIPMENT**

We advise readers that certain items of radio  
transmitting and telephone equipment which may  
be advertised in our pages cannot be legally used in  
the UK. Readers should check the law before buying  
any transmitting or telephone equipment, as a fine,  
confiscation of equipment and/or imprisonment can  
result from illegal use or ownership. The laws vary from  
country to country; readers should check local laws.

# EPE EVERYDAY PRACTICAL ELECTRONICS

**Now is the time to learn about PICs**

Spring is finally here and with it a warm welcome to the June issue of *EPE*. We have a cornucopia of exciting, informative and useful material for you this month; but top of my list is the start of a *PIC n' Mix* mini-series on the basics of designing and building PIC-based circuits. If you've never dabbled in this important area of electronics then now is the time to start.

**Troubleshooting...**

I enjoy just about every aspect of electronics: design is an ever-fascinating intellectual challenge; construction is a combination of skill, dexterity and arranging components in a neat, logical and satisfying manner; and even sourcing components has its pleasant challenges. However, there is one area that can drive me to distraction — fault finding and troubleshooting a problem. We've all been there, you check, check and check again, but your carefully designed, meticulously constructed circuit just refuses to behave. You go round in ever decreasing circles, hunting for errors, solder bridges, loose power connections... till you start to doubt your ability, or even your sanity.


Anything that can reduce this pain is to be welcomed, which is why all serious constructors of analogue or AM radio circuits should be pleased to see the publication this month of our *Audio Signal Injector/Tracer project*. It won't solve all your problems, but it might just give you the head-start you need to stay sane!

**EPE's got talent!**

Or rather I should say Jake does... I'm not normally a follower of ITV's 'Britain's Got Talent', but the show on Saturday, 16 April was an exception. Appearing live before a huge audience and a quartet of formidable judges was *EPE's* very own audio electronics guru — Jake Rothman. Performing with a 1996 version of his famous *EPE* Theremin design, Jake may not have exactly wowed the crowd, but he gets my vote simply for being one of the few (if not only) performer who actually designed and made the instrument used live on stage.



*Mail*

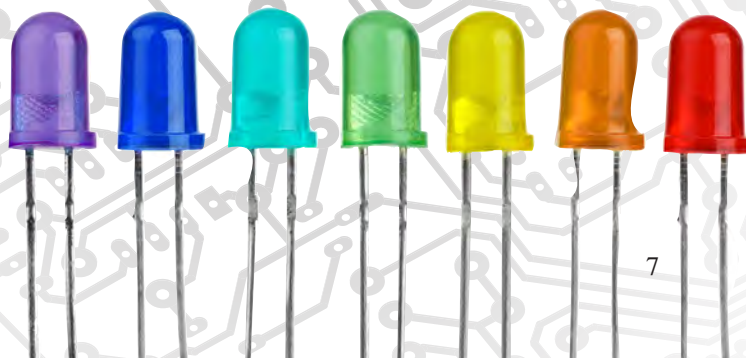

# NEWS

A roundup of the latest Everyday News  
from the world of  
electronics



## Portable jump start and screen burn – report by Barry Fox



Phone/tablet/camera charger and automotive jump starter

The Cobra CPP 8000 JumpPack costs £80, is around the size of a pack of cards and weighs 300g, with an internal 7500mAh lithium-cobalt battery. The battery is conventionally charged either by a 5V USB or car socket connector, and delivers 5V at 2.1A for rapid charging of portable devices such as mobile phones, tablets and digital cameras. Unconventionally, JumpPack also has a shuttered, twin-pin socket that takes short, fused leads with crocodile clips. These connect to a car battery and deliver bursts of 12V at around 200A. The makers say this is enough to 'jump start most vehicles'.

Normally, it would take a fully charged, big and heavy lead acid battery to deliver enough current to start a car engine. I was, therefore, a little wary, and put the device to a real-world test, deliberately draining the battery of a VW Polo with 1.4 litre petrol engine by leaving the headlights on, and then trying to start it with the JumpPack.

### Close, but...

The JumpPack delivered enough power to turn over the engine, several times, but not with enough speed and torque to start the engine running. I

followed the instructions and tried several times with short bursts. The JumpPack got pretty hot, but could not start the car engine.

I repeated the test with a different sample, in case the first unit had been faulty.

After again deliberately draining the car battery again I tried the 100% charged replacement JumpPack. The result was the same; the engine turned over but would not start.

As a final test I tried connecting both JumpPacks to the car battery, in parallel, and the car started.

So one JumpPack will be a life-saver when an engine just fails to start because the car battery is low or failing; but two JumpPacks may be needed when the car battery is fully flat.

Two JumpPacks will cost more than most car batteries but are a lot more convenient to carry – and also serve as very gutsy mobile phone, tablet and camera chargers.

### Return of the burn

Welcome (not) to the return of an old bugbear – screen burn, otherwise known as 'image retention' or 'image sticking'.

Cathode ray tubes (CRT) and plasma screens, which emit light, can physically change when used at high brightness for long periods. If the light is in a stationary pattern, the pattern imprints on the screen.

Old arcade games, where a games grid remained stationary for months

or even years, showed the grid even when turned off. The same thing happened on TVs and computers – to a lesser extent – with wordpro templates, logos, test patterns and TV station ID 'bugs' sticking to the screen.

That's how screen savers were born. Later, when LCD screens took over from CRTs and plasmas, the screen savers became totally unnecessary 'brain savers'. LCDs 'light gate' a backlight, so they do not suffer from burn.

OLEDs emit light so are at similar risk to CRT and Plasma displays. This is not an unfounded scare story. At a recent technical seminar held by Panasonic in Germany, Eric Gemmer, Director of Imaging Technology at THX in California, was noticeably careful about leaving a static test pattern on the OLED screen he was using to demonstrate the contrast difference between LCD and OLED displays.

'As with CRTs and plasmas' he explained, 'it starts as a temporary residual effect which disappears in around two hours, but can become permanent.'



Remember this? Screen burn on a gaming CRT display; this issue may be about to return with the rise of OLED displays



## DNA data storage breakthrough

**C**ompanies such as Google routinely build huge data centres to store all the kitten pictures and emails its users generate – and keep.

However, a new technique developed by the University of Washington (UW) and Microsoft researchers could shrink the space needed to store digital data that today would fill a factory-sized supercenter down to the size of a sugar cube.

The team of scientists and bio-engineers has created one of the first complete systems to encode, store and retrieve digital data using DNA molecules, which can store information millions of times more compactly than current archival technologies.

### Encode and retrieve data

In one experiment, the team successfully encoded digital data from four image files into the nucleotide sequences of synthetic DNA snippets. More significantly, they were also able to reverse that process – retrieving the correct sequences from a larger pool of DNA and reconstructing the images without losing a single byte of information.

‘Life has produced this fantastic molecule called DNA that efficiently stores all kinds of information about

your genes and how a living system works – it’s very, very compact and very durable,’ said co-author Luis Ceze, UW associate professor of computer science and engineering.

### Data explosion

The digital universe – all the data contained in computer files, archives, movies, photo collections and created by businesses – is expected to hit 44 trillion gigabytes by 2020.

That’s a tenfold increase from 2013, and will represent enough data to fill more than six stacks of computer tablets stretching to the moon. While not all of that information needs to be saved, the world is producing data faster than the capacity to store it.

DNA molecules can store information many millions of times more densely than existing technologies, such as flash drives, hard drives, magnetic and optical media. Those systems also degrade after a few years or decades, while DNA can reliably preserve information for centuries. DNA is best suited for archival applications, rather than instances where files need to be accessed immediately.

### From bits to DNA

The researchers have developed a

novel approach to convert the long strings of ones and zeroes in digital data into the four basic building blocks of DNA sequences – adenine, guanine, cytosine and thymine.

‘How you go from ones and zeroes to As, Gs, Cs and Ts really matters because if you use a smart approach, you can make it very dense and you don’t get a lot of errors,’ said co-author Georg Seelig, a UW associate professor. ‘If you do it wrong, you get a lot of mistakes.’

The data is chopped into pieces and stored by synthesising a massive number of tiny DNA molecules, which can be dehydrated or otherwise preserved for long-term storage.

The UW and Microsoft researchers are one of two teams nationwide that have also demonstrated the ability to perform ‘random access’ – to identify and retrieve the correct sequences from this large pool of random DNA molecules, which is a task similar to reassembling one chapter of a story from a library of torn books.

Currently, the largest barrier to viable DNA storage is the cost and efficiency with which DNA can be manufactured and sequenced (or read) on a large scale. But researchers say there’s no technical barrier to achieving those gains if the right commercial incentives are in place.

## UK’s first commercial computer

**M**ore than 60 years after it was first revealed to the public, Britain’s first mass-produced business computer, the Hollerith Electronic Computer (HEC), is now on display at The National Museum of Computing (TNMOC) at Bletchley Park.

The HEC was the prototype for the range of computers that were to become Britain’s best-selling first-generation computer and, as the first computer installed in many countries including India, New Zealand and East Africa, the machine played a key role in starting the global computer revolution.

The first version of the 2m x 3m HEC with its highly innovative magnetic drum store can be seen by visitors to the First Generation Gallery at TNMOC where it stands alongside other machines of the period: the ongoing reconstruction of the 1949 EDSAC computer and the original 1951 Harwell Dekatron / WITCH computer.

The HEC was commissioned by the British Tabulating Machine Company (BTM). Dr Raymond Bird, a skilled and enthusiastic electronics engineer, was tasked with its development.

Dr Bird explained the development process: ‘BTM was one of Britain’s largest suppliers of pre-computing punch-card systems and the company realised that computing was the company’s future. BTM had been approached by Professor Andrew Booth of Birkbeck College, London, who needed input and output technologies – punch cards – for a computer he was designing. A deal was struck and I was sent to make copies of Booth’s computer design.’



*Dr Raymond Bird demonstrates the HEC at the 1953 Business Efficiency Exhibition. Photo courtesy Dr Raymond Bird.*

## Smart contact lens




**S**amsung has been granted a patent for a smart contact lens that projects images directly into the wearer’s eye with a built-in camera that is controlled by blinking.

The patent shows that Samsung has been developing a contact lens with a tiny display, a camera, an antenna, and several sensors. It’s designed to be paired with an external device, such as a smartphone for image processing and data storage.

Samsung claim their smart contact lenses provide superior image quality than off-eye solutions such as Google Glass. Like Google Glass, however, these contact lenses will undoubtedly come under intense scrutiny over its privacy-eroding implications – they’re essentially hard-to-detect cameras that can be taken and used anywhere a person goes and on anything a person can see.

# microchip DIRECT

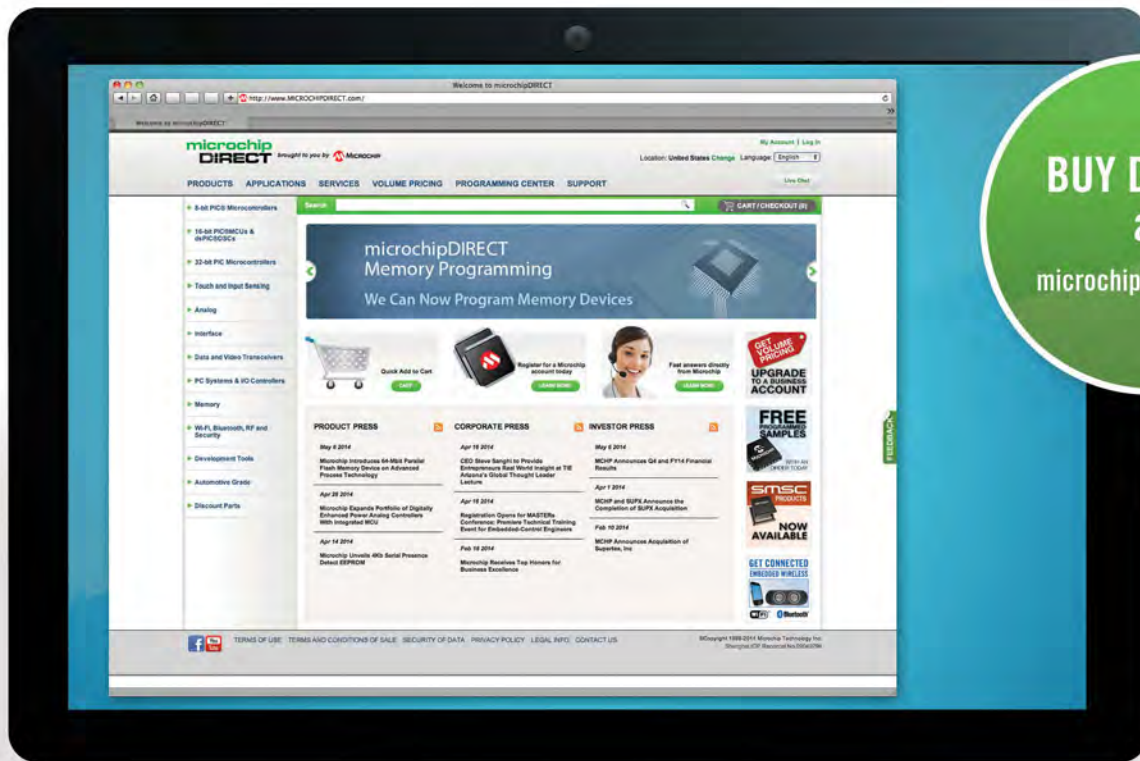

microchipDIRECT offers access to the world's largest inventory of Microchip products and the most comprehensive online resource for pricing and support directly from Microchip Technology. We invite you as a valued Microchip customer to experience our service 24 hours a day, 7 days per week.

Visit [www.microchipDIRECT.com](http://www.microchipDIRECT.com) and enjoy the confidence and convenience of buying from microchipDIRECT and take advantage of the following features:

- ▶ Direct stock from factory
- ▶ Direct customer service
- ▶ Secure ordering
- ▶ Volume pricing
- ▶ Credit lines
- ▶ Long-term orders and scheduling
- ▶ Programming and value add services
- ▶ Ability to adjust open orders
- ▶ Ship to your sites globally
- ▶ Online order status and notifications



**microchip**  
**DIRECT**  
[www.microchipdirect.com](http://www.microchipdirect.com)

 **MICROCHIP**  
[www.microchipDIRECT.com](http://www.microchipDIRECT.com)



# Proof at last!

## TechnoTalk

Mark Nelson

People who have long suffered pain and other ailments that they blamed on 'electronic smog' can finally refute the sceptics. New academic proof that these effects are not imaginary is Mark Nelson's subject this month.

### ELECTRONIC SMOG – DESCRIBED

As 'an unprecedented dense mesh of artificial magnetic, electrical and electromagnetic fields' – has been blamed for many ills. In 2008, radiation from mobile phone towers and power lines was cited as causing the collapse of bee colonies and declining sparrow populations by upsetting their migration paths. Even more disturbing were the allegations that humans were affected too, suffering symptoms of weakness and dizziness, or worse – death from brain tumours or throat and breast cancer. The Bioinitiative Working Group, an international study group of respected scientists and public health policy experts, stated in 2007: 'Chronic exposure to even low-level radiation (like that from cellphones), can cause a variety of cancers, impair immunity, and contribute to Alzheimer's disease and dementia, heart disease, and many other ailments. We now have a critical mass of evidence, and it gets stronger every day.'

### EHS

An allied ailment is EHS (electrical hypersensitivity), which is becoming more widespread. Some experts say up to three per cent of all people may be clinically hypersensitive and up to 30 per cent to a lesser degree. Symptoms attributed to EHS include fatigue, facial irritation, tinnitus, dizziness, and digestive disturbance. Exposure to computer screens, mobile phones and other everyday electronic equipment, as well as to Wi-Fi in the home or workplace, is the alleged culprit.

### The final truth?

Up to now, these allegations have been refuted time after time, with no definite medical evidence confirmed. Now, researchers at The University of Texas at Dallas in the US have provided scientific evidence to back up the anecdotal stories of people who reported abnormal sensations and neuropathic pain around cellphone towers and other devices that produce radio-frequency electromagnetic fields. 'Our study provides evidence, for the first time, that subjects exposed to cellphone towers at low, regular levels can actually perceive pain,' says Dr Mario Romero-Ortega, an associate

professor of bioengineering at the university. 'Our study also points to a specific nerve pathway that may contribute to our main finding.'

### Pain response in rats

Rats were exposed to a 915MHz radio signal (close to frequencies used by many cellphones) for ten minutes, once per week for eight weeks. The antenna delivered a power density equal to that measured at 39m from a local cellphone tower – a power density that a person might encounter outside of occupational settings. By the fourth week, 88 per cent of subjects in the nerve-injured group demonstrated a behavioural pain response, while only one subject in the sham group exhibited pain at a single time point, and that was during the first week. After remedial treatment the pain responses persisted. Professor Romero-Ortega concludes: 'In our study, the subjects with nerve injury were not capable of complex psychosomatic behaviour. Their pain was a direct response to man-made radio frequency electromagnetic energy.'

### Phase difference

Until recently, most electrical and electronic gadgets bought in North America would not work well or at all in Europe. It was not just the AC voltage that was different; but also the mains or line frequency. Today, many appliances use switch-mode power supplies and are frequency and voltage-agnostic, for which we can be truly thankful; but have you ever wondered why the Americans perversely chose 60Hz, at a time when 50Hz was used in (most of) the rest of the world? I wanted to know who made that strange choice and why.

The most plausible answer I found was given by Robert Frost, an instructor and flight controller at NASA, on the [Quora.com](http://www.Quora.com) website. He states: 'In 1891, Westinghouse selected 60Hz while at the same time, in Germany [and all of Europe in fact] they were selecting 50Hz. Westinghouse chose 60Hz because the arc-light carbons that were popular at that time worked better at 60Hz than at 50Hz. Either 50 or 60 works today, obviously, but they are both trade-offs. At lower frequencies

more copper and iron are needed (in motors and transformers) but at higher frequencies, more expensive plates are needed to prevent eddy losses.'

### Impractical everyday electronics

Today, using satellites for receiving TV ('200 channels and nothing on' as the cynics say) and calculating your location by GPS is commonplace. But who had the idea first?

Did you say Sir Arthur C. Clarke? 'Twas indeed he who proposed the use of geostationary satellites for communication purposes in the February 1945 issue of *Wireless World* magazine. He followed up this letter with a fully worked-out article in October of that year (<http://lakdiva.org/clarke/1945ww>). But, five years previously someone else beat him to it. This was another Brit by the name of John Bray, who later became Director of Research for Post Office Telecommunications (a little before it became British Telecom). His proposal was considered 'moonshine' at the time by his superiors, but he was unperturbed and went on to play a key role in global satellite communications. His prophetic words follow.

'Sitting in an armchair on the lawn at home in that summer of 1940, I began to consider the possibility of using the Moon as a passive communication satellite by beaming radio waves at its surface and picking up the scattered waves at any other location on Earth from which the Moon was visible. It might thus serve as a means of telegraph or telephone communication — for example, of encoded signals for military purposes.

'Calculations showed that, with microwave powers of about 1kW and dish aerials some three metres in diameter, the radiated energy could be concentrated in a beam about 0.5 degree wide that could illuminate the Moon at a distance of 250,000 miles and produce a scattered signal energy at the receiver adequate for a telephone channel of usable quality. However, the two-way transmission delay due to the finite velocity of radio waves, 186,000 miles per second, was about 2.5 seconds — unimportant for telegraph communication but a handicap for normal telephone conversation.'

# The 'Bad Vibes' Infrasonic Snooper

By Nicholas Vinen



Back in March 2014 we published the *Infrasound Detector* for low frequency measurements. Now you can 'listen' to low frequency vibrations with our *Infrasound Snooper*. It frequency shifts and amplitude modulates a frequency range of about 1Hz to 20Hz by about five or six octaves so that you can listen directly to wind turbines or elephants, crocodiles and other animals that communicate with infrasound.

OUR *Infrasound Snooper* uses digital signal processing (DSP) techniques in a PIC32MX170 microcontroller, an electret microphone, a DAC chip, a TL074 quad op amp and very little else, to drive a pair of headphones.

High levels of infrasound may have a negative impact on your health but you might not even know when you are being exposed to low frequency vibrations unless they excite harmonics by rattling window panes and similar, because they're otherwise inaudible.

In January last year, a study by Steven Cooper of Bridgewater Acoustics


attracted a great deal of controversy over its findings which support the notion that infrasound from wind turbines can cause negative health impacts on people some distance away.

At the author's offices, some staff recently experienced ill effects, including headaches and nausea, when a ground compacting machine was operating on a nearby building site. It evidently set up all sorts of standing waves in our building, as it moved around the construction site. Some 'nodes' in our building were quite unpleasant places to be.


So if you are living or working near potential sources of infrasound and are suffering from some of the potential symptoms, our *Infrasound Snooper* can certainly help.

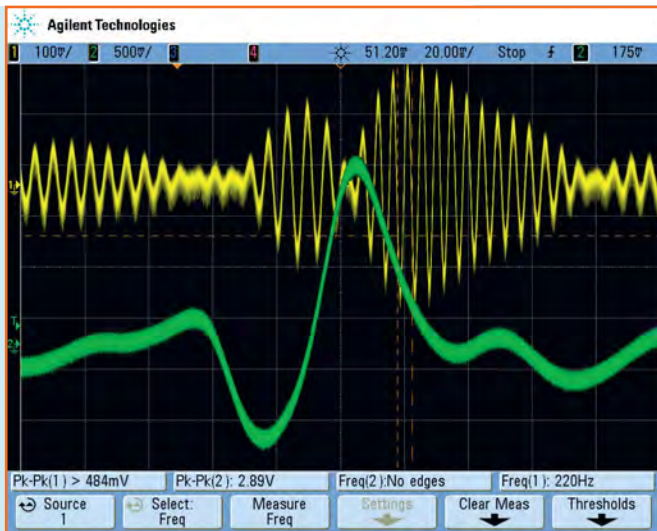Our *Infrasound Detector* (EPE, March 2014) allows you to measure the amplitude and frequency of infrasonic sound waves, but the results can be somewhat difficult to interpret since you cannot hear the phenomenon. The *Infrasound Snooper* lets you assess the amplitude and frequency of the waves but importantly, you can also hear the details – whether they





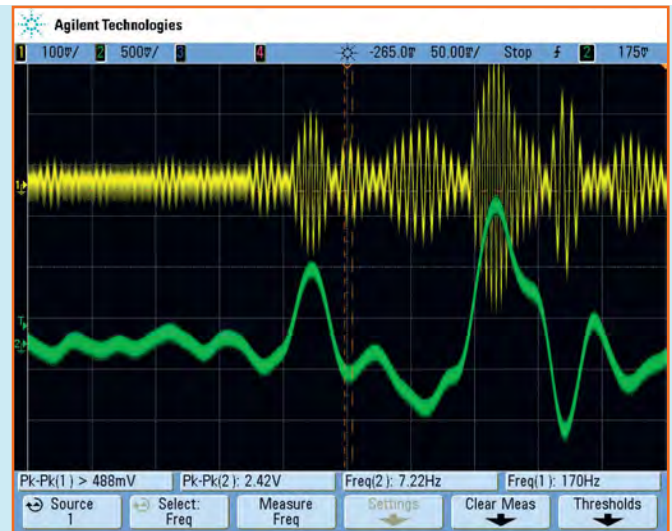**Scope1:** amplified infrasound output from IC2c (green) and the modulated signal to the headphones (yellow) for a low-frequency impulse of about 10Hz. The mode is AM+FM with low-frequency boost and you can see the output frequency shifting for the positive/negative infrasound signal as well as the delay from the low-frequency boosting filter.



**Scope2:** a similar impulse at a longer timebase than Scope1 (50ms/div rather than 20ms/div). The mode is AM+FM without low-frequency boost and thus the output waveform modulation corresponds very closely to the green input signal excursions. As before, positive excursions produce higher modulated frequencies than negative excursions.

are short, repetitive bursts, continuous waves or somewhere in between.


Our *Infrasound Snooper* is housed in a small plastic box and uses a double-sided PCB, which is available from the *EPE PCB Service*, (code 04104151) measuring 104 × 60.5mm. An electret microphone is mounted at one end of the case and a rotary switch on the lid offers a number of different listening modes.

## Circuit description

Fig.1 shows the circuit details. Infrasonic sound waves are sensed with the electret microphone (MIC1) or an external microphone plugged into CON4. A 6.8kΩ pull-up resistor from the 5V regulated rail provides the electret's operating current.


The electret signal is AC-coupled via a 1μF capacitor to the non-inverting input of op amp IC2b, one section of a TL074 quad JFET-input op amp. In conjunction with the 1MΩ resistor, this capacitor forms a low pass filter with a -3dB corner frequency at 0.2Hz. Thus, signals above 0.5Hz pass through with little or no attenuation. The 5V rail is used as a convenient DC bias point to bring the signal within IC2's supply rails, ie, roughly half-way between 0V and V<sub>CC</sub> which is typically 8.7V.

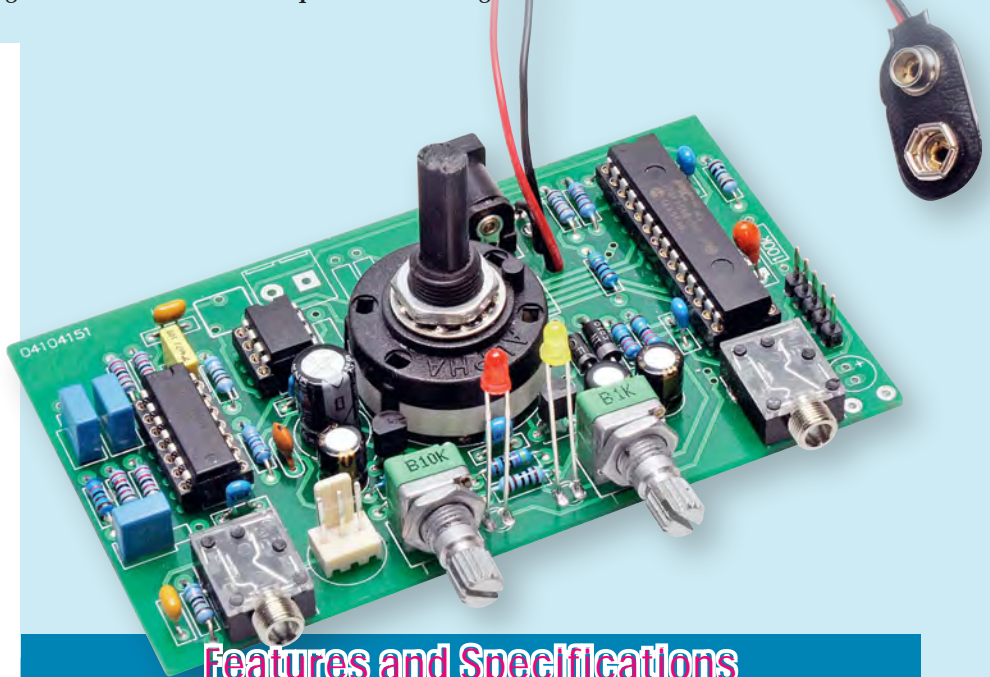IC2b operates as a simple buffer, feeding the following third-order active low-pass filter based around op amp stage IC2a, which has a gain of



## Features and Specifications

- Converts infrasonic sound waves to audible waves via frequency shift modulation
- Minimal delay between detection of infrasound and audible response; operates essentially in real time
- Output volume proportional to infrasonic wave amplitude
- Output pitch deviation indicates infrasonic wave polarity
- Optional digital filter to compensate for typical low-frequency microphone roll-off
- Quick response time allows listener to determine nature of infrasound (pulsed, continuous) as well as frequency and amplitude
- Operating input frequency range: approximately 1-20Hz
- Power supply: 9V battery, ~60mA current drain (9-15V DC plugpack can also be used)
- Five modes: AM+FM with or without microphone response compensation, AM only with or without microphone response compensation, FM only (fixed amplitude)

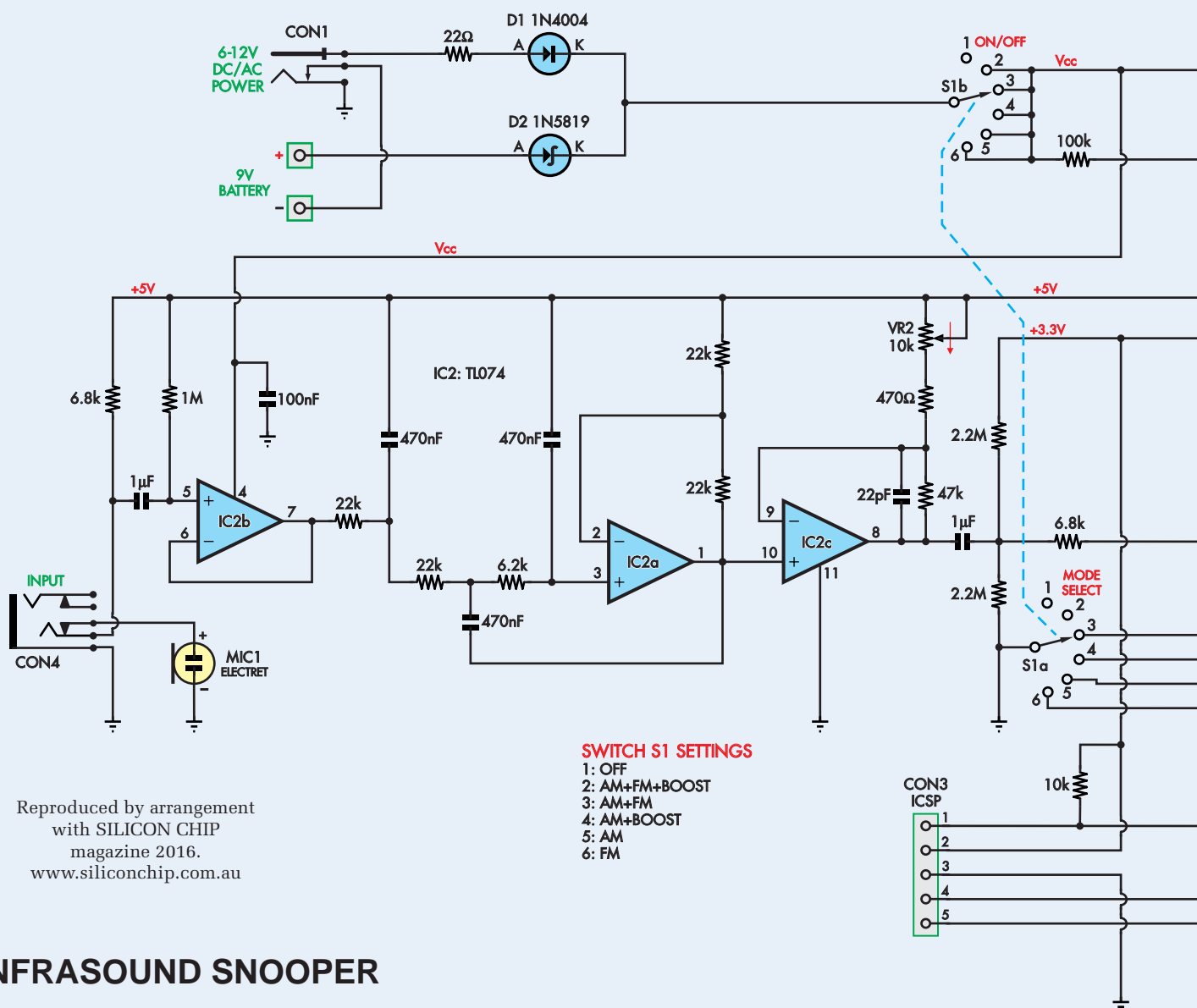

**Fig.1: the complete circuit diagram. The intrasound is picked up by an electret microphone and then buffered, filtered and amplified by IC2b-IC2a before being fed to microcontroller IC1. IC1 digitises the signal and carries out the necessary signal processing before feeding it to DAC IC3. IC3 then feeds gain stage IC2d, which in turn drives the output socket (CON5).**

two (set by the pair of 22k $\Omega$  resistors at its pin 2). The filter is a Butterworth type, which is pretty much flat from DC up to 20Hz, with gain rapidly falling off at higher frequencies.

This is important because we need to apply a fair bit of gain to the infrasonic signals to scale them to an appropriate level for the microcontroller's ADC (~1V RMS). Op amp IC2c provides the requisite gain, which is variable using VR2. So the gain ranges from a minimum of  $6 (47\text{k}\Omega \div (10\text{k}\Omega + 470\Omega) + 1)$  to a maximum of around 100 ( $47\text{k}\Omega \div (470\Omega + W) + 1$ , where W is VR2's wiper resistance). Thus, VR2 acts as the unit's sensitivity adjustment.

The signal must then have its DC bias shifted to suit the ADC of the PIC32MX microcontroller, which runs from a 3.3V regulated rail. Therefore, it is AC-coupled with a  $1\mu\text{F}$  capacitor and biased with a pair of  $2.2\text{M}\Omega$  resistors forming a voltage divider between the 3.3V rail and ground. This sets the DC level at pin 2 of IC1 at around 1.65V. The  $6.8\text{k}\Omega$  resistor protects IC1 from high voltages from IC2 during power-up, power-down and high signal excursions.


IC1 digitises the signal and then applies some DSP-based filtering to correct for low-frequency roll-off due to the two coupling stages and

the microphone's response. To create an audible signal, the infrasound signal is rectified and then used to amplitude modulate a sinewave at about 200Hz.

Some frequency modulation is normally also applied to this waveform, based on the pre-rectification signal. This allows the polarity of infrasonic excursions to be distinguished, based on the difference in resulting signal frequency.

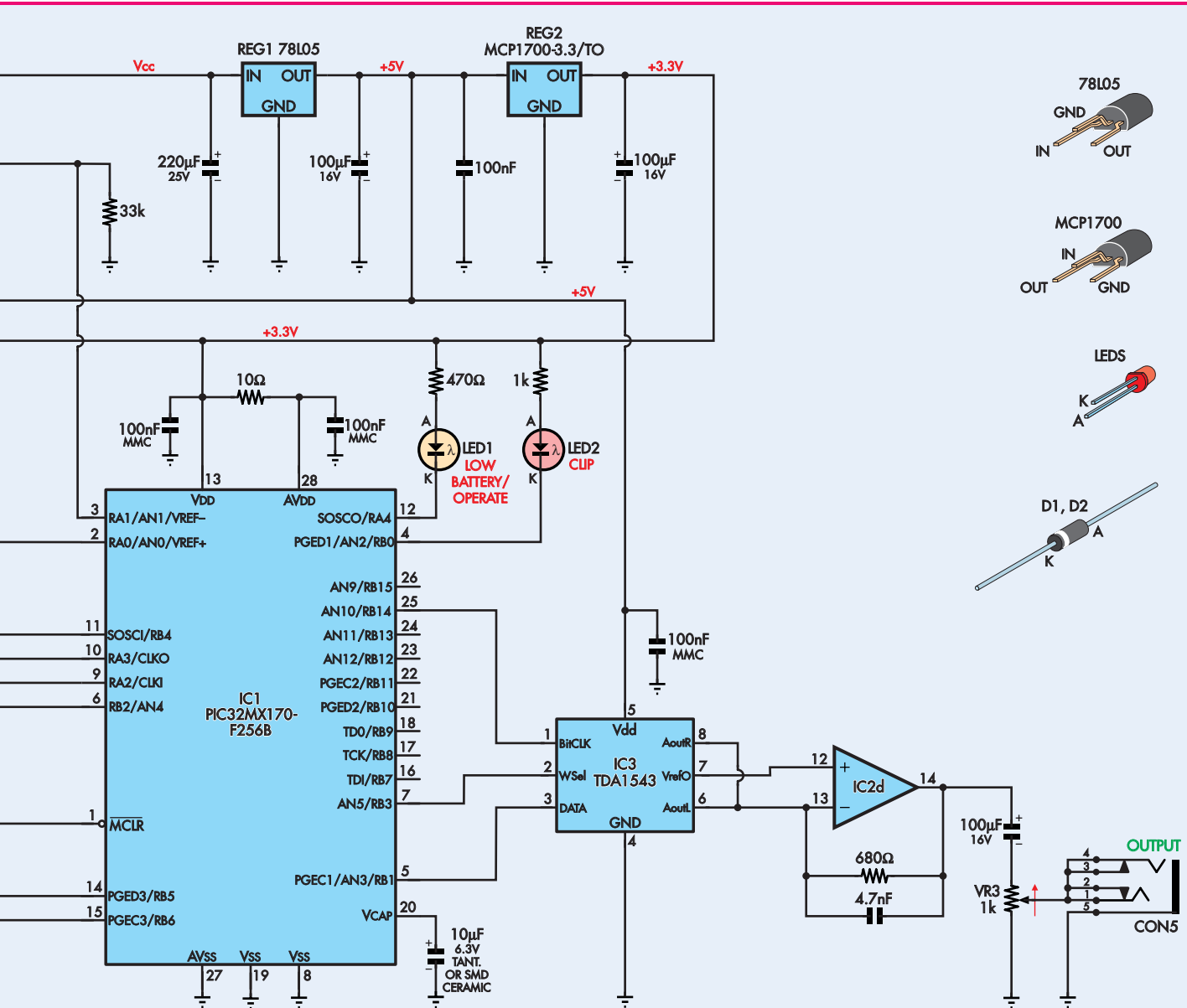This modulated signal appears in digital (I<sup>2</sup>S) format at pins 5, 7 and 25 of IC1. The serial audio data is produced at pin 5 (RB1) which is mapped to one of the two internal SPI peripherals so





that the data stream is uninterrupted. This data is clocked by a signal from pin 25 (RB14/SCK1). The left/right 'word' clock is produced at pin 7 (RB3), also by the SPI peripheral, using its audio framing feature.

These three signals pass to IC3, a TDA1543 16-bit oversampling DAC. We've used this chip for a number of reasons: it's available in an 8-pin DIL package that is easy to solder; it runs from a single 5V rail; it's quite cheap; it's easy to interface to and its audio performance is respectable.

Its outputs at pins 6 and 8 are current sink stages and since we only need a mono signal, they are simply


connected together, filtered (to remove the digital aliasing artefacts) and converted to a voltage by remaining op amp IC2d. The 680Ω resistor sets the output voltage swing.

IC2d's pin 12 non-inverting input is connected to the 2.2V reference voltage which sets the DC level of the resulting signal. The Vref (pin 7) of IC3 has a dual purpose; the current drawn from this pin is internally amplified and added to the current sink by the left and right output pins. However, in this case, the circuit works best with no extra current sink, hence there is no load on the Vref pin.

The DC in IC2d's output is blocked by a 100µF electrolytic capacitor and biased to ground by the track of VR3, the volume potentiometer. The headphones or earphones are connected to its wiper via CON5 with no extra buffering. This is a relatively crude system, but it works well enough. The main purpose is to allow the user to reduce the output to a comfortable level when used in conjunction with sensitive earphones.

## Power supply

The *Infrasound Snooper* is designed to run off a 9V battery, but a 9-15V DC plugpack can be used. The supply current therefore flows through one of two

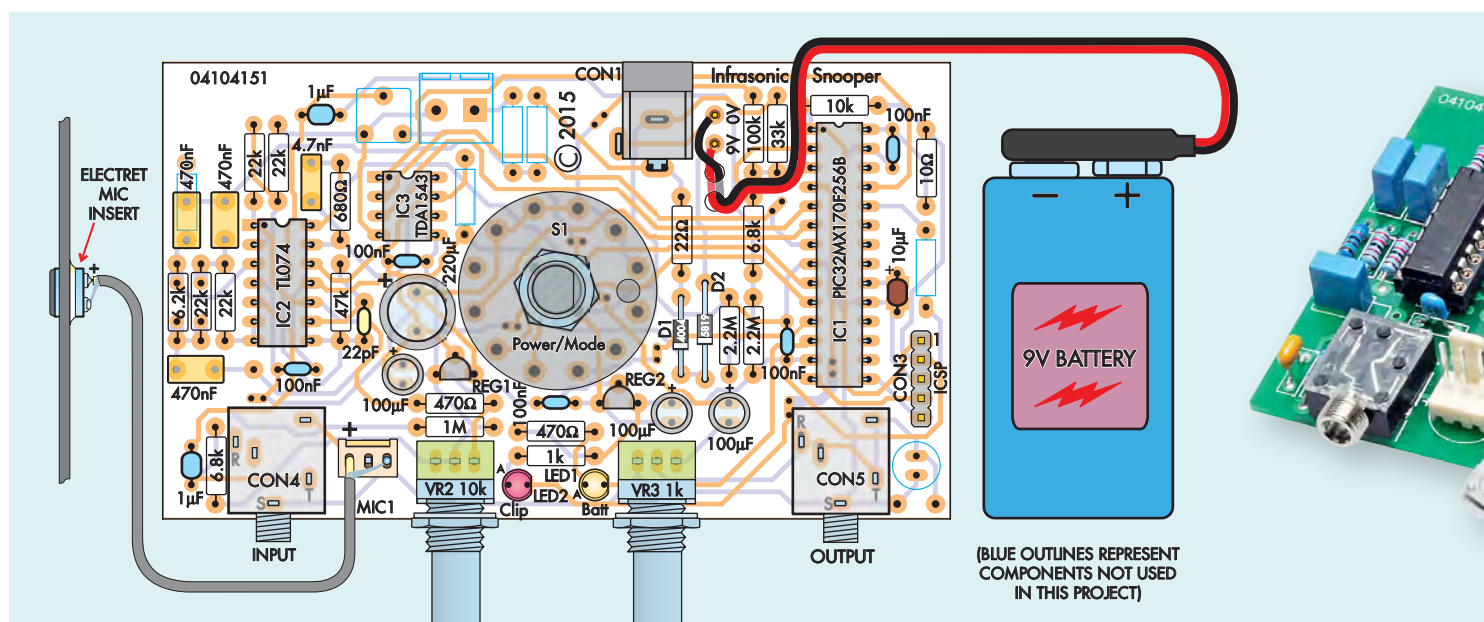

**Fig.2: follow this parts layout diagram to build the PCB. Take care to ensure that all polarised parts are correctly oriented and use a socket for microcontroller IC1. Sockets are optional for IC2 and IC3.**

reverse-polarity protection diodes, D1 for the plugpack or D2 for the battery. D2 is a Schottky diode to minimise voltage drop and hence extend battery life.

Rotary switch S1 acts as both the power and mode switch. One pole connects the power supply directly to IC2 as well as to the input of REG1. This regulator provides the 5V rail for DAC IC3, the electret supply and for signal biasing in the input filter. It also feeds REG2, a 3.3V low-dropout regulator that powers microcontroller IC1.

The other pole of S1 is connected to pins 6, 9, 10 and 11 of IC1, which are configured as inputs with internal pull-up currents enabled. Thus, IC1 can sense which position S1 is in by determining which of these inputs is pulled low. If none are, then the switch must be in the second position, as the circuit is not powered in the first position.

IC1 monitors the battery voltage via a 4:1 divider (100k $\Omega$ /33k $\Omega$ ), digitising the resulting voltage at its AN1 analogue input (pin 3). If the battery voltage is low (<7V), it illuminates the low-battery LED (LED2) via its pin 12 output (RA4). The 470 $\Omega$  current-limiting resistor sets the LED current to around 2-3mA.

Similarly, IC1 can light LED1 if there is an input signal overload, using its pin 4 output. The red LED is a little more efficient, so it operates at a lower current with a 1k $\Omega$  current-limiting resistor, resulting in around 1-1.5mA flowing.

CON3 is a programming header for IC1 (if required) with a 10k $\Omega$  pull-up resistor on its MCLR pin (pin 1) preventing unexpected reset events. IC1's analogue supply at pin 28 is low-pass filtered with a 10 $\Omega$  resistor and 100nF bypass capacitor, while a 10 $\mu$ F capacitor at pin 20 is required for its internal core regulator.

## Construction

All the parts except for the electret microphone are mounted on a double-sided PCB, which is available from the *EPE PCB Service*, coded 04104151 (104 × 60.5mm). This can be clipped into a standard UB3 jiffy box.

Fig.2 shows the parts layout on the PCB. Start by fitting the fixed resistors. Table 1 shows the resistor colour codes, although it's better to check the values using a DMM. Note that since the same PCB was used for the *Low Frequency Distortion Analyser* (EPE, April 2016) there are a number of component positions which are not populated (including some resistor locations).

Diodes D1 and D2 can go in next, noting that D1 is a 1N4004 while D2 is a 1N5819. Be sure to orient them correctly, with their striped cathode ends towards the bottom edge of the PCB.

Follow with the IC socket(s). It's a good idea to use a socket for microcontroller IC1, but they are not really necessary for IC2 and IC3. Instead, IC2 and IC3 can be soldered directly to the PCB for greater long-term reliability. Either

way, make sure that the pin 1 notch/dot of each IC goes towards the top of the board. This is vital if soldering the ICs in without sockets, since you can't easily remove them once they're in!


The two jack sockets are next on the list, followed by the ceramic and MKT capacitors. REG1 and REG2 can then go in, but be careful not to get them mixed up as they look similar. Their leads will need to be cranked out using needle nose pliers to suit the pad spacing on the PCB.

Now solder the DC socket in place, followed by the electrolytic capacitors. Be sure to orient them correctly, with the longer (positive) leads towards the top edge of the PCB (see Fig.2). If using a tantalum type rather than an SMD ceramic for the 10 $\mu$ F capacitor, it too is polarised and can go in now.

Now fit the two 9mm potentiometers. They're different values so don't get them mixed up (the 1kΩ pot may be marked '102' and the 10kΩ pot '103'). The polarised 3-pin header (for the microphone) can then be fitted with its keyway tab oriented as shown.

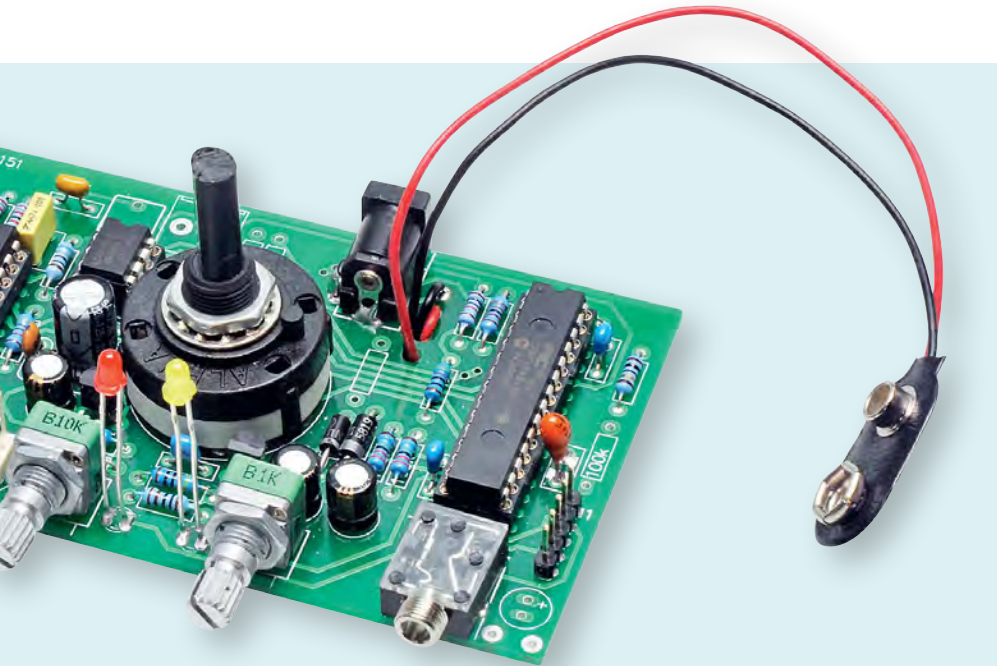The battery snap is next. Pass its leads through the two strain relief holes before soldering its leads to their respective pads on the top of the PCB, as shown in Fig.2. You can then pull the leads back through the holes to reduce the slack. Note that they will probably be a tight fit, to provide the necessary strain relief.





This view shows the completed PCB assembly. Note how the battery snap leads are looped through strain relief holes before being soldered to the top of the PCB.

The two 3.5mm switched jack sockets (CON4 and CON5) can now be mounted. Check that they sit flush against the PCB before soldering their pins. CON3, the ICSP header, can then go in – but can be omitted if you're using a pre-programmed microcontroller.

Rotary switch S1 is mounted after first cutting its shaft so that it's 30mm long, as measured from the top surface of the main body. This can be done using a hacksaw and the end of the shaft then cleaned up with a file to remove any burrs. It must be installed with its polarity-indicating plastic post oriented as shown on Fig.2 (ie, at the three o'clock position). Again, make

sure it's pushed down flat against the board before soldering its pins.

Finally, solder the two LEDs in place. The longer leads are the anodes and go into the pads indicated with 'A' on Fig.2. Tack solder these in place at full lead length; you can adjust the height and solder them properly once the box has been prepared.

## Microphone cable

The next job is to make up a cable to connect the microphone. That's done using a 70mm length of light-duty Fig.8 cable that is terminated at one end in a 2-way polarised header.

Begin by removing about 3mm of insulation from the leads at each end

## Table 2: Capacitor Codes

Value	$\mu\text{F}$ Value	IEC Code	EIA Code
1 $\mu\text{F}$	1 $\mu\text{F}$	1u0	105
470nF	0.47 $\mu\text{F}$	470n	474
100nF	0.1 $\mu\text{F}$	100n	104
4.7nF	.0047 $\mu\text{F}$	4n7	472
22pF	NA	22p	22

of the cable, then carefully solder and crimp the leads at one end to the header crimp pins. That done, the crimp pins can be slid into the header (the tang goes into the narrow channel) until they lock into position.

The next step is to determine which lead on the electret microphone is the positive and which is the negative. This may be marked, but if not, use your DMM (set to ohms) to determine which lead is connected to the case – this is the negative (ground) lead.

Next, slip 5mm-lengths of 3mm-diameter heatshrink over the insulation at the end of the cable leads, then solder these two leads to the microphone. Make sure that the positive lead from the header goes to the electret positive (the positive side is marked on the PCB, adjacent to CON4).

Once the two leads have been soldered, slip the heatshrink sleeves over the solder connections and shrink them down to provide strain relief (see photo).


## Testing

If using sockets, plug in the ICs, with their pin 1 dot or notch aligned as shown in Fig.2. If IC1 hasn't already


## Table 1: Resistor Colour Codes

	No.	Value	4-Band Code (1%)	5-Band Code (1%)
<input type="checkbox"/>	2	2.2M $\Omega$	red red green brown	red red black yellow brown
<input type="checkbox"/>	1	1M $\Omega$	brown black green brown	brown black black yellow brown
<input type="checkbox"/>	1	100k $\Omega$	brown black yellow brown	brown black black orange brown
<input type="checkbox"/>	1	47k $\Omega$	yellow violet orange brown	yellow violet black red brown
<input type="checkbox"/>	1	33k $\Omega$	orange orange orange brown	orange orange black red brown
<input type="checkbox"/>	4	22k $\Omega$	red red orange brown	red red black red brown
<input type="checkbox"/>	1	10k $\Omega$	brown black orange brown	brown black black red brown
<input type="checkbox"/>	2	6.8k $\Omega$	blue grey red brown	blue grey black brown brown
<input type="checkbox"/>	1	6.2k $\Omega$	blue red red brown	blue red black brown brown
<input type="checkbox"/>	1	1k $\Omega$	brown black red brown	brown black black brown brown
<input type="checkbox"/>	1	680 $\Omega$	blue grey brown brown	blue grey black black brown
<input type="checkbox"/>	2	470 $\Omega$	yellow violet brown brown	yellow violet black black brown
<input type="checkbox"/>	1	22 $\Omega$	red red black brown	red red black gold brown
<input type="checkbox"/>	1	10 $\Omega$	brown black black brown	brown black black gold brown

# Constructional Project

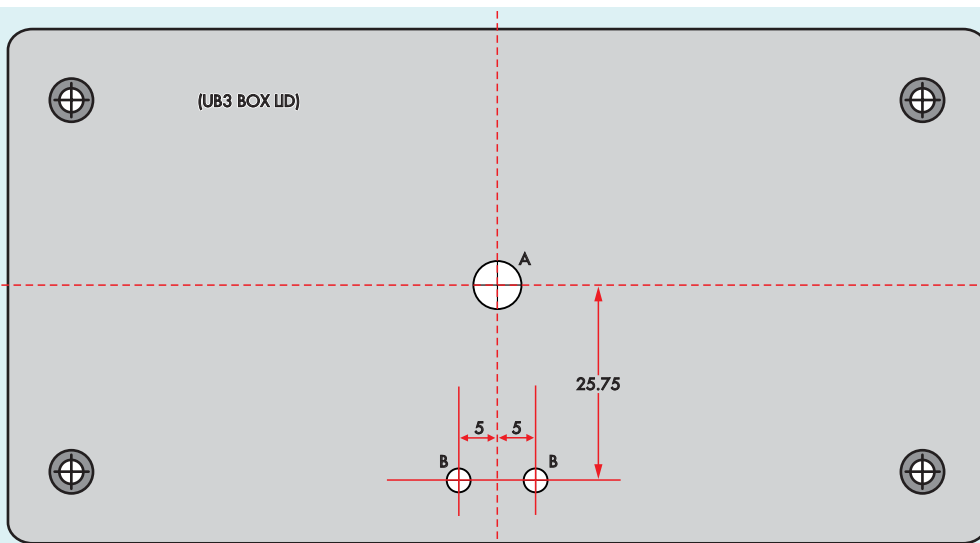

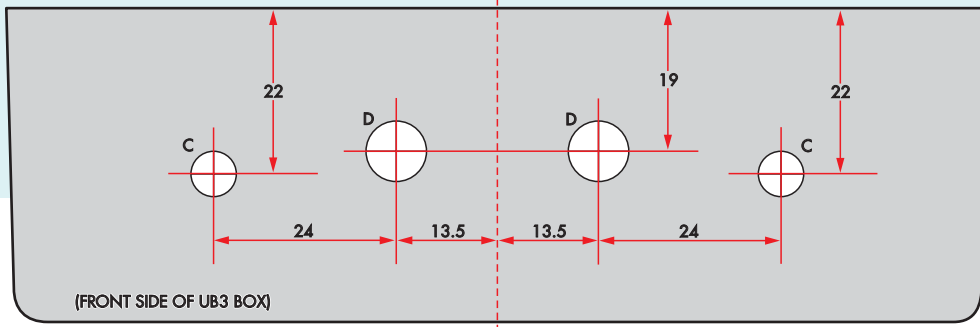HOLE SIZES: HOLE A 6.5mm DIAM, HOLES B 3.0mm DIAM HOLES C 6.0mm DIAM, HOLES D 8.0mm DIAM



ALL DIMENSIONS IN MILLIMETRES



Fig.4: this front panel artwork can be copied and used direct or a PDF version can be downloaded from the EPE website and printed onto photo paper or onto Dataplot/Dataflex label paper.

been programmed (you can buy a programmed micro from the SILICON CHIP Online Shop), do it now via CON3. External power can be supplied from the programmer (eg, a PICKit 3).

Once all the ICs are in place, you can test the unit as follows:

- 1) Rotate S1 to the off position (fully anti-clockwise), then connect the battery.

- 2) Rotate S1 one step clockwise and check that the yellow LED flashes briefly, then periodically.
- 3) Turn VR2 and VR3 all the way down and connect a pair of headphones or earphones to the unit.
- 4) Turn VR2 and VR3 up slowly and blow on the microphone insert. After turning the potentiometers up sufficiently, you should hear the

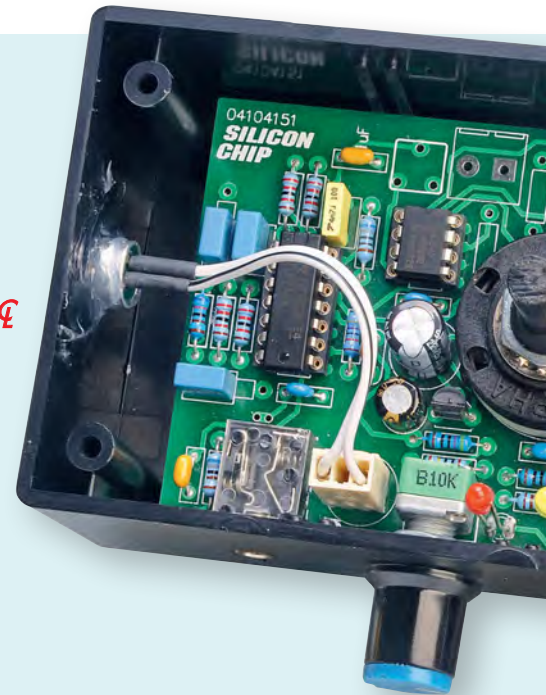


Fig.3 (left): use this full-size template to drill the holes in the lid and front side of the UB3 case.

modulated signal from the low frequency components of this sound. With the gain up high, if you blow hard enough, the overload (red) LED may light.

- 5) Switch S1 to the other positions and check that the sound produced by the unit changes.
- 6) Switch the unit off and remove the battery.

If it doesn't work as expected, carefully inspect the solder joints under magnification. Also check that the components are all in their correct positions and that the polarised parts (diodes, ICs, electrolytic capacitors) are oriented correctly.

## Case preparation

If fitting the PCB into a UB3 jiffy box, you will need to drill four holes in the side of the case for the microphone input and headphone output sockets, plus the gain and volume adjustment knobs. The bottom section of Fig.3 shows the relevant drilling template – this can be copied (or downloaded from the EPE website and printed out) and temporarily stuck to the side of the case (eg, using double-sided tape).

Note that the top edge of the template must be aligned with the top edge of the box and centred horizontally.

The holes must be accurately placed. Start by drilling pilot holes (eg, 3mm) in each location and then enlarge them using larger drill bits, a stepped drill





Above: the PCB is a snapfit inside the case; the battery sits on a piece of non-conductive foam (see text).

bit or a tapered reamer. Clean up any burrs, then remove the nuts from the two jack connectors, screw the nuts and washers all the way onto the potentiometers and check that the connectors and pots fit through the holes.

If you want to be able to run the unit from a plugpack, you will also

need to drill a 5.5mm hole in the other side, to allow access to the connector. The same template can be used; simply drill the hole for the power jack centred on the same location as that used for the volume control pot on the opposite side. If in doubt, check the location of the power socket on the board before drilling.

### Fitting the microphone

A hole also has to be drilled in the lefthand end of the case for the electret microphone. The hole should be positioned about 16mm down from the top of the case and centred horizontally. Start by drilling a small pilot hole, then carefully ream the hole out until the microphone is a tight fit.

Once the mic fits, adjust it so that its face is flush with the outside of the case. It can then be secured inside the case using a small amount of neutral-cure silicone adhesive and the assembly placed aside to cure while the case lid is drilled.

### Front panel drilling

Three holes are required in the case lid, for the two LEDs and switch S1. The drilling template is at the top of Fig.3 and it's just a matter of drilling the holes to size and checking that the LEDs and switch shaft fit.

The next step is to make and attach the panel label (Fig.4). This can be copied or downloaded and printed onto photo paper and affixed to the panel using silicone adhesive. Alternatively it can be printed onto Datapol/Dataflex label paper and stuck onto the lid. The three holes are then cut out using a sharp hobby knife.

### Final assembly

Assuming that the silicone around the microphone has cured, the PCB can now be installed in the case, it's just a matter of angling the front of the board down so that the sockets and pot shafts go into their respective holes, then pushing down on the back of the board until it snaps into the integral side-rails. If it won't go in, you may need to enlarge the holes slightly.

Now trial fit the lid. If the LED heights are wrong, you will need to remove the PCB and adjust them accordingly. Once they fit properly, re-solder their leads and re-install the board in the case. The potentiometer nuts can then be wound forwards until they're against the inside face of the case.

Next, rotate S1 to off (fully anti-clockwise), then connect the battery and place it on top of the PCB with a piece of non-conductive foam sandwiched in between. This will prevent

## Parts List

- 1 double-sided PCB, available from the *EPE PCB Service*, coded 04104151, 104 × 60.5mm
- 1 UB3 jiffy box (optional)
- 1 10k $\Omega$  9mm single-gang potentiometer (VR2)
- 1 1k $\Omega$  9mm single-gang potentiometer (VR3)
- 1 28-pin narrow DIL IC socket
- 1 14-pin DIL IC socket (optional)
- 1 8-pin DIL IC socket (optional)
- 1 piece non-conductive foam, approximately 65 × 40 × 8mm
- 1 PCB-mount DC socket (CON1)
- 2 3.5mm switched jack sockets (CON4, CON5)
- 1 2-pole 6-position rotary switch (S1)
- 1 medium-sized knob, to suit S1
- 2 small knobs, to suit VR2 and VR3
- 1 9V battery snap (BAT1)
- 1 9V alkaline battery (BAT1)
- 1 pair headphones or earphones

- 1 5-pin header, 2.54mm pitch (CON3) (optional – see text)
- 1 PCB-mount electret microphone insert
- 1 3-pin polarised header, 2.54mm pitch (CON6)
- 1 3-way polarised header plug
- 1 70mm-length light duty figure-8 cable
- 1 10mm length 3mm-diameter heatshrink

### Semiconductors

- 1 PIC32MX170F256B-I/SP 32-bit microcontroller programmed with 0420415A.HEX (IC1)
- 1 TL074 quad JFET-input op amp (IC2)
- 1 TDA1543 oversampling DAC (IC3)
- 1 78L05 5V regulator (REG1)
- 1 MCP1700-3.3/TO 250mA 3.3V LDO regulator (REG2)
- 1 red 3mm LED (LED1)

- 1 yellow/orange 3mm LED (LED2)
- 1 1N4004 1A diode (D1)
- 1 1N5819 1A Schottky diode (D2)


### Capacitors

- 1 220 $\mu$ F 25V electrolytic
- 3 100 $\mu$ F 16V electrolytic
- 1 10 $\mu$ F 6V tantalum or SMD ceramic (1210/1206/0805)
- 2 1 $\mu$ F 50V multi-layer ceramic
- 3 470nF 63V/100V MKT
- 5 100nF 50V multi-layer ceramic
- 1 4.7nF 63V/100V MKT
- 1 22pF disc ceramic


### Resistors (0.25W, 1%)

2 2.2M $\Omega$	2 6.8k $\Omega$
1 1M $\Omega$	1 6.2k $\Omega$
1 100k $\Omega$	1 1k $\Omega$
1 47k $\Omega$	1 680 $\Omega$
1 33k $\Omega$	2 470 $\Omega$
4 22k $\Omega$	1 22 $\Omega$
1 10k $\Omega$	1 10 $\Omega$

## Constructional Project

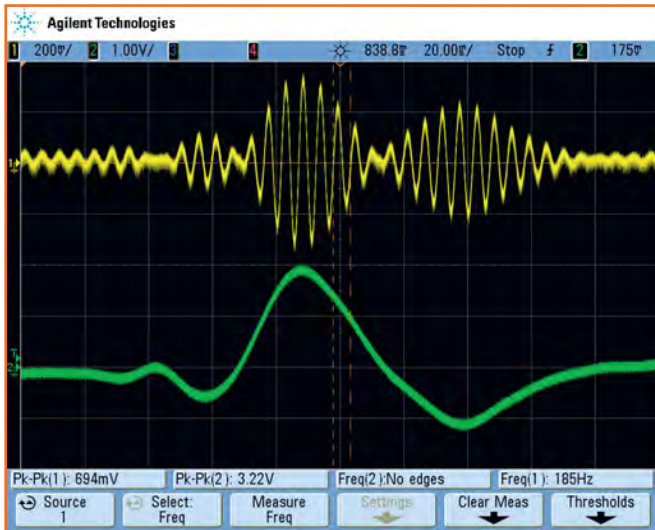

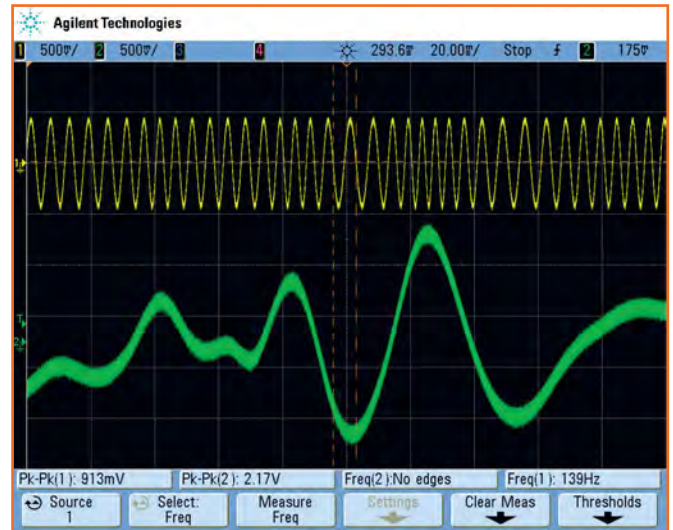**Scope3: amplitude modulation-only mode.** The output frequency is fixed at around 185Hz and only its amplitude varies, increasing for either polarity of infrasound pressure wave excursion. Each waveform shown here is at maximum sensitivity and this is how the unit should be used unless it is overloading due to intense infrasound.



**Scope4: frequency modulation mode.** The signal amplitude is constant and high (generally the output volume should be turned down in this mode) and only the frequency changes in response to infrasonic waves picked up by the microphone. As before, the frequency increases for one polarity of wave and decreases for the other.

shorts and also stop the battery from rattling around inside the case.

Finally, screw the lid in place, then attach the knobs for S1, VR2 and VR3 (the jack socket nuts aren't required).

### Using it

Typically, you would use the device with the gain somewhere near maximum and the volume adjusted to a level which is not excessive for the headphones or earphones being used. Due to the way the volume control works, this is likely to be somewhere near maximum too, although lower settings may be necessary for 'in-ear' earphones.

Sealed headphones or in-ear phones have the advantage that you can more easily determine the level of infrasound emitted from sources that also

produce audible frequencies. That's because they will do a better job of blocking those audible frequencies out and allow you to more clearly hear the output of the device.


An example of this would be a door slamming shut. This can generate quite a significant infrasonic pulse, but it may be difficult to hear the unit's response against the audible noise of the door slamming. Other sources which can be used to test the unit include large air-conditioning units, passing trucks and large idling engines.

When using one of the frequency modulation (FM) modes, it is possible to determine the polarity of an infrasonic pulse. One polarity will produce a sound which increases in frequency

while the other will produce a sound that decreases in frequency. Regular pulses from the same source will normally have a consistent polarity. Typically, a compression wave will precede an expansion wave.



Finally, note that a wind shield may be necessary for the microphone if the unit is used outdoors. As with the March 2014 *Infrasound Detector*, the windshield from a dynamic microphone could be used.

Alternatively, a separate external electret microphone (plugged into CON4) could be used instead of the inbuilt electret. Just make sure it has the required high sensitivity, a good low-frequency response and is able to operate from the ~0.5mA bias current supplied by the unit.

**HAMMOND  
MANUFACTURING®**

**Enclosures  
for the hobbyist**

- Raspberry Pi specific
- Arduino specific
- plastic
- die-cast aluminium
- many designs and sizes



**+ 44 1256 812812 • sales@hammondmfg.eu • www.hammondmfg.com**



# Win one of three Microchip PICkit 3 Debug Express Kits

**EVERYDAY PRACTICAL ELECTRONICS** is offering its readers the chance to win one of three Microchip PICkit™ 3 Debug Express Kits. The PICkit 3 Debug Express allows debugging and programming of PIC and dsPIC Flash microcontrollers at a low price point using the powerful graphical user interface of the MPLAB integrated development environment (IDE). The PICkit 3 Debug Express works with 8- and 16-bit PIC MCUs and dsPIC digital signal controllers (DSCs), and will support 32-bit PIC MCUs at a later date.

The PICkit 3 Debug Express kit includes: PICkit 3 debugger and programmer probe, 44-pin demo board populated with a PIC18F45K20 MCU, free MPLAB® IDE and free version of the MPLAB C Compiler for PIC18 MCUs. All this is supported by easy-to-understand lessons and tutorials, and a host of other software utilities, examples with source code and full documentation.



**WORTH  
\$69.99**

**(approx. £48.65)**

**EACH**

**February 2016 ISSUE WINNER**

**Mr Ian Mills, who works at MBDA, Wigan, UK**

**He won a PICDEM Lab II Development Platform valued at £65.00**


## HOW TO ENTER

For your chance to win a Microchip PICkit 3 Debug Express kit, visit:

<http://www.microchip-comps.com/epe-pickit3debug> and enter your details in the online entry form.
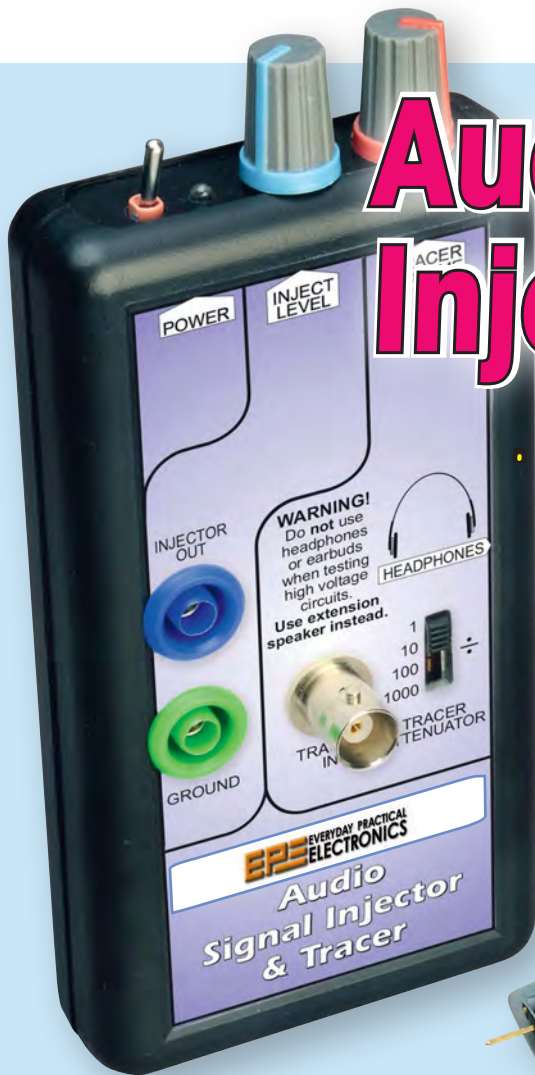
## CLOSING DATE

The closing date for this offer is 30 June 2016.




# Audio Signal Injector and Tracer

... with optional tiny add-on RF probe

This *Audio Signal Injector/Tracer* is ideal for troubleshooting AM radio and audio circuits. It comprises a 1kHz oscillator (the *Injector*) and an in-built preamp and amplifier with a headphone jack (the *Tracer*) so you can trace signals right through an amplifier or radio circuit to locate faults.

By JOHN CLARKE

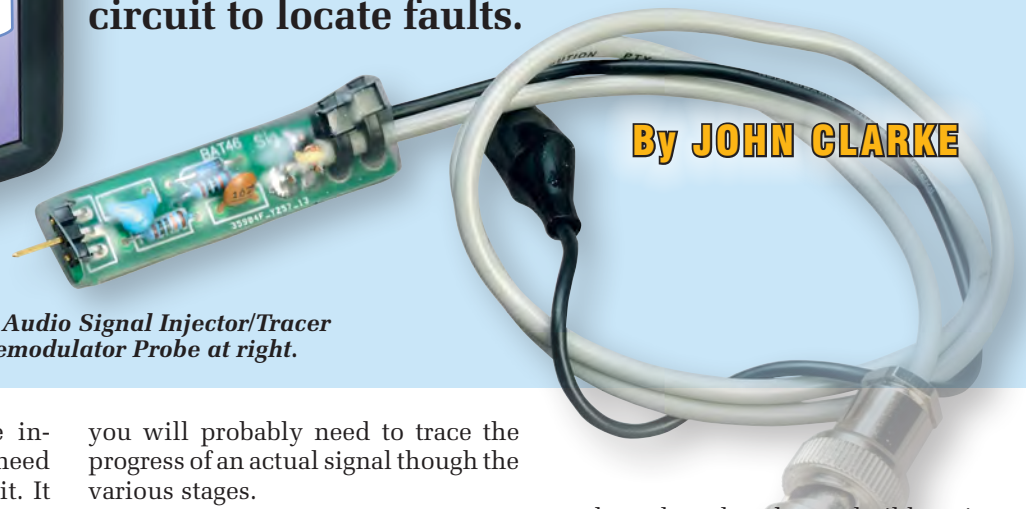This photo shows the complete *Audio Signal Injector/Tracer* together with its optional *RF Demodulator Probe* at right.



AT SOME STAGE, everyone involved in electronics will need to find a fault in an audio circuit. It might be a circuit you have just built, a repair job for a friend or a job to be done in your workplace. And while you can often check voltages if you have a circuit diagram, sooner or later

you will probably need to trace the progress of an actual signal through the various stages.

For example, you might feed a signal into the input and then find that it disappears as it feeds through a capacitor. The obvious conclusion would be that the capacitor is faulty (open) or it has not been properly soldered into circuit.

To do this sort of fault-finding, you need a suitable signal (one you can hear) and a small amplifier so you can listen to the signal at various stages in the amplifier or AM radio being tested. So, our *Audio Signal Injector/Tracer* has a 1kHz oscillator as the *Injector* and a small amplifier as the *Tracer*.

AM radio adds an extra complication because you need to listen to a modulated radio signal as it goes from stage to stage in the circuit. For that you need an optional RF demodulator

probe and we show how to build one in the next article of this issue – it's tiny!

Mind you, if you are repairing an amplifier, you may not need the *Injector's* audio signal, provided you have a CD player or even a smart phone which has music tracks.

On the other hand, a music signal is not always ideal if you are using an oscilloscope and want to see if the signal becomes distorted at a particular stage in the circuit. In that case, you might find the *Injector* more convenient as you trace a signal of known shape through the circuit.


As mentioned, our *Injector* is a 1kHz oscillator and you can see the shape in the scope grab designated 'Scope 1'. It looks a bit like a sinewave, but is actually a somewhat 'rounded' square wave. It has a maximum amplitude of
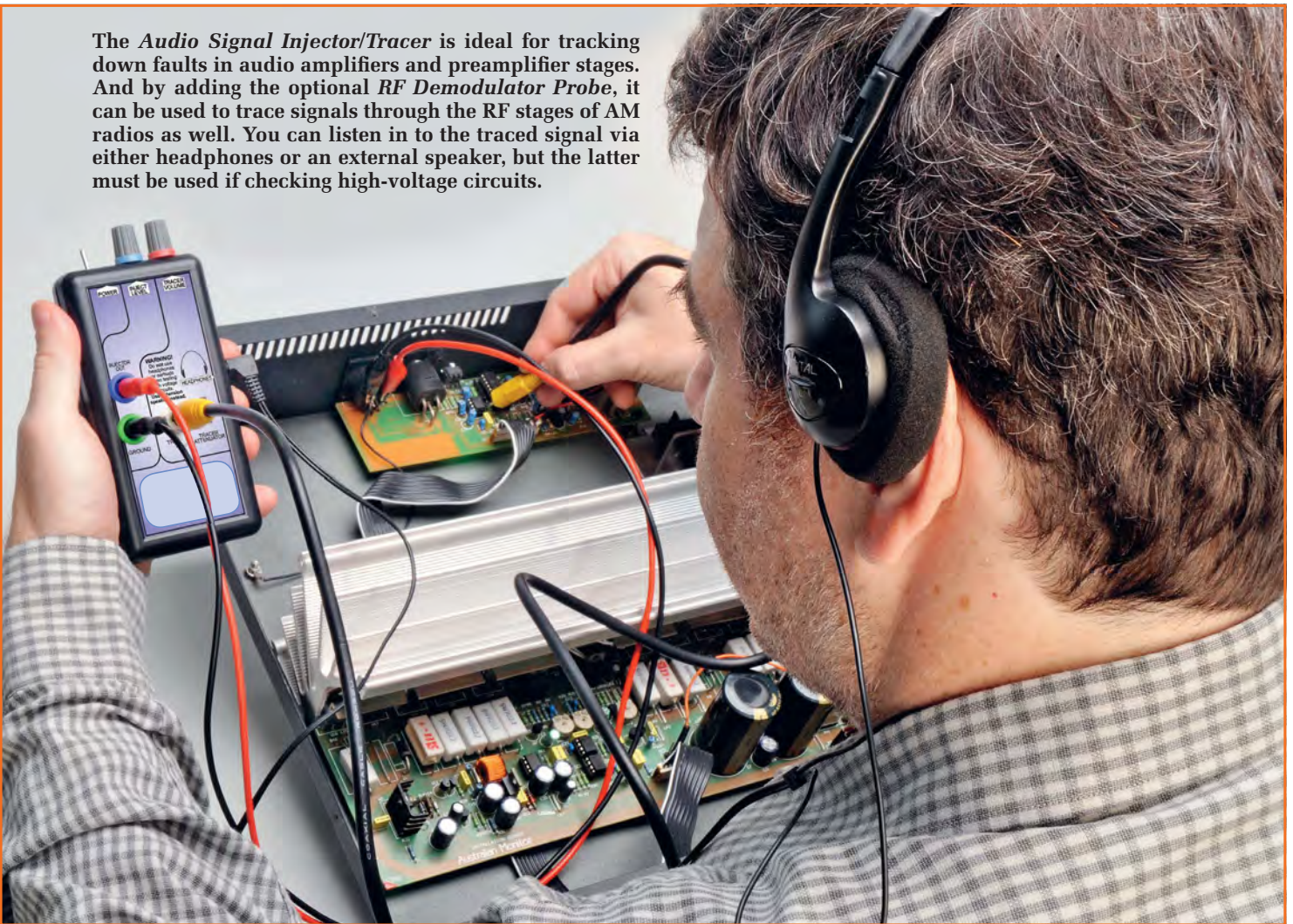
## Main Features

- Hand held and battery powered
- 1kHz injector output
- Adjustable injector level
- Tracer input attenuator
- Tracer volume control
- Audio output to headphones or small speaker
- Low battery indication
- Optional RF probe for AM modulation detection



The *Audio Signal Injector/Tracer* is ideal for tracking down faults in audio amplifiers and preamplifier stages. And by adding the optional *RF Demodulator Probe*, it can be used to trace signals through the RF stages of AM radios as well. You can listen in to the traced signal via either headphones or an external speaker, but the latter must be used if checking high-voltage circuits.



about 2V RMS but it can be adjusted down to just few millivolts.

This means it will cover virtually all signal tracing situations, from sensitive audio preamplifiers and the audio sections of AM/FM radios, right up to high-powered guitar and public address amplifiers.

Then we come to the *Signal Tracer*. It needs a small amplifier to listen to small signals in sensitive circuits, but it also needs an input attenuator so that it is not overloaded by the much larger signals, perhaps 50V or more, that you might find in a high-power amplifier. You also need a volume control so that your ears are not blasted as you step through a circuit.

Finally, both the *Injector* and *Signal Tracer* need to be protected from any high voltages that may be present in a solid-state or valve circuit. If you feed the *Injector* into a circuit operating at 300V DC, for example, you

don't want it to be blown to shreds and by the same token, if you touch the *Tracer* probe onto a similar high-voltage point, you don't want it to be 'cooked'. Our circuit takes care of those possibilities.

Our *Injector/Tracer* is housed in a compact plastic case with an internal battery compartment. It has a pair of jack sockets for the output of the *Injector* and a BNC socket for the

input to the *Tracer*. Next to that socket lies a 4-position slide switch for the Attenuator, which has settings of 1:1, 1:10, 1:100 and 1:1000.

### Input impedance

The input impedance of the *Tracer* is rather high, varying between about 10M $\Omega$  and 6.45M $\Omega$ , depending on the setting of the input attenuator. This means that the impedance of the

## Specifications

**Power:** 9V at 2.3mA

**Tracer input impedance:** ~6.45M $\Omega$  to 10M $\Omega$ , depending on attenuator setting

**Tracer signal gain:** adjustable from 2x to 20x

**Tracer attenuator:** 1:1, 1:10, 1:100 and 1:1000

**Tracer signal frequency response:** 70Hz to 3kHz

**Injector signal:** 1kHz rounded square-wave


**Injector signal level:** adjustable from 0-2V RMS (5.6V peak-peak) with a 9V supply

**Headphone output:** 6.6V peak-peak maximum into 16 $\Omega$  with a 9V supply

**Test circuit DC voltage:**  $\pm$ 300V DC maximum recommended



# Constructional Project

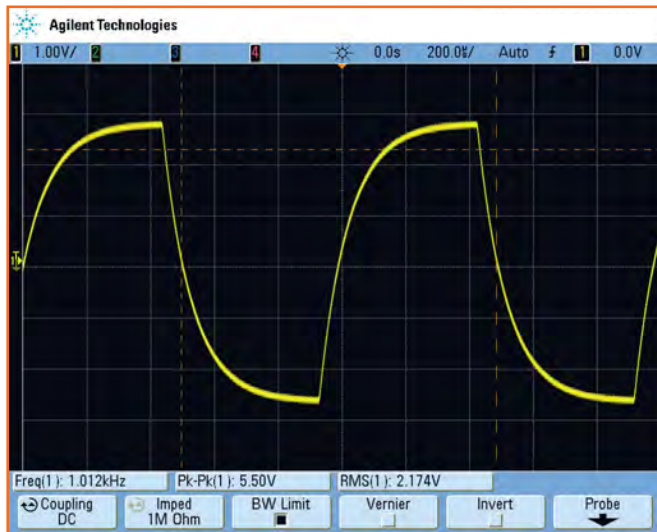

**Scope 1:** the 1kHz waveform generated by the oscillator looks a bit like a sinewave but is actually a 'rounded' square wave. It has a maximum amplitude of about 2V RMS but can be adjusted down to just a few millivolts.

*Tracer* will not load down or affect the operation of the circuit being tested. The high-impedance input also means that the *Tracer* probe can be used to directly test ceramic (crystal) phono cartridges or piezoelectric pick-ups on musical instruments such as a violins.

To connect a signal to the *Tracer* you can use a 1:1 oscilloscope probe or any shielded cable with a BNC plug at one end and a suitable connector at the other, such as an RCA plug or a pair of alligator clips. More about this later in the article.

The on/off switch, a power LED and the two knobs for the *Injector* level and *Tracer* volume controls are at one end of

the case, while the 3.5mm headphone jack is on the side, adjacent to the 4-position Attenuator switch.

## Circuit description

Let's now take a look at the circuit of the *Audio Signal Injector/Tracer* – see Fig.1.

As shown, it's based on an LMC-6482AIN CMOS dual rail-to-rail op amp and a handful of other components. One op amp is used for the *Signal Injector* while the other is used for the *Tracer*. The output frequency of 1kHz is set by the 100kΩ resistor and 6.8nF capacitor connected to pin 2, the non-inverting input.

The three resistors connected to the pin 3 inverting input set the threshold voltage (at pin 3) at 1/3V<sub>cc</sub> or 2/3V<sub>cc</sub>, depending on whether the output of IC1a is high or low. So with V<sub>cc</sub> = 9V, the input (threshold) voltage at pin 3 will be either +3V or +6V.

When power is applied to the circuit, the 6.8nF capacitor at pin 2 will be discharged (ie, 0V), so pin 2 will be lower than pin 3. Therefore, the output at pin 1 will be high (+9V) and this charges the 6.8nF capacitor via the 100kΩ resistor between pins 1 and 2. When the capacitor voltage rises just above 6V, pin 2 becomes higher than pin 3 and so the op amp's pin 1 output switches low, to 0V (remember, this is a 'rail-to-rail' op amp).

So now pin 3 is at 3V and the capacitor discharges via its 100kΩ resistor until pin 2 is just below pin 3, whereupon the pin 1 output goes high again



**Scope 2:** this scope grab shows the Schmitt trigger operation of IC1a. The yellow trace shows the charging and discharging of the 6.8nF capacitor from 3V to 6V, while the green trace shows the resultant square-wave output at pin 1.

to recharge the capacitor. This continuing cycle generates a 1kHz square wave that is filtered using a 6.8kΩ resistor and 22nF capacitor to give a 'rounded' waveform, as shown in Scope 1.

The Schmitt trigger operation of IC1a is demonstrated in Scope 2, which shows the charging and discharging of the 6.8nF capacitor from 3V to 6V in the yellow trace. The lower green trace shows the resultant square-wave output at pin 1. Note that the amplitude of the square-wave is shown as 9.8V – we used a fresh 9V battery.

Potentiometer VR1 connects across the 22nF capacitor to provide the *Injector* level control. This is AC-coupled to the output terminal via a 100nF 630V capacitor. We specified a high voltage rating for this capacitor so that the *Injector* output can be connected to a high voltage on the circuit under test without damage.

For the same reason, diodes D2 and D3 clamp any high voltage from an external circuit (eg, a valve radio being tested) at the wiper of VR1 to 0.7V above or below the 9V and 0V supply rails. The 10MΩ resistor across the 100nF capacitor is there to discharge the capacitor when it is disconnected from the circuit under test. The 1kΩ resistor in series with the *Injector* output limits peak current to the clamping diodes.

## Tracer circuit

The input signal from the BNC socket is fed to 4-way slider switch, S2 and the attenuator resistors. The resistors


## Warning!

When using the *Audio Signal Injector/Tracer* with high-voltage circuitry (eg, in a valve radio), take care not to touch any part of the circuit with your hand. Always treat the circuit as though it has mains voltage present.

As stated in the article, use a small extension speaker rather than headphones when using the unit with high-voltage circuitry. Small non-powered extension speakers are available for use with iPods and similar MP3/MP4 players.

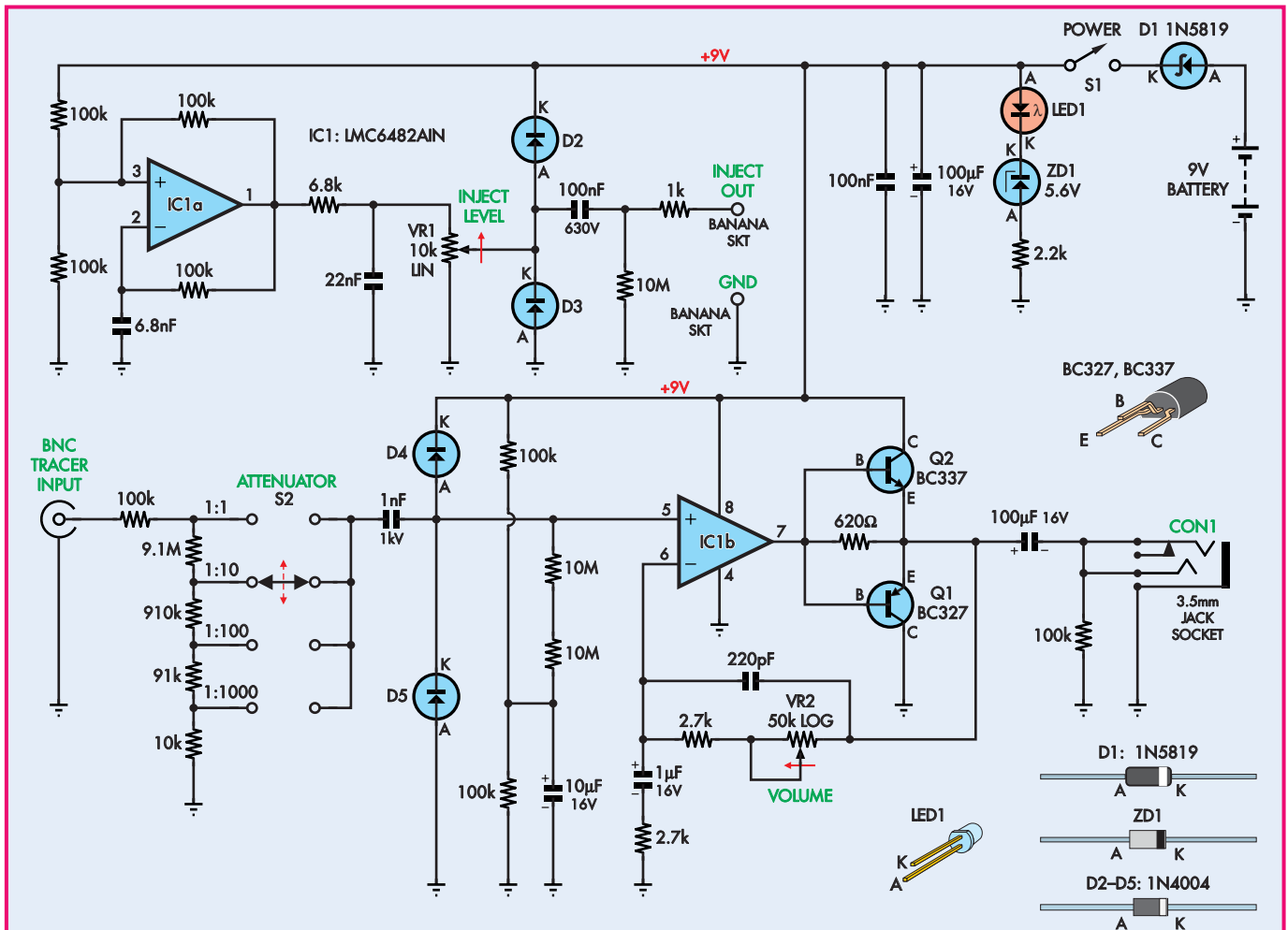The use of a small speaker will remove the possibility of deafening clicks or even a high-voltage shock should there be a fault within the *Audio Signal Injector/Tracer* or if the earth lead becomes disconnected.





## AUDIO SIGNAL INJECTOR & TRACER

Fig.1: the circuit is based on dual op amp IC1. IC1a operates as a Schmitt trigger oscillator and this generates the injector signal, with VR1 setting the output level. The traced signal is fed in via a switched attenuator and then fed to op amp IC1b. Its output signal is then buffered by Q1 and Q2 and fed to CON 1, while VR2 sets the op amp gain.

provide four division ratios of 1:1, 1:10, 1:100 and 1:1000.

Following S2, the signal is coupled via a 1nF 1kV ceramic capacitor to the pin 5 non-inverting input of IC1b. This is tied via two series-connected 10MΩ resistors to a voltage divider (two 100kΩ resistors) which provides a reference at 4.5V – ie, half the 9V supply.

Diodes D4 and D5 clamp any high voltage input signals to 0.6V above or below the 9V supply rails.

IC1b is connected as a non-inverting amplifier and its pin 7 output drives a complementary emitter-follower stage using transistors Q1 and Q2. These provide a buffered output to the headphone socket via a 100μF coupling capacitor.

Note that the emitter follower output stage is operated with no quiescent current, but is within the negative feedback loop of the op amp to minimise crossover distortion.

The 50kΩ volume control (VR2) is also in the op amp's feedback loop, connected in series with a 2.7kΩ resistor. In conjunction with the 1μF capacitor and series 2.7kΩ resistor from pin 6 to 0V, this allows the AC gain to be varied from between two and 20. The DC gain is unity, by virtue of the 1μF capacitor.

Note that while the amplifier is mainly intended to drive headphones, it can also be used to drive a small speaker and we recommend this if you are doing signal tracing in a high-voltage circuit which might cause deafening clicks when you touch the probe on high voltage points.

### Power supply



As already noted, the circuit operates from a 9V battery, fed in via toggle switch S1. Diode D1 gives protection if the battery is inadvertently

connected the wrong way around. A high-intensity red LED is used for power indication. It is bright when the supply is at 9V, but drops to a dim glow when the battery is flat, by virtue of ZD1, a 5.6V zener diode in series with the LED.

When the battery is fresh, ie, putting out 9V or maybe as much as 10V, we will have 1.8V across the red LED, 5.6V across ZD1 and 1.6V or more across the 1kΩ resistor, so that 1.6mA or more flows through LED1. As the voltage falls, the voltage across the 1kΩ resistor also falls. At a battery voltage of 7.4V or less, there is very little voltage across the 1kΩ resistor and so LED1 will be dim.
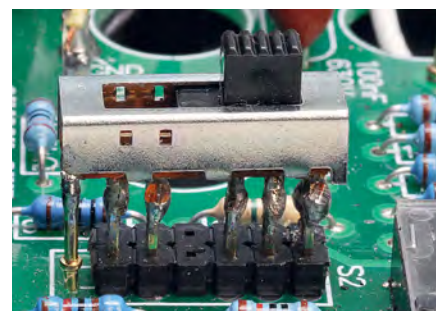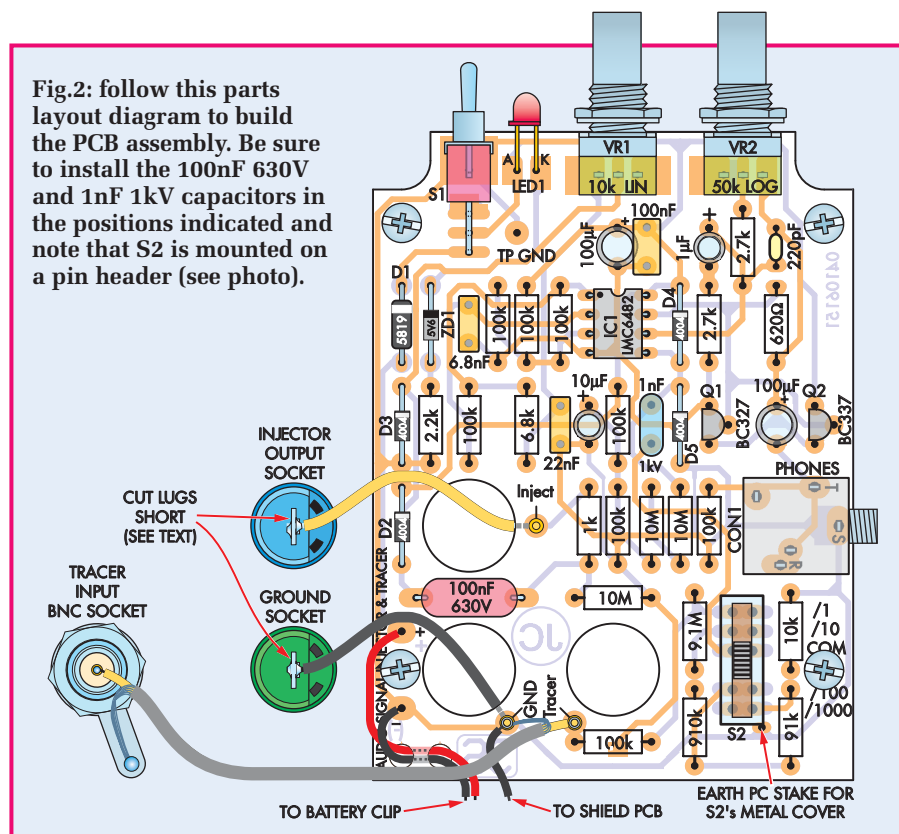
### RF demodulator probe

As previously noted, if you want to troubleshoot an AM radio with the Tracer, you need to have an additional



**This photo shows how switch S2 is mounted. It's soldered to a pin header so that its top metal face is 12.5mm above the PCB.**

fitted. These are installed at the five external wiring points, at TP GND (near LED1) and at the bottom right of S2. IC1 can then be soldered in place. Do not use a socket for this IC, as this would exacerbate noise pick-up.

## Installing switch S2

Switch S2 does not mount directly onto the PCB, but is instead raised off the PCB using a 6-way DIL pin header. Before installing this DIL header, remove a pin from each side so that there are three pins, then a gap, then two pins (ie, on each side of the header to correspond with the switch pins).

That done, position the header on the PCB with the longer pins facing upwards, then push each pin down so that it extends only 5mm above the top

### Table 2: Capacitor Codes

Value	μF Value	IEC Code	EIA Code
100nF	0.1μF	100n	104
22nF	0.022μF	22n	223
6.8nF	0.0068μF	6n8	682
1nF	0.001μF	1n	102
220pF	NA	220p	221

demodulator probe for the amplitude-modulated (AM) RF signals that should be present in the circuit being tested. As stated, a suitable RF demodulator probe is described in the next article.

## Construction

The *Audio Signal Injector/Tracer* is built on a double-sided PCB, which is available from the *EPE PCB Service*, coded 04106151 (85 × 63mm). This is housed in a plastic remote control case measuring 135 × 70 × 24mm. A panel label measuring 114 × 50mm is attached to the front of the case.

To make the assembly easy, the PCB is designed to mount onto the integral










 

mounting bushes within the case. The top of the PCB is also shaped to fit around the case mounting pillars at that end – see Fig.2 and photo.

Fig.2 shows the parts layout on the PCB. Begin by installing the resistors. Table 1 shows the resistor colour codes, but it's also a good idea to check each one with a digital multimeter before soldering it to the PCB.

The diodes can go in next. Note that there are two different types – D1 is a 1N5819, while D2-D5 are 1N4004s. Be sure to mount them with the correct polarity, then install zener diode ZD1, again taking care with its polarity.

The seven PC stakes can now be

### Table 1: Resistor Colour Codes

	No.	Value	4-Band Code (1%)	5-Band Code (1%)
	3	10MΩ	brown black blue brown	brown black black green brown
	1	9.1MΩ	white brown green brown	white brown black yellow brown
	1	910kΩ	white brown yellow brown	white brown black orange brown
	8	100kΩ	brown black yellow brown	brown black black orange brown
	1	91kΩ	white brown orange brown	white brown black red brown
	1	10kΩ	brown black orange brown	brown black black red brown
	1	6.8kΩ	blue grey red brown	blue grey black brown brown
	2	2.7kΩ	red violet red brown	red violet black brown brown
	1	2.2kΩ	red red red brown	red red black brown brown
	1	1kΩ	brown black red brown	brown black black brown brown
	1	620Ω	blue red brown brown	blue red black black brown



of the PCB. The pins on the underside can then be soldered to their respective pads, making sure that the header itself is flush against the PCB.

Once it's in position, switch S2 can be mounted by soldering its pins to the top of the header pins, so that its top metal face sits 12.5mm above the PCB (see photo). The best way to do this is to lightly tack-solder two diagonally-opposite pins first, then make any necessary adjustment before soldering the remaining pins. Don't forget to resolder the first two pins, to ensure reliable connections.

Once it's in position, the adjacent earth PC stake is soldered to the earth tag on S2's metal cover.

## Completing the PCB

Now for the capacitors. **Install the 100nF 630V polyester and 1nF 1kV ceramic capacitors in the positions shown**, then install the remaining MKT polyester types. The electrolytics can then go in, taking care to fit each one with the polarity as indicated on Fig.2. Note that the tops of the electrolytics must be no more than 12.5mm above the PCB, otherwise you will not be able to fit the case lid later on.

Follow with potentiometers VR1 and VR2, toggle switch S1 and the 3.5mm socket. VR1 is a 10kΩ linear potentiometer, while VR2 is a 50kΩ log potentiometer, so don't get them mixed up. LED1 can then be installed – it mounts horizontally with its leads bent down through 90° exactly 7mm from its lens, so that they go through the PCB pads. Push it down so that its horizontal lead sections sit exactly 6mm above the PCB (use a 6mm-wide cardboard spacer) and check that it is correctly oriented before soldering it to the PCB.

That completes the PCB assembly. It can now be checked and placed to one side while the case is drilled.

## Preparing the case

Figs.3 and 4 show drilling templates for the front panel and for the top of the case. They can either be photocopied from the magazine or downloaded as PDF files from the *EPE* website and printed out.

It's just a matter of cutting the templates out, temporarily attaching them to the case panels and then drilling the various holes. The top of the case requires holes for potentiometers VR1

and VR2, switch S1 and LED1, while the front panel is drilled to accept the two banana sockets, the BNC socket and slide switch S2.

The rectangular cut-out for S2 is best made by drilling a row of holes inside the cut-out area, joining these and then filing the job to shape. The two banana socket holes can simply be drilled and reamed to size, but the BNC socket hole needs to be shaped as shown on the template. It can be made by first drilling a small hole in the centre, then finalising its shape using small files, with the flat side positioned as shown.

A hole must also be cut in one side of the case to accept the 3.5mm jack socket. To do this, temporarily position the PCB in the case, mark out the socket position, then remove the board and make a semi-circular notch in the base using a small round file. Once that's been done, temporarily assemble the case and complete the hole by filing a matching semi-circular cut-out in the lid.

Finally, you have to remove an internal pillar inside the case lid so that it doesn't foul the nut for the earth banana socket. This can be done using side cutters. Note also that, as provided, the banana socket terminals are too long for the case and have to be shortened by 5mm. A fine-tooth hacksaw blade is the best tool for this job – do not bend the terminals, as they will break. File off any sharp edges after cutting them to length.

Having drilled all the holes, the front panel label can be attached. This can be downloaded from the *EPE* website, printed out (preferably onto photo paper) and affixed to the lid using either glue or neutral-cure silicone.

Alternatively, for a more rugged label, print it out as a mirror image onto clear overhead projector film (be sure to use film that suits your printer), so that the printed side will be on the back of the film when the label is affixed. The film will have to be attached using a light-coloured silicone applied evenly over the surface, as the lid is black.

Once the label is in position, cut out the holes using a sharp hobby knife.

## Making a shield PCB

Since the *Tracer* has such a high input impedance, it has the potential to pick up hum from transformers, but it will also pick up the *Injector* signal as

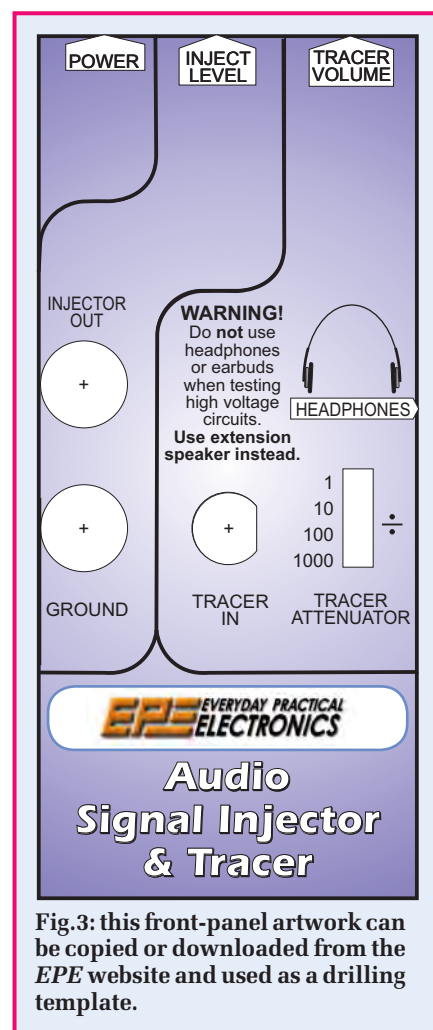


Fig.3: this front-panel artwork can be copied or downloaded from the *EPE* website and used as a drilling template.

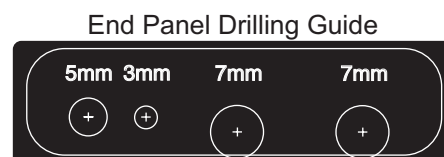


Fig.4: the end panel drilling template. Drill pilot holes first to ensure they are accurately positioned, then carefully enlarge them to size.

well, due to direct radiation of the *Injector* signal into the input attenuator and other components in the op amp's input circuitry.

We can reduce this by a significant amount by installing a small shield board, made from copper laminate, underneath the PCB, with its copper side earthed to the PCB's GND stake. The dimensions of this shield board are shown in Fig.5. It fits between the four integral pillars used to mount the PCB and it has a cut-out to clear the back of the *Injector* jack sockets.

Alternatively, if you don't wish to make your own shield board, you can

## Parts List

- 1 double-sided PCB, available from the *EPE PCB Service*, coded 04106151, 85 × 63mm
- 1 single-sided shield PCB, *EPE PCB Service*, coded 04106153, 62 × 63mm
- 1 remote control case, 135 × 70 × 24mm
- 1 panel label, 114 × 50mm
- 1 9mm square PCB-mount 10kΩ linear potentiometer (VR1)
- 1 9mm square PCB-mount 50kΩ log potentiometer (VR2)
- 1 SPDT PCB-mount toggle switch (S1)
- 1 DP4T PCB-mount slider switch (TE Connectivity STS2400PC04) (element14 Cat. 1291137) (S2)
- 1 PCB-mount 3.5mm stereo jack socket (CON1)
- 2 knobs to suit VR1 and VR2
- 1 panel-mount BNC socket
- 1 blue insulated banana socket
- 1 green insulated banana socket
- 1 9V alkaline battery
- 1 9V battery snap connector
- 4 No.4 × 6mm self-tapping screws
- 7 PC stakes

- 1 DIL 6-way pin header
- 1 150mm length of hookup wire
- 1 50mm length of single-core shielded wire

### Semiconductors

- 1 LMC6482AIN dual CMOS op amp (IC1)
- 1 3mm high-intensity red LED (LED1)
- 1 BC327 PNP transistor (Q1)
- 1 BC337 NPN transistor (Q2)
- 1 5.6V 1W zener diode (ZD1)
- 1 1N5819 Schottky diode (D1)
- 4 1N4004 diodes (D2-D5)

### Capacitors

- 2 100μF 16V PC electrolytic
- 1 10μF 16V PC electrolytic
- 1 1μF 16V PC electrolytic
- 1 100nF 630V polyester
- 1 100nF 63V or 100V MKT polyester
- 1 22nF 63V or 100V MKT polyester
- 1 6.8nF 63V or 100V MKT polyester
- 1 1nF 1kV ceramic
- 1 220pF disc ceramic

### Resistors (0.25W, 1%)

- 3 10MΩ
- 1 6.8kΩ
- 1 9.1MΩ
- 2 2.7kΩ

- 1 910kΩ
- 1 2.2kΩ
- 8 100kΩ
- 1 1kΩ
- 1 91kΩ
- 1 620Ω
- 1 10kΩ

## Test Leads

### Tracer In

**Option 1:** 1 × 1:1 oscilloscope probe

**Option 2:** 1 × BNC plug-to-RCA plug lead fitted with a PC stake and 5mm and 10mm heatshrink tubing (see text)

**Option 3:** 1 × BNC line plug, 1 × RCA line plug, 1 × 500mm-length of single-core shielded audio cable, 1 × M4 nut, 1 v PC stake and 2mm, 5mm and 10mm heatshrink tubing (see text)

### Injector Out

**Option 1:** 1 × multimeter lead set with accessory alligator clips

**Option 2:** 1 × red banana plug, 1 × black banana plug, 1 × red alligator clip, 1 × black alligator clip, 1 × 500mm length of red medium-duty hookup wire, 1 × 500mm length of black medium-duty hookup wire (made into two banana plug to alligator clip leads).

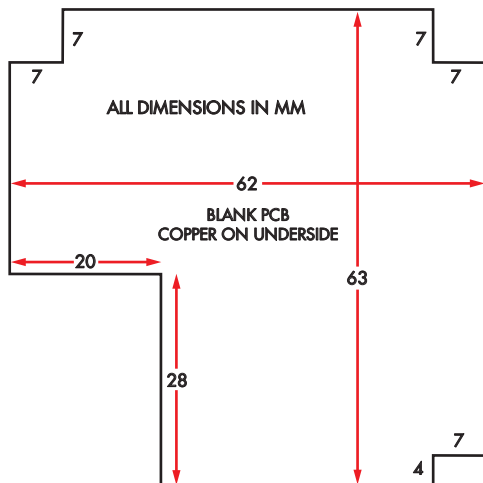


Fig.5: this diagram shows the dimensions of the blank shield PCB.

buy a ready-made board (available from the *EPE PCB Service*, code 04106153).

The shield board is installed in the case with its copper side facing downwards, away from the underside of the PCB (otherwise it would short the component pigtails!). Before doing this, solder a short piece of wire to the copper side and then connect its other end to the earth pin (GND) for

the BNC connection, on the PCB. The shield PCB is then secured inside the case using silicone adhesive.

## Final assembly

Now for the final assembly. First, attach the sockets to the front panel, then solder short lengths of hook-up wire to the Inject and GND terminals on the underside of the PCB. That done, pass these leads up through their respective holes in the PCB, ready to solder to the banana socket terminals.

Next, attach a short shielded cable (for the BNC socket) to the GND and *Tracer* PC stakes on the top of the PCB. The 9V battery snap can then be fitted. Its leads are fed through from the battery compartment before being looped through stress relieving holes in the PCB and soldered to the '+' and '-' terminals.

The next step is to fit the end panel to the potentiometers, switch and LED and install this into the base of the case. The PCB is then secured using four No.4 × 6mm self-tapping screws that go into integral mounting pillars.

Once it's in place, complete the wiring to the banana sockets and the BNC

socket, then secure the lid to the base using the supplied screws. **You will need to make sure that the wires do not interfere with the banana sockets – if they are sandwiched beneath the banana sockets, they will prevent the lid from fully closing.**

Similarly, any wires running over the battery compartment or over the slider switch will prevent the case from closing. If necessary, move the wires out of the way using a small screwdriver as the case is being closed.


Finally, fit the battery and the assembly is complete.
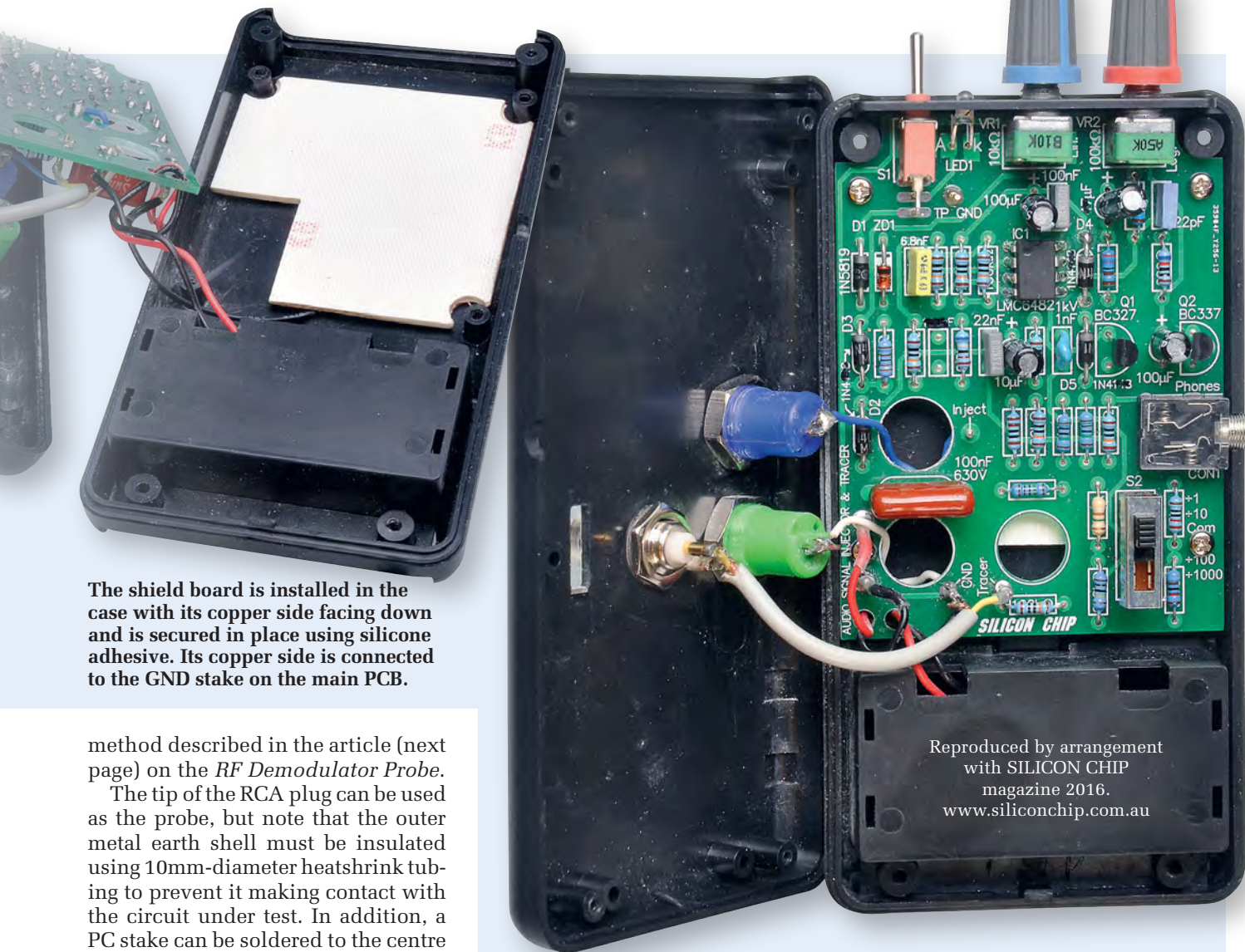
## Test leads

As mentioned earlier, a 1:1 oscilloscope probe makes a suitable test lead for the *Audio Signal Injector/Tracer's* BNC input. Alternatively, a cheaper test probe can be made using a BNC-to-RCA lead. This can be a commercial lead, but these tend to be made from stiff large-diameter cable.

A do-it-yourself cable using a line RCA plug, a line BNC plug and standard shielded audio cable will be much more flexible. The connections to the BNC plug can be made using the





The shield board is installed in the case with its copper side facing down and is secured in place using silicone adhesive. Its copper side is connected to the GND stake on the main PCB.

method described in the article (next page) on the *RF Demodulator Probe*.

The tip of the RCA plug can be used as the probe, but note that the outer metal earth shell must be insulated using 10mm-diameter heatshrink tubing to prevent it making contact with the circuit under test. In addition, a PC stake can be soldered to the centre pin of the RCA plug to extend it. That's done by first drilling a 1mm hole in the end of the plug's tip, then inserting the PC stake and soldering it.

It's a good idea to cover the RCA plug's centre terminal with 5mm diameter heatshrink tubing, leaving only the PC stake 'probe' exposed. This will help prevent inadvertent shorts when probing closely-packed circuits.

The *Injector* signal can be fed out using a multimeter probe. Alternatively, you can use a lead fitted with a banana plug at one end and an alligator clip lead at the other. A banana plug-to-alligator clip lead can also be used for the ground lead.

### Testing

To check that the unit is working correctly, connect the 'Injector Out' signal to the 'Tracer In' (BNC) socket, then plug in headphones (or earphones) and listen for the 1kHz signal. Assuming that it's present, check that the level varies when the 'Inject Level'

This is the view inside the completed unit. Make sure that the wiring leads to the banana sockets aren't squashed under them as the lid is closed (push the leads towards the outer edge of each hole using a small screwdriver).

potentiometer, the 'Tracer Volume' potentiometer and the 'Tracer Attenuator' switch are adjusted.

As noted above, if the *Tracer* input is disconnected from a circuit, the unit will pick up hum and the 1kHz *Injector* signal due to the *Tracer* circuit's high input impedance (ie, the 1kHz signal will be heard even when there is no connection). The pick-up level will depend on the capacitance of the input cable, the attenuator setting (S2), the *Injector* level setting (VR1) and the gain (Volume) setting (VR2).

Obviously, it will be at a maximum when the attenuator is set to 1:1 and VR1 and VR2 are at maximum, but this combination of settings would not be used in practice. Basically, it's just a

matter of choosing settings to suit the job at hand and to minimise extraneous noise pick-up.

Under normal use and when connected to a circuit for testing, the cross-talk from the *Injector* will be minimal and will be swamped by the signal from the circuit under test.

### Ground connections

Finally, note that when using the *Audio Signal Injector/Tracer*, the Ground banana socket must be connected to the ground of the circuit under test. This can be done using a lead fitted with an alligator clip as described above or by using the earth lead on the 1:1 oscilloscope probe.

Now turn to the next page for the optional *RF Demodulator Probe*.

Reproduced by arrangement  
with SILICON CHIP  
magazine 2016.  
[www.siliconchip.com.au](http://www.siliconchip.com.au)

By JOHN CLARKE

Simple unit uses just a handful of parts . . .

# AM RF Demodulator Probe for Signal Tracers

If you want to troubleshoot an AM radio with the *Signal Tracer/Injector* described in this issue, you need a demodulator probe to detect the amplitude-modulated RF signals that should be present in the circuit being tested. This one is compact and easy to build.

Fig.1 shows the circuit details of the *RF Demodulator Probe*. It uses a fast BAT46 Schottky diode (D1) as the detector and its output is filtered with a 1nF capacitor to remove the RF signal, leaving the audio modulation which can then be fed to the *Tracer*.

The audio frequency response of the probe is about -3dB down at 1.6kHz, as set by the 1nF capacitor and associated 100k $\Omega$  resistor. Since the RF probe is intended for use in valve AM radios, its 100pF capacitor is a 1kV-rated ceramic type.

Note that the probe is a passive device and requires no external power.

### Construction


The *RF Probe* is built on a PCB, available from the *EPE PCB Service*, coded 04106152 (45 × 11mm) – see Fig.2. Install the two 100k $\Omega$  resistors and the two capacitors first, followed by the diode. Check that the diode is correctly oriented (ie, banded end towards the right).

The probe tip is made using a 3-way right-angle pin header. Solder

this in place and then cut the outer two pins flush with the end of the PCB, leaving just the centre pin.

PC stakes are used to terminate the three external wiring connections. Fit these to the PCB, then attach the earth wire to the GND stake and the shielded cable to the SIG and GND terminals. The shielded wire and the earth wire are then secured to the PCB using two cable ties.

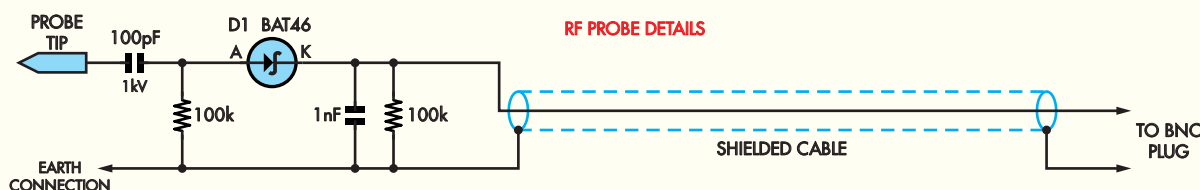
Once all the parts are in place, the assembly is covered in a 55mm length of 16mm-diameter heatshrink




### RF DEMODULATOR PROBE

Fig.1: the circuit uses a BAT46 Schottky diode (D1) as the detector plus a 1nF capacitor to filter out the RF signal. The 100pF 1kV input capacitor blocks DC signals, while the 100k $\Omega$  resistor sets the frequency response to -3dB at 1.6kHz.



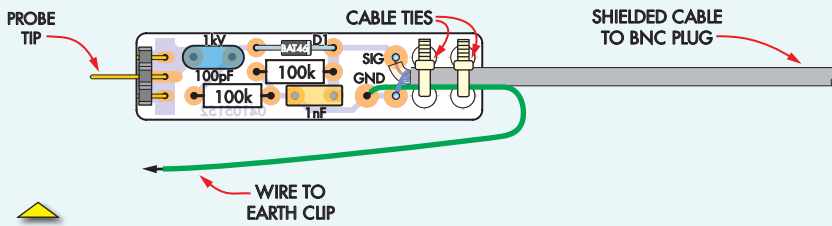

**Fig.2:** the parts layout on the small PCB. Make sure the 100pF capacitor is rated at 1kV and take care with the orientation of Schottky diode D1. The photo at right shows the completed PCB before the heatshrink sleeve was fitted.

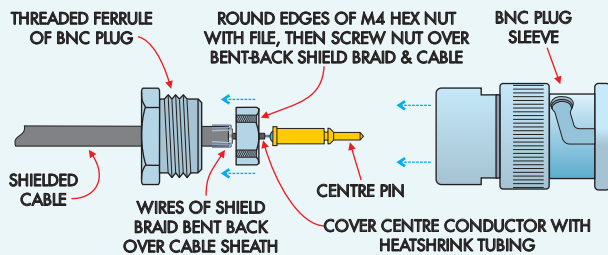

**Fig.3:** this diagram shows how the shielded audio cable is connected to the BNC plug (see text).

## RF Probe parts list

- 1 PCB, available from the *EPE PCB Service*, coded 04106152, 45 × 11mm
- 1 BNC line plug
- 1 right-angle 3-way SIL header
- 1 500mm-length of single-core shielded wire
- 1 black alligator clip
- 1 300mm-length of black hook-up wire
- 1 BAT46 Schottky diode (D1)
- 1 1nF MKT polyester or ceramic capacitor
- 1 100pF 1kV ceramic capacitor
- 2 100kΩ 0.25W resistors
- 2 100mm cable ties
- 1 M4 metal nut
- 3 PC stakes
- 1 55mm-length of 15mm-diameter heatshrink tubing
- 1 5mm-length of 2mm-diameter heatshrink tubing

tubing that's shrunk down with a heat-gun.


The far end of the earth lead can be terminated in an alligator clip or a hook clip, while the shielded cable goes to the BNC plug. Note that this type of plug is designed for use with a larger-diameter shielded cable than the shielded audio cable used here. However, a satisfactory connection can be made if an M4 metal nut is used as part of the assembly hardware.

Fig.3 shows the details. The first step is to file the six corners off the M4 nut, so that it will fit into the back of the BNC plug. Once that's


done, strip the outer insulation and the centre wire insulation as shown in Fig.3 and solder the centre wire to the BNC socket's centre pin.

Next, bend the shield wires back along the cable and twist the M4 nut on over these wires. A short length of 2mm-diameter heatshrink tubing is then used to cover (and stiffen) the centre wire before it meets the centre pin, after which the plug sleeve can be fitted and the threaded ferrule tightened to secure the assembly.

Finally, the wire can be secured inside the threaded ferrule using neutral-cure silicone sealant.

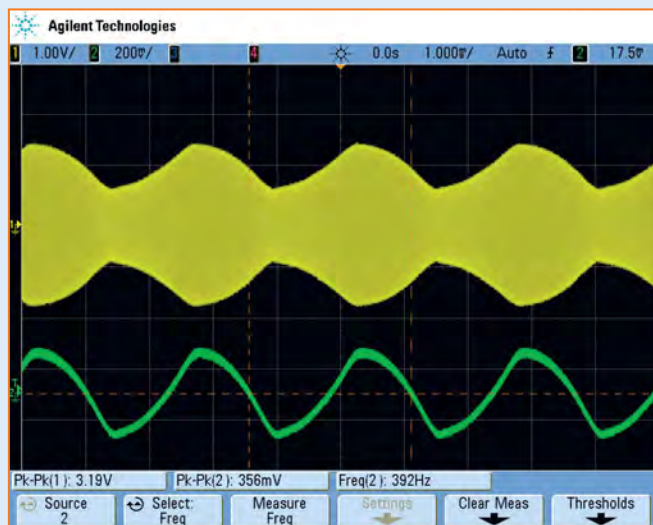

**Fig.3:** the yellow trace in this scope grab shows a 1MHz carrier from an old Leader signal generator, amplitude modulated with a 400Hz audio signal. The modulation depth is about 30%. The green trace shows the 400Hz (actually 392Hz) audio modulation from the RF probe. Note that the recovered modulation is a somewhat distorted sinewave.

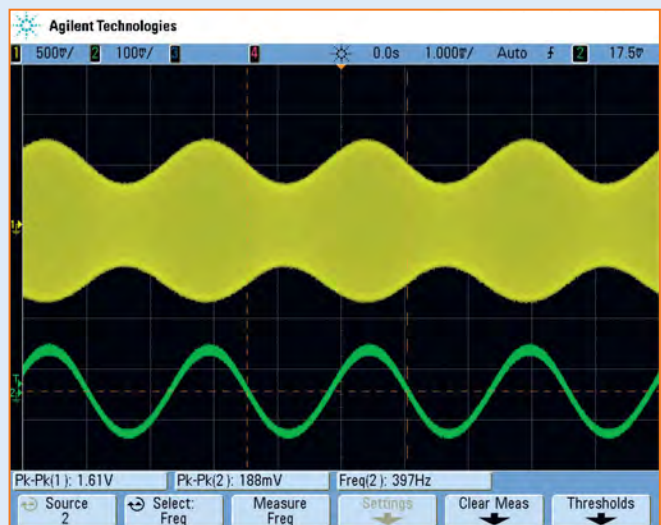

**Fig.4:** the yellow trace in this scope grab shows a 1MHz carrier from an old Marconi signal generator, amplitude modulated with a 400Hz audio signal. The modulation depth is about 30%. The green trace shows the 400Hz (actually 397Hz) sinewave audio modulation from the RF probe.

# Champion Preamp



You can use this simple unit as a general-purpose stereo preamp or as a dual-channel preamp, with a microphone for one channel and guitar in the other. One channel can have fixed gain while the other is variable with an on-board trimpot or external potentiometer. Better still, it gives good performance and will work over a wide range of supply voltages.

Over the years we have offered very many amplifiers. Early designs were of course quite bulky by today's standards, and with the inexorable march of technology it is now possible to offer much more sophistication and power in a very compact module. So, with that thought in mind, here is a superb pre-amplifier in a very small package.

I should state at the outset that this 2-channel preamp is not an absolutely brand-new design. It is based on the preamp section of the *Champion* amplifier module which was featured in the January 2014 issue. The major feature of that article was the tiny AN7511 monolithic amplifier chip, which can deliver up to 7W peak power, depending on load and supply voltage. The preamp section might have been seen almost as an afterthought, but it would be a pity for it to have passed mostly unnoticed.

## Main features

- 2-channel preamplifier configurable for different inputs
- Low distortion
- Low current drain: 2mA
- Signal-to-noise ratio: ~80dB
- Operating voltage range: 6-12V with LP2950CZ-5.0 5V LDO regulator; 12-20V with 78L09 9V regulator

This is partly why we have decided to devote an article just to the preamp; that and the fact that we have recently had a number of requests for preamps which would be neatly answered by this design.

So what is good about it? First, it can use one of two dual rail-to-rail op amps and these have the outstanding feature of maximum output voltage swing. So, for example, if you have a 9V supply rail, the maximum undistorted output voltage can be within a whisker of 9V peak-to-peak; about 8.5V p-p, to be more precise. This in itself is very handy, much better than the old *PreChamp* design and you don't have to tweak the input bias to obtain it.

Another advantage is that the specified rail-to-rail op amps can be designed into a preamp with a very high input impedance. This is highly desirable if you want a preamplifier to suit a ceramic phono cartridge or a piezoelectric pick-up in a musical instrument such as a violin. In both cases, an input impedance of 5M $\Omega$  is useful when chasing good bass response.

## Optional electret microphone

One of the attractions of the *PreChamp* was that you could install an on-board electret microphone. The only modification required was to add a bias resistor. That feature can also be in-

cluded in this 2-channel design and you could, in fact, have two electret microphones, **although for useful channel separation you would need to install them both on shielded leads.**

## Circuit details


The circuit is similar to but not exactly the same as the preamp in the January 2014 article. Fig.1 shows the details. Both channels are shown and the dual op amp is an LMC6482.

Since we are employing a single DC supply rail, we need a half-supply reference from which to bias the inputs of both op amps. This reference is derived from the supply rail via a voltage divider consisting of two 10k $\Omega$  resistors bypassed with a 100 $\mu$ F electrolytic capacitor. We can use such high-value resistors for the divider because the bias current drawn by each input of the op amps is a just a fraction of a pico-amp. On the other hand, we want that bypassed half-supply to have quite a low impedance, hence the relatively large capacitor value of 100 $\mu$ F.

Both op amp circuits are identical, although it is possible to have different gains in each channel, depending on your application. For the moment though, let's assume that both are identical and we will just describe channel 1, based on op amp IC1a.

The input signal from CON2 passes through a low-pass filter consisting



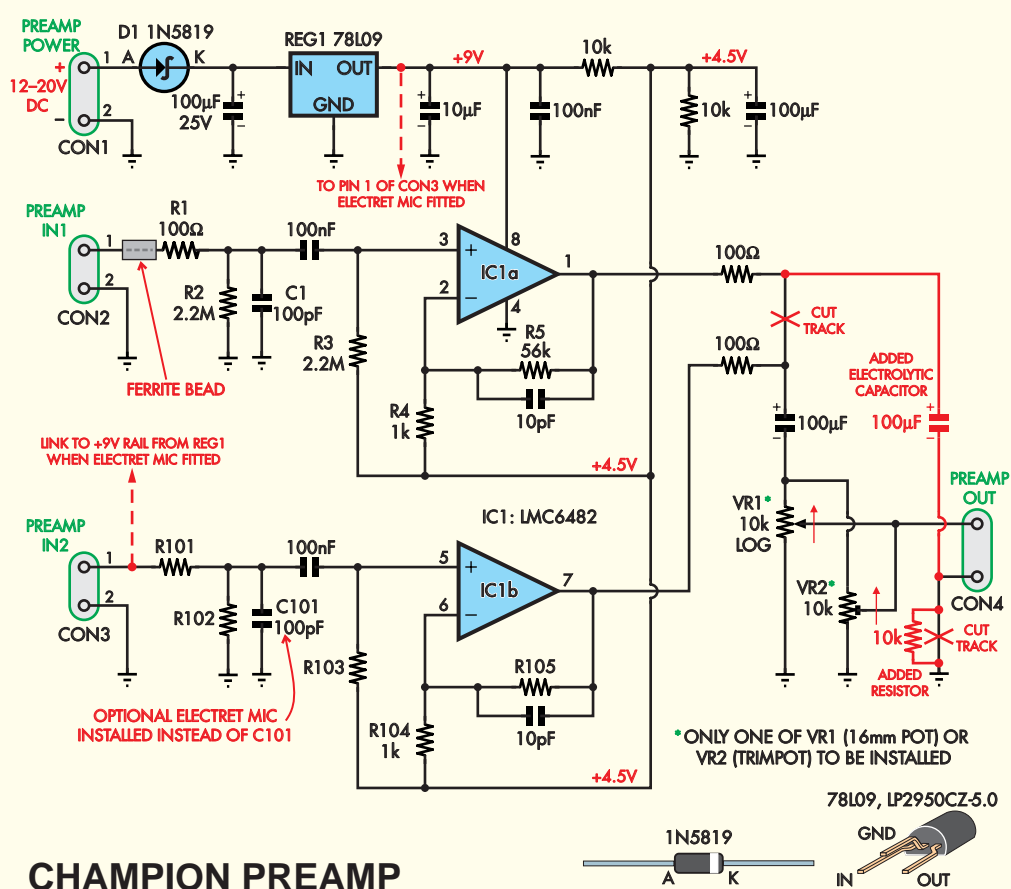

**Fig.1: the preamplifier circuit. It's based around dual rail-to-rail op amp IC1. The signal from each input is AC-coupled and biased to half supply, then amplified and re-biased to 0V DC before being fed to CON4.**

of a 100Ω resistor (R1) and a small ferrite bead in series, together with a 100pF capacitor connected to the 0V line (C1). This is to attenuate any RF signals that may be picked up by the input leads. There is also a 2.2MΩ resistor to pull the input signal to ground (R2).

If you are going to feed the preamp with an iPod or similar player you will need to use a much lower value of, say,  $1k\Omega$  to provide it with sufficient load current. For the moment though, the values we have shown on the circuit for channel 1 are selected to suit the pick-up in an electric guitar.

The signal is then AC-coupled via a 100nF capacitor to pin 3 of IC1a and a 2.2M $\Omega$  resistor biases the op amp's input to the half-supply rail. This ensures that the output waveform will swing symmetrically within the supply rails of dual op amp IC1. The two 2.2M $\Omega$  resistors on either side of the 100nF AC-coupling capacitor are in parallel as far as the signal source is concerned, setting the unit's input impedance to around 1.1M $\Omega$ .

IC1a buffers and amplifies the signal from CON2, while IC1b does the same for the signal from CON3. Gain is set at 57 times (35dB) by the 56k $\Omega$  (R5) and 1k $\Omega$  (R4) feedback resistors. The 10pF feedback capacitor reduces the gain for high-frequency signals, giving a little extra stability and noise filtering.

## Changing the gain

Note that this high gain suits a musical instrument such as a guitar, but you can easily increase or reduce the gain by changing R5, and you can change the input impedance as well.

For example, if you want to configure it for a dynamic microphone, R2 and R3 are changed to 100k $\Omega$  each to give an input impedance of 50k $\Omega$ , while R5 is changed to 100k $\Omega$  to give a gain of 101 times (41dB).

If you want to install an electret microphone insert on the PCB, you would install it in place of 100pF capacitor C101. At the same time, R101 is changed to 10k $\Omega$  and it provides the bias current for the electret. The other end of the 10k $\Omega$  resistor is connected to the positive supply rail, from REG1.

Finally, R102 is omitted, R103 is 220k $\Omega$  and the gain is set to 23 (27dB) with R105 being 22k $\Omega$ .

### Ceramic cartridge

Another interesting application is to use the *Champion* preamp with a stereo ceramic cartridge (don't laugh; this was a standard fitment on millions of record players and many people are dragging them out to listen to their old record collections). Ceramic cartridges require a high input impedance and this is an option with this preamp. Both R2 are specified at 10M $\Omega$ , giving an input impedance of 5M $\Omega$  which is good for bass response.

The gain does not need to be high though, and so we can set R5 to 2.7k $\Omega$ . This gives a gain of 3.7 (11.3dB). The same configuration can be used for a piezo pick-up on a musical instrument such as a violin.

So to summarise, depending on what type of source you are using and the gain required, you can easily obtain the required input impedance and gain. Table 1 shows the values to use.

**Table 1: RC gain selection values**

Input	Gain	R1/101	C1/101	R2/102	R3/103	R4/104	R5/105
Guitar	57	100Ω	100pF	2.2MΩ	2.2MΩ	1kΩ	56kΩ
Microphone	101	100Ω	100pF	100kΩ	100kΩ	1kΩ	100kΩ
Electret	23	10kΩ*	–	–	220kΩ	1kΩ	22kΩ
MP3	28	100Ω	100pF	1kΩ	220kΩ	1kΩ	27kΩ
Piezo pick-up	3.7	100Ω	–	10MΩ	10MΩ	1kΩ	2.7kΩ

\* Connect one end of this resistor to the +9V rail from REG1.

# Constructional Project

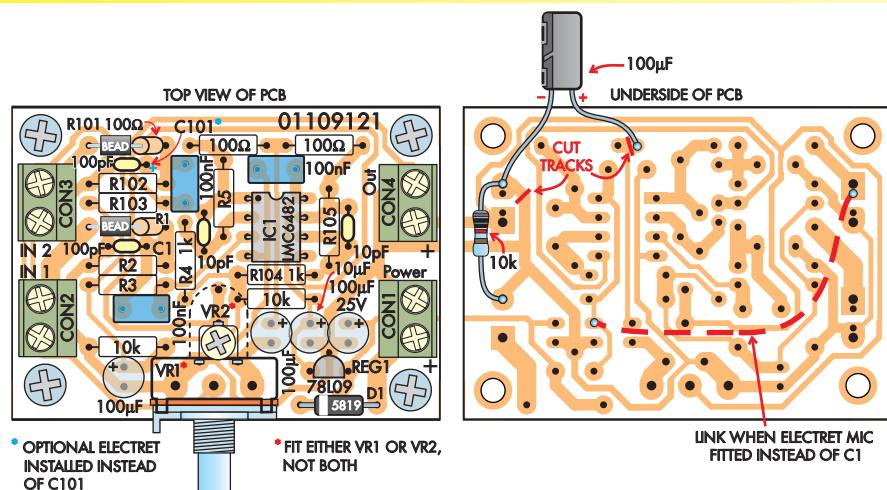


Fig.2: follow this layout diagram to assemble the PCB. It's best to cut the tracks first and then check with a continuity meter before fitting the parts.

## Table 2: Resistor Colour Codes

Value	4-Band Code (1%)	5-Band Code (1%)
10MΩ	brown black blue brown	brown black black green brown
2.2MΩ	red red green brown	red red black yellow brown
220kΩ	red red yellow brown	red red black orange brown
100kΩ	brown black yellow brown	brown black black orange brown
56kΩ	green blue orange brown	green blue black red brown
27kΩ	red violet orange brown	red violet black red brown
10kΩ	brown black orange brown	brown black black red brown
2.7kΩ	red violet red brown	red violet black brown brown
1kΩ	brown black red brown	brown black black brown brown
100Ω	brown black brown brown	brown black black black brown

## Two outputs

In the original *Champion* preamplifier, the outputs of the two op amp stages are mixed using a pair of resistors and then AC-coupled to potentiometer VR1 or VR2, depending on which is installed. In our application, we want two separate outputs and so if an output level control is to be used, it can only affect one channel. As shown on the circuit of Fig.1, the output of IC1b connects to VR1 (or VR2) via a 100Ω resistor and 100μF DC blocking capacitor. The wiper of VR1 then connects to one terminal on CON4.

The output of IC1a is also fed via a 100Ω resistor with a second blocking capacitor and bias resistor added under the board. This output goes to the other terminal on CON4. Note that two track cuts on the PCB need to be made, in order to give this independent two-channel operation.

IC1 is powered via a 78L09 low-power 3-terminal 9V regulator, assuming you are using a DC plugpack with an output of 12V or more (up to 20V DC). This regulator is fed from CON1 via Schottky diode D1 which protects against reversed supply polarity.

## Table 3: Capacitor Codes

Value	μF Value	IEC Code	EIA Code
100nF	0.1μF	100n	104
100pF	NA	100p	101
10pF	NA	10p	10

Note that if you intend using a 9V battery for this project, you may want to employ the LP2950CZ-5.0 5V regulator. No other modifications are required if you make this change, but the preamplifier will inevitably have a reduced output voltage swing and therefore a reduced overload margin for strong input signals.

## Construction

You will be using the *Champion* PCB for this project (available from the *EPE PCB Service*, coded 01109121/22) and you will need to cut off the section for the AN7511 audio amplifier. Don't discard it – it's a handy little amplifier module in its own right and the AN7511 amplifier chip is quite cheap.

The remaining preamplifier PCB measures just 57 × 41mm. It has provision for mounting pillars at its four corners and four 2-way connector blocks.

## Parts List

- 1 PCB, available from the *EPE PCB Service*, coded 01109121/22, 57 × 41mm (see text)
- 1 PCB-mount electret microphone insert (optional; see text)
- 1 10kΩ log PCB-mount 16mm potentiometer (VR1) OR
- 1 10kΩ mini horizontal trimpot (VR2)
- 2 ferrite beads, Jaycar LF1250
- 4 mini 2-way terminal blocks (CON1-CON4) (omit one if electret is installed)
- 1 8-pin DIL socket
- 4 M3 × 10mm tapped nylon spacers
- 4 M3 × 6mm machine screws
- 1 short length hookup wire (60mm)
- Semiconductors**
- 1 LMC6482 or LMC6032 dual op amp (IC1)
- 1 78L09 or LP2950CZ-5.0 5V LDO regulator (REG1) – see text
- 1 1N5819 Schottky diode (D1)

## Capacitors

- 1 100μF 25V electrolytic
- 3 100μF 16V electrolytic
- 1 10μF 16V electrolytic
- 3 100nF MMC or MKT
- 2 100pF ceramic (omit one if electret is installed)
- 2 10pF ceramic

## Resistors (0.25W, 1%)

- 3 10kΩ
- 2 100Ω
- See Table 1 for R1-R5

**Note:** Jaycar sell a kit of parts for this project: Cat. KC-5531.

One of those blocks is used as the terminals for the two preamplifier outputs.

Since there are changes to the component layout, this means that you will have to follow the parts layout of Fig.2 and ignore most of the resistor values shown on the screen-printed layout on the PCB itself. You also need to cut the copper tracks of the PCB in two places, as shown on Fig.2.

Having cut the tracks, start the assembly by installing the resistors. You will need to refer to Table 1 for the values for R1-R5 and R101-R105. Table 2 shows the colour codes, but it is good idea to also check each value with a multimeter. A ferrite bead should be slipped over one leg of each 100Ω input resistor, if fitted (ie, R1 and R101).



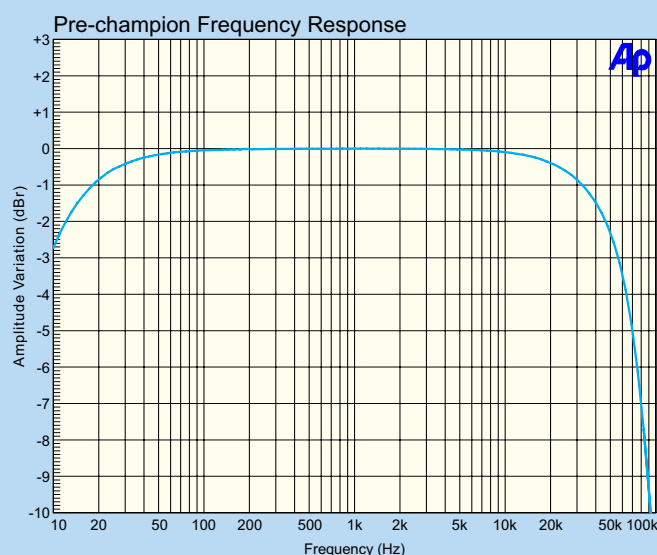


Fig. 3: frequency response is within +0, -0.5dB between 30Hz and 20kHz with -3dB points around 8Hz and 55kHz. It's less than 1dB down at 20Hz.



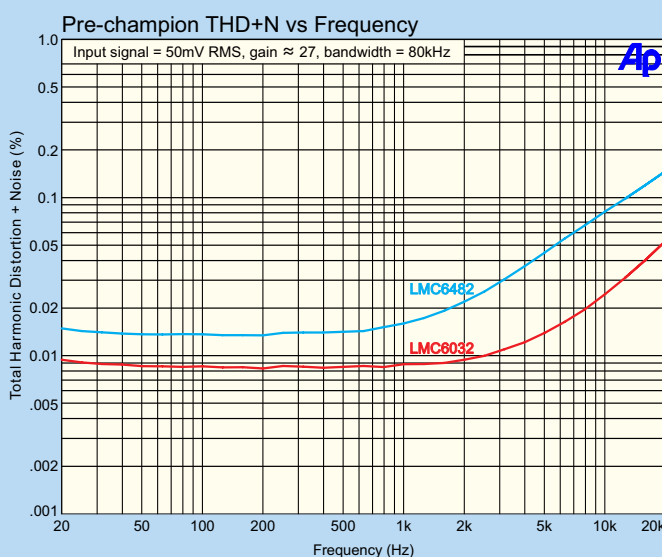


Fig. 4: the LMC6032 has about half the noise of the LMC6482. The LMC6032 requires slightly more operating current than the LMC6482, but still under 1mA.

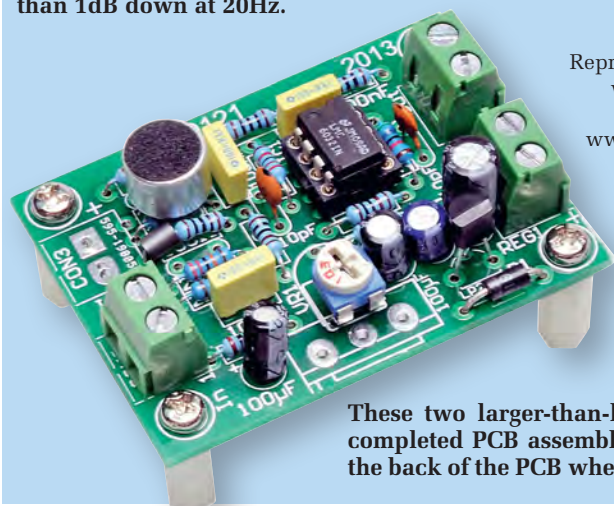

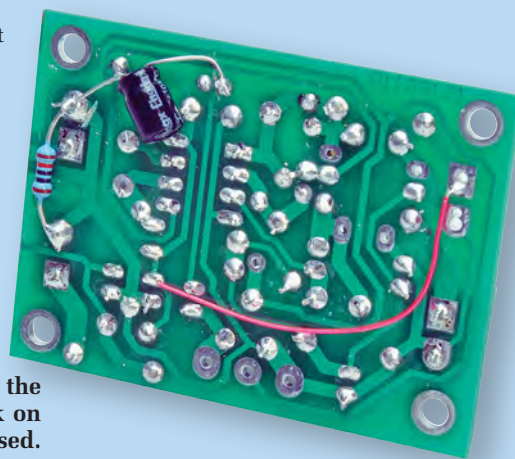Reproduced by arrangement  
with SILICON CHIP  
magazine 2016.  
[www.siliconchip.com.au](http://www.siliconchip.com.au)



These two larger-than-life-size views show the completed PCB assembly. Note the wire link on the back of the PCB when an electret mic is used.

Follow with diode D1 and then fit the IC socket with its pin 1 notch oriented as shown. Next, fit the 78L09 or LP2950CZ-5.0 regulator, REG1. Follow with the ceramic and monolithic capacitors.

The 2-way terminal blocks are next, each installed with their wire entry holes facing outwards. Note that CON3 is not installed if you have fitted an electret microphone insert for channel 2.

The next step is to decide whether to fit potentiometer VR1 or trimpot VR2. It will only control the output signal level from one channel and you may decide to link it out. You can then fit all the electrolytic capacitors. In each case, the longer lead goes into the hole marked with a '+' sign.

Once those parts are in, fit the M3 × 10mm tapped spacers to the corner mounting positions using M3 × 6mm machine screws.

If you are installing an electret, wire a 10kΩ resistor in the position for R101

and connect the end adjacent to CON3 to the output of the 3-terminal regulator. We show this with a dotted red line on Fig. 2. In addition, R102 and C101 are omitted.

## Electret orientation

**Make sure that the electret mic is correctly oriented. Its positive terminal must go to the side marked with a blue '+' sign on Fig. 2. Connect the electret via shielded cable if you want to mount it off the PCB.**

If you are going to use only one channel of the preamplifier, it's a good idea to short the unused channel's input to 0V by using a wire link for resistor R1 (or R101) and by shorting the two terminals of CON2 (or CON3).

When you have carefully checked your assembly and soldering against the circuit of Fig. 1, Table 1 and the overlay diagram of Fig. 2, you are ready to apply power. Check that the output

of REG1 is 9V (or close to it) if a 78L09 has been fitted. If an LP2950CZ-5.0 has been fitted, REG1's output should be close to 5V.

Next, turn off the power, insert the op amp (carefully), power back on and then check the DC voltage at pins 1 and 7. In each case, they should be sitting at half supply; 4.5V for a 9V supply and 2.5V for a 5V supply.

## Performance

Figs. 3 and 4 show the frequency response and total harmonic distortion curves of the preamplifier. Note that of the two op amps we've specified, the LMC6032 gives the best performance but it isn't as easy to get as the more common LMC6482.

To achieve a THD+N this low, the preamp will need to be installed in an earthed metal box. Otherwise, hum and RF pick-up will reduce the signal-to-noise ratio and consequently the total harmonic distortion performance.



# Teach-In 2016

## Exploring the Arduino

### Part 5: 1-Wire interface

by Mike and Richard Tooley



**Welcome** Welcome to *Teach-In 2016: Exploring the Arduino*. This exciting new series has been designed for electronics enthusiasts wanting to get to grips with the immensely popular Arduino microcontroller, as well as coding enthusiasts who want to explore hardware and interfacing. So, whether you are considering what to do with your Arduino, or maybe have an idea for a project but don't know how to turn it into reality, our new *Teach-In 2016* series will provide you with a one-stop source of ideas and practical information.

In last month's *Teach-In 2016: Exploring Arduino*, we looked at ways in which the Arduino can sense and

act upon what's going on in the real world. *Arduino Workshop* looked at the Arduino's analogue ports, while *Arduino World* introduced some low-cost devices that can sense temperature. Our programming feature, *Coding Quickstart*, explained the functions that will let you use serial communication via the Arduino's USB port. Finally, *Get Real* showed you how you can build a simple thermostatic controller based on the Arduino Uno.

#### This month

In this month's *Teach-In 2016: Exploring the Arduino* we will be looking at ways in which an Arduino can handle

multiple sensors using a limited number of wire connections. To help with this task, *Arduino Workshop* introduces the highly versatile 1-wire bus system, while *Arduino World* looks at temperature sensors that have their own integrated ADC offering a much higher resolution than the ADC converters built into the Arduino Uno. Our programming feature, *Coding Quickstart*, shows you how to use some code to store your valuable data on an ordinary SD card. Finally, our *Get Real* project takes the form of a stand-alone environmental monitoring system that can capture large amounts of data, conveniently processing and storing it on a conventional SD memory card.

### Arduino Workshop: using the 1-Wire interface

Developed by the Dallas Semiconductor Corporation, the '1-Wire' bus offers a means of exchanging low-speed data between a microcontroller and a sensor or other device using just one or two wires, plus a ground connection. The bus allows for a single 'master' to control and exchange data with a virtually unlimited number of 'slaves' connected to the same bus line. A device is supplied pre-programmed with a unique 64-bit identification number, which incorporates an 8-bit family code to identify the type of device and its function. Many 1-Wire devices are capable of operating without a separate power supply connection; instead, they derive their supply from the bus itself in what's referred to as a 'parasitic supply' arrangement.

Just about the most basic 1-Wire device is one that just supplies its own unique 64-bit identification when demanded by the bus master. This might not sound very useful, but by pairing a microcontroller with a unique slave device it becomes possible to have a very high level of authentication. Put simply, if the device isn't the expected slave then either the system won't work or some other appropriate action can

be taken. Many other 1-Wire devices are available, including temperature sensors, timer/counters, and non-volatile memories. Later in *Arduino World* we will show how a low-cost, high-resolution temperature sensor can be connected using the 1-Wire bus.

A notable advantage of the 1-Wire bus is that it offers a simple multi-drop capability in which a number of slave devices can all share the same bus line. This keeps the wiring extremely simple and, where a parasitic bus-powered supply is used, only two wires are needed to link all of the sensors together, as shown in Fig.5.1.

Using the 1-Wire bus, commands and data are sent with the least-significant bit first. To prevent potential conflict, 1-Wire devices must be interfaced to the bus by means of an open-drain tri-state port. This allows the bus to be released for other devices to use when data is not actually being transmitted (the tri-state device enters a high-impedance state

when not being used). In order to ensure that the bus line is taken high when idle, an external pull-up resistor of typically 4.7k $\Omega$  is connected between the positive supply and the bus line. A typical bus interface is shown in Fig.5.2. Note the open-drain connection to the bus.

If for any reason a transaction needs to be suspended, the bus must be left in the idle state so that the transaction can be resumed. Infinite recovery time can occur between bits so long as the 1-Wire bus is in the inactive (high) state during the recovery period. If the bus is held low for more than 480 $\mu$ s, all components on the bus will be reset. Several signal types are defined in the 1-Wire protocol, including reset pulse, presence pulse, write 0, write 1, read 0, and read 1. With the exception of the presence pulse, the bus master initiates all of these signals. *Arduino World* picks up this theme as we look at temperature sensors that incorporate a built-in 1-Wire interface.

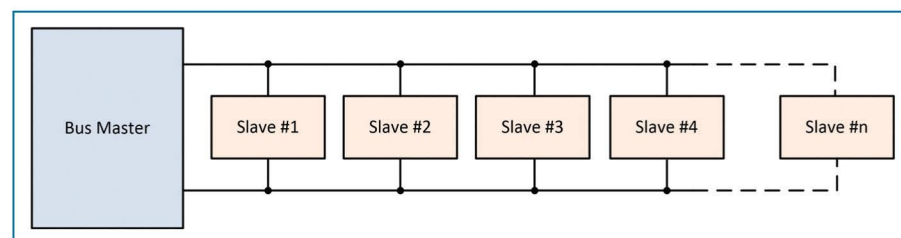


Fig.5.1. Single and multi-drop bus arrangements



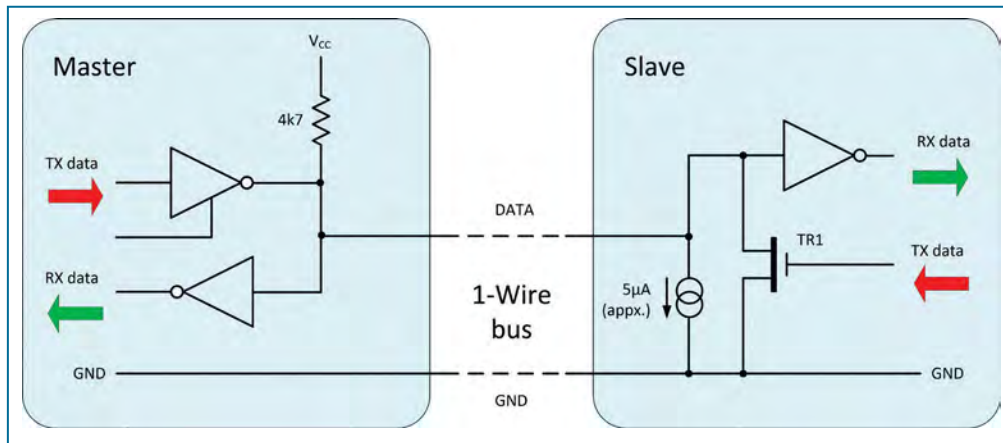


Fig.5.2. A typical 1-Wire bus interface

## Arduino World: Bus-connected temperature sensors

Last month, we introduced two popular and inexpensive families of temperature sensors. These simple 10-bit sensors are ideal for many simple Arduino temperature-sensing applications, but where increased resolution and multiple sensors are needed there are some better solutions. Chief among these is the family of 1-Wire bus temperature sensors from Dallas Semiconductor (see Fig.5.3).

The 1-Wire bus makes it possible to use a single microcontroller to communicate with a large number of sensors distributed

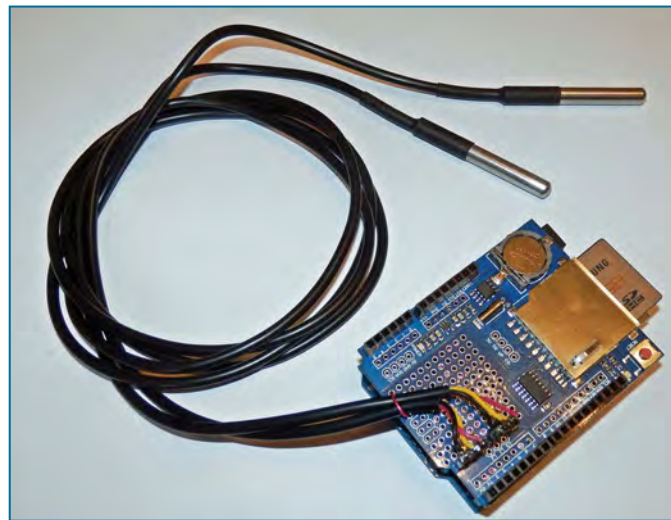


Fig.5.3. I/O connections for SPI communication

over a large area. Applications that can benefit from this feature include heating, ventilation and air conditioning (HVAC), environmental controls and temperature monitoring systems, as well as process monitoring and control systems.

### The DS18B20

The DS18B20 1-Wire temperature sensor provides a resolution of up to 12-bits. In addition, the device incorporates an alarm function with user programmable upper and lower thresholds that can be stored in on-board non-volatile memory. The device operates over a temperature range of  $-55^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$  with a

nominal accuracy of  $\pm 0.5^{\circ}\text{C}$  in the range of  $-10^{\circ}\text{C}$  to  $+85^{\circ}\text{C}$ . In addition, the DS18B20 can derive power directly from the data line using a parasitic power supply (see *Arduino Workshop*), eliminating the need for an external power supply.

### Resolution

The DS18B20 1-Wire temperature sensor can be configured for resolutions of either 9, 10, 11, or 12 bits. These respectively correspond to temperature

increments of  $0.5^{\circ}\text{C}$ ,  $0.25^{\circ}\text{C}$ ,  $0.125^{\circ}\text{C}$ , and  $0.0625^{\circ}\text{C}$  (note that the device has a default resolution of 12-bits).

### Operation

On power-up, the temperature sensor enters an idle state and then waits until the bus master sends a command to initiate temperature measurement and analogue-to-digital conversion. Following the conversion, the resulting temperature data is stored in a two-byte temperature register in the sensor's scratchpad memory, after which the sensor reverts to the idle state.

The sensor's output temperature data is calibrated in degrees Celsius. In applications where Fahrenheit indications are required, it will become necessary to use a conversion routine or a lookup table of corresponding values. Temperature data is stored as a 16-bit sign-extended two's complement number in the temperature register (see Fig.5.4). The sign bits (S) indicate if the temperature is positive or negative: for positive values  $S = 0$  and for negative values  $S = 1$ .

If the DS18B20 is configured for 12-bit resolution (as it will be by default), all bits in the temperature register will

### Listing 5.1 Using the 1-Wire bus to connect multiple sensors

```
/* DS18B20 temperature sensors connected using the 1-Wire bus */

#include <OneWire.h> // Include the 1-Wire and Dallas
#include <DallasTemperature.h> // Temperature libraries
#define ONE_WIRE_BUS 7 // Use digital I/O pin-7 for the bus

OneWire oneWire(ONE_WIRE_BUS); // Setup the 1-Wire interface
DallasTemperature sensors(&oneWire);

void setup(void)
{
  // start serial port
  Serial.begin(9600);
  sensors.begin();
}

void loop(void)
{
  Serial.print("Requesting temperature ... ");
  sensors.requestTemperatures(); // Request temperatures
  Serial.println("DONE");
  Serial.print("Temperature for Sensor 1 (index 0) is: ");
  Serial.print(sensors.getTempCByIndex(0));
  Serial.println(" deg.C");
  Serial.print("Temperature for Sensor 2 (index 1) is: ");
  Serial.print(sensors.getTempCByIndex(1));
  Serial.println(" deg.C");
  delay(1000); // Wait one second
}
```

**Table 5.1 Digital output data and corresponding temperature indications for 12-bit resolution**

Temperature (°C)	Digital output (binary)	Digital output (hex)
+125	0000 0111 1101 0000	07D0h
+25.0625	0000 0001 1001 0001	0191h
+0.5	0000 0000 0000 1000	0008h
0	0000 0000 0000 0000	0000h
-0.5	1111 1111 1111 1000	FFF8h
-55	1111 1100 1001 0000	FC90h


contain valid data. For 11-bit resolution, bit 0 is undefined whereas, for 10-bit

resolution, bits 1 and 0 are undefined, and for 9-bit resolution bits 2, 1, and 0 are undefined. Table 5.1 gives examples of digital output data and the corresponding temperature reading for 12-bit resolution conversions. In order to identify individual sensors connected on the 1-Wire bus, each DS18B20 has a 64-bit serial code stored in an on-board ROM. This number is unique and cannot be

changed. Data conversion time is a maximum of 750ms, which is adequate for most practical temperature sensing applications.

### Coding

In conjunction with the 1-Wire bus, the DS18B20 sensor is very easy to use. You simply need to include the 1-Wire and Dallas Semiconductor libraries (`OneWire.h` and `DallasTemperature.h` respectively) and then configure the bus for operation with the temperature sensor. Thereafter, readingsensorvalues into variables within your code is extremely straightforward, as the example in Listing 5.1 shows.

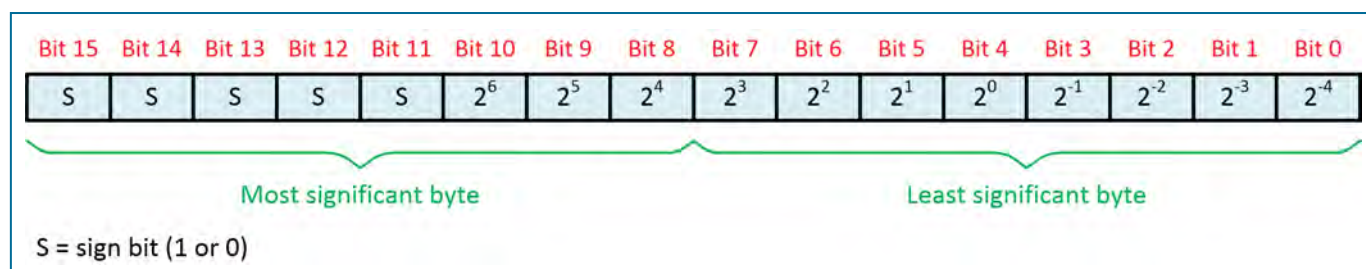

**Fig.5.4. Temperature data is stored as a 16-bit signed extended two's complement number**

## Coding Quickstart: using SD cards

For many applications it can be useful to store data in the form of a file that can be saved and later recalled or transferred to another system for further processing and analysis. This can be accomplished with the aid of an ordinary SD card and some simple code to handle the necessary file processing. There are several different ways that you can connect an SD card, including (in rough order of cost):

1. An outboard SD card module with an SPI bus interface
2. A datalogger shield such as those produced by Adafruit (these have the added bonus that they usually incorporate a real-time clock for 'date stamping' your data)
3. An Ethernet shield fitted with an SD card slot.

Regardless of which of the above is used, the interface between the microcontroller and the SD card module is achieved by means of the Arduino's Serial Peripheral Interface (SPI) bus. SPI is a communication bus that is used to interface one or more peripheral devices (known as 'slaves')

to a microprocessor or microcontroller (referred to as the 'master'). In addition to SD card modules, a large number of SPI devices are available, including analogue-to-digital converters (ADC), digital-to-analogue converters (DAC), general purpose input/output (GPIO) expansion chips, temperature sensors and accelerometers. The bus is capable of operating at high speed over short distances (faster than the I<sup>2</sup>C bus) but it normally requires a four-wire connection with one additional chip select wire for each peripheral SPI device.

The SPI bus is a synchronous (serial clocked) bus capable of supporting data transfer in both directions, master to slave and slave to master, at the same time (this is referred to as 'full duplex' operation). The Arduino's SPI implementation uses four signal wires (plus ground). These are listed in Table 5.2 together with the pin connections conventionally used on the Uno.

It is important to be aware that conventional SD cards are designed for operation from a 3.3V supply and thus it is necessary to ensure that the I/O levels and supply voltage are level-shifted within the hardware interface. This is normally the case with Arduino shields and modules, but it is important to check when modules may have been designed for operation with other systems and may have links or switches fitted.

### Using the SD Library

The Arduino's built-in SD Library provides you with a set of tools that you can use to

read from and write to an SD card. The library supports the popular FAT16 and FAT32 file systems commonly used with standard SD and SDHC cards. Filenames should follow the normal '8 + 3' convention and can include paths separated by forward-slashes, /. It is worth noting that, because the working directory is always the root of the SD card, a name refers to the same file *whether or not* it includes a leading slash. Thus, `mydata.dat` is the same as `/mydata.dat`. The SD library currently supports multiple file opening.

To communicate with an SD card you will need to make use of the SPI bus (see earlier) which is available on digital I/O pins 11, 12, and 13 of the Arduino Uno. A further pin must be used to select the SD card via the chip select (CS) pin. On the Uno this is usually pin-10 (the hardware SS pin) but an alternative pin can be specified in the call to `SD.begin()`. Note that even if you don't use the hardware SS pin, it must be left as an output or the SD library will not function.

At the start of your code you will need to include the SPI and SD card libraries:

```
// Include the SD and SPI libraries
#include <SPI.h>
#include <SD.h>
```

Next you will need to set up the variables that you will use in the SD library:


```
// Set up variables for use with the SD library
Sd2Card card;
SdVolume volume;
SdFile root;
```

The next step is rather important because you will need to specify the pin number

**Table 5.2 SPI implementation in the Arduino Uno**

Designation	Function	Direction	Uno pin
SCLK	Serial clock	Output from Uno	13
MOSI	Master output/slave input	Output from Uno	11
MISO	Master input/slave output	Input to Uno	12
CS/SS	Chip select/slave select	Output from Uno	10
GND	Ground	Common	GND



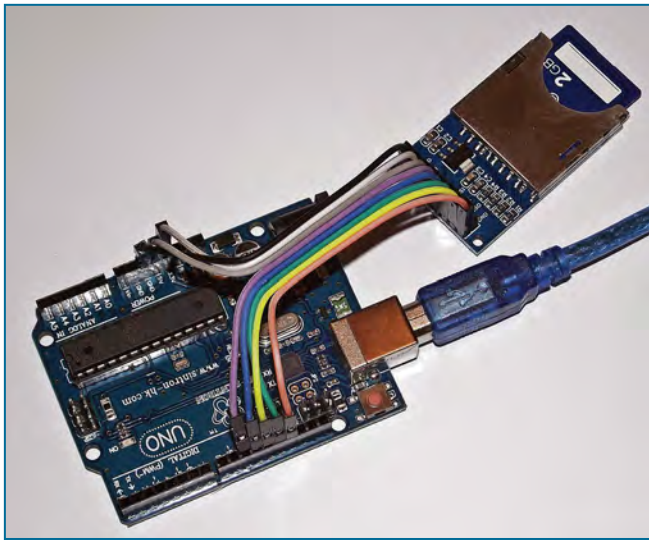

**Fig.5.5. An SD card module connected to an Arduino Uno using the SPI bus**

that will be used for the chip select (CS) signal to the SD module. Because this varies with SD card modules and shields from different manufacturers you will need to check the documentation supplied. The standard Arduino Ethernet shield and several types of stand-alone SD card module use pin-4, while Adafruit SD shields and others appear to use pin-10, and Sparkfun shields use pin-8. In the code fragment that follows we have used pin-10 for use with the SD card module shown in Fig.5.5.

```
// CS signal (change as required)
const int chipSelect = 10;
```

### Testing the SD card interface


The best way to test an SD card module or shield and (also to get information on the SD card that you're using) is to use the CardInfo program supplied with the examples in the Arduino IDE. To locate this program you need to select the File option from the main menu and then Examples followed by SD from within the section marked 'Examples from libraries'. Finally, you can select CardInfo at the top of the list, as shown in Fig.5.6 and upload it to your Arduino. At this point you might need to modify the example program so that the correct pin number is used for the card's chip select (CS) signal, as described above.

The CardInfo example first checks that the interface is working and that there's an SD card present. If this is not the case an error message like that shown in Fig.5.7 will appear when you first open the Serial Monitor in the Arduino IDE. If everything is working correctly and the card is functional you will be presented with summary information like that shown in Fig.5.8. Note that this displays some useful data on your card, including the file system (FAT16 in this case) and the size of the card (2GB in this case). You should also be presented with a list of files present on the card. In this case, four files are stored on the SD card; one text file, one web page, one data file, and one image file (see Fig.5.8). The date and size of each of these files is given in bytes. Note that the files are shown here sorted in order of size, with the smallest first.

### Reading and writing data

Data can be very easily written to an SD card or read from it. First you will need to initialize the card. This can be done using a few lines of code:

```
Serial.print("Initializing SD card...");
if (!SD.begin(10)) {
  Serial.println("Card not ready!");
  return;
}
Serial.println("Card ready!");
```

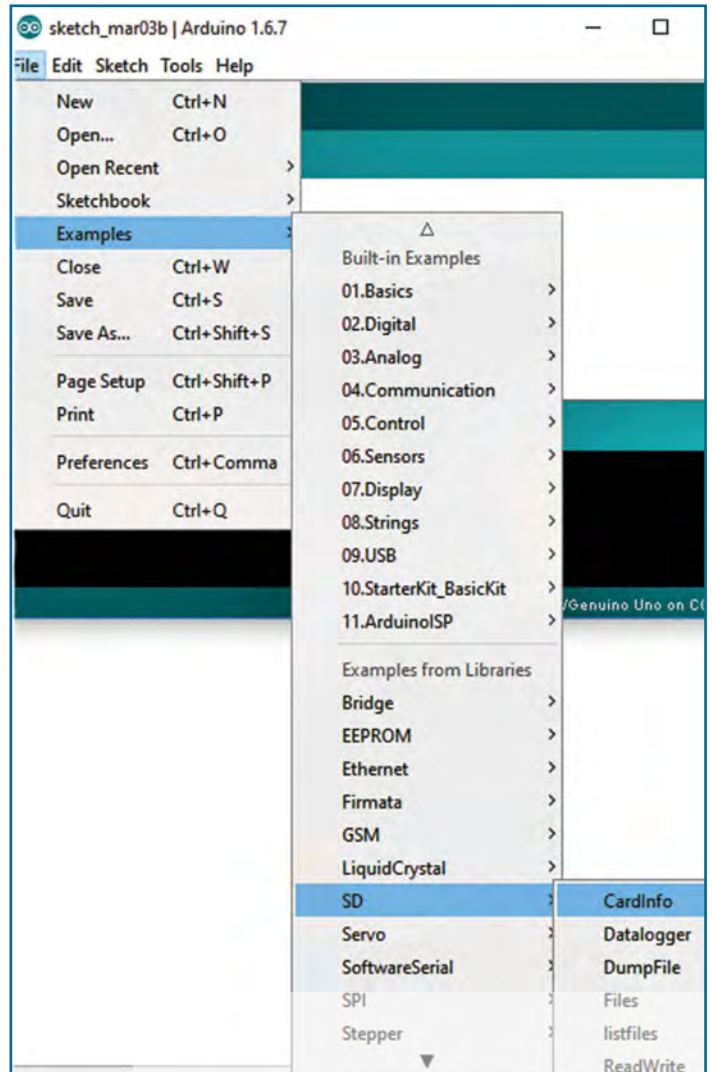


**Fig.5.6. Selecting the CardInfo example program**

Notice in this code that we've explicitly stated the pin used for the CS signal (in this case pin-10). We could do this in a more elegant way by defining the chip select pin as an integer at the start of the code, like this:

```
const int chipSelect = 10; // CS on pin-10
```

We would then need to change the initialising code so that it reads as follows:

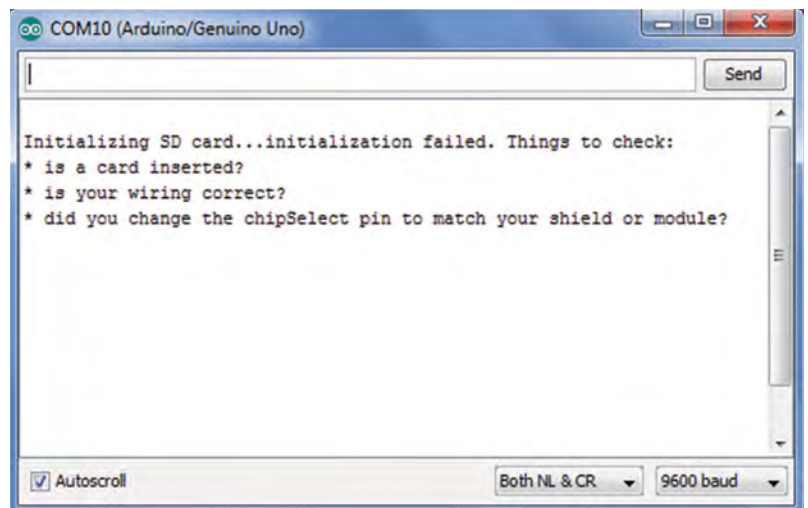

**Fig.5.7. When an SD card is not present or non-functional an error message will appear in the Serial Monitor window**

```
Serial.print("Initializing SD card...");
if (!SD.begin(chipSelect)) {
  Serial.println("Card not ready!");
  return;
}
Serial.println("Card ready!");
```

Before you can write to a file you need to open it using the `SD.open()` function, as follows:

```
myFile = SD.open("data.dat", FILE_WRITE);
```

If the file opens without an error you will be able to write to it. If `myFile` returns true, then the file has been opened, but if `myFile` is false, then an error will have occurred and you will be unable to write to the file. Here's some code that writes a series of values to the file that we've (hopefully) just opened (note that you will need to close the file when you have finished writing to it):

```
if (myFile) {
  Serial.print("Writing file ...");
  myFile.println("207, 188, 219, 155, 0");
  myFile.close(); // Close the file
  Serial.println(" done.");
} else {
  // It didn't open so print an error message
  Serial.println("Error opening the file!");
}
```


Reading a file is just as easy. First you need to open the file for reading:

```
myFile = SD.open("test.txt");
```


Then you need to read data from the file, sending it to the Serial Monitor until you reach the end:

```
if (myFile) {
  Serial.println("test.txt:");
  while (myFile.available()) {
    Serial.write(myFile.read());
  }
  myFile.close(); // Close the file
} else {
  // It didn't open so print an error message
  Serial.println("Error opening the file!");
}
```


If you need to see an example of how this code works, take a look in the Example file under the heading SD and ReadWrite in the Arduino IDE.

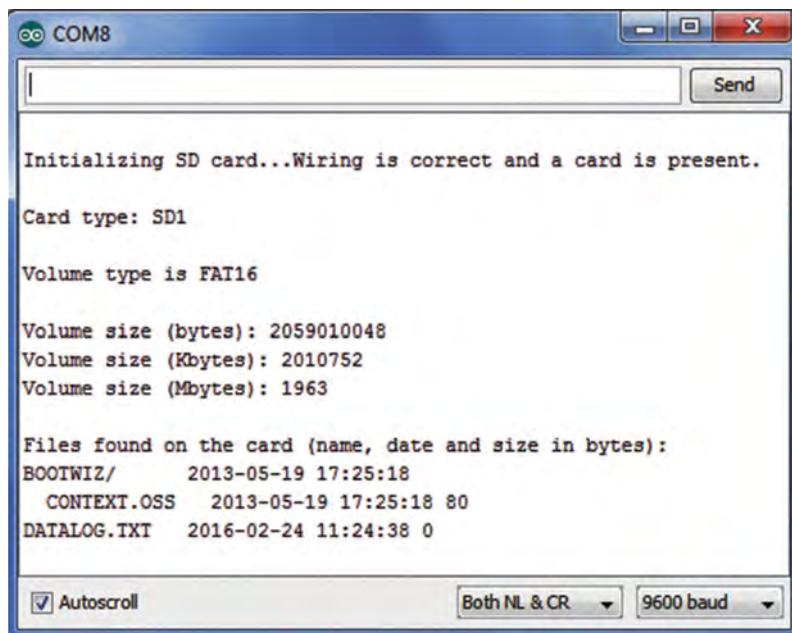

**Fig.5.8. CardInfo displays some useful information about the SD card**

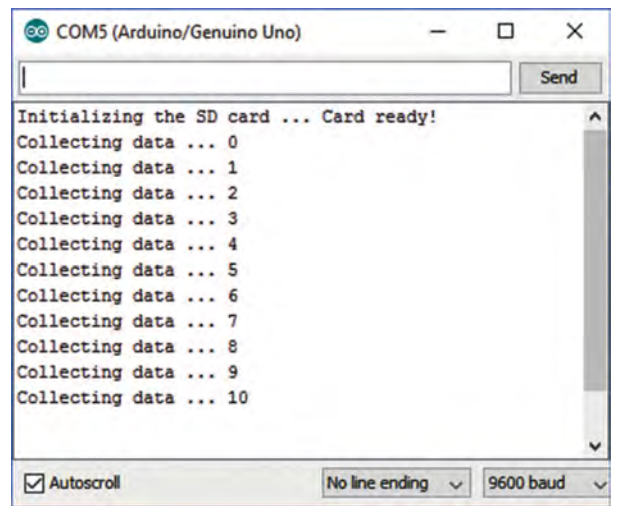

**Fig.5.9. The Serial Monitor confirms that the SD card is ready and that data is being captured**

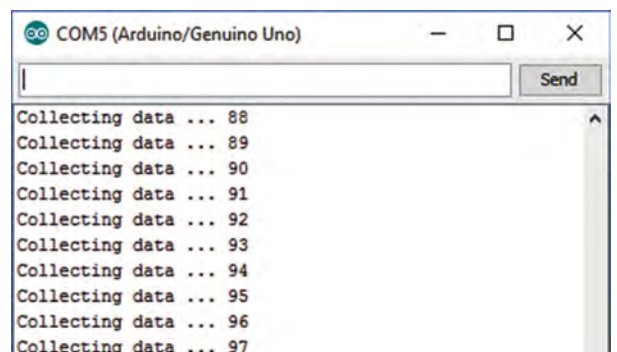

**Fig.5.10. After 100 data values have been logged and saved the data file is complete**

## Get Real: environmental monitor

In this month's *Get Real* we will be describing another useful project that has a wide range of applications in the home and at work. This takes the form of an environmental monitor that will record relative humidity, temperature (in °C and °F), and heat index. Large amounts of data can be captured and stored on a standard SD card and then used for later analysis with virtually any spreadsheet package. The environmental monitor uses a popular low-cost temperature sensor, the DHT11. A typical application for this *Get Real* project would be monitoring the humidity and temperature in a greenhouse, or in any area where plants are cultivated.

### You will need:

- Arduino Uno with power supply
- USB Type-A to Type-B cable
- Computer with an available powered USB port
- 1 DHT11 humidity/temperature sensor
- 1 Arduino Uno SD card shield
- 1 SPST switch, S1
- 1 4.7kΩ resistor, R1 (see text)
- 1 9V battery or DC power supply, B1
- Connecting wires and PCB headers



### Listing 5.2 A simple Arduino data logging application

```
/* SD card datalogger - reads analogue input A0 and records 100
data values, one every second */

#include <SPI.h> // Include the SPI library
#include <SD.h> // Include the SD library


const int chipSelect = 10; // Change as required by the hardware
const int analogPin = 0; // Input to analogue A0
File outputFile;

void setup()
{
  Serial.begin(9600); // Open the serial monitor
  while (!Serial) {
    ; // Wait for the serial port to connect
  }
  Serial.print("Initializing the SD card ... ");
  if (!SD.begin(chipSelect)) {
    Serial.println("Card not ready!");
    while (1) ;
  }

  Serial.println("Card ready!");

  outputFile = SD.open("voltage.dat", FILE_WRITE);
  if (!outputFile) {
    Serial.println("Could not open the file!");
    while (1) ; // Error so wait for user intervention
  }
}

void loop()
{
  int count = 0; // Loop counter
  while (count < 100) {
    Serial.print("Collecting data ... ");
    Serial.println(count);
    String dataString = ""; // Create a string to hold the data
    int input = analogRead(analogPin); // Read the input
    dataString += String(input); // Add it to the string
    outputFile.println(dataString); // Write data to the file
    outputFile.flush(); // and then flush the buffer
    // Take 1 measurement every second
    delay(1000);
    count = count + 1; // Increment the count
  }
  Serial.println("Data file created/appended!");
  while (1) ; // Finished so wait for user intervention
}
```

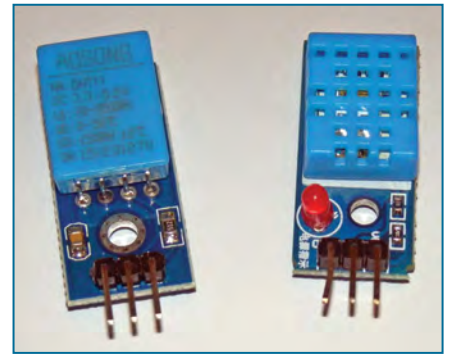

**Fig.5.12. Two DHT11 combined humidity/temperature sensors**

components and shows just how easy it can be to use an Arduino in a simple but worthwhile application. If you would prefer not to use an SD card shield, you can make use of an SD card module like the one that we used earlier in *Coding Quickstart* – the choice is yours!

The SD card shield mounts directly over the Arduino Uno and it provides a convenient and low-cost way of assembling the components and making connections to the Uno's I/O and power headers. The DHT11 humidity/temperature sensor is normally supplied already mounted on a small printed circuit board (see Fig.5.12) and it will only require three short male/female leads to make the required connections to the Uno's I/O and power connections. If necessary, the DHT11 can be mounted in a small enclosure, taking care to ensure that the sensor is exposed to the external environment. For obvious reasons it should not be mounted in a sealed enclosure!


If you look carefully at Fig.5.12 you will notice that the basic DHT11 sensor is supplied in a small four-pin package, while the printed circuit board has only three pin connections. These pins are often labelled, GND, OUT (for data), and Vs, as shown in Fig.5.13. Note that differently labelled connections are used by different manufacturers, so it is wise to check the actual pin markings on the particular module that you use. Note also that if you are using the basic sensor in its four-pin package you will need to ensure that a 10kΩ resistor is connected between the data terminal (OUT) and the positive supply (Vs or Vcc). This 'pull-up' resistor is not needed if your sensor is supplied already mounted on printed circuit board which has its own 'pull-up' resistor fitted.

When outputting raw temperature and humidity values the 8-bit resolution of the DHT11 humidity/temperature sensor supplies only the decimal part of each, keeping the fractional part zero. The more expensive (and also more accurate) DH21 and 22 sensors fill the fractional parts with data. However, with the lower-cost device the fractional part is not really important as it is usually less than the accuracy of the sensor (which is quoted as

### Circuit

The complete circuit of our Arduino Uno environmental monitor is shown

in Fig.5.11. Apart from the DHT11 humidity/temperature sensor and the SD card shield, the circuit uses very few

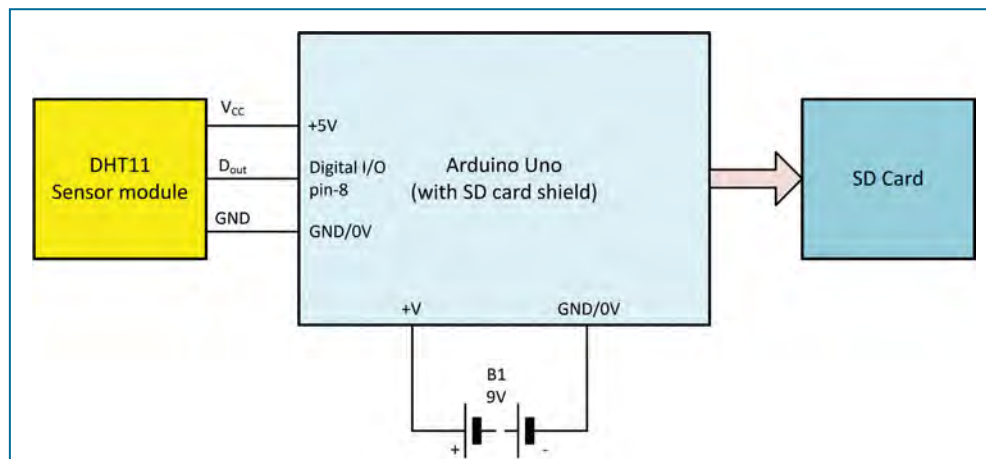

**Fig.5.11. Complete circuit of the Arduino-Uno-based environmental monitor**

typically  $\pm 4\%$  of relative humidity and  $\pm 2^\circ\text{C}$  for temperature). The DHT11 device is specified for a temperature range from  $0^\circ\text{C}$  to  $50^\circ\text{C}$  and relative humidity from 20% to 90%. The sensor has a typical response time of 10s and is specified for a maximum cable length of about 20m.

### Code

Listing 5.3 shows the complete code for the Arduino Uno environmental monitor. As always, we've included numerous comments in the code to help you understand what's going on. The code requires three libraries: DHT.h, SPI.h and SD.h. The first of these provides functions that facilitate the use of the DHT family of humidity/temperature sensors, while the second deals with the serial peripheral interface (SPI) used by the sensor. The third provides the functions associated with reading from and writing to the SD card. Note that if you are using an earlier version of the Arduino IDE you might also need to include the mathematics library that provides the function for rounding the temperature values before they are stored on the SD card, math.h. The rounding function is important to remove the fractional part of the values returned from the DHT11 sensor which might otherwise confuse a conventional spreadsheet program (it might regard the data as text rather than numerical).

For demonstration purposes we've restricted the number of data values captured to 20. We've also kept the interval between capturing data values to the minimum recommended. In practice, you would want to increase the number of times around the loop and also the interval between readings. For stand-alone applications you will also need to remove the serial monitor functions because they will normally only be required for local testing.

As with our previous *Get Real* projects, the code should first be entered into the IDE and then saved before compiling and uploading to the Uno, as described in last month's *Arduino Workshop*. When you have debugged and corrected your code don't forget to save it by clicking on 'File' and 'Save' or 'Save As...'. Next, click on 'Sketch' and 'Verify/Compile'. Any compilation errors will then be reported in the window at the bottom of the IDE. Don't forget that, if they are not already present, you may need to add library files using the IDE's File Manager. The procedure for adding and managing library files was described in Part Three of *Teach-In 2016*.

### Testing

When you've corrected any coding errors that the compiler reports you will be ready to upload your code to the Uno. Just click on the upload arrow and watch the progress report. After the Uno performs a reset you should open the serial monitor and check that the SD card has been detected. If the SD card is not present, or if the SD card

### Listing 5.3 Code for the simple Arduino-Uno-based environmental monitor

```
/* Humidity, temperature and heat index data logging with a
DHT11 sensor. Records data on an SD card */

#include "DHT.h"          // Include the sensor library
#include <SPI.h>           // Include the SPI library
#include <SD.h>            // Include the SD library
#define DHTPIN 8          // Sensor connected to digital I/O pin-8
#define DHTTYPE DHT11
DHT dht(DHTPIN, DHTTYPE);
File outputFile;
const int chipSelect = 10; // Change as required for the SD card

void setup() {
    dht.begin();
    Serial.begin(9600); // serial monitor commands can be removed

    if (!SD.begin(chipSelect)) {
        Serial.println("SD card not present or not recognized");
        return;
    }
    outputFile = SD.open("htsdata.dat", FILE_WRITE);
    Serial.println("Ready .... collecting data!");
}

void loop()
{
    int count = 0; // Loop counter
    while (count < 20) { // Change as required
        delay(10000); // Set the interval between measurements
        float h = dht.readHumidity();
        // Read temperature as Celsius (the default)
        float t = dht.readTemperature();
        // Read temperature as Fahrenheit (isFahrenheit = true)
        float f = dht.readTemperature(true);
        // Compute heat index in Fahrenheit (the default)
        float hif = dht.computeHeatIndex(f, h);
        // Compute heat index in Celsius (isFahreheit = false)
        float hic = dht.computeHeatIndex(t, h, false);
        // Prepare data to be written to the card as an ASCII string
        String dataString = ""; // Create a string to hold the data
        dataString += String(round(h)); // Add humidity
        dataString += ","; // Comma separator
        dataString += String(round(t)); // Add raw temp in deg.C
        dataString += ","; // Comma separator
        dataString += String(round(f)); // Add raw temp in deg.F
        dataString += ","; // Comma separator
        dataString += String(round(hic)); // Centigrade heat index
        dataString += ","; // Comma separator
        dataString += String(round(hif)); // Fahrenheit heat index
        outputFile.println(dataString); // Write the data to the file
        outputFile.flush(); // ... and then flush the buffer
        count = count + 1; // Increment the count
    }
    outputFile.close();
    Serial.println("Finished ... data ready!");
    while (1) ; // Finished so wait for user intervention
}
```

interface is not functioning correctly, the program will stop and an error message will appear. If this is the case the first thing to check is that you have set the chip select line correctly. Depending on the type of SD card interface, this will usually be 4, 8 or 10.

Once the interface is ready it will start to collect data, writing it to the SD card on each pass through the loop. You should always wait until the program terminates before attempting to remove the SD card so that you can transfer the data to a PC or other device. If you run the program several times (without

removing the SD card) you will find that further data will be appended to the file. If necessary, you can always remove the SD card, place it in a PC card reader slot and simply rename the file manually.

The data stored on the SD card is in comma-delimited format. Each time round the loop five data values are stored in the file, namely:

1. The relative humidity (as a percentage)
2. The raw temperature in  $^\circ\text{C}$
3. The raw temperature in  $^\circ\text{F}$
4. The Centigrade heat index
5. The Fahrenheit heat index.



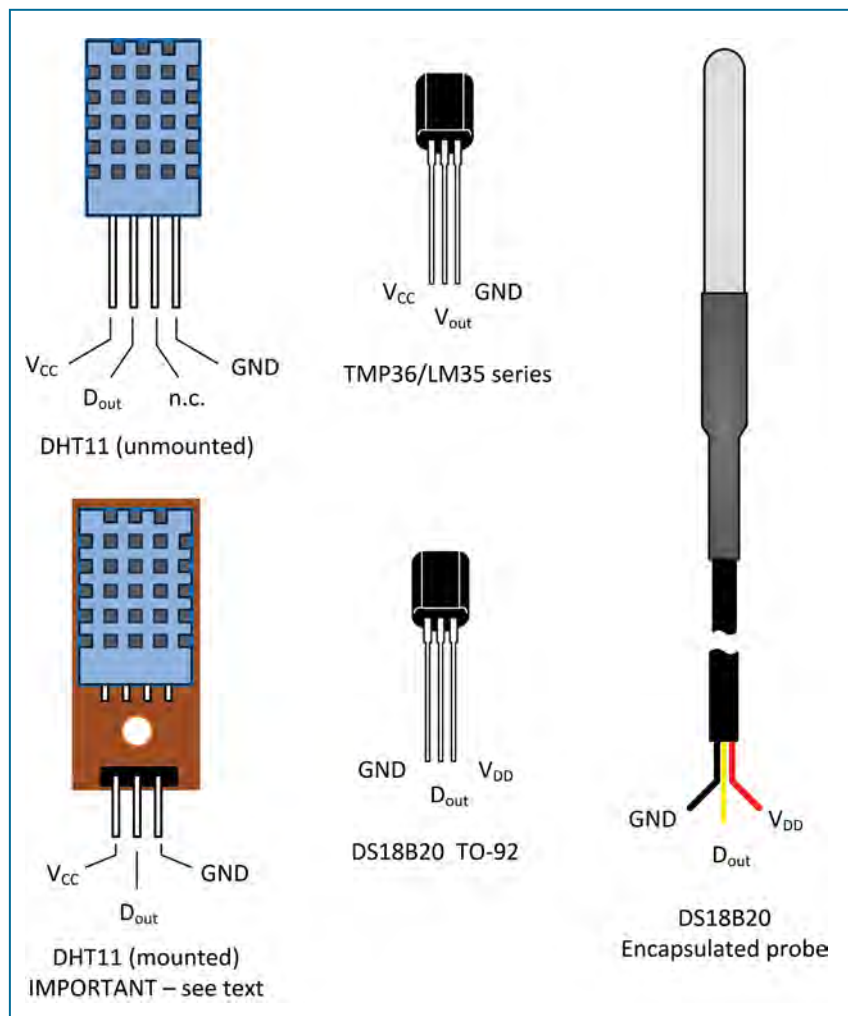


Fig.5.13. Pin connections for various humidity/temperature sensors

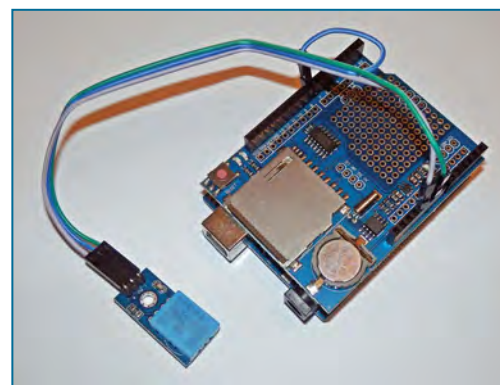


Fig.5.14. Complete Arduino Uno environmental monitor showing the SD card shield / DHT11 humidity/temperature sensor

	A	B	C	D	E	F
1	25	29	91	31	88	
2	25	30	86	28	83	
3	26	31	88	29	85	
4	26	32	90	30	87	
5	27	32	90	30	87	
6	26	33	91	31	89	
7	26	34	93	33	91	
8	25	35	95	34	93	
9	25	36	97	35	95	
10	24	37	99	36	97	
11	24	37	99	36	97	
12	24	38	100	38	100	
13	24	38	100	38	100	
14	24	38	100	38	100	
15	23	36	97	33	101	
16	23	36	97	33	101	
17	23	39	102	39	102	
18	23	40	104	40	105	
19	23	40	104	40	105	
20	22	41	106	42	107	

Fig.5.15. Captured data is easily imported into a spreadsheet package for analysis

If you don't require all of these values you can simply comment out the ones that you don't need. However, if you import the data into a spreadsheet (such that each set of values appears in a different column) you can easily operate on just those that you need. Note that, in common with many spreadsheet packages, if you open the data file in Excel you will need to specify that the file uses 'delimiters' and that the character used as the delimiter is a comma. Fig.5.15 shows how a typical set of data appears when imported into Excel, while Fig.5.16 shows how the data can be represented visually within Excel.


#### Going further

As always, there's a great deal of scope for going further with our Arduino-based environmental monitor. Alarms could be set when critical values are detected and outputs could be used to operate indicators, piezoelectric sounders or relays. Another refinement might be date/time stamping of the filename (we will be looking at this in a later instalment of *Teach-In 2016*) so that unique names are generated each time the program is run. All of this is relatively simple to do and will provide you with a great opportunity to further develop your coding skills.

#### Next month

In next month's *Teach-In 2016* we will be looking at ways in which an Arduino can communicate with remote devices using low-cost wireless modules. To this end, *Arduino Workshop* will introduce wireless modules while *Arduino World* looks at short-range wireless systems that will allow you to send data from one Arduino to another. Our programming feature, *Coding Quickstart*, introduces the RadioHead Packet Radio library for embedded microprocessors. Finally, our *Get Real* project will take the form of a simple wireless-linked rain alarm.

Fig.5.16. A graph produced by Microsoft Excel showing how the humidity (blue line) and temperature (orange line) vary during a period in which 20 sets of data have been captured by the Arduino Uno environmental monitor

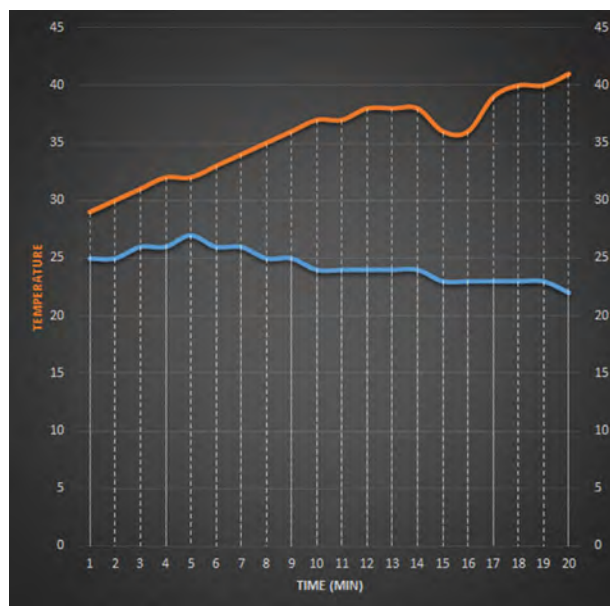

Today, Lord Alan Sugar is perhaps best known for his appearances on television as the gruff hirer and firer in *The Apprentice*. However, if you grew up in the 1970s, 80s or 90s then it will be his market-dominating, keenly priced electronic equipment that you associate with the name 'Sugar'. Alan Winstanley reviews the entertaining autobiography of a giant of Britain's retail electronics industry.

**ALAN SUGAR** is the name behind 'Amstrad', a brand that will be familiar to European consumers of audio and home computer equipment from the 1980s onwards. His story is a genuine and warming rags-to-riches tale and his autobiography charts the ascent of Alan (now Lord) Sugar from boyhood. As a lad from the East End of London, his opportunistic approach to life took shape early on, as he describes how, aged 11, he collected woollen offcuts from a garment factory to re-sell to a rag-and-bone merchant; he wheeled pramloads of tar-impregnated wooden blocks from roadworks and resold them as firelighters; he would even bottle and sell ginger beer. He progressed into amateur photography and repackaged large cans of 35mm film into cartridges to resell to his schoolmates: anything to earn some precious pocket-money.

He describes the incomprehension felt when he was gradually cold-shouldered by his East-End friends, simply because he came from a Jewish family. Undeterred, he writes how he left school and sought a 'scientific' job but failed an interview for a trainee programmer with IBM. Very satisfyingly, 24 years later he would sign a licensing agreement with IBM and snatch 30 percent of the European PC market away from them; he also bought IBM's European HQ in London for £112 million (\$168 million), he writes with justifiable pride.

The principles of business were fast sinking in, and he learned some painful lessons along the way. Seizing


opportunities, sourcing products, marketing and reselling almost anything for a profit, business became his lifeblood. As a young salesman for various electrical wholesalers, he learned of brands, customers, profit margins and how the 'electricals' sector worked. One shop has a stack of faulty TV sets going free, so Alan Sugar hit upon the idea of reconditioning and reselling them himself. Eventually this lucrative sideline allowed him to quit the day job and set up his own business and the AMS Trading Company was born, selling car aerials.

His rise to success in Europe's audio and computer market would be spectacular. Along the way he introduced injection-moulded record deck covers, vinyl-covered loudspeakers (a tough sell!), the 'tower' Hi-Fi and twin-cassette decks, all industry firsts in their time. The book describes in captivating detail how he launched his own British-made audio range at affordable prices, dealing with retail chains like Comet, Dixons, Laskys, Currys and others. He shares some comical nuggets about Amstrad product development (using buttons from the hotel sewing kit to mark out the apertures for a CB handset, for example). An unswerving hands-on man, the book is a treasure trove of detail that spells out the nitty-gritty of his career in those pioneering days: you can almost smell the solder fumes at times.
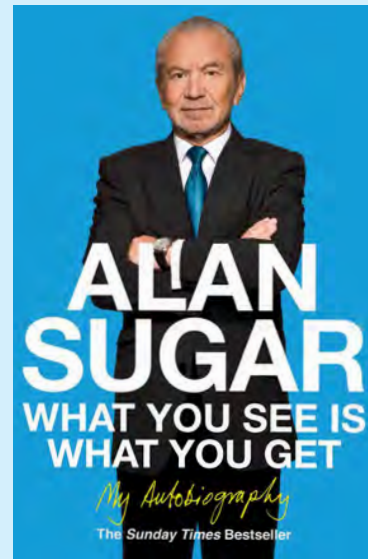
#### From Hi-Fi to PCW

The audio market then peaking, I will be forever grateful that Alan Sugar diversified in the mid-1980s and produced a highly successful self-contained word processor, the famous Amstrad PCW range – a machine that played a role in shaping my own early career. Amstrad then rescued the Sinclair brand, and the autobiography lays bare the almost unbelievable gamble that he took before closing this groundbreaking computer deal.

As you would expect, *What You See Is What You Get* is a very frank, candid and often abrasive insight into Lord Sugar's success story, written exactly as he speaks and his opinions on some British brands and institutions (unprintable in EPE!) pull no punches. It charts his life from a council-flat upbringing all the way to his entry to the House of Lords and the firm's acquisition by BSkyB. As someone whose life embraced the Amstrad brand in the 1980s and 1990s, I found Alan Sugar's story an enthralling and inspirational one and I simply could not put the book down. Readers of my generation will certainly enjoy it.



**What You See Is What You Get**  
Alan Sugar  
First published 2010  
Pan Books  
ISBN 978-0-330-52047-8

Get the answer you've been looking for



Vist the EPE Chat Zone  
**[www.epemag.com](http://www.epemag.com)**



## ZEN50

### Zener Diode Analyser (inc. LEDs, TVSs etc)

#### New product!

Introducing the new *Atlas ZEN* (model ZEN50) for testing Zeners (including Avalanche diodes) and many other components.

- Measure Zener Voltage (from 0.00 up to 50.00V!)
- Measure Slope Resistance.
- Selectable test current: 2mA, 5mA, 10mA and 15mA.
- Very low duty cycle to minimise temperature rise.
- Continuous measurements.
- Single AAA battery (included) with very long battery life.
- Gold plated croc clips included.
- Can measure forward voltage of LEDs and LED strings too.



**£39.00**  
£32.50+VAT

## LCR45

### LCR and Impedance Meter with Auto and Manual modes

#### New product!

Introducing a new powerful LCR meter that not only identifies and measures your passive components (Inductors, Capacitors and Resistors) but also measures complex impedance, magnitude of impedance with phase and admittance too! Auto and Manual test modes allow you to specify the test frequency and component type.

- Continuous fluid measurements.
- Improved measurement resolution: (<0.2μH, <0.2pF).
- Test frequencies: DC, 1kHz, 15kHz, 200kHz.
- Measure the true impedance of speakers and more.
- Great for hobbyists and professionals.



**£90.00**  
£75.00+VAT

## DCA55

### Semiconductor Analyser - Identify your semi's

#### New low price!

Connect any way round to identify the type of component and the pinout! Also measures many parameters including transistor gain, base-emitter voltages, MOSFET thresholds, LED voltages etc. Complete with a comprehensive illustrated user guide. Includes an Alkaline battery so you're ready to go straight away.

- Transistors (including NPN/PNP, darlington, silicon and germanium).
- Diodes and LEDs.
- MOSFETs.
- Measure  $h_{FE}$ .
- Gold plated hook probes.
- Free technical support.
- 2 year warranty.




**£48.00**  
£40.00+VAT

## DCA75

### Advanced Semiconductor Analyser and Curve Tracer
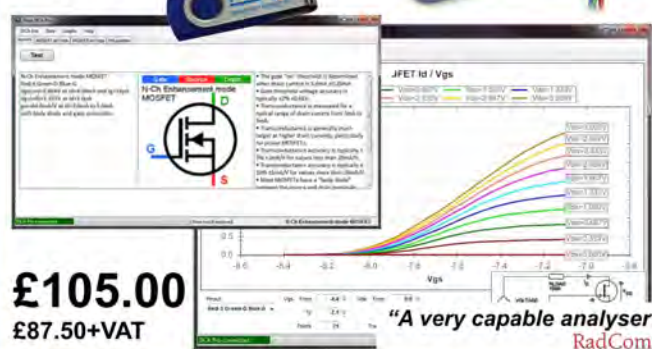
#### New low price!

The *DCA Pro* features a new graphics display showing you detailed component schematics. Built-in USB offers amazing PC based features too such as curve tracing and detailed analysis in Excel. PC software supplied on a USB Flash Drive. Includes Alkaline AAA battery and comprehensive user guide.



**£105.00**  
£87.50+VAT

"A very capable analyser"  
RadCom

It's only possible to show summary specifications here. Please ask if you'd like detailed data. Further information is also available on our website. Product price refunded if you're not happy.

Tel. 01298 70012  
[www.peakelec.co.uk](http://www.peakelec.co.uk)  
[sales@peakelec.co.uk](mailto:sales@peakelec.co.uk)

Atlas House, 2 Kiln Lane  
Harpur Hill Business Park  
Buxton, Derbyshire  
SK17 9JL, UK

Follow us on twitter  
for tips, tricks and  
news.  
 @peakatlas



We can supply back issues of *EPE* by post, most issues from the past five years are available. An *EPE* index for the last five years is also available at [www.epemag.com](http://www.epemag.com). Where we are unable to provide a back issue a photocopy of any one article (or one part of a series) can be purchased for the same price. Issues from Jan. 99 are available on CD-ROM or DVD-ROM – and back issues from recent years are also available to download from [www.epemag.com](http://www.epemag.com). Please make sure all components are still available before commencing any project from a back-dated issue.

## DID YOU MISS THESE?



## BACK ISSUES ONLY £5.00 (each inc. UK p&p.)

Overseas prices £5.80 each surface mail, £6.80 each airmail.

We can also supply issues from years: 2006 (except Jan., Feb., Mar., Apr., May, July), 2007 (except June, July, Aug), 2008 (except Aug, Nov, Dec) 2009 (except Jan, Mar, Apr.), 2010 (except May, June, July, August, Oct, Nov, Dec) 2011 (except Jan) Jan 2014.

### APR '15

**PROJECTS** • A Rubidium Frequency Standard For A Song • USB/RS-232C Interface • Building Our New Super Smooth, Full-Range, 10A/230V Speed Controller For Universal Motors – Part 2 •

**FEATURES** • Techno Talk • Teach-In 2015 – Part 3 • Interface • Net Work • Circuit Surgery • PIC n' Mix • Audio Out • Max's Cool Beans • RPI16OUT •

### MAY '15

**PROJECTS** • Low-cost Precision 10V DC Reference For Checking DMMs • Deluxe Fan Speed Controller • RGB LED Strip Driver •

**FEATURES** • Techno Talk • Teach-In 2015 – Part 4 • Practically Speaking • Net Work • Circuit Surgery • PIC n' Mix • Audio Out • Max's Cool Beans •

### JUNE '15

**PROJECTS** • Touch-Screen Digital Audio Recorder – Part 1 • Burp Charge Your Batteries •

**FEATURES** • Techno Talk • Teach-In 2015 – Part 5 • Interface • Net Work • Circuit Surgery • PIC n' Mix • Audio Out • Max's Cool Beans • Raspberry Pi For Dummies Book Review • Half A Century Of Power! •

### JULY '15

**PROJECTS** • L-O-O-O-N-G Gating Times For The 12-Digit High-Resolution Counter • Threshold Voltage Switch • Touch-Screen Digital Audio Recorder – Part 2 •

**FEATURES** • Techno Talk • Teach-In 2015 – Part 6 • Practically Speaking • Net Work • Circuit Surgery • PIC n' Mix • Audio Out • Max's Cool Beans •

### AUG '15

**PROJECTS** • Build The Nirvana Valve Sound Simulator • Resistor-Capacitor Decade Substitution Box • Tempmaster Thermostat MK3 •

**FEATURES** • Techno Talk • Teach-In 2015 – Part 7 • Interface • Net Work • Circuit Surgery • PIC n' Mix • Audio Out • Max's Cool Beans •

### SEPT '15

**PROJECTS** • Opto-Theremin – Part 1 • Wideband, Active Differential Oscilloscope Probe • Mini-D Stereo 10W/Channel Class-D Audio Amplifier •

**FEATURES** • Techno Talk • Teach-In 2015 – Part 8 • Practically Speaking • Net Work • Audio Out Special – Product Review • Circuit Surgery • Electronic Building Blocks • Audio Out • Max's Hot Beans •

### OCT '15

**PROJECTS** • Digital Effects Processor For Guitars And Musical Instruments • Opto-Theremin – Part 2 • Courtesy LED Lights Delay For Cars •

**FEATURES** • Techno Talk • Teach-In 2015 – Part 9 • Interface • Net Work • PIC n' Mix • Circuit Surgery • Electronic Building Blocks • Audio Out • Max's Cool Beans •

### NOV '15

**PROJECTS** • The Currawong 2x10W Valve Amplifier – Part 1 • 48V Dual Phantom Power Supply For DI Boxes And Condenser Microphones • Programmable Mains Timer With Remote Switching •

**FEATURES** • Techno Talk • Teach-In 2015 – Part 10 • Practically Speaking • Net Work • PIC n' Mix • Circuit Surgery • Electronic Building Blocks • Audio Out • Max's Hot Beans •

### DEC '15

**PROJECTS** • High-Energy Multi-Spark CDI For Performance Cars – Part 1 • The Currawong 10W Valve Amplifier – Part 2 • TDR Dongle For Oscilloscopes •

**FEATURES** • Techno Talk • Review – Dremel 3D Idea Builder • Interface • Net Work • PIC n' Mix • Circuit Surgery • Electronic Building Blocks • Audio Out • Max's Cool Beans •

### JAN '16

**PROJECTS** • Isolating High Voltage Probe For Oscilloscopes • High-Energy Multi-Spark CDI For Performance Cars – Part 2 • The Currawong 10W Valve Amplifier – Part 3 •

**FEATURES** • Techno Talk • Practically Speaking • Net Work • PIC n' Mix • Circuit Surgery • Electronic Building Blocks • Audio Out • Max's Cool Beans •

### FEB '16

**PROJECTS** • Spark Energy Meter – Part 1 • 6-Digit Retro Nixie Clock – Part 1 • CGA-to-VGA Video Converter •

**FEATURES** • Techno Talk • Teach-In 2016 – Exploring The Arduino – Part 1 • Audio Out • Gold Standard – The Art Of Electronics (3<sup>rd</sup> Edition) • Interface • Net Work • PIC n' Mix • Circuit Surgery • Electronic Building Blocks • Max's Hot Beans •

### MAR '16

**PROJECTS** • Spark Energy Meter – Part 2 • 6-Digit Retro Nixie Clock – Part 2 • Modifying The Currawong Valve Amplifier •

**FEATURES** • Techno Talk • Teach-In 2016 – Exploring The Arduino – Part 2 • Audio Out • Practically Speaking • Audio Out Special – Product Review • Net Work • PIC n' Mix • Circuit Surgery • Electronic Building Blocks • Max's Cool Beans •

### APR '16

**PROJECTS** • Appliance Insulation Tester • Low Frequency Distortion Analyser • Really Bright 12/24V LED Oyster Light •

**FEATURES** • Techno Talk • Teach-In 2016 – Exploring The Arduino – Part 3 • Audio Out • Interface • Net Work • PIC n' Mix • Circuit Surgery • Electronic Building Blocks • Max's Cool Beans •

### MAY '16

**PROJECTS** • 2-Channel Balanced Input Attenuator For Audio And Digital Scopes • Appliance Leakage Tester • 4-Output Universal Voltage Regulator •

**FEATURES** • Techno Talk • Teach-In 2016 – Exploring The Arduino – Part 4 • Practically Speaking • Net Work • PIC n' Mix • Circuit Surgery • Electronic Building Blocks • Max's Cool Beans •

## ORDER FORM – BACK ISSUES – PHOTOCOPIES – INDEXES

☐ Send back issues dated. ....

☐ Send photocopies of (article title and issue date) ....

Name .....

Address .....

Tel: .....

☐ I enclose cheque/P.O./bank draft to the value of £ .....

☐ Please charge my Visa/Mastercard/Maestro £ .....

Card No ..... Maestro Issue No .....

Valid From ..... Card Expiry Date ..... Card Security Code .....

(The last 3 digits on or just under the signature strip)

SEND TO: Everyday Practical Electronics, Wimborne Publishing Ltd., 113 Lynwood Drive, Merley, Wimborne, Dorset BH21 1UU.

Tel: 01202 880299. Fax: 01202 843233.

E-mail: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk) On-line Shop: [www.epemag.com](http://www.epemag.com)

Payments must be in £ sterling – cheque or bank draft drawn on a UK bank. Normally posted within seven days of receipt of order. Send a copy of this form, or order by letter if you do not wish to cut your issue. M06/16



GET THE  
LATEST COPY  
OF OUR  
TEACH-IN SERIES  
AVAILABLE  
NOW!

ON SALE in WHSmith and other  
independant newsagents from  
28th April 2016

**FREE CD-ROM**

# ELECTRONICS TEACH-IN 7

£8.99

FROM THE PUBLISHERS OF  
**EP&E** EVERYDAY PRACTICAL  
ELECTRONICS

## DISCRETE LINEAR CIRCUIT DESIGN

- Understand linear circuit design
- Design simple, but elegant circuits
- Learn with 'TINA' – modern CAD software
- Five projects to build: Pre-amp, Headphone Amp, Tone Control, VU-meter, High Performance Audio Power Amp




**FREE CD-ROM**  
ALL THE CIRCUIT  
SOFTWARE FOR  
THE TEACH-IN 7  
SERIES




**PLUS...**  
**AUDIO OUT**  
An analogue expert's take  
on specialist circuits

**PRACTICALLY SPEAKING**  
The techniques of project  
building

ISBN 978-1-898805-28-1



'A complete introduction to the design of analogue electronic circuits. Ideal for everyone interested in electronics as a hobby and for those studying technology at schools and colleges. Supplied with a free Cover-Mounted CDROM containing all the circuit software for the course, plus demo CAD software for use with the Teach-In series'

GET YOUR COPY TODAY JUST CALL 01202 880299  
OR VISIT OUR SECURE ONLINE SHOP AT [WWW.EPEMAG.COM](http://WWW.EPEMAG.COM)



# NET WORK

by Alan Winstanley



## It's a cardboard world

**I**n a former career, the writer designed, amongst other things, all kinds of consumer product packaging, even down to the humblest cardboard box. The joys and qualities of corrugations (known as 'flutes') of an 0201 double-wall corrugated carton (palletloads of them) made of 150 Kraft/Test B/C flute frequently received his earnest attention. The integrity of packing cases was tested by shipping full ones all the way to London and back, and if the contents were still intact on arrival then we had a winner. If you're interested, the industry styles for common cartons are depicted on manufacturers' websites such as: [www.allpack.co.uk/styles.htm](http://www.allpack.co.uk/styles.htm)

The applications for corrugated cardboard are legion, and the material's surprising strength can be realised by utilising the flutes perpendicular to the direction in which they run: it wraps around things easily in one direction, but if you roll some up into a solid shape the result is so strong that you can stand on its ends without a qualm. The world of virtual reality has also been harnessing the merits of corrugated board: specifically, 'Google Cardboard' is the name for Google's VR application and cheap and cheerful VR viewers made from cardboard now permit smartphone owners to immerse themselves in a virtual world, powered by the Internet. Now that you're intrigued, this month's *Net Work* gets to grips with Cardboard!

### VR headsets

Readers might have noticed online or TV adverts featuring the latest wave of VR headsets – large plastic visors held in place with headbands while the wearer turns and bobs around in any direction to view a 3D virtual environment (looking up at stars and galaxies, for example). These wrap-around viewers contain a smartphone running an app with fixed 'spectacle' lenses focussing on the phone's LCD screen. More expensive models might have adjustable lenses to focus the wearer's eyes on the display. Split-screen footage is viewed stereoscopically through the lenses and the wearer can 'travel' in three dimensions, perhaps taking a virtual tour of the Large Hadron Collider (LHC) or going on a rollercoaster ride. Movies can also be viewed privately this way.

Google Cardboard is a nifty example of lateral thinking that aims to bring the virtual world experience to anyone with a smartphone. There's no need to buy expensive, elaborate plastic visors when a Google Cardboard-compatible viewer can be produced cheaply from, er... cardboard! Google released blueprints for their viewer as open source, showing the dimensions and direction of those all-important flutes. Anyone can manufacture Cardboard viewers to this standard and a good variety is now readily available online. As smartphone screen sizes have grown within the last couple of years, Google's original effort announced in 2014 proved too small to contain the latest-generation phones, so Cardboard V2 is intended to accept any modern Android phone or iPhone up to 6-inch screen size. The new Cardboard V2 is also much easier to build than its predecessor (think of assembling R-Kive banker's



*Google Cardboard V2 viewer showing the smartphone positioned inside. The rear flap is secured with the Velcro fastener on top*

boxes, only smaller) and V2 has an improved 'switch', more of which shortly.

A Cardboard V2 viewer arrives in a small carton (what else?) that is precision diecut from E-flute corrugated sheet with an oleophobic (oil-repellant) skin-safe coating. To assemble, simply fold back the sides of the carton and secure them using the Velcro dots already in situ, which takes seconds.

### Board's eye view

All Google V2 Cardboard-compliant viewers are licensed to the same specification. For my own tests I chose the 'Minkanak Cardboard V2', which costs about £14 (\$20). The plastic stereoscopic lenses are the standard 80° 34mm (visible) Google spec. with 64mm, IPD (interpupillary distance) and the viewer has that all-important capacitive switch: this is effectively an elaborate cardboard lever that, when pressed, delivers a gentle 'tap' to the touchscreen using a small pillow of metallised conductive foam. This allows you to use on-screen menus and controls, or explore the virtual environment by pressing the button like a camera shutter to tap the screen. A stick-on piece of foam rubber, included as an extra, greatly improves comfort on the nose when holding the viewer up to your eyes: it's a must-have. An elastic headband is also bundled with the kit, which can be stuck onto the box using some Velcro strips supplied to make the visor hands-free. The purpose of a mysterious elastic band supplied with the kit is not explained anywhere. In fact, it acts as a simple grip to prevent the smartphone from sliding around. It's fitted on the base of the rear flap near the hinge perforation.

### Set up and use

Setting up and using Cardboard V2 could not be simpler. Some QR codes (see *Net Work*, August and September





*A capacitive button applies a gentle tap to the screen when pressed – this idea works well*

2011) printed on the instructions can be scanned to play an assembly video and also download some 3D apps for Android or iPhone. The Cardboard app is soon installed and a 'Viewer Profile' QR code printed on the viewer is scanned by the smartphone. This programs the Cardboard app for that individual visor's screen-to-lens distance, separation and other parameters incorporated by the manufacturer.


Also supplied is a blank NFC tag to stick inside the viewer, so by using a suitable app such as NFC Tools, users can make their NFC-enabled phone run the separate Cardboard app with one tap. (Details of using Near-Field Communications were outlined in *Net Work*, February 2014.) To program the NFC tag, open NFC Tools and choose to Add an Application Record, selecting Google Cardboard from the list of apps. Then write this to the NFC tag by tapping the tag with the phone, and then you can stick the programmed tag onto the rear flap. In future, the Cardboard app will open automatically on your phone when you tap the tag.

Users will soon recognise the new Cardboard icon that appears in compatible videos or apps. By tapping it, the smartphone switches to VR split-screen mode with a bold white line down the centre: this aligns with the V-notch in the viewer aperture, and then the phone is placed in the viewer and secured using the cardboard flap and Velcro fastener. The principle was effective enough with the author's HTC One phone.

The Cardboard app includes virtual tours and a basic Google Street View demo. Menus can be accessed on-screen by moving the VR viewer to align a dot or circle with a menu item, then press the 'camera button'. It works very well and in no time the author was taking a virtual tour of the Palace of Versailles, the brief tour enhanced by the stereo sound of the HTC One. With last month's column in mind, a very interesting virtual 360° tour of a Google data centre can also be taken.



*Smartphone in split-screen VR mode*

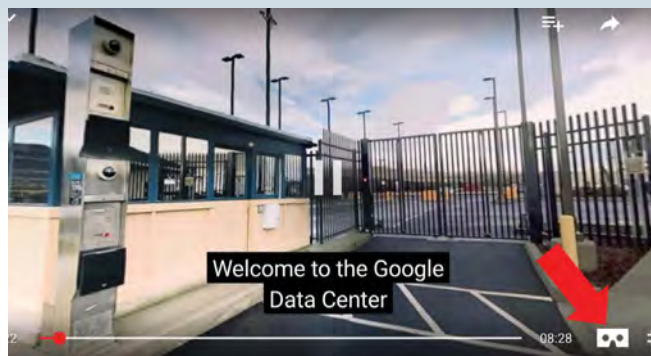

*A 360° Cardboard-compatible video, with Cardboard icon (arrowed)*

The Google Street View app takes on a whole new dimension – literally – when viewed through Cardboard. Traditionally, Windows PC users are probably used to opening Google Maps in a web browser and then dropping the yellow 'Pegman' icon onto a street to launch Street View at that location. An Android mobile phone includes a stand-alone Street View app, so if Wi-Fi is available you can open Street View and choose the 'Explore' menu. Swipe around to find a place of interest or type a location into the Search box. Pegman soon appears on the map and photo snapshots of that locality displays on-screen. Click a photo to enter Street View mode: if necessary, tap or swipe at the top to display the menu and the Cardboard icon will appear. Tap it and the screen changes to split-screen mode and the smartphone can now be inserted into the Cardboard viewer. If you're used to mousing around on a widescreen web browser then this setting-up process on a phone screen is pretty fiddly.

#### **Follow the arrows**

Navigating or looking around in Street View means turning one's head – the display changes view accordingly – and pressing the button when a Street View arrow icon is in view will move you to the next snapshot, in the same way that the PC-based version works. It is worth remembering that Google Street View may have several iterations of the same scene if Google re-photographs the locality several years later, and users can find themselves suddenly going back in time if the display reverts to an earlier version. This was the case with Wimborne's town centre, for example, which mysteriously changed to show a one-way traffic scene with smart new shops, before reverting to the old scene from years earlier. It is sometimes frustrating to get 'trapped' in a location and you may have to remove the phone and start again.

Over on Youtube, some videos are shot in 360° and can be viewed on Cardboard the same way. Other apps to explore are offered by the Cardboard app, or visit <https://www.google.com/get/cardboard/apps> or the Google Play Store to fetch more VR apps. Some file sizes are huge (350MB or more) and Wi-Fi is a must, and do note that a few may tempt you with in-app purchases too. Sadly, some promising-looking VR apps were a bit unstable on the author's phone and were quickly uninstalled, and one or two tended to flicker, which is possibly a hardware problem. However, the VR guide tour of a Google data centre worked perfectly and it was fascinating to experience the sight and sounds of a typical server building.

The cardboard casing itself is reasonably hardwearing and I estimate it should last a few months or so. The need to open and close the rear flap contributes most to wear and tear. Small Bluetooth wireless controllers are sold separately, which acts as a gamepad (joystick and button controller) or camera shutter. This removes the need to press the Cardboard button and will be handy if you wear the viewer using headbands; it means you can navigate around menus and options in hands-free mode.

Be warned that sometimes a lot of head-swivelling (body too!) comes as part of the deal, and sitting on my office swivel chair helped an awful lot! The 'floaty' feel of some apps may

bother some users and some scenes can sometimes drift a little. After a while, the process can become a bit dizzying, which can induce a little nausea if users overdo it – some users can only manage a few minutes before stopping. It's like getting used to life at sea.

Google Cardboard makes virtual reality more accessible and it is a remarkable achievement given the extent of technology and resources being offered to us, just for the price of a cardboard box. The Minkanak Cardboard V2 viewer, along with many alternatives, is readily available on Amazon and eBay, so now you can explore virtual reality cheaply and easily.

Still on a VR theme, cutting-edge virtual reality has also been applied to a familiar old retro toy in the shape of the View-Master Viewer that many of us grew up with as youngsters. Remember those enchanting circular film discs? Mattel's View-Master VR is the latest iteration of the classic toy, which uses an app and 'Experience Packs' such as Destinations or Space on a smartphone to produce an augmented and virtual reality experience through its viewer. It is intended for children aged seven years or older. More details are at: [www.view-master.com](http://www.view-master.com) or the YouTube channel at: <http://preview.tinyurl.com/j2jmkrg>. The View-Master VR viewer is readily available in major stores and online.

### 21st century radio


Somewhere in the bottom of a wardrobe – Ah, there it is! – lies our faithful old portable radio, which my counterparts on sister magazine *Radio Bygones* will recognise instantly. The Bush TR130 is a British design icon from the 1960s and apart from its crackly potentiometers, my one plays as well as ever. Its large air-spaced tuning capacitor is visible through the tuning scale, and its germanium transistors have held up well over the decades.



*In with the new... Goodman's Oxford BT is a fresh new version of the classic Bush TR130 portable radio*

Like the Mattel View-Master, the Bush TR130 has recently enjoyed a 21st Century makeover, taking the shape of a delightful remake sold under the popular Goodman's brand. The Goodman's Oxford BT is a cute DAB/FM portable radio in the same retro style housing of the Bush, with a modern technological twist up its sleeve. Bluetooth is built in, and there is also an NFC icon on the side of the radio. By tapping it with an NFC-enabled phone, the Goodman's Oxford BT pairs instantly with it to become a retro-styled Bluetooth loudspeaker.

I found this idea irresistible and treated the household to an Oxford BT moulded in an attractive sky blue plastic (other colours are available). The radio is extremely simple to use and the familiar-looking tuning control scrolls through a list of DAB stations. Reception and audio quality were crystal-clear. The Bluetooth pairing and NFC functions were totally flawless and – here's the *Net Work* interest – using my smartphone on Wi-Fi I quickly accessed music stored on my Synology NAS and played it over the Goodman's portable radio. NFC is still seen as a bit of a novelty and it was encouraging to see NFC being used sensibly in this way.

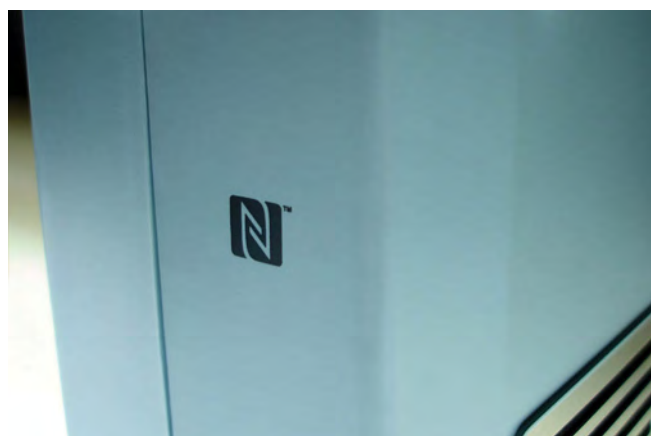


*Tap an NFC-enabled smartphone to pair it to the Goodman's Oxford BT*

Overall, it's a welcome and charming redesign of an old family favourite that works perfectly, drawing admiring comments from several visitors too. The Goodman's Oxford BT is battery (6 × C cells) or mains powered and is available from several online retailers including [very.co.uk](http://very.co.uk). Please check carefully before you buy: if you want the Bluetooth connectivity then be sure to seek out the newer BT version (also called Oxford II) and not the *earlier* Oxford radio, which is not Bluetooth or NFC enabled. More details are at: [www.goodmans.co.uk/product-oxford-bt.html](http://www.goodmans.co.uk/product-oxford-bt.html). Retro-styled tabletop 'heritage' radios are also available from Goodman's, which also offer Bluetooth connectivity the same way, providing a novel way of listening to your music over your local network.

See you next month, when I will bring you more news of current trends and online developments. You can email the author at: [alan@epemag.demon.co.uk](mailto:alan@epemag.demon.co.uk)

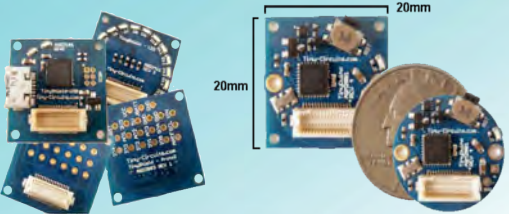
## Arduino Electronics

Upgrade your Arduino Electronics to the Next Generation with  
**TinyDuino**  
 As powerful as the Arduino Uno but smaller than a 2 pence coin.  
 Available from our eShop



All the power of the Arduino in a fraction of the space, great for building intelligence in to your projects.

Ultra Compact Shields




Total Stackup Height: 23.7mm (with 40 pins) with 5 Headers and Case Load Header

Complete with a wide and growing range of **TinyShields** - where will your next project take you?


Move up to the Next Generation!

Fantastic for schools especially D&T and Computing, meets the new requirements



As an authorised reseller with an educational and training focus we can support all aspects of this outstanding piece of kit!

Get yours today via our **eShop**



[www.eshop.icsat.co.uk](http://www.eshop.icsat.co.uk)



## Raspberry Pi 3

**IT DOES NOT** seem that long ago that the Raspberry Pi 2 Model B was launched, but the new Raspberry Pi 3 Model B (Fig.1) is now readily available. It was launched exactly four years after the original version was released onto the market, and sales of the various Raspberry Pi boards now exceeds eight million. Version 2 did not look significantly different to its predecessor, the Model B+, and visually there is not a great deal of difference between the new Raspberry Pi and the two previous versions (Fig.2). The audio, HDMI video, Ethernet, and four USB 2.0 ports are all there on the board, and in more or less the same places as before. Of more importance in the current context, it still has a 40-pin GPIO port that is unchanged from the B+ and Model 2 B, and with a suitable lead it can be used with hardware designed for use with the original 26-pin GPIO port.

### Lead free

There are some important enhancements on the new Raspberry Pi, in the form of wireless connectivity. It has both Bluetooth and Wi-Fi built-in. In addition to making it easier to connect the unit to the Internet, this should make it possible to use it with a wide range of hardware such as printers, keyboards, mice, and headphones without the need for any leads. The Raspberry Pi boards are all quite small, and unless fixed to something fairly substantial, a Pi board tends to go where the leads dictate, rather than where you would like to position it. The thicker leads can put quite a strain on the port connectors. Fewer leads might ease the situation, in addition to reducing the tangle of 'connection spaghetti' that you seem to end up with before too long.

The processor has been upgraded to a 1.2GHz 64-bit quad core ARM Cortex-A53 CPU. The higher clock speed and other improvements are said to give a speed increase of about 50 to 60 per cent compared to version 2 boards, and a potential tenfold increase over the original Raspberry Pi. With software that cannot exploit the four cores of the



Fig.1. The new Raspberry Pi 3 Model B retains the all-important GPIO port, which is a 40-pin type that is compatible with hardware for earlier versions. The new Pi also has built-in Wi-Fi and Bluetooth wireless connectivity

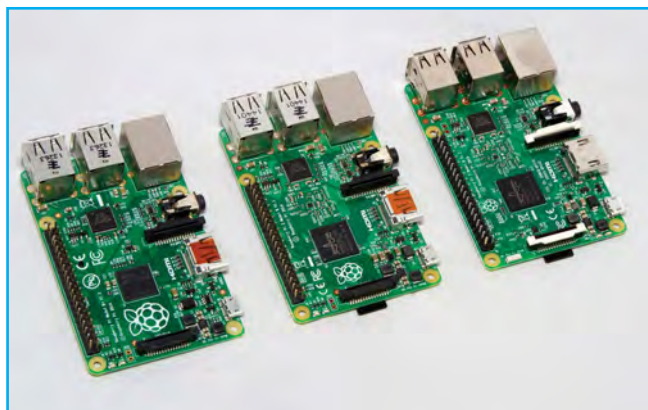


Fig.2. If you've seen one, you've seen 'em all. Visually there is little difference between the Model B+ (left), the Pi 2 Model B (middle), and the Pi 3 Model B (right)

processor, the new version is still about 2.5-times faster than the original model A/B boards.

There is more power available from the four USB ports, making it possible to use some peripherals directly, where a powered USB hub would be required with previous versions. However, a 2.5A power supply is now needed in order to ensure that the board itself, plus the USB ports do not pull the supply to an inadequate voltage and crash the computer. An approved 5.1V, 2.5A mains adapter is available (Fig.3), but for some reason this is not recommended for use as a general-purpose power supply for gadgets that have a mini USB power connector.

Adaptors with a lower current rating can be used with the Raspberry Pi 3, but the power available from the USB ports will be reduced accordingly. Also, it has to be borne in mind that the extra hardware of the new version, together with its higher clock frequency, result in the board itself



Fig.3. More power is needed to fully exploit the USB ports of the new Raspberry Pi. This is the official 5.1V, 2.5A mains power supply, complete with adaptors that enable it to be used internationally

having a higher current consumption than its predecessors. An adapter that is just about adequate with a previous version might not be up to the task of powering a version 3 board. I found that it worked all right with a 1.6A supply, but this probably leaves little current available for peripherals connected to the USB and GPIO ports. The USB ports are still of the USB 2 variety, not USB 3.

For the time being at any rate, no earlier versions are being discontinued with the introduction of the Raspberry Pi 3. If all you need is something like a model B+, then it should still be available.

### Counting on it

An ultra-simple capacitance meter project for the Raspberry Pi was described in the previous *Interface* article. This had limitations due to its use of the built-in timing facilities of Linux and the Python programming language. Better results can be obtained in many applications by using an external binary counter and clock oscillator. It is possible to count pulses on a GPIO input line, but using a Python program it is likely that pulses will be missed at input frequencies of anything more than a few kilohertz. An inexpensive binary counter chip can typically handle input frequencies of up to about 100MHz. The built-in timing facilities seem to struggle with even 1ms (one millisecond) resolution, but using an external crystal oscillator a resolution of 100ns (0.0001ms) is easily achieved.

The 74HC4040 is a good choice for a binary counter for use with a Raspberry Pi, since it is reasonably inexpensive, and works well on a 3.3V supply. This enables it to operate with the GPIO input/output lines without the need for any level shifting. The high-

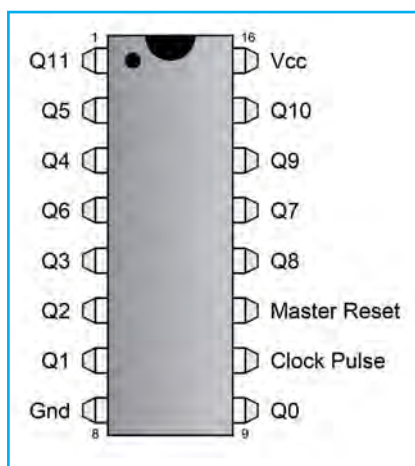


Fig.4. The pin functions for 16-pin DIL versions of the 74HC4040 and 4040B binary counter chips. Using a 3.3V supply the 74HC4040 can operate with clock frequencies up to at least 50MHz

speed CMOS version is preferable to the ordinary 4040B CMOS device because it can operate at much higher frequencies when a 3.3V supply must be used. The maximum clock frequency depends on the particular example of the chip and the load capacitance, but it should operate up to at least 50MHz, and in most cases it will go to 90MHz or more. The 4040B is limited to operation at no more than about 2MHz when used with a 3.3V supply, although this is certainly adequate for some applications.

Pin functions for the 16-pin DIL version of the 74HC4040 and 4040B chips are shown in Fig.4. It is basically a series of twelve divide-by-two circuits, with the outputs available on Q0 to Q11. This gives the required binary counter action, with Q0 and Q11 respectively providing the least- and most-significant bits of the count. The input signal is applied to the

negative-edge-triggered Clock Pulse input. Taking the Master Reset input high blocks the clock pulses and sets all twelve outputs low. Placing this input low activates the device, and the input pulses are then counted. If the maximum count of 4095 is exceeded, the count cycles back to zero and starts again from there. Any number of counters can be used in series to give a higher maximum count. It is just a matter of connecting the Q11 output of one counter to the Clock Pulse input of the next one in the chain. The Master Reset inputs are simply connected together and driven in unison.

### Throw of the die

As an initial experiment with an external counter I tried the circuit of Fig.5, which is intended to be used as the basis of a random number generator, and an electronic die. A common way of generating random numbers digitally is to have a counter that cycles through its full range at high speed. In order to produce a random number, it is just a matter of halting the count and reading the value stored in the counter. There is no way of predicting the number held in the counter at the instant the count is stopped, as it could be at any number in the full range of values covered by the counter. This method is analogous to some mechanical methods of generating random numbers, such as roulette wheels.

The clock signal is generated by a crystal-controlled Colpitts oscillator based on Tr1, which operates as an emitter follower. Crystal X1 effectively forms a centre-tapped tuned circuit in conjunction with C2 and C3. The voltage gain through Tr1 is slightly less than unity, and is not sufficient to sustain oscillation. However, in-phase feedback from the emitter of

Tr1 to the centre tap does produce oscillations due to the voltage step-up through the tuned circuit. Tr2 operates as a common-emitter amplifier, which ensures that there is a sufficiently strong output signal to drive the counter circuit reliably.

IC1 is the 74HC4040 binary counter. With a clock frequency of 10MHz it is essential to use a 74HC4040 for IC1, and not an ordinary CMOS 4040B. The Master Reset input at pin 11 is simply connected to the 0V supply rail because the starting count is unimportant in this application, and the counter must

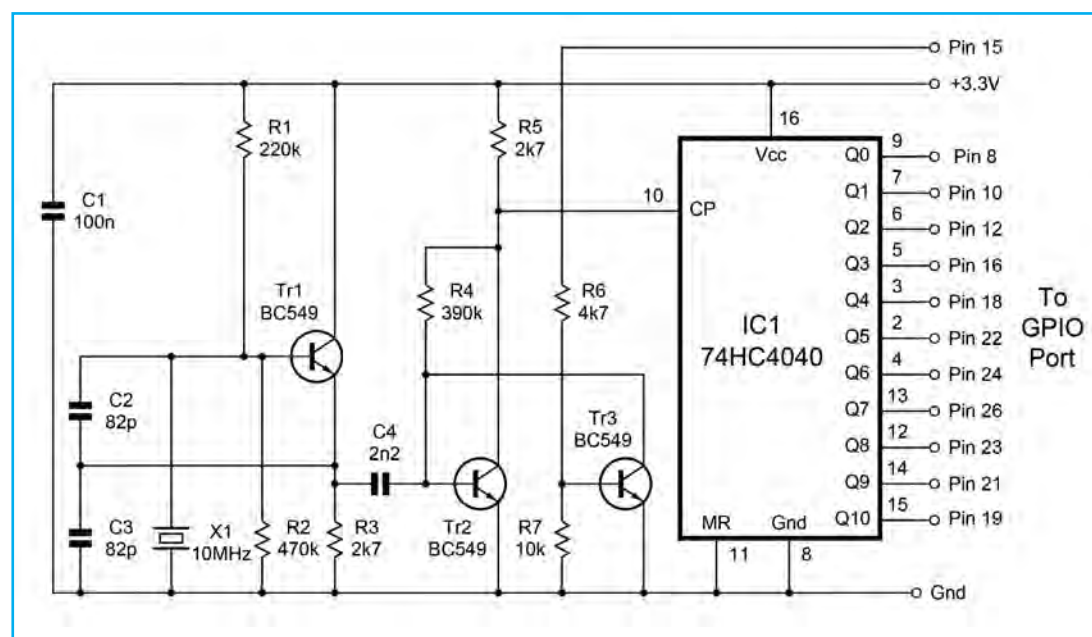


Fig.5. The circuit diagram for the random number generator. A high control signal from the GPIO port is used to switch on Tr3 and halt the count so that a reading can be taken.



cycle until it is halted by stopping the clock signal. This gating of the clock signal is achieved by using an output of the GPIO port (GPIO 17 at pin 15) to control Tr3, which is used as a simple switching transistor. With a low control signal, Tr3 is switched off and the circuit functions normally. A high control signal switches on Tr3, which in turn cuts off the base current to Tr2, switching it off and blocking the clock signal. This is only done briefly while the counter is read, and the control signal is then returned to the low state.

I only implemented 11 of the 12 outputs, because subsequent counter projects would only require a 10-bit count plus an additional bit to act as an overflow counter. Simply omit the connections for the most-significant bits if less than an 11-bit count is required. There are plenty of unused lines left on the GPIO port, so the twelfth bit could be implemented, if required. In fact, with a 40-pin GPIO port there are sufficient lines to handle all 24 outputs of two 74HC4040s connected in series.

The 74HC4040 is a CMOS device, and it therefore requires the usual anti-static handling precautions. Any fairly high gain silicon NPN transistors can be used for Tr1, Tr2, and Tr3. The exact clock frequency is not important in this application. It simply needs to be quite high, and a crystal oscillator provides an easy way of generating a suitable clock signal. Any crystal having an operating frequency in the range 4MHz to 16MHz should work well in this circuit.

### Software

The Python program of Listing 1 generates and prints a random number in the range 0 to 2047, and uses some simple mathematics to produce from this the die simulation, with a number from 1 to 6 being printed on the screen. The first section of the program does the usual initial setting up, and then the next section sets the appropriate eleven GPIO lines as inputs, and one as an output. At the beginning of the main section of the program, the output at pin 15 is set high (True), which halts the count.

The variable called 'byte' is then set to an initial value of zero. The eleven inputs are then read one-by-one, and 'byte' is augmented by the appropriate value if a bit is set high. This eventually builds up the full 11-bit value in 'byte', which is then printed on the screen. Pin 15 is then set low again so that the counter starts cycling through its range of values again. A do... while loop is used to repeatedly deduct 6 from the value stored in 'byte', stopping when the value is no longer greater than 5. This gives a number in the range 0 to 5, and 1 is added to it to give a number from 1 to 6, which is then printed on the screen.

With the aid of an external binary counter and a clock generator it is possible to produce some useful and interesting Raspberry Pi projects. This is something that will be explored further in the next *Interface* article, with an improved capacitance meter project.

### Listing 1

```
import RPi.GPIO as GPIO
GPIO.setmode(GPIO.BOARD)
GPIO.setwarnings(False)

GPIO.setup(8, GPIO.IN)
GPIO.setup(10, GPIO.IN)
GPIO.setup(12, GPIO.IN)
GPIO.setup(16, GPIO.IN)
GPIO.setup(18, GPIO.IN)
GPIO.setup(22, GPIO.IN)
GPIO.setup(24, GPIO.IN)
GPIO.setup(26, GPIO.IN)
GPIO.setup(23, GPIO.IN)
GPIO.setup(21, GPIO.IN)
GPIO.setup(19, GPIO.IN)
GPIO.setup(15, GPIO.OUT)

GPIO.output(15, True)
byte = 0
if GPIO.input(8):
    byte = byte + 1
if GPIO.input(10):
    byte = byte + 2
if GPIO.input(12):
    byte = byte + 4
if GPIO.input(16):
    byte = byte + 8
if GPIO.input(18):
    byte = byte + 16
if GPIO.input(22):
    byte = byte + 32
if GPIO.input(24):
    byte = byte + 64
if GPIO.input(26):
    byte = byte + 128
if GPIO.input(23):
    byte = byte + 256
if GPIO.input(21):
    byte = byte + 512
if GPIO.input(19):
    byte = byte +
1024
print (byte)
GPIO.output(15, False)
while byte > 5:
    byte = (byte - 6)
print (byte + 1)

GPIO.cleanup()
print ("Finished")
```



**Looking to advertise?**  
**Contact Stewart Kearn on:**  
**01202 880299**  
**or email**  
**stewart.kearn@wimborne.co.uk**



**Laser**  **Why tolerate when you can automate?**

 <b>Home Automation</b>	 <b>C-Bus Shop</b> <b>C-Bus and</b> <b>C-Bus Wireless</b>
 <b>KAT5 AV transmission</b> <b>and IR control system</b>	<b>www.cbushop.com</b>
 <b>Barix Ethernet based</b> <b>MP3, communications</b> <b>and control systems</b>	<b>www.laser.com</b>
<b>Integrators, Installers, Trade</b> <b>and Retail customers welcome</b>	<b>Laser Business Systems Ltd</b> <b>Tel: +44 (0) 20 8441 9788</b> <b>Fax: +44 (0) 20 8449 0430</b> <b>Email: info@laser.com</b> <b>16 Garthland Drive, EN5 3BB</b>

# STORE YOUR BACK ISSUES ON CD-ROMS



**Order on-line from**  
[www.epemag.com](http://www.epemag.com) (go to the UK store)  
 or by phone, fax, email or post



**ONLY**  
**£16.45**  
 (£29.95 FOR 5 YEAR)  
 each including VAT and p&p

- VOL 1: BACK ISSUES** – January 1999 to June 1999  
 Plus some bonus material from Nov and Dec 1998
- VOL 2: BACK ISSUES** – July 1999 to December 1999
- VOL 3: BACK ISSUES** – January 2000 to June 2000
- VOL 4: BACK ISSUES** – July 2000 to December 2000
- VOL 5: BACK ISSUES** – January 2001 to June 2001
- VOL 6: BACK ISSUES** – July 2001 to December 2001
- VOL 7: BACK ISSUES** – January 2002 to June 2002
- VOL 8: BACK ISSUES** – July 2002 to December 2002
- VOL 9: BACK ISSUES** – January 2003 to June 2003
- VOL 10: BACK ISSUES** – July 2003 to December 2003
- VOL 11: BACK ISSUES** – January 2004 to June 2004
- VOL 12: BACK ISSUES** – July 2004 to December 2004
- VOL 13: BACK ISSUES** – January 2005 to June 2005
- VOL 14: BACK ISSUES** – July 2005 to December 2005
- VOL 15: BACK ISSUES** – January 2006 to June 2006
- VOL 16: BACK ISSUES** – July 2006 to December 2006
- VOL 17: BACK ISSUES** – January 2007 to June 2007
- VOL 18: BACK ISSUES** – July 2007 to December 2007
- VOL 19: BACK ISSUES** – January 2008 to June 2008
- VOL 20: BACK ISSUES** – July 2008 to December 2008
- VOL 21: BACK ISSUES** – January 2009 to June 2009
- VOL 22: BACK ISSUES** – July 2009 to December 2009

- VOL 23: BACK ISSUES** – January 2010 to June 2010
- VOL 24: BACK ISSUES** – July 2010 to December 2010
- VOL 25: BACK ISSUES** – January 2011 to June 2011
- VOL 26: BACK ISSUES** – July 2011 to December 2011
- VOL 27: BACK ISSUES** – January 2012 to June 2012
- VOL 28: BACK ISSUES** – July 2012 to December 2012
- VOL 29: BACK ISSUES** – January 2013 to June 2013
- VOL 30: BACK ISSUES** – July 2013 to December 2013
- VOL 31: BACK ISSUES** – January 2014 to June 2014
- VOL 32: BACK ISSUES** – July 2014 to December 2014

**NEW**  
**Vol.33**

**VOL 33: BACK ISSUES** –  
 January 2015 to June 2015

**FIVE YEAR**  
**DVD/CD-ROMs**  
**NOW AVAILABLE**

## FIVE YEAR CD/DVD-ROMs

- No.1 – Jan '03 to Dec '07**
- No.2 – Jan '04 to Dec '08**
- No.3 – Jan '05 to Dec '09**
- No.4 – Jan '06 to Dec '10**
- No.5 – Jan '07 to Dec '11**
- No.6 – Jan '08 to Dec '12**
- No.7 – Jan '09 to Dec '13**
- No.8 – Jan '10 to Dec '14**

**NEW**  
**No.8**

**NOTE:** These DVD/CD-ROMs are suitable for use on any PC with a DVD/CD-ROM drive. They require Adobe Acrobat Reader (available free from the Internet – [www.adobe.com/acrobat](http://www.adobe.com/acrobat))

## WHAT IS INCLUDED

All volumes include the *EPE Online* content of every listed issue. **Please note that we are unable to answer technical queries or provide data on articles that are more than five years old. Please also ensure that all components are still available before commencing construction of a project from a back issue.**

## BACK ISSUES DVD/CD-ROM ORDER FORM

Please send me the following Back Issue DVD/CD-ROMs.

Volume Numbers: .....

.....

**Price £16.45 each, £29.95 for Five Year DVD/CD-ROMs** – includes postage to anywhere in the world.

Name .....

.....

Address .....

.....

.....

Post Code .....

☐ I enclose cheque/P.O./bank draft to the value of £ .....

☐ please charge my Visa/Mastercard/Maestro £ .....

Card No. ....

Card Security Code ..... (The last 3 digits on or just under the signature strip)

Valid From ..... Expiry Date .....

Maestro Issue No. ....



**SEND TO: Everyday Practical Electronics,**  
**Wimborne Publishing Ltd., 113 Lynwood Drive, Merley,**  
**Wimborne, Dorset BH21 1UU.**

Tel: 01202 880299. Fax: 01202 843233.

**E-mail: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk)**

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally posted within seven days of receipt of order.



# PIC n' Mix

Mike O'Keeffe

Our periodic column for PIC programming enlightenment

## PICs and the PICkit 3: A beginner's guide – Part 1

**M**ICROCHIP'S recent release of their new cloud-based integrated development environment (IDE) – MPLAB Xpress – means this is a great time to return to basics and look at why and how you should design, build and program your own PIC-based projects. This new series is intended for anyone who's curious about the PIC, but doesn't know where to start. It's also for those of you, who may have plenty of experience, but wouldn't mind a refresher. MPLAB Xpress is a great opportunity for newbies to take the plunge and start 'PICing'.

### Why use the PIC?

First off, a simple question: 'why use a PIC, and why not an Arduino or a Raspberry Pi?' I could write pages and pages about the differences between a wide variety of electronic platforms, but let's do a brief comparison with the Arduino and Raspberry Pi, two of the most popular non-PIC routes to adding intelligence to a project.

### Microcontrollers and Microprocessors

Let's be clear, the PIC, Arduino and Raspberry Pi are all very different beasts. The PIC is a microcontroller and also just a single component. The Arduino is a microcontroller-based kit, and the Raspberry Pi is a multi-component, single-board computer with a microprocessor. That doesn't tell us too much, so let's examine the difference between a 'microprocessor' and a 'microcontroller'. A microprocessor contains a central processing unit (CPU), which contains registers, clocks, memory and programmable logic. We control this with a piece of software stored in memory that alters the registers and the programmable logic at a specific clock speed. This is a simplification, but it will suffice for the moment, as we will be returning to explain these concepts when we begin to code.

Building upwards from that we have a microcontroller, which contains a microprocessor with all its registers, *but* it also contains programmable input and output peripherals. Peripherals are our bridge to the outside world, whether it be a simple LED, an analogue sensor or a sophisticated

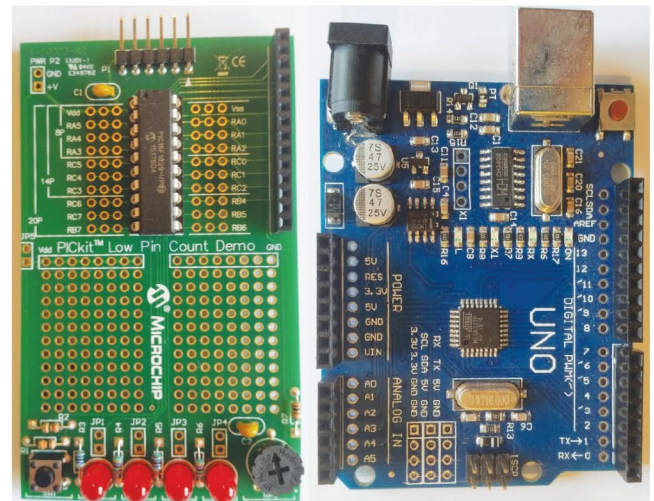


Fig.2. (left) Low Pin Count Demo Board, our PIC board of choice for beginners and (right) the popular Arduino Uno

motor controller. It can also contain much more memory space than a microprocessor. Think of a microprocessor as the brain, but a microcontroller is a brain with arms, legs, sensory capability and everything else you'd want in a fully functioning 'body'. The advantage of having the full body is that you can program it to do anything and everything. The PIC range, with its choice of inputs and outputs is one such example of a microcontroller. The AVR family of devices from manufacturer Atmel is another microcontroller. It was actually the ATmega128 (one of the AVR family of ICs) that was used in the original Arduino board. See Fig.1 for a comparison of the PIC and the AVR – they do look alike.

It is interesting to note that although the AVR from Atmel is a direct competitor of Microchip's PIC microcontrollers, Microchip recently bought Atmel. Now, this doesn't necessarily mean we'll see PICs in the same Arduino format, because Arduino is actually an Italian company that just happens to use Atmel's ICs. But it does mean some interesting changes in the future for hobbyists and professionals alike.

Back to our comparison – the PIC is a single integrated circuit. To operate it needs to be connected to a board, with a power supply and some extra components. Atmel's AVR is exactly the same. Arduino provides the AVR, the power supply and everything else, ready to go. Not only do Arduino provide this beautiful little hardware platform, but also they provide the software via 'Sketch', which is their free-to-download, proprietary development environment (see later for what this is), which comes with a huge, easy-to-use software library. You can build a huge range of little projects simply by buying one of these Arduino kits without ever having to use a soldering iron.

### Microchip playing catch-up

Microchip have been a little slow to the game in providing an alternative to the Arduino, but along with their new cloud-based IDE, they've also released their \$10 Xpress

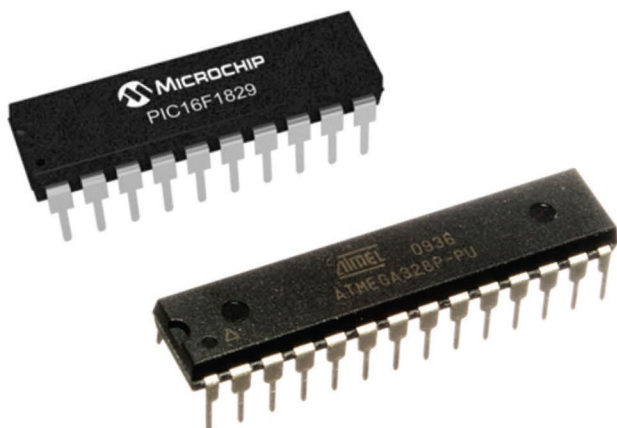


Fig.1. (top) Microchip's 8bit PIC16F1829-I/P and (bottom) ATMEAL's 8bit AVR ATMEGA328P



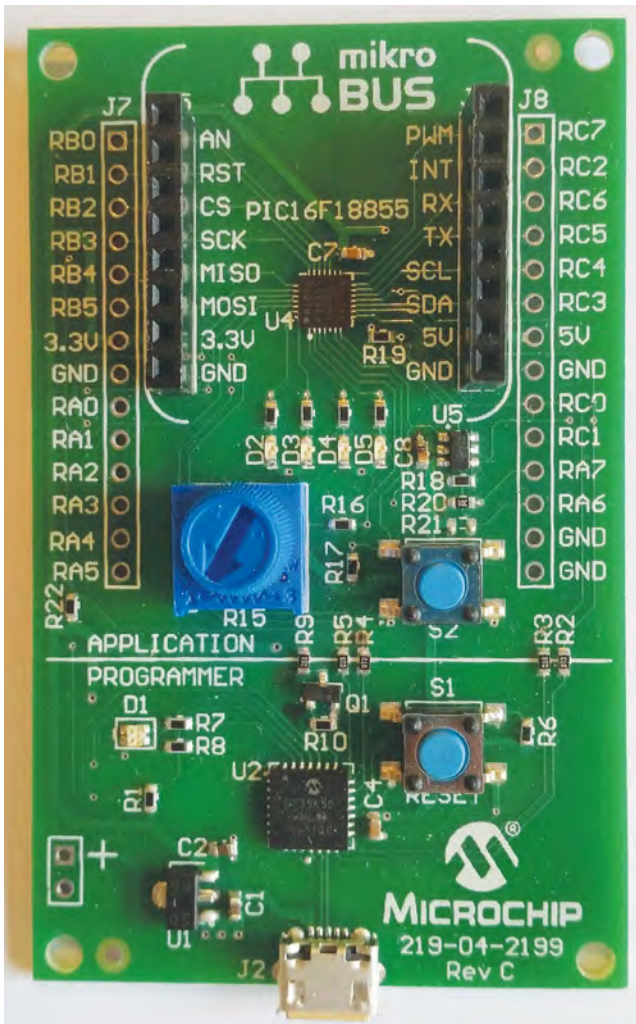


Fig.3. Microchip's Xpress Evaluation Board – it is similar to an Arduino in that it uses a bootloader and hence avoids the need for a separate external programmer

Evaluation Board (see Fig.3 or <http://www.microchip.com/mplab/mplab-xpress>). It doesn't have as catchy a name as the Arduino, but they are aiming for the same maker/hobbyist market. Much like the Arduino, you don't need a programmer to get up and running with the Xpress Evaluation Board. To make things happen you just plug in a USB cable, download the drivers and load up MPLAB Xpress. The Xpress Evaluation Board also uses a commonly used mikroBus header, allowing you to use a wide range of off-the-shelf modules from mikroElektronika. MPLAB X and the new MPLAB Xpress (cloud-based) are not as easy to use as Arduino's Sketch, but they are definitely more powerful, which I will cover later.

With this new board, it is finally in the running with Arduino. Microchip gave away the first 2000 for free, you may even have one, if you're lucky. Unfortunately, it's not fully available yet, so I am going to stick with an older board for the next few months. I hope to write a guide for the Xpress Evaluation Board when it is ready to purchase.

### Demo board

The board I will be discussing over the next few articles is the 'Low Pin Count Demo Board' from Microchip. It can be purchased from the link below. It's not really fair to compare Arduino's easy-to-use hardware and software to this board. The Demo Board wasn't designed to be an Arduino competitor. The Arduino is more expensive and the software easier to use, whereas the Demo Board is less expensive and the software is harder to use, but it gives you much greater control and encourages better coding practices. Which is better or more suited for particular applications is a hotly debated subject – both have their place, but in certain areas the PIC wins hands down and that

is why we are having this series. (Arduino fans do of course have the current *Teach-In 2016* series of articles from Mike and Richard Tooley) Plus, I'm biased, I love using PICs! I have developed projects with the Arduino boards and I have found them great to use, but I've been infuriated with their locked software libraries. The full control in the PIC really appeals to me. It might be harder in the beginning, but the rewards in the long term easily outweigh this.

### PICs and Raspberry Pi

So what about the Raspberry Pi? This is a different beast altogether (see Fig.4). It really is a computer, comparable to your laptop or desktop PC. Plug in a power supply, keyboard, mouse and a monitor and you've now got a very small, very inexpensive computer. It runs with the Linux operating system (competitor to Windows and Mac OS) and you can write fully functional programs to do a lot of things really easily. It is leagues away from the low-level input/output control of microcontrollers. The Raspberry Pi works with a microprocessor and a large number of external peripherals. The real difference here is that the Pi operates at a much higher level to our microcontrollers. Using the Pi we write code, which talks to other code, which is executed by the microprocessor, which then talks to peripherals. By contrast, with PICs, we simply write code that talks directly to our peripherals, cutting out software and hardware middle men, and resulting in *much faster* operation. This is not a trivial difference – PICs really are leagues ahead of the Raspberry Pi and Arduino if you need fast operation.

Another vital difference is size and power requirements. To add some 'smarts' or control to a project you can 'simply' drop a PIC into a PCB design and run the device off existing power supplies used for the rest of the circuit. With luck your PCB won't even grow in size. However, with Arduino and the Raspberry Pi you are adding a pre-built box of tricks, connecting up wires and you may well need an extra PSU. Overall, it's clear that a PIC solution can be cheaper, neater, smaller *and* much more powerful!





### Programmer – enter the PICKit 3

Now we know a little bit about PIC microcontrollers and why we should use one over the Arduino or Raspberry. I mentioned the Low Pin Count Demo Board earlier, which is what I'm going to be working with. Although it has some similarities to the Arduino, for example, it has headers on either side to easily connect peripherals, its biggest difference lies in programming its on-board PIC. When we want to program it we'll need an additional piece of hardware called a 'programmer'. In terms of cost/performance, the best programmer to use is Microchip's own PICKit 3 (see Fig.5). This is powered by USB and connects to one side of the demo board. You use the PICKit 3 to not only power the Demo Board, but also to upload your new code to it – hence 'programmer'. You may come across Microchip's previous programmer – yes you guessed it, the PICKit 2 – as well as the more sophisticated Microchip ICD3 programmers. Being older, the PICKit 2 doesn't support all of the latest PICs and the ICD3 is an In Circuit Debugger, which is more powerful and more expensive. In reality the ICD3 will only be used for greater debugging control and faster code upload. We will use the PICKit 3; it's reasonably priced, a great bit of kit and can do everything we need.

It's worth pointing out that the Arduino doesn't need a separate programmer; it was cleverly designed to use what's known as a 'bootloader'. This is a special program written to a safe place in memory (which cannot be written to afterwards) that allows the user to connect their Arduino board to their computer with just a USB cable. This bootloader allows the user to upload their code via the USB interface instead of needing an external programmer. It is yet another reason why the Arduino's became so popular among the maker communities.

So what exactly is the PICKit 3 programmer and what does it do? The programmer takes our (converted) code and copies it to the target PIC. It can also power our project if we want it to. Its other main function is its debug ability. This is the ability to walk through our code as it is executed

and look at various registers and variables to see if our code is behaving the way we want it to. This is a very powerful capability, and helps us debug our code when we run into problems.

#### Compilers

Taking a step back from the programmer and the actual microcontrollers themselves. It's good to look at exactly what it is that we load into our microcontroller. Our micro will only understand 'machine language' or binary (ones and zeros). Binary is a numerical representation of a transistor output in either one of two states – on or off. So our code, which we write in the much more human-friendly 'C' software language or simpler 'assembly' language needs to be converted into these ones and zeros.

This is what a 'compiler' does. It will take our human-understandable code and convert it into machine-readable binary code. Again this is an over simplification. They really do a lot more than this, but for now let's keep things simple. Binary code is often stored as 'hex' files. Hexadecimal is a numerical representation, similar to decimal or binary, except it uses the base 16 (with alphanumeric symbols 0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F). It's commonly used in programming as an easier (more compact) way to represent larger binary numbers. Take the number 'F' in hexadecimal, this is '15' in decimal and '1111' in binary. So you can immediately see that F is only one character compared to the two characters for decimal 15 and four in binary.

The commonly used compilers for PICs are called 'XC8', 'XC16' and 'XC32'. These are freely available from Microchip's website. There are other compilers available, but these are the easiest to start off with. To improve your code in compile time, you can run what's called optimisations, the compilers handle these. The optimiser in the compiler can improve upon your code with regards speed, performance or memory usage. Unfortunately, you need to purchase a licence for these optimisations in Microchip's compilers. Microchip have recently updated their licensing structure so you can pay \$30 per month instead of one large flat fee of \$1000. You can even pay for just one month when you are nearing the end of your project and optimise it for better performance.

#### Development environments

Moving up the chain of design, we come to the IDE or 'integrated development environment'. This is where we write our code, select the behaviours of our device and even debug our code. MPLAB X is Microchip's IDE of choice, with MPLAB Xpress as their new online equivalent. It is an incredibly powerful platform and very useful when designing and building our projects. I will be covering this in much greater detail in next month's article.

#### What you will need

I'll be walking you through the setup, building and programming of our very own PIC projects, and I recommend getting your hands on the following software and hardware, so you can follow me as I introduce ideas and techniques:

1. Purchase the PICKit 3 Low Pin Count Demo Board (<http://tinyurl.com/h2jj2ek>)
2. Purchase the PICKit 3 Programmer + USB Cable (<http://tinyurl.com/zcpx3le>)
3. Download PICKit 3 Starter Kit User's Guide (<http://tinyurl.com/jyqfeuk>)
4. Download MPLAB X IDE (<http://tinyurl.com/hmehqja>)
5. Download XC8 Compiler (<http://tinyurl.com/h5g9k5l>)
6. PC with an internet connection to download the IDE, compiler and user guide.

#### Next month

I hope this has been helpful in laying a foundation for microcontroller development. While there is a lot of information, I want to try and keep it relevant and useful, without becoming boring. The plan is to spend the next few months building upon our foundations and from there designing some really interesting projects.



Fig.5. Microchip's PICKit 3 USB Programmer – a powerful, reasonably priced bit of kit that will be at the heart of our PIC activity.

**Not all of Mike's technology tinkering and discussion makes it to print.**

**You can follow the rest of it on Twitter at @MikePOKeeffe, up on EPE Chat Zone as mikepokeeffe and from his blog at [mikepokeeffe.blogspot.com](http://mikepokeeffe.blogspot.com)**

## State machines – Part 1

**REGULAR** EPE Chat Zone contributor *atferrari* asked about microcontroller implementation of state machines:

'I am not C conversant; I do all in assembly for 18F micros. I've been thinking of implementing a basic elevator controlled by a micro. After reading several articles and references, I see that a state machine is frequently (if not always) mentioned – what I understand is the way to consider the problem.'

'I then browsed two pieces of software implementing the basics (I regret losing track of them) and depending on whether or not they were written in (maybe) C or assembly, what they did was create long blocks of 'switch case' chains or something similar... I found this quite a crude way to implement it, but I cannot see any other way of doing it. My question: is this the actual way you implement a state machine with a micro?'

### State machine basics

At first sight this may not seem to a circuit-related issue, however, state machines are important in both digital hardware design and software development. An understanding of the basic principles of state machines is very useful for anyone interested in designing electronic circuits and systems, so we will expand this topic to discuss state machines in general.

The state machine concept developed as part of computational theory within what is called automata theory. It is not necessary to study all this theory and mathematics in depth to make use of state machines in basic digital circuit and software development. However, it is worth mentioning that Alan Turing, the famous English pioneer of computer science and World War II code breaker (cryptanalyst) made very important contributions to the development of automata theory, in particular with the concept of the Turing Machine.

The operation of many systems with which we interact in daily life can be described (modelled) in terms of state machines – even if they were not explicitly designed using a state machine approach. Elevators, as mentioned by *atferrari*, are a classic example, as are combination locks, traffic lights and vending machines. The user interface controls in products such as digital clocks and radios provide further examples. We will look at such an example in more detail later.

### Concept of 'state'

In digital electronics a number of common circuits can readily be described using state machines (and hence designed using a state-machine approach). Perhaps the most obvious examples are counter circuits, but circuits which identify particular digital input sequences are another classic example.

As is indicated by the name, *state* is a key concept here – at any given time a state machine has, or is in, a particular state called the *current state*. In practical terms, the state is held in a memory – in flipflops in a digital circuit or in a variable or other data structure in software (thus requiring memory usage in the microcontroller/computer). Typically, each state is identified in some unique way (by a name, symbol or number) and may correspond to some specific external actions performed by the state machine or a system that it is controlling.

The memory requirement implies a physical limit to the number of possible states that a real state machine can have (limited by the size of available memory). Thus, in more formal discussions the term 'finite state machine' (FSM) is used to reflect this limit. Theoretical state machines (or other types of automata) can have an infinite number of states – at least in mathematical descriptions. In this context, one can even consider such things as the maximum amount of information that could be theoretically stored in a given volume of space and even how much information the universe contains. This of course goes beyond what you have to worry about to design a state machine circuit, but gives some idea of the potential depth of the subject of automata a whole.

### State actions and transitions

The actions associated with a state may simply be that a particular output value, pattern or symbol is produced (for example a counter circuit outputs the number it has currently counted to). The action may be also defined in more specific physical terms (eg, in this state the motor which opens the elevator door is switched on). Not all states may produce unique actions or physical outputs. For example, a simple combination lock may have a number of states representing conditions part way through input of the correct combination, but all states apart from the one detecting the correct combination will result in a 'locked' output, and, for obvious reasons in this case, the user will not otherwise know what the current state is.

A state machine will change to a different state if certain conditions or events occur – this is called a 'transition'. The transition determines the *next state*, which becomes the new current state after the transition has occurred. Thus a state machine is defined in terms of its states and the possible transitions between states (specified in terms of the current state, next state and the condition required for the transition to occur in each case).

A transition resulting from a given input condition will result in change to a single defined next state – at least that is the case if we dealing with a *deterministic* state machine. If this is not the case – an input condition can lead to more than one next state – we have a *nondeterministic* state machine, which is again beyond the realms of what we need to discuss here.

In addition to performing actions associated with states, state machines may perform actions (produce specific outputs) associated with transitions. Typically, what happens is that the machine is given a state and an input changes, this (almost) immediately causes an output change and (maybe) subsequently causes a state change when the machine next updates its state. The change in state may cause the output to change again, in which case the particular output condition may occur only during the transition (the time from the input changing to the machine achieving the next state).

Thus the current output from a state machine may directly depend solely on the current state – in which case it is called a 'Moore machine', or the output may depend directly on the current inputs as well as the current state – this is a known as 'Mealy machine'.



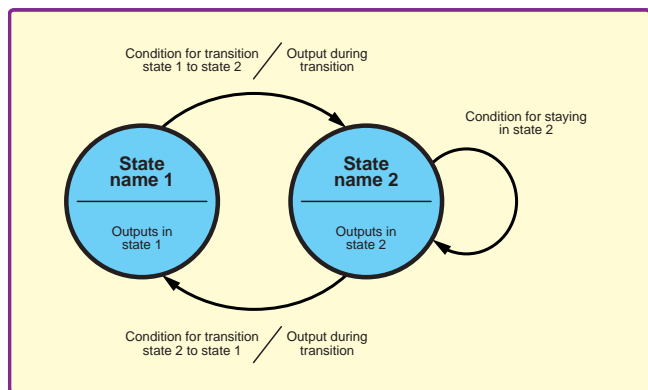


Fig.1. Elements of state diagrams – this is not meant to representing a meaningful machine

## State diagrams

State machines can be defined using state diagrams, which are very useful for visualising the behaviour of the machine. Typically, when designing a circuit or software state machine you will start by drawing the state diagram – possibly changing it several times as you think through the behaviour of the machine you have currently drawn with respect to the requirements of what you are designing, working your way towards the correct solution.

Fig.1 shows the elements used in drawing state diagrams – they comprise a set of circles (square boxes can be used if you prefer) which represent the states, connected by arrows representing the transitions. The state circles are labelled with the state name and (below the name) with the outputs (or actions) produced in that state (if applicable).

The transitions are labelled with the condition required for that transition to occur and if (and only if) the transition results in specific outputs (as discussed above) these are shown next to or under the transition condition, separated by a line or dash. In some cases it is necessary to define the condition for staying in a particular state, in which case an arrow is drawn returning to the same state (known as a ‘self-loop’). It is essential that the drawing and labelling of the transitions from each state fully and unambiguously define the behaviour of the machine in that state.

As previously mentioned, many everyday systems can be described using state machines. An example of such a state diagram is shown in Fig.2. This represents the behaviour of a microwave oven; it is simplified a little in comparison to the real microwave on which it was based to make our

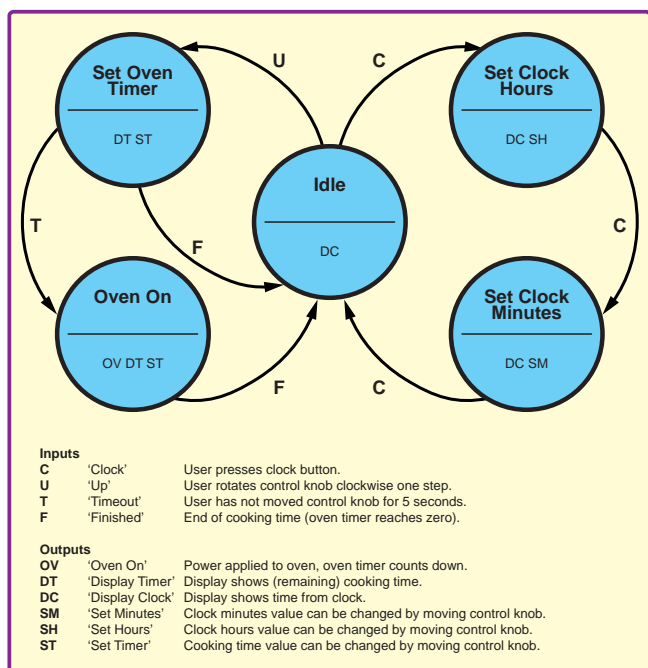


Fig.2. Example of a state machine based on a simplified microwave oven user interface

discussion more manageable. The purpose of this example is to show how the operation of a system like this can be defined in terms of a state machine. This will illustrate some of the thinking involved in developing and describing this machine. Similar approaches could be used when developing other designs (such as *atferrari's* elevator).

## Microwave state machine example

The oven has two controls – a ‘Clock’ pushbutton which is employed if the user wishes to set current time on the clock, and an ‘up/down’ rotary control which is used to set the clock time and cooking time (this could be implemented using a rotary encoder and some associated logic). There is also a display which shows the time of day, unless the oven is being used, in which case it shows the cooking time (or timing remaining during cooking).

We can start to describe the behaviour of the microwave oven's controlling state machine by defining an ‘Idle’ state, which it is in when the oven is not being used. In this state the action it performs is to display the time of day. We can call this action/output ‘Display Clock’, abbreviated to DC on Fig.2. We can assume that the system contains a real-time clock and a timer to control the cooking time and has some means to select which of these outputs to the display at any given time. We have defined another output/action called display time’ (DT) which selects the timer for display.

This representation (Fig.2) is abstract and may need to be refined if we actually implemented the system. For example, in digital circuit implementation we might use a single bit with 0 and 1 selecting the clock or timer. In which case it might be better to define a single state machine output called ‘Display Select’ (DS) and write DS=0 or DS=1 as the output on the state diagram, as appropriate. Alternatively, if we were coding the state machine in software we might define an enumeration data type that could have two values: DT and DC, in which case Fig. 2 would be more directly representative.

A more abstract representation may help with the thought processes when trying to understand or define the system of interest. For a user, the state diagram using DT and DC is probably more directly expressive of what the system is doing than DS=0 / DS=1. The approach does not really matter as long as the state machine's behaviour is unambiguously defined. In this case, there is a potential issue in that it might not be obvious (unless we clearly state it) that DT and DC cannot both be active at the same time.

## Setting the clock

If the user presses the clock button when the machine is in the idle state then the hours value of the clock can be changed. This represents a transition to a new state – the condition is ‘clock button pressed’ which abbreviate to C. In Fig.2 there is an arrow from the Idle state to the ‘Set Clock Hours’ state, which is labelled C to show that this is the condition for the transition.

When the machine is in the Set Clock Hours state the user can change the hours value using the rotary control. Note that this behaviour is not fully described by the state diagram alone. This is in effect an assumption (if we are modelling), or a design decision (if we are designing), that the rotary control is connected directly to the clock module/function and the state machine provides a control signal to the clock module to say, ‘now use the rotatory control (up and down) signals to set the hours’. We have called this control signal ‘Set Hours’, abbreviated SH. The clock module itself could (most likely) also be described as a state machine – which illustrates the fact that systems are often built from sets of interconnected state machines.

If the machine is in the Set Clock Hours state and the user presses the clock button the machine transitions to the ‘Set Clock Minutes’ state, which is very similar to the Set Clock Hours state. Here the machine outputs a ‘Set Minutes’ (SM) control signal to the clock module in a similar manner to Set Hours discussed above. In the Set Clock Minutes state, pressing the clock button again returns the machine to the Idle state.

The instructions to the user relating to the state machine operations just discussed would be something like: ‘To set the time, when the oven is not being used press the clock button and then rotate the control to set the hours. When the hours are connect press the clock button again and rotate the control to set the minutes. To finish and restore normal operation of the clock press the clock button again’.

### Operating the oven

Continuing the instructions, using the oven might be described as follows. ‘Rotate the control clockwise to set the required cooking time, which will be shown on the display. If you need to reduce the time rotate the control anticlockwise. To cancel cooking reduce the time to zero. Once the desired time is set, leave the control – cooking will start after five seconds with the display showing the remaining time. During cooking the time can be adjusted with the control and stopped by reducing it to zero’.

### Creating the state machine

To obtain the state machine we need to make some assumptions about the structure of the system. First, we assume there is a timer module which can be set directly from the up and down signals from the rotary control when enabled to do so – this is similar to the clock setting. Thus, we need a state machine output signal ‘Set Timer’ (ST) to allow the timer to respond to the rotary control.

We can also assume there is a five-second timeout function, activated if the timer setting has not been changed. Specifically, we assume there is an output from the timer module which deactivates as soon as it receives an up or down signal and activates five seconds after the up or down signals stop changing. This is an input to the state machine called ‘Timeout’ (T). The state machine also needs to know when the cooking has finished, which can be provided by another signal from the timer. This activates when the time is zero (either because the timing has finished or because it has been reduced to zero by the rotary control – to account for the cancel capability). We will call this signal ‘Finished’ (F).

To describe the part of the state machine related to cooking we again assume we are starting from the Idle state. Cooking is initiated by rotating the control clockwise – which implies it is outputting an ‘up’ signal. Thus an Up input (U) causes a transition to a state in which the user can set the cooking time. This state is called ‘Set Oven Timer’. In this state, the machine activates the Display Timer (DT) and Set Timer (ST) outputs, which have both been defined above.

When in the Set Oven Timer state, if the user winds the time down to zero the timer module will activate the Finished (F) signal, which will cause the machine to transition back to the Idle state (cooking is cancelled before it is started).

When in the Set Oven Timer state, if the user does not move the rotary control for 5 seconds the timer module will activate the Timeout (T) signal. This will cause a transition to the ‘Oven On’ state. In this state, the machine outputs the Oven On (OV) signal which activates the oven (assuming the door is shut). We do not have to worry about things such as the oven power level here as that is controlled separately. In the Oven On state the rotary control needs to still be able to adjust the timer so Display Timer (DT) and Set Timer (ST) are active. When the timer reaches zero, or the time is reduced to zero by the control, the timer activates the Finished (F) signal and the machine transitions back to the Idle state (where the oven is switched off).

### Checking our initial state machine

At this point we have created our state machine and we may like to check if it can be simplified, or any ambiguities removed. Readers might have notices that the DT and ST outputs are always active at the same time. We could reduce them to a single signal, say ‘Use Timer’ (UT). This is shown in Fig.3. Referring back to our discussion on DC and DT we note that UT and DC are also mutually exclusive and have modified the output definition to reflect this.

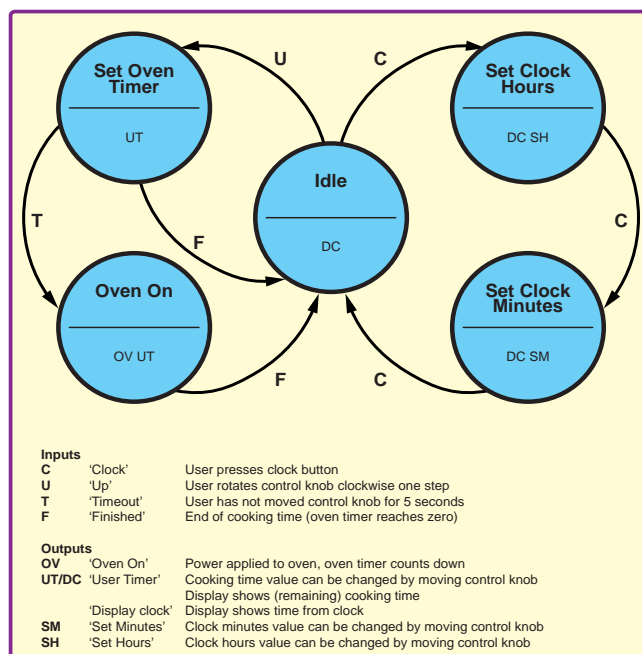


Fig.3. State machine from Fig.2 with simplified outputs. Further refinements next month

This illustrates the fact that we may go through several versions of a state machine as we develop our thinking. Furthermore, the machine shown in Fig.3 is not the only possibility given the general scenario discussed. For example, we have described the timer module controlling the five second timeout function, but this functionality could be controlled by the main state machine instead (we might add an additional state to reset an independent five-second timer when U or D where are active).

More generally, any attempt to design state machine may result in redundancies (equivalent outputs or states). There are formal/mathematical approaches that can process state machine descriptions to identify and merge states that are equivalent.

### Implementing a state machine

Once we have a state diagram we happy with we can move on to implementing it in more detail. We can create the machine in digital logic hardware or in software. Software running on a microcontroller such as a PIC may seem an obvious choice for something like this oven example, although it could be implemented in hardware. In other cases, a hardware approach may be more appropriate than software. In general, the idea of hardware implementation may seem daunting due to the possibility of needing many basic logic chips (gates and flip-flops) to build the state machine. However, a better approach (if hardware is the best choice) may be to use a single programmable logic device (CPLD – complex programmable logic device or FPGA – field programmable gate array). Of course, these technologies require the use of design tools (which you have to learn to use), but that is equivalent to needing a software development tool to write code for a microcontroller.

The state machine is a powerful technique for designing digital electronic and software systems, although they are not always used where they could be. This is often the case when the design is created incrementally, rather than being set up as a state machine in the first place. Such designs could potentially be converted to a more structured form by modelling their behaviour in terms of state machines, but it may not always be worth the effort.

This article has looked at state machines at a relatively abstract level. Next month, we will resolve some issues with the current version of the example machine diagram and look at implementation in more detail. However, before finishing, *atferrari's* question should not be left hanging. The answer is 'yes' switch/case statements are commonly used to implement state machines in software (and hardware description languages).





**CONTACT INFO:**  
T: +44 (0) 1388 818502  
E: [steveheatley52@gmail.com](mailto:steveheatley52@gmail.com)  
**WEARDALE ELECTRONICS**  
10 Mount Pleasant Close  
Spennymoor  
DL16 6EU  
Callers Strictly by  
Appointment only.  
UK VAT Registered

---

**Choose Weardale Electronics for  
Top Quality Components etc at  
Bargain Prices!**  
Below is just a small selection of  
what I can supply!  
**Free quotes & Qty discounts.**

CUSTOM MADE LEADS, **AUDIO/TV LEADS**, **LED'S**, **INDUCTORS**,  
**EDUCATIONAL KITS**, **CAPACITORS**, **RESISTORS**, **MODULES**,  
**SWITCHES**, **ARDUINO BOARDS**, **BREADBOARDS**, **CABLE**, **GLANDS**,  
**IC'S**, **TRANSISTORS**, **BARGAIN PACKS**, **KNOBS**, **PLUGS**, **SOCKETS**  
**DIODES**, **HEATSHRINK**, **COMPUTER PARTS**, **ELECTRICAL PARTS**,  
**FANS**, **POTS**, **HARDWARE**, **TRANSFORMERS**, **LIGHTING**, **ADAPTORS**,  
**GUITAR PARTS**, **RELAYS**, **SPEAKERS & SOUNDERS** ETC ETC  
**NEW ITEMS ADDED EACH WEEK!**  
**WEBSITE & PRINTED CATALOGUE COMING SOON!**

 Find us on:  
**facebook.**

**"LIKE" Weardale Electronics on Facebook**  
for details of Clearance, One off's & Special Offers  
<https://www.facebook.com/weardaleelectronics>



Visit our  
**ebay**  
store

**VISIT THE EBAY  
WEARDALE ELECTRONICS  
SHOP FOR LATEST ITEMS.**



Secure Payments by  
**PayPal**  
VISA MASTERCARD AMERICAN EXPRESS

**<http://stores.ebay.co.uk/weardaleelectronics>**



**CRICKLEWOOD  
ELECTRONICS**  
Established 1981



Frustrated with your supplier?  
Visit our component packed  
website for a vast range of  
parts - old and new,  
many unavailable elsewhere!  
[www.cricklewoodelectronics.com](http://www.cricklewoodelectronics.com)


**1000's OF PRICES REDUCED!**

Alternatively phone us on  
020 8452 0161 with your  
requirements.



**Visit our Shop, Call or Buy online at:**  
**[www.cricklewoodelectronics.com](http://www.cricklewoodelectronics.com)**  
**020 8452 0161** Visit our shop at:  
40-42 Cricklewood Broadway  
London NW2 3ET

**NEW**



**PicoScope® 2000 Series  
PC OSCILLOSCOPES**

**LIKE A BENCHTOP OSCILLOSCOPE,  
ONLY SMALLER AND BETTER**



- 2 channel, 4 channel and MSO models
  - Up to 100 MHz bandwidth
  - Up to 128 MS buffer memory
  - Function generator and AWG
  - Decode 15\* serial protocols
  - USB-connected and powered
- Windows, Linux and Mac software
  - Prices from £79 to £749





All models include full software and 5  
year warranty. Software includes  
measurements, spectrum analyzer,  
advanced triggers, color persistence,  
masks, math channels, all as standard.

\*Serial decoding (15 protocols  
including 1-Wire, CAN, Ethernet, I<sup>2</sup>C,  
I<sup>2</sup>S, LIN, RS-232, SENT, SPI, USB 1.1)  
with FREE updates.  
Free Software Development Kit.

**25 years of PC Oscilloscopes**  
**[www.picotech.com/PS461](http://www.picotech.com/PS461)**

# AUDIO OUT

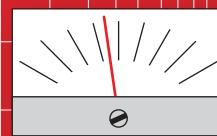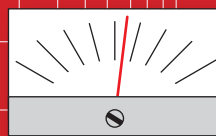

By Jake Rothman

## Super-simple retro amp-speaker combo – Part 1

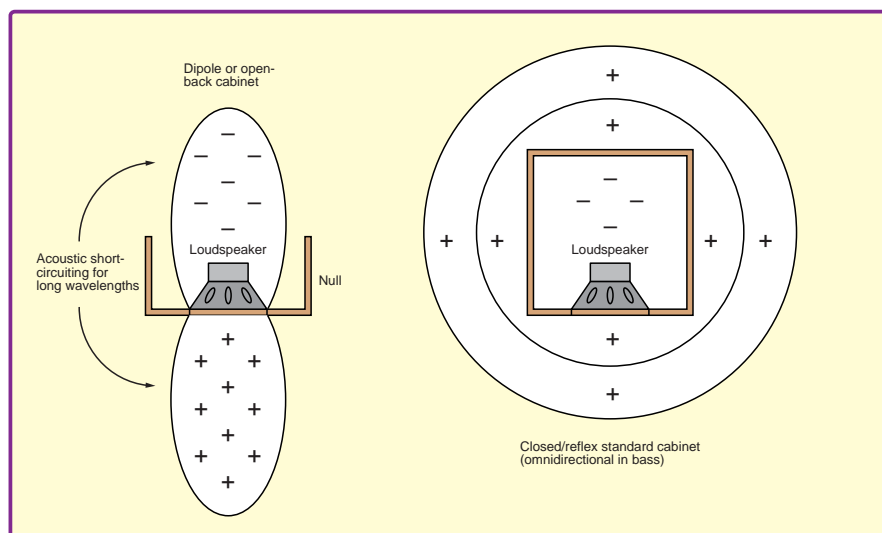


Fig.1. Comparing low-frequency radiation from open-back dipole and closed speaker cabinets.

### That old-fashioned sound

I recently sold an old Bush valve radio just used for FM Radio 4 in the kitchen. Despite its greatly superior specification, the replacement, a pair of Tannoy M20 speakers and a Leak 2000 receiver, did not work well in this role. The Hi-Fi system, although excellent on music, failed utterly with low-level speech. My audio-obsessed friends agreed that two-way speakers with extended bass reduced the clarity

of speech because the crossover was right in the middle frequency range. Also, radio speech on Hi-Fi speakers has a tendency to 'boom' when playing closely-miked speech radio. Finally, since the Leak amplifier operated in class AB, it was not happy running at very low volumes.

The old radio had a single Celestion 6 × 4-inch elliptical, light-weight, paper cone speaker in an open-back cabinet. This avoided the boom

problem because the figure-of-eight dipole radiation pattern from such enclosures does not excite room resonances as much as normal (enclosed) speakers, which have an omnidirectional bass radiation characteristic, as shown in Fig.1 ([www.linkwitzlab.com](http://www.linkwitzlab.com) has some good data on this topic). The radio's amplifier was also a major part of its sound, comprising a single-ended UL84 pentode valve running in class-A, which ensured a good sound at low volumes. The circuit's relatively high output impedance was also a factor in reducing distortion in the speaker.

### 'Quiet' speakers

So, rather than sticking with the Tannoy/Leak Hi-Fi option, I decided to replicate the radio's quiet, non-fatiguing 'mid-fi' sound, reminiscent of an old radiogram. Of course, this goes against the grain for physics-driven audio engineers like me, but the proof of the pudding is in the listening, and I liked the spoken-word sound of the old radio. The radio's limited-bandwidth sound can be especially useful during electronics R&D, where scratchy computer speakers and big 'boom and tizz' Hi-Fi systems seem to steal bandwidth from my brain!

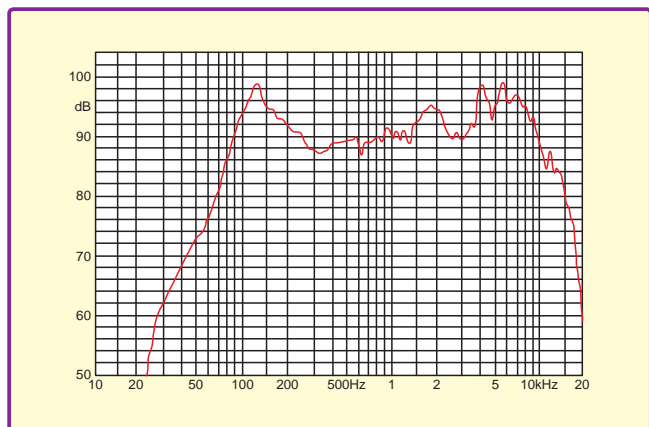


Fig.2. Frequency response of a Philips elliptical 6 × 4-inch AD46727 speaker – lots of little peaks.

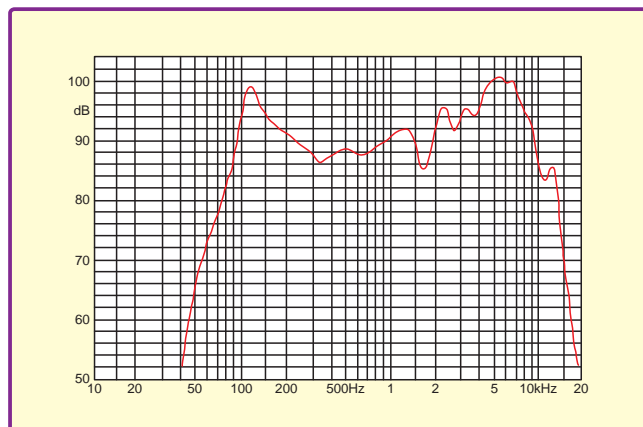


Fig.3. Frequency response of a 5-inch circular AD55725 speaker – a few big peaks.

Note that both the speakers in Fig.2 and Fig.3 have the same motor system and thus show just the difference purely from the cone shape. (Both curves are from the Mullard Technical Handbook – Part 6 Loudspeakers, 1986.)



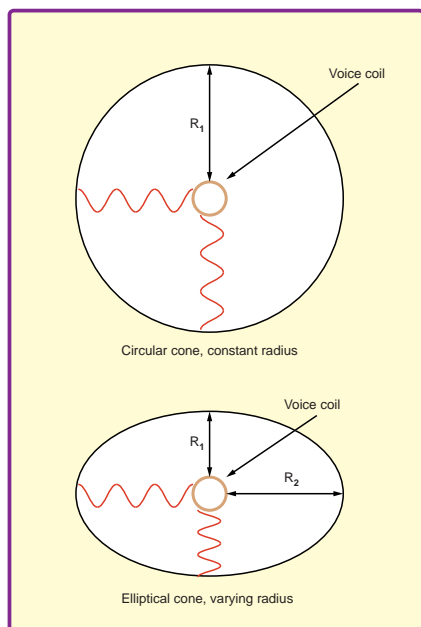


Fig.4. The different path lengths from the voice coil to the cone edge distribute the breakup frequencies. In the circular cone they coincide and reinforce.

This also applies when composing and tracking music on the computer late into the night.

### Elliptical argument

Along with class-A valve amps, ellipse-shaped speakers are another technology mostly lost to modern designers. They died out because they became associated with dreadful TV slot speakers, had difficult tooling requirements and weren't as loud as circular ones. EMI were famous for their elliptical drivers, their main researcher, Dr GF Dutton emphasised their lower colouration from delayed resonance. This was a result of the multitude of small break-up resonances rather than the fewer higher magnitude ones produced by circular cones – see Fig.2 and Fig.3. This desirable property was because of the differing path lengths from the voice coil to the edge of the cone, as shown in Fig.4. The hangover from undamped

radial breakup modes in some circular cones was shown to be impossible to equalise by DEL Shorter at the BBC research department in 1958. His paper, *The Development of High Quality Monitoring Loudspeakers* (accessible on the BBC website) even showed 3D delayed resonance curves, derived mechanically – before computers. The difference between the cone shapes was more pronounced with the efficient light-weight paper-cones of the past compared with today's plastic-coned rubber surround type units. Peter Baxandall was also an elliptical cone enthusiast, producing a design for *Wireless World* in August 1968. This used an Elac 8 × 5-inch unit with a damping compound on the surround and a passive LCR equaliser.

There appears to be an optimum ratio range for the dimensions for an elliptical speaker, which is 1:1.4 to 1:1.62 (the latter being the golden ratio). I have some old 8 × 2-inch TV speakers and other 'slot-shaped' sizes with ratios over 1:1.8 that have nasty 'N' shaped frequency response anomalies (see Fig.5, 1.5-2kHz). The optimum standard sizes seem to be 6 × 4, 8 × 5 and 10 × 6-inch (note that a 6 × 4-inch elliptical cone has the same radiating area as a 5-inch circular unit). For best dispersion an elliptical unit should always be mounted with its longest dimension (the major axis) vertical. Another aspect of cone geometry, shown in Fig.6, is that straight cross-section cones have a higher amplitude upper breakup peak than curvilinear one. This is good for high-power bass and compensating for the sideband cutting of AM radio, but gives a more coloured response, ie a mid-range boost over 1-4kHz.

In one of my germanium transistor hunts in an electronics shop in Cheltenham I found a load of old 30Ω 9 × 6-inch EMI 93870 AW elliptical speakers with

curvilinear soft felted-paper cones. They must have been from the 1960s since they had Alnico magnets as opposed to ferrite ones. Their liberation from the loft had finally arrived and I hooked one up to the *Test Bench Amp* (EPE, Nov 2014) set to constant current output and the much-missed valve radio sound was almost there. The system's efficiency was very high because of the very low moving mass of the speaker diaphragm/coil assembly. However, the power handling capacity was low due to the short (5mm) voice-coil, which tended to jump out of the magnetic gap at around 5W. Interestingly, modern drive units with their heavy long coils wound on aluminium formers in wide gaps, as shown in Fig.7 need around 5W just to get going. That is the price paid for high power handling.

The resonant frequency of the EMI speaker was around 70Hz, giving a response down to about 100Hz in the enclosure. The high-frequency response extended to about 7kHz,

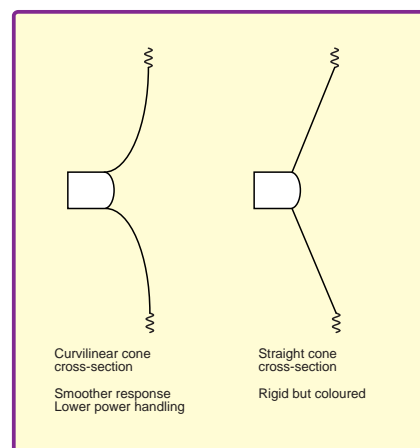


Fig.6. Straight cross-section vs curvilinear cones – the curved cones have smoother break-up and better dispersion. However, they are not as resistant to bending from high-power bass.

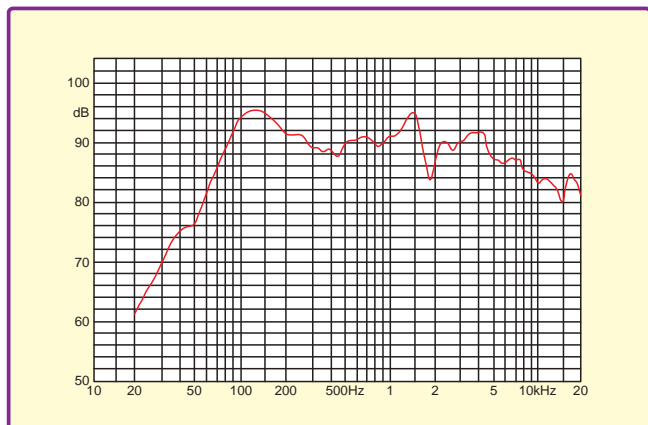


Fig.5. Frequency response of an AD38903 3 × 8-inch 'slot' elliptical speaker – note the nasty glitch.



Fig.7. Modern high-power voice coil with aluminium former and low-power voice coil wound on paper.

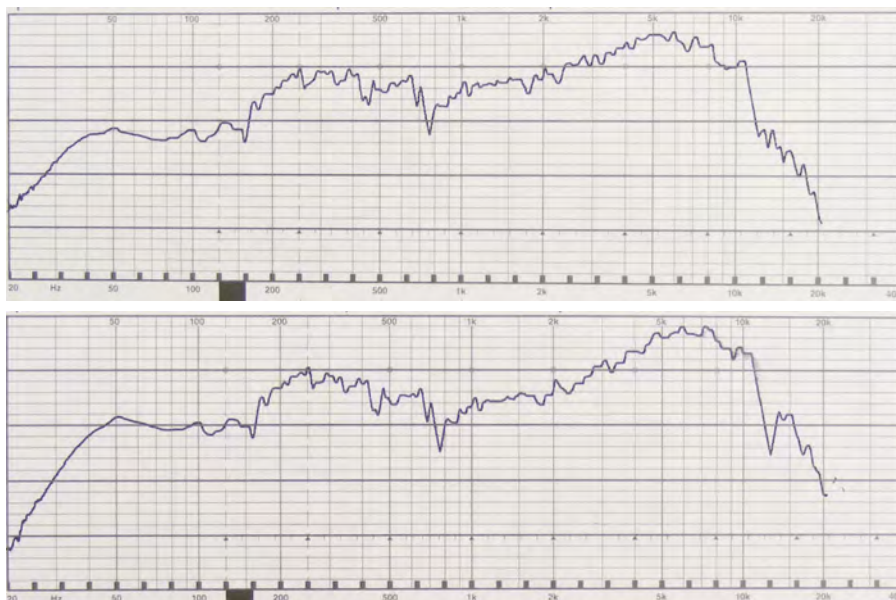


Fig.8. a) (top) Response of an EMI 93870 AW elliptical speaker in an open-back cabinet. It shows a rising response, which is good for speech, but it needs greater high-frequency cut for music use. b) (bottom) Response of the same unit but using current drive. There is only a small difference between these two curves, but there was a real improvement with sound quality using the current drive circuit. (Note the (vertical) amplitude divisions are 2dB.)

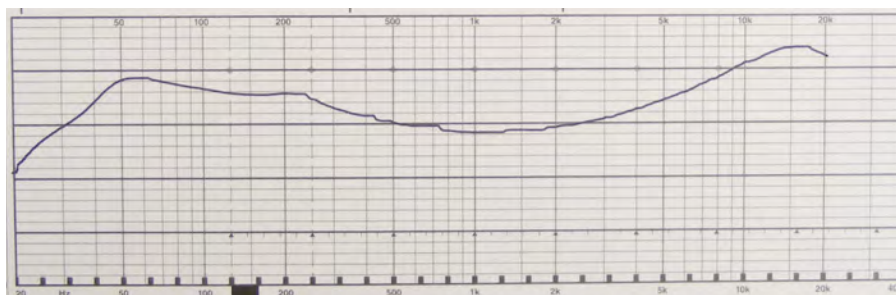


Fig.9. Frequency response of the amplifier's voltage output using the current drive. (Note the (vertical) amplitude divisions are 1dB.)

so definitely not 20Hz-20kHz Hi-Fi!. A forgotten idea in loudspeaker design to obtain a tonally balanced sound is that limited bass should be compensated by a corresponding high frequency cut (above 7kHz). *The Radio Designer's Handbook* (an essential analogue reference) states the product of the two frequency limits should equal around 600,000. Plastic computer speakers often go

from 200Hz to 14kHz. The response of the EMI driver is shown in Fig.8a, and using current drive and a bit of bass boost it is as shown in Fig.8b. The voltage output of the amplifier with the speaker connected is shown in Fig.9. It's a little too bright for music, but good for speech. A suitable open-back cabinet is shown in Figs 10a and b. Open-back cabinets need to be relatively shallow to avoid bass

resonance. The parallel sides should be lined with foam or felt to avoid reflections. Someday, I'd love to make a baffle from a piece of curved perspex with non-parallel sides, as shown in Fig.11. The size is not critical, but the longer the path length from the front of the driver to the back the better the bass response.

### Simulating valves

In April's *Audio Out* column I described an interesting buffer circuit based on the *Wireless World* (June 1973) PL Taylor 30W and Nelson-Jones circuits. I said then it would lead to a new class-A power amplifier, and that is the project we are starting here. Since the EMI speaker could be driven with just 1W, there would be none of the usual thermal problems associated with class-A operation. 2W maximum, just like the valve radio, should be enough. This transistor circuit does sound valve-like until it clips – there is no output transformer to smooth out the square edges, plus it has high negative feedback.

### Current drive

An inherent distortion problem with electromagnetic loudspeakers is due to their cone movement being the result of a changing current in a magnetic field. When loudspeakers are voltage driven, as is normally the case, the conversion of voltage to current takes place in the impedance of the voice-coil. Unfortunately, this impedance varies according to the position of the voice-coil. (Also, possibly there are hysteresis-distorted eddy currents induced in the magnetic pole-pieces and aluminium voice-coil formers.) These effects make the current response to the voltage drive non-linear, inducing considerable intermodulation distortion. These effects are generally



Fig.10. Front and rear views of the EMI unit in its cabinet – size: 410mm H × 255mm W × 200mm D.



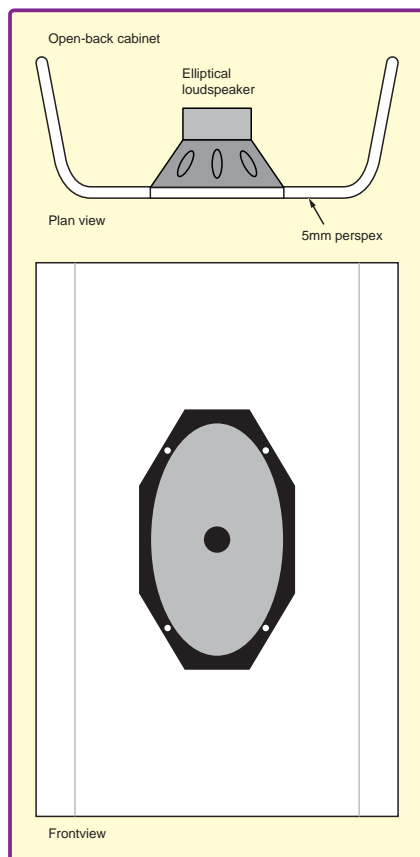


Fig.11. Idea for a curved perspex loudspeaker cabinet. Elliptical speakers should always be mounted vertically for best horizontal dispersion.

worse in low-power speakers with short voice-coil geometry. If the speaker is current driven from a high impedance rather than the almost zero-ohm output impedance of standard power amplifiers, the distortion has been shown to drop by a factor of almost ten. The amplifier controls the current rather than the speaker. It is a very noticeable effect, more so than most amplifier differences. The ATC SCM20SL (my monitor speaker of choice) is the only loudspeaker where these distortion problems are removed, but its huge long-gap

magnet and patented non-conducting pole pieces don't come cheap (around £4000 per pair).

One side effect of current drive is that there is no speaker damping of the main resonance. In a closed box where the Q and frequency of the resonance have been pushed up by the enclosed air this is a major problem. In an open baffle/back cabinet it can compensate for the bass loss due to the acoustical short-circuiting (see Fig.1). This also increases cone excursion, but this is not a problem with low power levels. Another side effect is boosted high frequencies due to the inductive impedance rise, which can be corrected with a bit of cut in the high frequency response of the amplifier.

The pentode valve amplifier in the radio inherently had a high output impedance. Also the output transformer prevented the application of much negative feedback because of the risk of instability. Inadvertently, the valve radio had built in loudspeaker distortion reduction. This was part of the effect because current driving a speaker removes a characteristic hard 'loudspeaker sound'. There is an interesting book called *Current-Driving of Loudspeakers* by Esa Meriläinen, which is the most complete work on the subject, although it appears to be a translation of a Finnish MSc thesis. In the UK, Essex University-based Prof Hawksford's work is also worth reading (google him!).

### Current drive topology

In the amplifier in this project, an inverting configuration is used, since a low input impedance is not a problem. This is shown in Fig.12 in op-amp form. Negative feedback is taken from the top of a current-sense resistor connected in the speaker ground lead. An additional benefit is that any distortion from the output electrolytic capacitor is also reduced, allowing a polymer type to be used. There is also a degree of high frequency cut applied through the network consisting of R4 and C3.

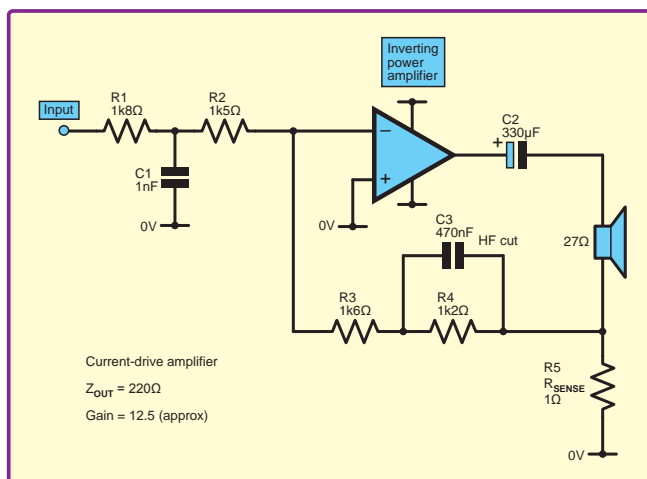


Fig.12. Op-amp 'representation' of the 2W class-A amplifier.

### Next month

That just about wraps it up for this month; next month we will examine this amplifier circuit in detail and look at its construction.

# PoLabs

For more information or software download please visit

[www.poscope.com/epe](http://www.poscope.com/epe)

## PoKeys Connect, Control



PoKeys is a successful story about versatile and extremely powerful controller.

Save your time with **fast** connectivity and easy configuration of advanced features.


Enjoy rare moments in life while PoKeys is taking care over your house or garden.

Take a break while PoKeys is controlling stepper motors in your CNC or 3D printer.

Let PoKeys make your imagination come true using our intuitive software and plugins for Mach3/4.
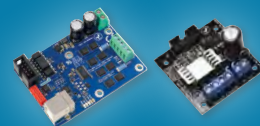
## Stepper motor drivers Drive

Safest and most efficient force for your motors.



## PoScope Mega1+ Measure



Do you need a really powerful and portable oscilloscope that will save your time, money and make your life with measurements easier?

PoScopeMega1+ is lowest power consumption USB oscilloscope, function generator and logic analyzer all-in-one available on the market.



HP 34401A Digital Multimeter 6 1/2 Digit



HP 54600B Oscilloscope Analogue/Digital Dual Trace 100MHz



MARCONI 2955B Radio Communications Test Set



FLUKE/PHILIPS PM3092 Oscilloscope 2+2 Channel 200MHz Delay TB, Autoset etc

LAMBDA GENESYS	PSU GEN100-15 100V 15A Boxed As New	£325
LAMBDA GENESYS	PSU GEN50-30 50V 30A	£325
HP34401A	Digital Multimeter 6.5 digit	£275-£325
HP33120A	Function Generator 100 microHZ-15MHZ	£260-£300
HP53131A	Universal Counter 3GHZ Boxed unused	£500
HP53131A	Universal Counter 225MHZ	£350
HP54600B	Digital Oscilloscope 100MHZ 20MS/S	from £75
IFR 2025	Signal Generator 9KHz - 2.51GHZ Opt 04/11	£900
Marconi 2955B	Radio Communications Test Set	£800
R&S APN62	Syn Function Generator 1HZ-260KHZ	£195
Fluke/Philips PM3092	Oscilloscope 2+2 Channel 200MHZ Delay etc	£250
HP3325A	Synthesised Function Generator	£195
HP3561A	Dynamic Signal Analyser	£650
HP6032A	PSU 0-60V 0-50A 1000W	£750
HP6622A	PSU 0-20V 4A Twice or 0-50V 2A Twice	£350
HP6624A	PSU 4 Outputs	£350
HP6632B	PSU 0-20V 0-5A	£195
HP6644A	PSU 0-60V 3.5A	£400
HP6654A	PSU 0-60V 0-9A	£500
HP8341A	Synthesised Sweep Generator 10MHZ-20GHZ	£2,000
HP83731A	Synthesised Signal Generator 1-20GHZ	£1,800
HP8484A	Power Sensor 0.01-18GHZ 3nW-10uW	£75
HP8560A	Spectrum Analyser Synthesised 50HZ - 2.9GHZ	£1,250
HP8560E	Spectrum Analyser Synthesised 30HZ - 2.9GHZ	£1,750
HP8563A	Spectrum Analyser Synthesised 9KHZ-22GHZ	£2,250
HP8566B	Spectrum Analyser 100HZ-22GHZ	£1,200
HP8662A	RF Generator 10KHZ - 1280MHZ	£750
Marconi 2022E	Synthesised AM/FM Signal Generator 10KHZ-1.01GHZ	£325
Marconi 2024	Synthesised Signal Generator 9KHZ-2.4GHZ	£800
Marconi 2030	Synthesised Signal Generator 10KHZ-1.35GHZ	£750
Marconi 2305	Modulation Meter	£250
Marconi 2440	Counter 20GHZ	£295
Marconi 2945	Communications Test Set Various Options	£2,500
Marconi 2955	Radio Communications Test Set	£595
Marconi 2955A	Radio Communications Test Set	£725
Marconi 6200	Microwave Test Set	£1,500
Marconi 6200A	Microwave Test Set 10MHZ-20GHZ	£1,950
Marconi 6200B	Microwave Test Set	£2,300
Marconi 6960B with	6910 Power Meter	£295

Tektronix TDS3012	Oscilloscope 2 Channel 100MHZ 1.25GS/S	£450
Tektronix 2430A	Oscilloscope Dual Trace 150MHZ 100MS/S	£350
Tektronix 2465B	Oscilloscope 4 Channel 400MHZ	£600
Cirrus CL254	Sound Level Meter with Calibrator	£40
Farnell AP60/50	PSU 0-60V 0-50A 1KW Switch Mode	£195
Farnell H60/50	PSU 0-60V 0-50A	£500
Farnell B30/10	PSU 30V 10A Variable No Meters	£45
Farnell B30/20	PSU 30V 20A Variable No Meters	£75
Farnell XA35/2T	PSU 0-35V 0-2A Twice Digital	£75
Farnell LF1	Sine/sq Oscillator 10HZ-1MHZ	£45
Racal 1991	Counter/Timer 160MHZ 9 Digit	£150
Racal 2101	Counter 20GHZ LED	£295
Racal 9300	True RMS Millivoltmeter 5HZ-20MHZ etc	£45
Racal 9300B	As 9300	£75
Black Star Orion	Colour Bar Generator RGB & Video	£30
Black Star 1325	Counter Timer 1.3GHZ	£60
Ferrograph RTS2	Test Set	£50
Fluke 97	Scopemeter 2 Channel 50MHZ 25MS/S	£75
Fluke 99B	Scopemeter 2 Channel 100MHZ 5GS/S	£125
Gigatronics 7100	Synthesised Signal Generator 10MHZ-20GHZ	£1,950
Panasonic VP7705A	Wow & Flutter Meter	£60
Panasonic VP8401B	TV Signal Generator Multi Outputs	£75
Pendulum CNT90	Timer Counter Analyser 20GHZ	£750
Seaward Nova	PAT Tester	£95
Solartron 7150	6 1/2 Digit DMM True RMS IEEE	£65
Solartron 7150 Plus	as 7150 plus Temp Measurement	£75
Solartron 7075	DMM 7 1/2 Digit	£60
Solartron 1253	Gain Phase Analyser 1mHZ-20KHZ	£600
Tasakago TM035-2	PSU 0-35V 0-2A 2 Meters	£30
Thurby PL320QMD	PSU 0-30V 0-2A Twice	£160-£200
Thurby TG210	Function Generator 0.002-2MHZ TTL etc Kenwood Badged	£65


## STEWART OF READING

17A King Street, Mortimer, near Reading, RG7 3RS

Telephone: 0118 933 1111 Fax: 0118 9331275


USED ELECTRONIC TEST EQUIPMENT

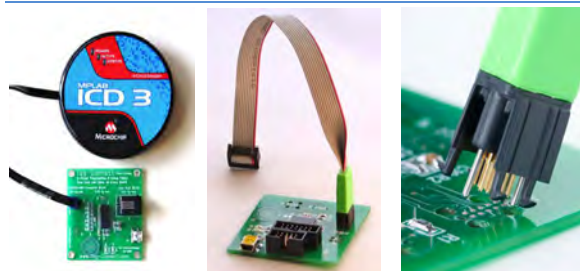Check website [www.stewart-of-reading.co.uk](http://www.stewart-of-reading.co.uk)



**JTAG Connector Plugs Directly into PCB!!**

**No Header! No Brainer!**

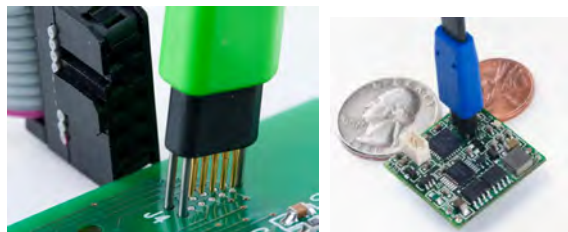

Our patented range of Plug-of-Nails™ spring-pin cables plug directly into a tiny footprint of pads and locating holes in your PCB, eliminating the need for a mating header. Save Cost & Space on Every PCB!!


Solutions for: PIC . dsPIC . ARM . MSP430 . Atmel . Generic JTAG . Altera Xilinx . BDM . C2000 . SPY-BI-WIRE . SPI / IIC . Altium Mini-HDMI . & More

[www.PlugOfNails.com](http://www.PlugOfNails.com)

Tag-Connector footprints as small as 0.02 sq. inch (0.13 sq cm)

ONLY  
£8.99!

# ELECTRONICS TEACH-IN 6

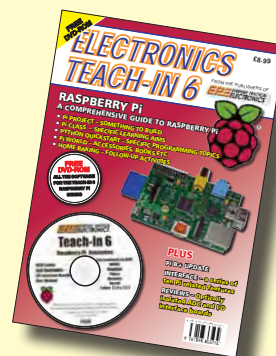

Available from our Direct Book Service  
priced £8.99 including P&P

**Tel: 01202 880299**

Or order your copy from our online shop at:

[www.epemag.com](http://www.epemag.com)



# DIRECT BOOK SERVICE



## Teach-In 2016 Exploring the Arduino

### ARDUINO FOR DUMMIES John Nussey


Arduino is no ordinary circuit board. Whether you're an artist, a designer, a programmer, or a hobbyist, Arduino lets you learn about and play with electronics. You'll discover how to build a variety of circuits that can sense or control real-world objects, prototype your own product, and even create interactive artwork. This handy guide is exactly what you need to build your own Arduino project – what you make is up to you!

- **Learn by doing** – start building circuits and programming your Arduino with a few easy examples – right away!
- **Easy does it** – work through Arduino sketches line by line, and learn how they work and how to write your own.
- **Solder on!** – don't know a soldering iron from a curling iron? No problem! You'll learn the basics and be prototyping in no time.
- **Kitted out** – discover new and interesting hardware to turn your Arduino into anything from a mobile phone to a Geiger counter.
- **Become an Arduino savant** – find out about functions, arrays, libraries, shields and other tools that let you take your Arduino project to the next level
- **Get social** – teach your Arduino to communicate with software running on a computer to link the physical world with the virtual world

438 Pages

Order code ARDDUM01

£19.99

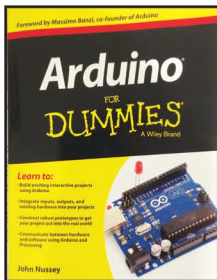

### EXPLORING ARDUINO Jeremy Blum

Arduino can take you anywhere. This book is the roadmap.


Exploring Arduino shows how to use the world's most popular microcontroller to create cool, practical, artistic and educational projects. Through lessons in electrical engineering, programming and human-computer interaction this book walks you through specific, increasingly complex projects, all the while providing best practices that you can apply to your own projects once you've mastered these. You'll acquire valuable skills – and have a whole lot of fun.

- Explore the features of several commonly used Arduino boards
- Use the Arduino to control very simple tasks or complex electronics
- Learn principles of system design, programming and electrical engineering
- Discover code snippet, best practices and system schematics you can apply to your original projects
- Master skills you can use for engineering endeavours in other fields and with different platforms

357 Pages

Order code EXPARD01

£26.99

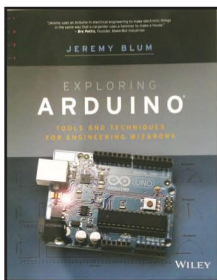

## THEORY AND REFERENCE

### PRACTICAL ELECTRONICS HANDBOOK – 6th Edition, Ian Sinclair

440 pages

Order code NE21

£33.99



### STARTING ELECTRONICS – 4th Edition Keith Brindley

296 pages

Order code NE100

£18.99

### ELECTRONIC CIRCUITS – FUNDAMENTALS & APPLICATIONS – Third Edition Mike Tooley

400 pages

Order code TF43

£25.99

### FUNDAMENTAL ELECTRICAL AND ELECTRONIC PRINCIPLES – Third Edition C.R. Robertson

368 pages

Order code TF47

£21.99

### A BEGINNER'S GUIDE TO TTL DIGITAL ICs R.A. Penfold

142 pages

OUT OF PRINT BP332

£5.45

### UNDERSTANDING ELECTRONIC CONTROL SYSTEMS Owen Bishop

228 pages

Order code NE35

£36.99

## PROJECT CONSTRUCTION

### IC 555 PROJECTS

E. A. Parr

167 pages

Order code BP44

£5.49

### ELECTRONIC PROJECT BUILDING FOR BEGINNERS R. A. Penfold

135 pages

Order code BP392

£5.99

### PRACTICAL FIBRE-OPTIC PROJECTS R. A. Penfold

132 pages

Order code BP374

£5.45

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last page.

FOR A FULL  
DESCRIPTION OF THESE  
BOOKS AND  
CD-ROMS SEE THE SHOP  
ON OUR WEBSITE  
[www.epemag.com](http://www.epemag.com)

All prices include  
UK postage

## MICROPROCESSORS

### INTERFACING PIC MICROCONTROLLERS – SECOND EDITION Martin Bates

298 pages

Order code NE48

£34.99

### PROGRAMMING 16-BIT PIC MICROCONTROLLERS IN C – LEARNING TO FLY THE PIC24 Lucio Di Jasio (Application Segments Manager, Microchip, USA)

496 pages +CD-ROM

Order code NE45

£38.00

### INTRODUCTION TO MICROPROCESSORS AND MICROCONTROLLERS – SECOND EDITION John Crisp

222 pages

Order code NE31

£29.99

### THE PIC MICROCONTROLLER YOUR PERSONAL INTRODUCTORY COURSE – THIRD EDITION. John Morton

270 pages

Order code NE36

£25.00

### PIC IN PRACTICE (2nd Edition) David W. Smith

308 pages

Order code NE39

£24.99

### MICROCONTROLLER COOKBOOK Mike James

240 pages

Order code NE26

£36.99

## BOOK ORDERING DETAILS

All prices include UK postage. For postage to Europe (air) and the rest of the world (surface) please add £3 per book. Surface mail can take up to 10 weeks to some countries. For the rest of the world airmail add £4 per book. CD-ROM prices include VAT and/or postage to anywhere in the world. Send a PO, cheque, international money order (£ sterling only) made payable to **Direct Book Service** or card details, Visa, Mastercard or Maestro to: **DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LIMITED, 113 LYNWOOD DRIVE, MERLEY, WIMBORNE, DORSET BH21 1UU.**

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery – more for overseas orders. Please check price and availability (see latest issue of *Everyday Practical Electronics*) before ordering from old lists.

For a full description of these books please see the shop on our website.

Tel 01202 880299 Fax 01202 843233. E-mail: [dbs@wimborne.co.uk](mailto:dbs@wimborne.co.uk)

Order from our online shop at: [www.epemag.com](http://www.epemag.com)

## FAULT FINDING AND TEST EQUIPMENT

### GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

96 pages


Order code BP239 £5.49

### PRACTICAL ELECTRONIC FAULT FINDING AND TROUBLESHOOTING

Robin Pain

274 pages

Order code NE22 £41.99

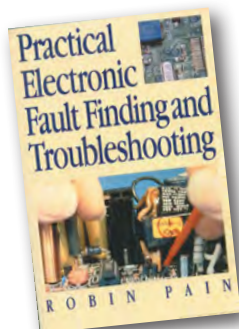

### HOW ELECTRONIC THINGS WORK – AND WHAT TO DO WHEN THEY DON'T

Robert Goodman

394 pages

Order code MGH3 £21.99

### OSCILLOSCOPES – FIFTH EDITION

Ian Hickman

288 pages

Order code NE37 £36.99

## AUDIO & VIDEO

### VALVE AMPLIFIERS – Second Edition

Morgan Jones

288 pages

Order code NE33 £40.99

### BUILDING VALVE AMPLIFIERS

Morgan Jones

368 pages

Order code NE40 £29.00

### ELECTRONIC PROJECTS FOR VIDEO ENTHUSIASTS

R.A. Penfold

109 pages

Order code BP356 £5.45

## COMPUTING AND ROBOTICS

### NEWNES INTERFACING COMPANION

Tony Fischer-Cripps

295 pages

Order code NE38 £41.00

### HOW TO BUILD A COMPUTER MADE EASY

R.A. Penfold

120 pages

Order code BP707 £8.49

### EASY PC CASE MODDING

R.A. Penfold

192 pages + CDROM

Order code BP542 £8.99

### FREE DOWNLOADS TO PEP-UP AND PROTECT YOUR PC

R.A. Penfold

128 pages

Order code BP722 £7.99

### WINDOWS XP EXPLAINED

N. Kantaris and P.R.M. Oliver

264 pages

Order code BP514 £7.99

### THE INTERNET – TWEAKS, TIPS AND TRICKS

R. A. Penfold

128 pages

Order code BP721 £7.99

### eBAY – TWEAKS, TIPS AND TRICKS

R. A. Penfold

128 pages

Order code BP716 £7.50

### AN INTRODUCTION TO eBAY FOR THE OLDER GENERATION

Cherry Nixon

120 pages

Order code BP709 £8.49

### COMPUTING FOR THE OLDER GENERATION

Jim Gatenby

308 pages

Order code BP601 £8.99

### ANDROIDS, ROBOTS AND ANIMATRONICS

Second Edition – John Iovine

224 pages

Order code MGH1 £16.99

### ROBOT BUILDERS COOKBOOK

Owen Bishop

366 pages

Order code NE46 £26.00

### INTRODUCING ROBOTICS WITH LEGO MINDSTORMS

Robert Penfold

288 pages +

Order code BP901 £14.99

### MORE ADVANCED ROBOTICS WITH LEGO MINDSTORMS – Robert Penfold

298 pages

Order code BP902 £14.99

### HOW TO FIX YOUR PC PROBLEMS

R. A. Penfold

128 pages

Order code BP705 £8.49

### WINDOWS 7 – TWEAKS, TIPS AND TRICKS

Andrew Edney

120 pages

Order code BP708 £8.49

### GETTING STARTED IN COMPUTING FOR THE OLDER GENERATION

Jim Gatenby

120 pages

Order code BP704 £8.49

### WINDOWS 8.1 EXPLAINED

Noel Kantaris

180 Pages

Order code BP747 £10.99

## ELECTRONICS TEACH-IN 5

### ELECTRONICS TEACH-IN 5

Jump Start – 15 design and build circuit projects dedicated to newcomers or those following courses in school and colleges. The projects are: Moisture Detector, Quiz Machine, Battery Voltage Checker, Solar-Powered Charger, Versatile Theft Alarm, Spooky Circuits, Frost Alarm, Mini Christmas Lights, iPod Speaker, Logic Probe, DC Motor Controller, Egg Timer, Signal Injector Probe, Simple Radio Receiver, Temperature Alarm.

#### PLUS:


PIC 'N MIX – starting out with PIC Microcontrollers and PRACTICALLY SPEAKING – the techniques of project construction.

**FREE CD-ROM** – The free CD-ROM is the complete Teach-In 2 book providing a practical introduction to PIC Microprocessors plus MikroElektronika, Microchip and L-Tek PoScope software.

160 Pages

Order code ETI5 £8.99

FREE  
CD-ROM

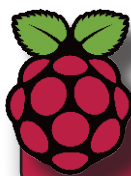

## RASPBERRY PI

## ELECTRONICS TEACH-IN 6

### ELECTRONICS TEACH-IN 6 – A COMPREHENSIVE GUIDE TO RASPBERRY PI

Mike & Richard Tooley

Teach-In 6 contains an exciting series of articles that provides a complete introduction to the Raspberry Pi, the low cost computer that has taken the education and computing world by storm.


This latest book in our Teach-In series will appeal to electronic enthusiasts and computer buffs wanting to get to grips with the Raspberry Pi.

Anyone considering what to do with their Pi, or maybe they have an idea for a project but don't know how to turn it into reality, will find Teach-In 6 invaluable. It covers: Programming, Hardware, Communications, Pi Projects, Pi Class, Python Quickstart, Pi World, Home Baking etc.

The book comes with a FREE cover-mounted DVDROM containing all the necessary software for the series so that readers can get started quickly and easily with the projects and ideas covered.

160 Pages

Order code ETI6 £8.99

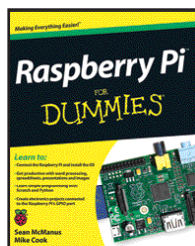

### RASPBERRY PI FOR DUMMIES

Sean McManus and Mike Cook

Write games, compose and play music, even explore electronics – it's easy as Pi! The Raspberry Pi offers a plethora of opportunities, and this great resource guides you step-by-step, from downloading, copying, and installing the software to learning about Linux and finding cool new programs for work, photo editing, and music. You'll discover how to write your own Raspberry Pi programs, create fun games, and much more! Open this book and find: What you can do with Python; Ways to use the Raspberry Pi as a productivity tool; How to surf the web and manage files; Secrets of Sonic Pi music programming; A guide to creating animations and arcade games; Fun electronic games you can build; How to build a 3D maze in Minecraft; How to play music and videos on your Raspberry Pi.

400 Pages

Order code RPIDUM01 £17.99

### RASPBERRY PI MANUAL: A practical guide to the revolutionary small computer

176 pages

Order code H001 £17.99

### RASPBERRY PI USER-GUIDE – Third Edition

262 pages

Order code JW001 £16.99

### PROGRAMMING THE RASPBERRY PI

192 pages

Order code MGH4 £10.99

### GETTING STARTED WITH RASPBERRY PI


164 pages

Order code OR01 £11.50

**ON SALE**  
**28TH APRIL 2016**  
**ELECTRONICS**  
**TEACH-IN 7**  
**£8.99**  
**(SEE PAGE 47 IN THIS ISSUE)**  
**ORDER YOUR COPY**  
**NOW**  
**01202 880299**



# FULL COLOUR COMPUTING BOOKS

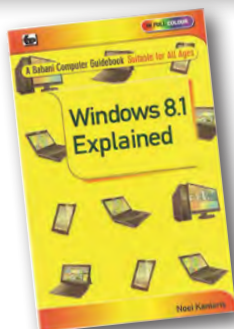

## WINDOWS 8.1 EXPLAINED

Windows 8.1 is the latest version of Microsoft's operating system. It is installed on all new Windows Desktop, Laptop and X86 tablet computers and is also available as a free upgrade. Whether you choose to use the touch screen Tile interface or the mouse operated Desktop interface, a good working knowledge of the operating system is essential to get the most from your computer and this book will help you to do just that.

The book applies to Windows 8.1, Windows 8.1 Pro and the vast majority of Windows 8.1 Enterprise. Also parts of the book should be applicable to windows RT 8.1 which is built on the same foundation as Windows 8.1 but is a restricted version designed specifically for ARM tablets.

Among the many topics covered are: An overview of the Tile Interface, Desktop, Taskbar, Tray Notification Area, Charms bar and running Apps; managing Windows settings, personalising your PC and creating User Accounts; using the Desktop File Explorer, SkyDrive, Internet Explorer and the E-mail App; working with and organising digital photographs, using Media Player to play and store music and to burn CDs and installing Media Center to play DVDs; connecting to wireless networks, setting up a HomeGroup, sharing a printer and networked PCs; using mobility tools to keep your laptop running while away from home; accessibility features should you have dexterity or eyesight problems; keeping your computer healthy and backing up important files; And much more besides....

180 Pages **Order code BP747** **£10.99**

## HOW TO FIX YOUR PC PROBLEMS

R.A. Penfold

128 pages **Order code BP705** **£8.49**

## AN INTRODUCTION TO WINDOWS VISTA

P.R.M. Oliver and N. Kantaris

120 pages **Order code BP703** **£8.49**



## KINDLE FIRE HDX EXPLAINED

This book is written to help users get to grips, quickly and easily, with the amazing Kindle Fire HDX tablet. You will be guided through the configuration and use of the Kindle Fire HDX's facilities and functions. This book was written using the 7" HDX but it is also applicable to the 8.9" model.

Among the many topics covered are: An overview of the Kindle Fire HDX. Charging and setting up, connecting to a Wi-Fi network, registering the device and connecting to Social Networks; setting up and using the 1-Click Amazon account for buying and downloading books, music and other content that you have searched for. Explaining the use of the Carousel. Starting screen Apps. Web and Device settings and the May-day facility; browsing the web with Silk Internet explorer, using Bookmarks and History, printing web pages, documents and messages; connecting to a server to send and receive e-mail messages, using and saving attachments. Creating and organising your Contacts and Calendar appointments; using the Kindle Fire camera to take photos and videos. Watching TV, listening to music you bought, imported and from the radio. Using the X-ray feature with books and other media; Using the OfficeSuite to view your documents, upgrading to OfficeSuite Professional 7 to allow both viewing and creation of Word documents. Excel spreadsheets and PowerPoint presentations. And more besides...

This book will help you acquire the skills needed to understand and make the most of your Kindle Fire HDX.

118 Pages **Order code BP743** **£8.99**

## COMPUTING WITH A LAPTOP FOR THE OLDER GENERATION


R.A. Penfold

120 pages **Order code BP702** **£8.49**

## AN INTRODUCTION TO EXCEL SPREADSHEETS

Jim Gatenby

18 pages **Order code BP701** **£8.49**

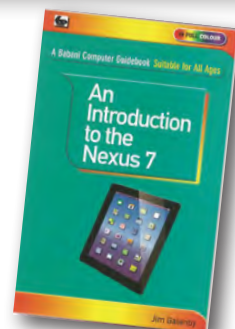

## AN INTRODUCTION TO THE NEXUS 7

This book is intended for the new user of the Nexus 7, although much of it will also apply to the Nexus 10. It is easy to understand being written in plain English and avoiding technical jargon wherever possible.

Among the many useful topics covered are: An overview of the main features of the Nexus 7; setting up the Nexus 7; charging the battery; connecting to the Internet and signing up for Gmail; touch-screen operation and navigating around the various screens; installing Apps from the Google Play Store; setting a password and other precautions to keep your files safe; connecting accessories such as a USB Drive, mouse and keyboard; enjoying entertainment such as eBooks, games, music and videos; searching the Internet, including speaking in keywords; using e-mail, Skype and social networking; installing the free Google Drive app to save your documents in the cloud; using Google Docs free word processing and spreadsheet software; printing a document using Google Cloud Print, Exporting Nexus 7 files to laptop and desktop computers; and much more besides....

Even if you are a complete beginner, this book will help you to easily acquire the skills needed to understand and make the most of the Nexus 7.

118 Pages **Order code BP744** **£8.99**

## BOOK ORDER FORM

Full name: .....

Address: .....

.....

.....

..... Post code: ..... Telephone No: .....

Signature: .....

☐ I enclose cheque/PO payable to DIRECT BOOK SERVICE for £ .....

☐ Please charge my card £ ..... Card expiry date: .....

Card Number ..... Maestro Issue No: .....

Valid From Date ..... Card Security Code ..... (The last three digits on or just below the signature strip)

Please send book order codes: .....

.....

Please continue on separate sheet of paper if necessary



## THE BASIC SOLDERING GUIDE HANDBOOK

**LEARN TO SOLDER SUCCESSFULLY!**  
ALAN WINSTANLEY

The No.1 resource to learn all the basic aspects of electronics soldering by hand.

With more than 80 high quality colour photographs, this book explains the correct choice of soldering irons, solder, fluxes and tools. The techniques of how to solder and desolder electronic components are then explained in a clear, friendly and non-technical fashion so you'll be soldering successfully in next to no time! The book also includes sections on Reflow Soldering and Desoldering Techniques, Potential Hazards and Useful Resources. Plus a Troubleshooting Guide.

Also ideal for those approaching electronics from other industries, the Basic Soldering Guide Handbook is the best resource of its type, and thanks to its excellent colour photography and crystal clear text, the art of soldering can now be learned by everyone!

86 Pages **Order code AW1** **£9.99**



# Max's Cool Beans

By Max The Magnificent

## Pull up a rock

I'm not sure if you remember this, but a few years ago I picked up a really nice 1950s wooden television cabinet. Admittedly, it was a little the worse for wear, but now it's been refinished it looks very tasty indeed.

Ever since I acquired this cabinet, I had the idea of creating a caveman diorama inside. Sad to relate, this project ended up on the back burner for quite some time because I didn't have a clue how to make the cave itself. I fought several battles with chicken wire and *papier mâché*, but to no avail.

My wife, Gina, is an estate agent, and as part of her job she really tries to get to know what people are looking for. Sometime last summer she met a couple. The guy, whom we'll call Mike (because that's his name), wanted a really large room upstairs. It turns out that Mike – a retired Apache attack helicopter pilot – builds large railway dioramas as a hobby. However, although he's great at landscapes and stuff, he knows next to nothing about electronics.

Mike told Gina he wanted to add lights to his streets and houses and trains and suchlike, but he wasn't sure how to control them all. Well, it was like a modeling match made in heaven – on the one hand we have Mike who knows how to implement the landscape stuff; on the other hand I'm the king of the flashing light people. Mike and I now meet up in my office on Saturday mornings and spend a happy few hours doing a mix of electronics and diorama building.

Just to give you a feel for what I'm talking about, the current state of play is shown in Fig.1. This is the underlying cardboard structure. We will be applying plaster-cloth and plaster to add a rock-like look this coming weekend. I should point out that we've spent several months experimenting with dummy ledges and rocks – shaping them and painting them to achieve a photo-realistic appearance. I flatter myself that we've actually become rather good at all of this.

## Welcome to the pleasure dome

Let's take a quick stroll around the cave to see where we're going with this. On the left we have a ledge with a tunnel half way up the wall. There will be a small waterfall coming out of this tunnel, falling into the pool below. Not real water of course, but you can achieve some spectacular effects if you work at it (<http://bit.ly/236PQ02>).

We already have some tri-colored NeoPixels at the back of the tunnel (See my earlier NeoPixel columns...). I wish you could see how cool this looks with a dull, pulsing red

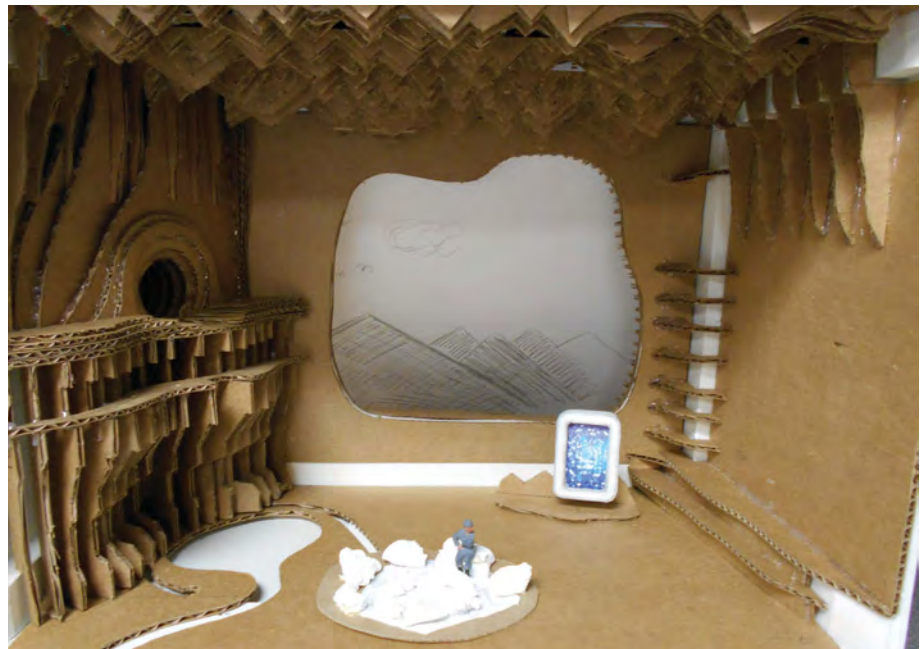


Fig.1. The current state of the caveman diorama


glow (we're also experimenting with a very interesting 'electric arc welder' type of effect). Furthermore, we're thinking of having two Morlock figures crouching on the ledge spying down at the scene below.

Although this isn't apparent in Fig.1, the pool is going to protrude below the level of the cave floor, thereby adding to the illusion of depth. The pool will also be illuminated with NeoPixels (a low, eldritch-green glow is particularly effective, we've found). It might also be worth pointing out that we have 155 NeoPixels hidden in the roof. We aren't sure what we're going to do with these little scamps yet, but – as a general rule of thumb – you can't have too many flashing lights. (You may think this is a simple philosophy, but it's served me well over the years).

The mountains we see looking out of the mouth of the cave are currently just sketched on white card. In the fullness of time, however, we will replace this with a flat-screen computer monitor that will display a 3D-generated Tolkien-like scene. This will reflect what's happening in the real world – daytime here will be daytime there; nighttime will be nighttime; if it's stormy here there will be thunder and lightning in the diorama, etc. There will be two cavemen standing on the ledge at the mouth of the cave looking into the distance. Another caveman will be standing on a ladder creating a cave painting on the right-hand wall of the cave.

Towards the front of the scene (near the television's screen) will be a fire with several cavemen sitting around discussing the events of the day. We're working at 1/32 scale, so a 6-foot tall man will be 2¼-inches



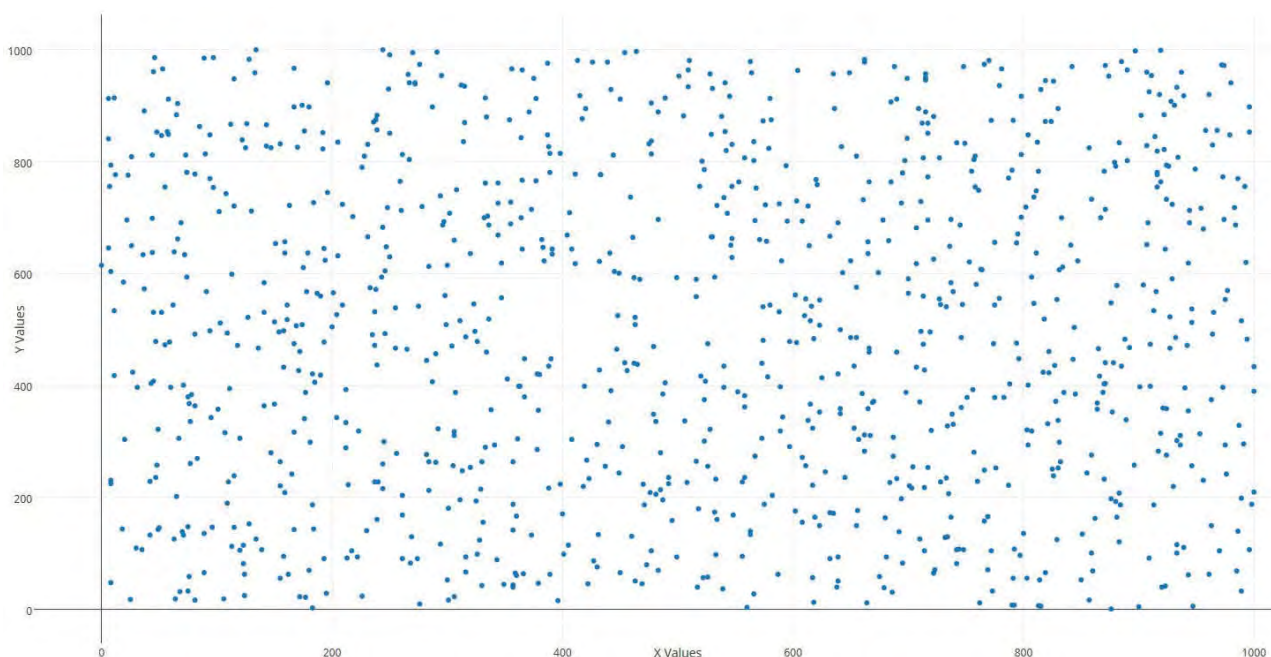

**Fig.2. The X-Y pairs presented on an X-Y plot**

tall in the diorama (the soldier figure sitting next to the fire pit in Fig.1 is there only to provide a sense of scale).

One of the figures sitting around the fire will be a depiction of yours truly wearing shorts and a Hawaiian shirt. The time portal floating in the far-right corner of the cave explains my presence in the scene, along with any other anachronisms, such as the Morlocks.

### Lords of chaos

One thing we'll need to achieve in the various effects we envisage is a good source of random or pseudo-random numbers. In the case of the caveman diorama, we're using a number of Arduino Nanos to control the various effects. The Arduino does, of course, provide a `random()` function, but just how 'random' are the numbers it returns?

Some people may simply trust this sort of thing in the belief that whoever created the Arduino and its supporting environment knew what they were doing. Personally, I don't trust anybody or anything, except my mother, of course, but she really doesn't have much to offer regarding random numbers and chaos-related topics (she prefers to generate her own chaos wherever she goes).

The bottom line is that I don't like to take anything like this for granted; I'd feel really silly if I generated say 1,000 random numbers, each between 0 and 999, and used them to generate my special effects, only to discover that the vast majority of these numbers landed between 200 and 600, for example.

Thus, in order to perform a 'cheap-and-cheerful' verification of the Arduino's `random()` function, I threw a simple program together that loops around creating 1000 X-Y pairs, where each X and Y value is a randomly generated integer between 0 and 999. The core of this code is as follows:

```
for (int i = 0; i < 1000; i++)
{
    x = random(0, 1000);
    y = random(0, 1000);
    Serial.print(x);
    Serial.print(",");
    Serial.println(y);
}
```

As we see, I streamed the comma-separated X-Y pairs out to the Serial Monitor in the Arduino's IDE. I then cut-and-pasted these values into a NotePad \*.txt file (you can access these values at <http://bit.ly/23cb40b> if you want to play with them yourself). I then used an online tool called 'plotly' (<https://plot.ly>) to plot these results on an X-Y graph, see Fig.2.

You can access a full-size version of the resulting plot at: <http://bit.ly/1PUorVS>. As you'll see, the result is a reasonably gratifying even distribution. Of course, this is a somewhat simplistic verification technique, but 'it's better than a poke in the eye with a sharp stick,' as they say. Based on this test, I felt comfortable proceeding to the next step, which was to create a flickering fire effect.

### Quest for fire

As I mentioned earlier, we're really trying to make this diorama look mega-realistic. The fire around which the cavemen will be sitting is a case in point – if this is less than stellar, the overall effect will suffer. To kick off our experiments, we took just three regular LEDs – one red, one orange, and one yellow – and put them in a box with a hole cut in the top. Then we took some twigs and charred the ends and placed them around the hole. Next we used a snippet of code a bit like the following to control the brightness of the LEDs using the Arduino's pseudo-analogue (PWM) outputs:

```
int redVal, orangeVal, yellowVal;

while (1) {
    redVal    = random(155,255);
    orangeVal = random(155,255);
    yellowVal = random(155,255);

    digitalWrite(redPin,    redVal);
    digitalWrite(orangePin, orangeVal);
    digitalWrite(yellowPin, yellowVal);

    delay( random(1, 100) );
}
```



**Fig.3.** The original array (top left) versus the new array (top right); the glass bead cone (bottom left) versus the crushed glass cone (bottom right).

As you can see, this provides ‘random’ with regard to both intensity and duration. And, even though it’s really simple, it actually provides a reasonably interesting effect as you can see in this YouTube video: <http://bit.ly/1RSDXDH>. However, although this looks OK when the ambient light is low, it’s almost impossible to see in regular lighting conditions.

The solution is to use more and brighter LEDs. Yes, of course I’m talking about NeoPixels. Having said this, another consideration with the above code is that, although the delay is random, all of the pixels change at the same time, resulting in a less-than-optimal effect when you are using a bunch of LEDs.

### **GLOW, SPARK and DARK modes**

To cut a long story short, we implemented a simple time wheel where each ‘tick’ occupies one millisecond. We also decided that each pixel would randomly adopt one of three modes – GLOW, SPARK, or DARK – where these modes are ‘weighted’ such that GLOW is the most common.

In the case of the GLOW mode, that pixel’s color – red, orange, or yellow – is randomly selected (weighted so that red is more prevalent than orange, which is more prevalent than yellow). Also, the intensity and duration values for the pixel are randomly selected. By comparison, SPARK mode adds more colors (white and purple) and pixel flares up and fades away. Last but not least, in DARK mode the pixel is turned off for some random duration. The end result is that each pixel can be ‘doing its own thing’ completely independent of all of the other pixels (you can access the entire Arduino program here: <http://bit.ly/1Xk6E0d>).

With regard to the physical implementation, we started off with an array of 16 pixels created from segments of NeoPixel strip in a 5-6-5 arrangement. We also created a small cone of glass pebbles stuck together using clear epoxy. The idea behind the pebbles was to bring the light up to the logs while also reflecting and refracting it to add visual interest. The end result was pretty good, but not great; also, the array consumed too much area (sad face).

Happily, while rooting around the [Adafruit.com](http://adafruit.com) website, we realised that a 7-NeoPixel Jewel (<http://bit.ly/22g53tt>) fits exactly inside a 12-NeoPixel Ring (<http://bit.ly/1ULy6G6>). The result is a grouping with more LEDs than our original array (19 versus 16) that occupies a smaller (1.5-inch diameter) footprint. Also, this is where we had a bit of a brainwave – we re-created the

cone that sits on top of the pixels using crushed glass and clear epoxy (Fig.3).

The result of having 19 NeoPixels means that the fire is more than visible even in bright ambient light. Meanwhile, as you can see in this YouTube video (<http://bit.ly/1YhHmjs>), the crushed glass cone reflects and refracts light like you wouldn’t believe.

When you are watching the video, observe the occasional flashes of white and purple light; these are from the SPARK mode. Although you may think all of this is a bit ‘over the top,’ remember that we’re going to place charred ‘logs’ around the glass cone, so you’ll only be able to see the ‘fire’ through the chinks in these logs.

As you’ll see from our code, everything is fully parameterised. Thus far, we’re pretty much using the original parameter values we threw into the mixing pot – I think we’ll be able to achieve increasingly realistic effects by varying these parameters. If you decide to build one of these to play with yourself, we’d love to hear your thoughts on the optimal parameter settings.

### **Future developments**

Now we’re about to start work on the time portal, which we’re hoping to have working by yesterday – perhaps even the day before if we’re lucky. I will report further details in a future *Cool Beans* column. Until then, have a good one!

Any comments or questions? – please feel free to send me an email at: [max@CliveMaxfield.com](mailto:max@CliveMaxfield.com)



# EPE IS PLEASED TO BE ABLE TO OFFER YOU THESE ELECTRONICS CD-ROMS

From  
£49.00

## TINA Design Suite V10

**Analogue, Digital, Symbolic, RF, MCU and Mixed-Mode Circuit Simulation and PCB Design with TINA**

FEATURED IN  
OUR TEACH-IN  
2015 SERIES

TINA Design Suite V10 is a powerful yet affordable software package for analysing, designing and real time testing analogue, digital, MCU, and mixed electronic circuits and their PCB layouts. You can also analyse RF, communication, optoelectronic circuits, test and debug microcontroller applications.

Enter and analyse any circuit up to 100 nodes (student), or 200 with the Basic (Hobbyist) version within minutes with TINA's easy-to-use schematic editor. Enhance your schematics by adding text and graphics. Choose components from the large library containing more than 10,000 manufacturer models. Analyse your circuit through more than 20 different analysis modes or with 10 high tech virtual instruments.

Present your results in TINA's sophisticated diagram windows, on virtual instruments, or in the live interactive mode where you can even edit your circuit during operation.

Customise presentations using TINA's advanced drawing tools to control text, fonts, axes, line width, colour and layout. You can create and print documents directly inside TINA or cut and paste your results into your favourite word processing or DTP package.

TINA includes the following Virtual Instruments: Oscilloscope, Function Generator, Multimeter, Signal Analyser/Bode Plotter, Network Analyser, Spectrum Analyser, Logic Analyser, Digital Signal Generator, XY Recorder.

This offer gives you a CD-ROM – the software will need registering (FREE) with Designsoft (TINA), details are given within the package.


**Get TINA Basic V10 (Hobbyist) for £129 or Student V10 version for £49**

Prices include VAT and UK postage

✚ get a 1 year free subscription for TINACloud the breakthrough cloud version of TINA which you can run on most operating systems and computers, including PCs, Macs, thin clients iPads and other tablets – even on many smart phones, smart TVs and e-book readers.

To order please either fill out and return the order form, or call us on 01202 880299

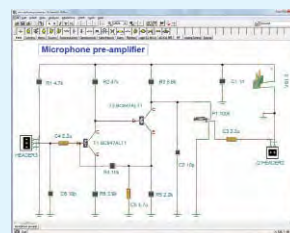Alternatively you can order via our secure online shop at: [www.epemag.com](http://www.epemag.com)



### ELECTRONICS TEACH-IN 2

#### ELECTRONICS TEACH-IN 2 CD-ROM USING PIC MICROCONTROLLERS A PRACTICAL INTRODUCTION

This Teach-In series of articles was originally published in EPE in 2008 and, following demand from readers, has now been collected together in the Electronics Teach-In 2 CD-ROM.

The series is aimed at those using PIC microcontrollers for the first time. Each part of the series includes breadboard layouts to aid understanding and a simple programmer project is provided.

Also included are 29 PIC N' Mix articles, also republished from EPE. These provide a host of practical programming and interfacing information, mainly for those that have already got to grips with using PIC microcontrollers. An extra four part beginners guide to using the C programming language for PIC microcontrollers is also included.

The CD-ROM also contains all of the software for the Teach-In 2 series and PIC N' Mix articles, plus a range of items from Microchip – the manufacturers of the PIC microcontrollers. The material has been compiled by Wimborne Publishing Ltd. with the assistance of Microchip Technology Inc.

CD-ROM Order code ETI2 CD-ROM £9.50

### ELECTRONICS TEACH-IN 3

#### ELECTRONICS TEACH-IN 3 CD-ROM

The three sections of this CD-ROM cover a very wide range of subjects that will interest everyone involved in electronics, from hobbyists and students to professionals. The first 80-odd pages of Teach-In 3 are dedicated to Circuit Surgery, the regular EPE clinic dealing with readers' queries on circuit design problems – from voltage regulation to using SPICE circuit simulation software.

The second section – Practically Speaking – covers the practical aspects of electronics construction. Again, a whole range of subjects, from soldering to avoiding problems with static electricity and identifying components, are covered. Finally, our collection of Ingenuity Unlimited circuits provides over 40 circuit designs submitted by the readers of EPE.

The CD-ROM also contains the complete Electronics Teach-In 1 book, which provides a broad-based introduction to electronics in PDF form, plus interactive quizzes to test your knowledge, TINA circuit simulation software (a limited version – plus a specially written TINA Tutorial).

The Teach-In 1 series covers everything from Electric Current through to Microprocessors and Microcontrollers and each part includes demonstration circuits to build on breadboards or to simulate on your PC.

CD-ROM Order code ETI3 CD-ROM £8.50

### ELECTRONICS TEACH-IN 4

#### ELECTRONICS TEACH-IN 4 CD-ROM

A Broad-Based Introduction to Electronics.

The Teach-In 4 CD-ROM covers three of the most important electronics units that are currently studied in many schools and colleges. These include, Edexcel BTEC level 2 awards and the electronics units of the new Diploma in Engineering, Level 2.

The CD-ROM also contains the full Modern Electronics Manual, worth £29.95. The Manual contains over 800 pages of electronics theory, projects, data, assembly instructions and web links.

A package of exceptional value that will appeal to all those interested in learning about electronics or brushing up on their theory, be they hobbyists, students or professionals.

CD-ROM Order code ETI4 CD-ROM £8.99

### ELECTRONICS TEACH-IN BUNDLE – SPECIAL BUNDLE PRICE £14 FOR PARTS 1, 2 & 3

CD-ROMs

Order code ETIBUNDLE

Bundle Price £14.00



# PICmicro TUTORIALS AND PROGRAMMING


## HARDWARE

### PICmicro Multiprogrammer Board and Development Board

*Suitable for use with the three software packages listed below*

This flexible PICmicro microcontroller programmer board and combination board allows students and professional engineers to learn how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40 pin devices from the 12, 16 and 18 series PICmicro ranges. For experienced programmers all programming software is included in the MLoader utility that is free to download when you buy the multiprogrammer board. For those who want to learn, choose one or all of the packages below to use with the hardware.

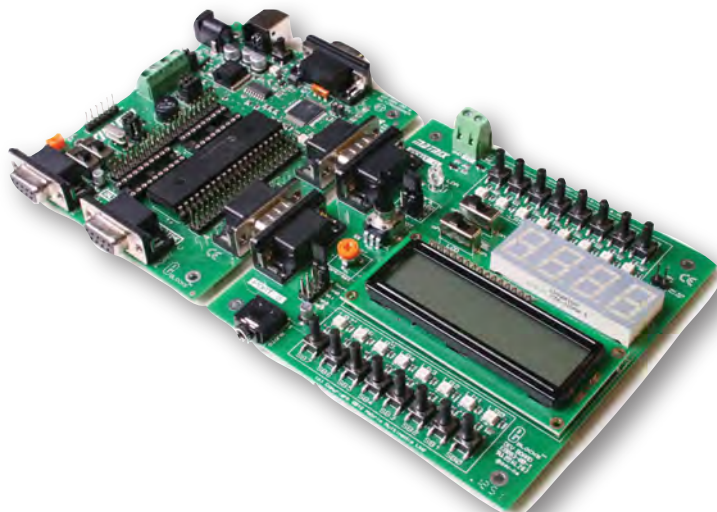- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 16 individual LEDs, quad 7-segment display and alphanumeric LCD display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- USB programmable
- Compatible with the E-blocks range of accessories



**£167 including VAT and postage, supplied with USB cable and free to download programming software**

## SOFTWARE


### ASSEMBLY FOR PICmicro V5

(Formerly PICtutor)

Assembly for PICmicro microcontrollers V3.0 (previously known as PICtutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes.

The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro microcontroller, this is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed, which enhances understanding.

- Comprehensive instruction through 45 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.

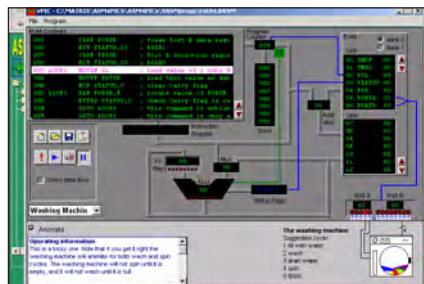


### 'C' FOR 16 Series PICmicro Version 5

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD-ROM contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

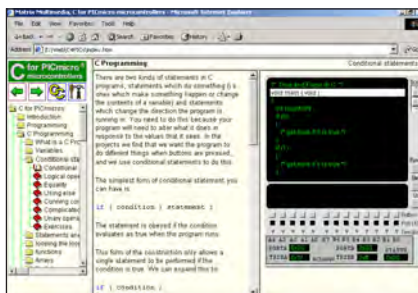- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.




Minimum system requirements for these items: Pentium PC running, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.  
Flowcode will run on XP or later operating systems

### FLOWCODE FOR PICmicro V6

Flowcode is a very high level language programming system based on flowcharts. Flowcode allows you to design and simulate complex systems in a matter of minutes. A powerful language that uses macros to facilitate the control of devices like 7-segment displays, motor controllers and LCDs. The use of macros allows you to control these devices without getting bogged down in understanding the programming. When used in conjunction with the development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols
- Full on-screen simulation allows debugging and speeds up the development process.
- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 18, 28 and 40-pin devices
- 16-bit arithmetic strings and string manipulation
- Pulse width modulation
- I2C.

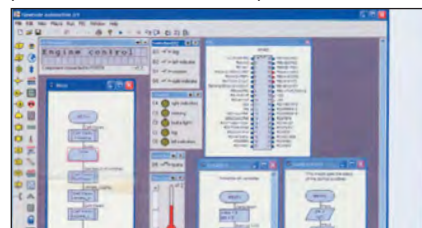**Please note:** Due to popular demand, Flowcode PICmicro, AVR, DSPIC, PIC24 & ARM V6 are now available as a download. Please include your email address and a username (of your choice) on your order. A unique download code will then be emailed to you. If you require the CDROM as a back-up then please add an extra £14 to the price.



## PRICES

Prices for each of the CD-ROMs above are:  
(Order form on next page)

(UK and EU customers add VAT to 'plus VAT' prices)

Hobbyist/Student .....	£58.80	inc VAT
Professional (Schools/HE/FE/Industry) .....	£150	plus VAT
Professional 10 user (Network Licence) .....	£499	plus VAT
Site Licence .....	£999	plus VAT

Flowcode (choose PIC, AVR, ARM, dsPIC, PIC24) . . . £94.80 plus VAT




# CIRCUIT WIZARD

Circuit Wizard is a revolutionary software system that combines circuit design, PCB design, simulation and CAD/CAM manufacture in one complete package. Two versions are available, Standard or Professional.

By integrating the entire design process, Circuit Wizard provides you with all the tools necessary to produce an electronics project from start to finish – even including on-screen testing of the PCB prior to construction!

\* Circuit diagram design with component library (500 components Standard, 1500 components Professional) \* Virtual instruments (4 Standard, 7 professional) \* On-screen animation \* Interactive circuit diagram simulation \* True analogue/digital simulation \* Simulation of component destruction \* PCB Layout \* Interactive PCB layout simulation \* Automatic PCB routing \* Gerber export \* Multi-level zoom (25% to 1000%) \* Multiple undo and redo \* Copy and paste to other software \* Multiple document support

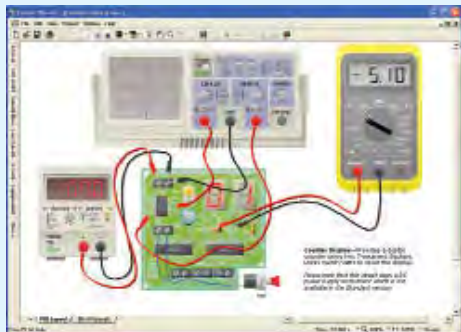

This software can be used with the *Jump Start* and *Teach-In 2011* series (and the *Teach-In 4* book).

Standard £61.25 inc. VAT. Professional £75 plus VAT.

# GCSE ELECTRONICS



Suitable for any student who is serious about studying and who wants to achieve the best grade possible. Each program's clear, patient and structured delivery will aid understanding of electronics and assist in developing a confident approach to answering GCSE questions. The CD-ROM will be invaluable to anyone studying electronics, not just GCSE students.

\* Contains comprehensive teaching material to cover the National Curriculum syllabus \* Regular exercises reinforce the teaching points \* Retains student interest with high quality animation and graphics \* Stimulates learning through interactive exercises \* Provides sample examination questions with model solutions \* Authored by practising teachers \* Covers all UK examination board syllabuses \* Caters for all levels of ability \* Useful for self-tuition and revision
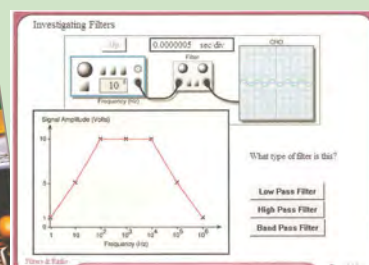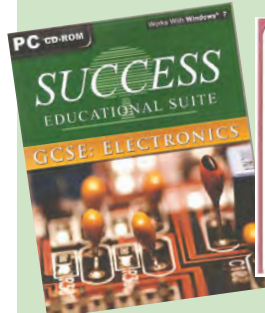
## SUBJECTS COVERED

Electric Circuits – Logic Gates – Capacitors & Inductors – Relays – Transistors – Electric Transducers – Operational Amplifiers – Radio Circuits – Test Instruments

Over 100 different sections under the above headings



£12.50 inc. VAT and P&P

## Please send me: CD-ROM ORDER FORM

- ☐ Assembly for PICmicro V5  
☐ 'C' for 16 Series PICmicro V5

- Version required:  
☐ Hobbyist/Student  
☐ Professional  
☐ Professional 10 user  
☐ Site licence



Note: The software on each version is the same, only the licence for use varies.

- ☐ Flowcode for PICmicro V6 (DOWNLOAD ONLY)  
☐ Flowcode for AVR V6 (DOWNLOAD ONLY)  
☐ Flowcode for ARM V6 (DOWNLOAD ONLY)  
☐ Flowcode for dsPIC V6 (DOWNLOAD ONLY)  
☐ Flowcode for PIC24 V6 (DOWNLOAD ONLY)

Email: .....

Username: .....

- ☐ PICmicro Multiprogrammer Board and Development Board V4 (hardware)

- ☐ Circuit Wizard – Standard  
☐ Circuit Wizard – Professional  
☐ GCSE Electronics

- ☐ Teach-In 2  
☐ Teach-In 3  
☐ Teach-In 4  
☐ Teach-In Bundle

- NEW** ☐ TINA Design Suite V10 Basic (Hobbyist)  
☐ TINA Design Suite V10 (Student)

Full name: .....

Address: .....

Post code: ..... Tel. No: .....

Signature: .....

☐ I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £ .....

☐ Please charge my Visa/Mastercard/Maestro: £ .....

Valid From: ..... Card expiry date: .....

Card No: ..... Maestro Issue No. ....

Card Security Code ..... (The last 3 digits on or just under the signature strip)

Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 2000/ME/XP, mouse, sound card, web browser.

## ORDERING ALL PRICES INCLUDE UK POSTAGE

Standard/Student/Basic (Hobbyist)  
Version price includes postage to most countries in the world  
EU residents outside the UK add £5 for airmail postage per order

Professional, Multiple User and Site License Versions – overseas readers add £5 to the basic price of each order for airmail postage (do not add VAT unless you live in an EU (European Union) country, then add VAT at 20% or provide your official VAT registration number).

Send your order to:  
Direct Book Service  
Wimborne Publishing Ltd  
113 Lynwood Drive, Merley,  
Wimborne, Dorset BH21 1UU

To order by phone ring

01202 880299. Fax: 01202 843233

Goods are normally sent within seven days

E-mail: orders@wimborne.co.uk

Online shop:

**www.epemag.com**

# ELECTRONIC BUILDING BLOCKS

BY JULIAN  
EDGAR

QUICK AND EASY  
CONSTRUCTION

GREAT RESULTS ON  
A LOW BUDGET

## USB BOOST CHARGER

Large complex projects are fun, but they take time and can be expensive. Sometimes you just want a quick result at low cost. That's where this series of *Electronic Building Blocks* fits in. We use 'cheap as chips' components bought online to get you where you want to be... FAST! These projects range from around £15 to under a fiver... bargains!

### Charge a USB device from lower voltages

Here's a cheap module that will provide a charging source for any USB-charged device – a phone, tablet, even a rechargeable torch. The beauty of this device is that it is a boost converter, so it can do this charging while using an input voltage well below 5V.

### Tiny but mighty

A tiny  $33 \times 18 \times 13\text{mm}$ , the module is claimed to work at input voltages from 0.9 to 6V and output up to one amp. In real-world use on typical USB-charged devices, we found that indeed an output current of up to 1A was available. However, the unit showed good voltage regulation only with input voltages from 1.5 to 5.5V.

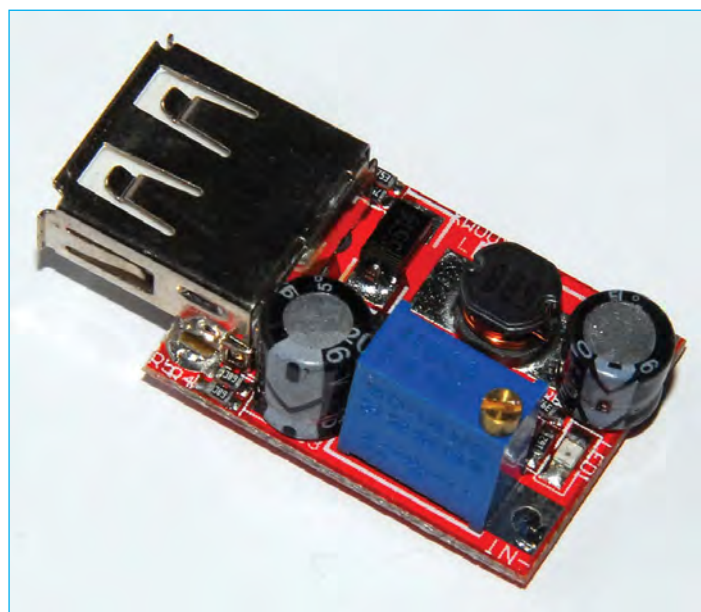


Fig.1. This tiny module is able to charge your phone or other USB-charged device while being powered from voltages well below the 5V USB nominal output.

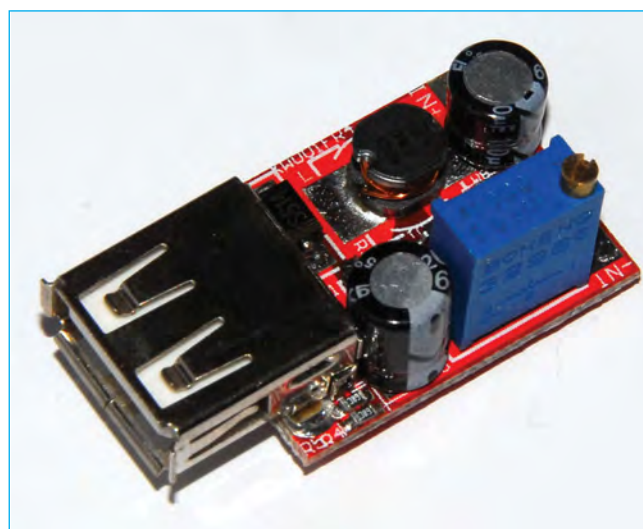


Fig.2. A normal USB cable plugs into the on-board socket, while power and ground feeds need to be soldered to pads located at the other end of the board.

### Control and efficiency

The module features a pot that allows you to adjust the output voltage to precisely 5V, with an adjustable output range of 3.3 to 9V.

Conversion efficiency is claimed to be 94 per cent and while we did not directly measure this, in operation the module stayed quite cool.

### Use with flat batteries

So what use is this device? Well, the major use is as an emergency charger for a phone. Place the module in a small box along with a dual AA cell holder, add a switch and you have an emergency supply that can be used to charge a phone, using only readily-available AA cells.

Another use is if you get sick of throwing away batteries that, while down a bit in voltage, are not fully discharged. This can be the case if you use devices that freeze if the voltage drops too far – so you end up with a bunch of cells still showing 1.3 or 1.4V. What a waste to throw them away!

Place two cells in series and this module will charge a USB device – even when the series cells' voltage is down to just 2V!



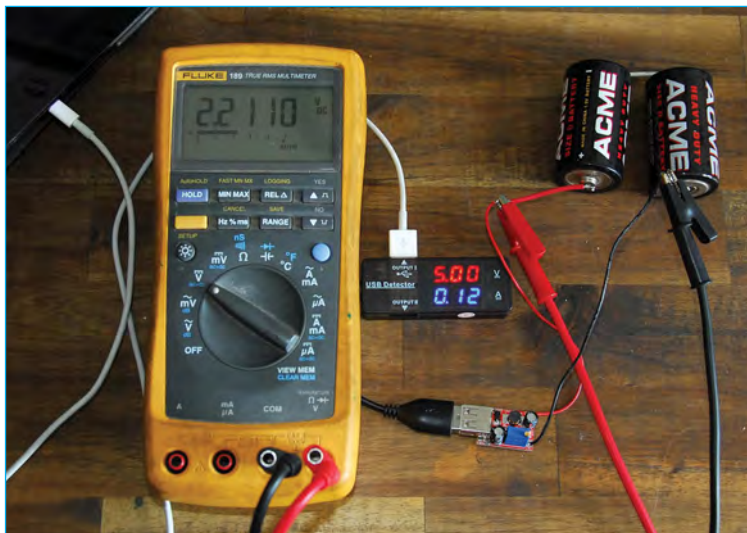


Fig.3. Here's the charging module in action. Being powered by two near-flat D cells (series voltage of the pair is just 2.2V, as shown on the multimeter), the module is charging an iPad Air at 120mA and 5.0V. The tiny module is nearly lost from sight in this pic – it's at the middle, bottom of the photo.

### Not all of them are the same...

Not all of these *USB boost converters* are the same! This one, also purchased, proved to have poor performance. In real-world charging use we were unable to gain a greater output than 240mA and output voltage regulation was poor.

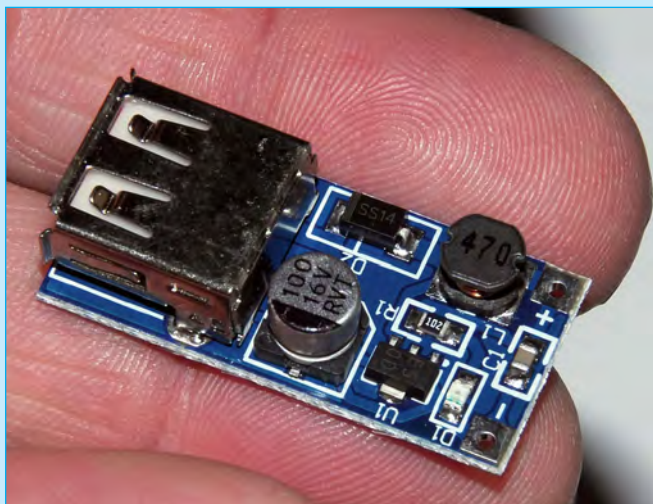


Fig.4. A 'dud' – be careful what you buy!

However, there's a qualification that needs to be made. Batteries in most modern USB-charged devices have a lot of capacity. Charging via a couple of AA cells (or even two D cells!) isn't going to take your iPad from empty to full – the cells don't have enough stored energy capacity. But as an emergency charge if you're back-packing or hiking, sure.

While we didn't try it, this may also be a useful module to use with solar cells developing less than 5V.

### Sourcing


And what will the module cost you? Well under £2, delivered to your letter box!

At the time of writing, it could be found on eBay by searching for item No. 141662415264.

You may also be able to find it by searching under 'USB Solar Boost DC-DC 3V-5V Adjustable Power Supply Voltage Converter Module NEW', or variants of that phrase.
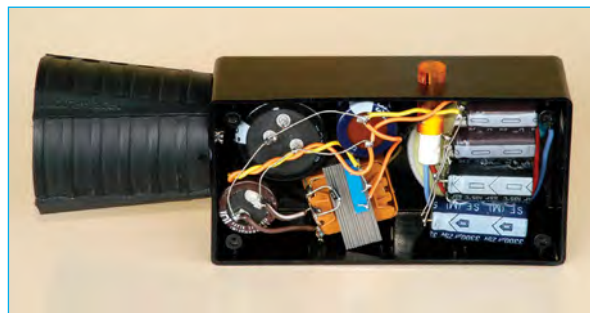
### Next month

Here's a project that is not just good fun, but you end up with a useful torch that will never get flat batteries and will last a very long time.



Next month – Build your own hand-powered LED torch!

# Radio Bygones

The magazine for all vintage radio enthusiasts.

Covers:

- Domestic radio and TV
- Amateur radio
- Military, aeronautical or marine communications
- Radar or radio navigation
- Broadcasting
- Radio systems

Subscribe to Radio Bygones (available by postal subscription):

1 year (4 issues)

UK £18.00; Europe £19.50; Rest of the World £23.00

OR

Download your PDF copies, only £8.00 for one year

Tel: 01202 880299 or visit: [www.radiobygones.com](http://www.radiobygones.com)



# PCB SERVICE

CHECK US OUT ON THE WEB



Basic printed circuit boards for most recent *EPE* constructional projects are available from the *PCB Service*, see list. These are fabricated in glass fibre, and are drilled and roller tinned, but all holes are a standard size. They are not silk-screened, nor do they have solder resist. Double-sided boards are **NOT plated through hole** and will require 'vias' and some components soldering to both sides. **NOTE: PCBs from the July 2013 issue with eight digit codes** have silk screen overlays and, where applicable, are double-sided, plated through-hole, with solder masks, they are similar to the photos in the relevant project articles.

All prices include VAT and postage and packing. Add £2 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Wimborne Publishing Ltd., 113 Lynwood Drive, Merley, Wimborne, Dorset BH21 1UU. Tel: 01202 880299; Fax 01202 843233; Email: orders@epemag.wimborne.co.uk. On-line Shop: www.epemag.com.** Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).

**NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail.**

**Back numbers or photocopies of articles are available if required – see the Back Issues page for details. WE DO NOT SUPPLY KITS OR COMPONENTS FOR OUR PROJECTS.**

PROJECT TITLE	ORDER CODE	COST
<b>FEB '15</b>		
Audio Delay For PA Systems	01110131	£13.42
Teach-In 2015 – Part 1 Pre-Amp	905	£9.33
<b>MARCH '15</b>		
Stereo Echo & Reverb Unit	01110131	£13.42
Super Smooth, Full-range, 10A/230V Speed Controller for Universal Motors	10102141	£11.80
<b>APRIL '15</b>		
A Rubidium Frequency Standard For A Song	04105141	£8.02
USB/RS-232C Interface	07103141	£7.48
Teach-In 2015 – Part 3	906	£8.75
<b>MAY '15</b>		
Deluxe Fan Speed Controller	10104141	£10.72
RGB LED Strip Driver	16105141	£8.56
Low-cost Precision 10V DC Reference For Checking DMMs	04104141	£7.48
<b>JUNE '15</b>		
Burp Charge Your Batteries	14103141	£13.40
Teach-In 2015 – Part 5	907	£8.55
<b>JULY '15</b>		
L-o-o-n-g Gating Times For The 12-Digit High-Resolution Counter	04106141	£11.55
Threshold Voltage Switch	99106141	£10.15
Touch-Screen Digital Audio Recorder – Part 2	01105141	£13.70
<b>AUG '15</b>		
Nirvana Valve Simulator – Main PCB	01106141	£15.05
– Front Panel	01106142	£8.30
TempMasterMK3	21108141	£12.00
Teach-In 2015 – Part 7	908	£8.75
<b>SEPT '15</b>		
Opto-Theremin – Part 1		
– Main Theremin	23108141	£14.25
– Volume Control Board	23108142	£6.95
Mini-D Stereo 10W/Channel Class-D Audio Amplifier	01110141	£7.45
Wideband, Active Differential Oscilloscope Probe		
– Main PCB	04107141	} £11.80
– Screening PCB	04107142	
<b>OCT '15</b>		
Digital Effects Processor For Guitars And Musical Instruments	01110131	£16.40
Courtesy LED Lights Delay For Cars	05109141	£8.55
Teach-In 2015 – Part 9	909	£10.70
<b>NOV '15</b>		
The Currawong – Part 1		
– Main Board	01111141	£47.20
– Front Panel	01111142	} £24.75
– Rear Panel	01111143	
48V Dual Phantom Power Supply	18112141	£9.37
Programmable Mains Timer With Remote Switching		
– Main Board	19112141	£11.80
– Front Panel	19112142	£16.40

PROJECT TITLE	ORDER CODE	COST
<b>DEC '15</b>		
TDR Dongle For Oscilloscopes	04112141	£7.20
High-Energy Multi-Spark CDI For Performance Cars	05112141	£11.80
<b>JAN '16</b>		
Isolating High Voltage Probe For Oscilloscopes	04108141	£11.80
The Currawong – Part 3		
– Remote Control Board	01111144	£6.95
<b>FEB '16</b>		
Spark Energy Meter		
– Main Board	05101151	£20.75
– Zener Diode Board	05101152	} £7.50
– Calibrator Board	05101153	
<b>APRIL '16</b>		
Appliance Insulation Tester	04103151	£11.80
– Front Panel	04103152	£11.80
Low Frequency Distortion Analyser	04104151	£7.50
<b>MAY '16</b>		
2-Channel Balanced Input Attenuator for Audio Analysers and Digital Scopes		
– Main Board	04105151	£16.40
– Front Panel	04105152	} £20.75
– Rear Panel	04105153	
Appliance Earth Leakage Tester		
– Main Board	04203151	} £16.40
– Insulation Board	04203152	
– Front Panel	04203153	£16.40
4-Output Universal Voltage Regulator	18105151	£7.50
<b>JUNE '16</b>		
Infrasound Snooper	04104151	£7.48
Audio Signal Injector and Tracer	04106151	£9.64
– Shield Board	04106153	£7.48
Champion Preamp	01109121/22	£8.29

\* See NOTE left regarding PCBs with eight digit codes \*

Please check price and availability in the latest issue.

A large number of older boards are listed on, and can be ordered from, our website.

Boards can only be supplied on a payment with order basis.

## EPE SOFTWARE

Where available, software programs for *EPE* Projects can be downloaded free from the Library on our website, accessible via our home page at: [www.epemag.com](http://www.epemag.com)

## PCB MASTERS

PCB masters for boards published from the March '06 issue onwards are available in PDF format free to subscribers – email [fay.kearn@wimborne.co.uk](mailto:fay.kearn@wimborne.co.uk) stating which masters you would like.

## EPE PRINTED CIRCUIT BOARD SERVICE

Order Code      Project      Quantity      Price

Name .....

Address .....

Tel. No. ....

I enclose payment of £..... (cheque/PO in £ sterling only)

to:

**Everyday Practical Electronics**



Card No. ....

Valid From ..... Expiry Date .....

Card Security No. .... Maestro Issue No. ....

Signature .....

**Note:** You can also order PCBs by phone, Fax or Email or via the Shop on our website on a secure server:

<http://www.epemag.com>





# CLASSIFIED

## ADVERTISEMENTS

If you want your advertisements to be seen by the largest readership at the most economical price our classified page offers excellent value. The rate for semi-display space is £10 (+VAT) per centimetre high, with a minimum height of 2.5cm. All semi-display adverts have a width of 5.5cm. The prepaid rate for classified adverts is 40p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. **VAT must be added.** Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, 113 Lynwood Drive, Merley, Wimborne, Dorset, BH21 1UU. Phone: 01202 880299. Fax: 01202 843233. Email: [stewart.kearn@wimborne.co.uk](mailto:stewart.kearn@wimborne.co.uk). For rates and information on display and classified advertising please contact our Advertisement Manager, Stewart Kearns as above.

Everyday Practical Electronics reaches more UK readers than any other UK monthly hobby electronics magazine, our sales figures prove it.

We have been the leading monthly magazine in this market for the last twenty-six years.

**ELECTRONICS: Home Study Software, Apps & eBooks £1.95**

[www.eptsoft.com/HomeStudy](http://www.eptsoft.com/HomeStudy)

### SPRING END OF LINE BARGAINS

FOR HOME ELECTRONIC BUILDERS  
CONNECTORS; SWITCHES;  
HARDWARE; ENCLOSURE'S; PANELS

[www.partridgeelectronics.co.uk](http://www.partridgeelectronics.co.uk)

### CANTERBURY WINDINGS

UK manufacturer of toroidal transformers  
(10VA to 3kVA)

All transformers made to order. No design fees.  
No minimum order.

[www.canterburywindings.co.uk](http://www.canterburywindings.co.uk)

01227 450810

**ADVERTISE HERE FOR  
JUST £25 +VAT CALL  
STEWART KEARN  
ON 01202 880299  
STEWART.KEARN@WIMBORNE.CO.UK**

### BOWOOD ELECTRONICS LTD

*Suppliers of Electronic Components*

[www.bowood-electronics.co.uk](http://www.bowood-electronics.co.uk)

Unit 10, Boythorpe Business Park, Dock Walk, Chesterfield,  
Derbyshire S40 2QR. Sales: 01246 200 222

Send large letter stamp for Catalogue

### MISCELLANEOUS

**VALVES AND ALLIED COMPONENTS IN STOCK.** Phone for free list. Valves, books and magazines wanted. Geoff Davies (Radio), tel. 01788 574774.

**PIC DEVELOPMENT KITS, DTMF kits and modules, CTCSS Encoder and Decoder/Display kits.** Visit [www.cstech.co.uk](http://www.cstech.co.uk)

**KITS, TOOLS, COMPONENTS. S.A.E. Catalogue.** SIR-KIT ELECTRONICS, 52 Severn Road, Clacton, CO15 3RB, <http://sir-kit.webs.com>

## ADVERTISERS INDEX

BETA LAYOUT . . . . .	80	QUASAR ELECTRONICS . . . . .	2/3
BRUNNING SOFTWARE . . . . .	5	STEWART OF READING . . . . .	66
CRICKLEWOOD ELECTRONICS . . . . .	61	TAG-CONNECT . . . . .	66
ESR ELECTRONIC COMPONENTS . . . . .	6	WEARDALE ELECTRONICS . . . . .	61
HAMMOND ELECTRONICS Ltd . . . . .	20		
iCSAT . . . . .	50	<b>ADVERTISEMENT OFFICES:</b>	
JPG ELECTRONICS . . . . .	80	113 LYNWOOD DRIVE, MERLEY, WIMBORNE,	
LABCENTER . . . . .	Cover (iv)	DORSET BH21 1UU	
LASER BUSINESS SYSTEMS . . . . .	53	<b>PHONE:</b> 01202 880299	
MICROCHIP . . . . .	Cover (ii), Cover (iii) & 10	<b>FAX:</b> 01202 843233	
PEAK ELECTRONIC DESIGN . . . . .	45	<b>EMAIL:</b> <a href="mailto:stewart.kearn@wimborne.co.uk">stewart.kearn@wimborne.co.uk</a>	
PICO TECHNOLOGY . . . . .	61	<b>WEB:</b> <a href="http://www.epemag.com">www.epemag.com</a>	
POLABS D.O.O. . . . .	65	<b>For editorial address and phone numbers see page 7</b>	

# Next Month

Content may be subject to change

## Driveway Monitor – Part 1

Based on a Honeywell magneto-resistive sensor, this *Driveway Monitor* provides an audible and visual indication when a vehicle is detected. Alternatively, it can be made to activate a remote-controlled mains switch to turn on lights for a preset time.

## Install USB charging points in your car

New cars often have more than one USB socket for charging phones and other devices, but older cars have none. This tiny PCB will let you add one or two USB sockets and the total charge current can be up to 2.5A, more than enough for phones, satnavs or dash cameras.

## Intelligent Charger for Nicad and NiMH Batteries

Cheap chargers supplied with original equipment can – and often do – damage the battery. Proper chargers are usually expensive. This cheap and easy-to-build Nicad/NiMH charger is suitable for automatically charging a wide range of batteries.


## Teach-In 2016 – Part 6

In July's *Teach-In 2016* we examine how an Arduino can communicate wirelessly. *Arduino Workshop* will introduce wireless modules and *Arduino World* will look at short-range wireless systems to send data between Arduinos. *Coding Quickstart* introduces the RadioHead Packet Radio library for embedded microprocessors, and the *Get Real* project will be a simple wireless-linked rain alarm.

## PLUS!

All your favourite regular columns from *Audio Out* and *Circuit Surgery* to *Electronic Building Blocks*, *PIC n' Mix* and *Net Work*.

**JULY '16 ISSUE ON SALE 2 JUNE 2016**

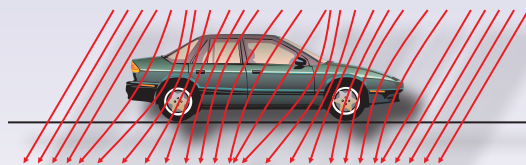


## WELCOME TO JPG ELECTRONICS

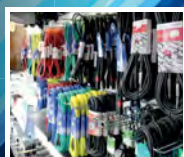**Selling Electronics in Chesterfield for 29 Years**

**Open Monday to Friday 9am to 5:30pm  
And Saturday 9:30am to 5pm**

- Aerials, Satellite Dishes & LCD Brackets
- Audio Adaptors, Connectors & Leads
- BT, Broadband, Network & USB Leads
- Computer Memory, Hard Drives & Parts
- DJ Equipment, Lighting & Supplies
- Extensive Electronic Components
  - ICs, Project Boxes, Relays & Resistors
- Raspberry Pi & Arduino Products
- Replacement Laptop Power Supplies
- Batteries, Fuses, Glue, Tools & Lots more...



**T: 01246 211 202**

**E: [sales@jpgelectronics.com](mailto:sales@jpgelectronics.com)**

**JPG Electronics, Shaw's Row,  
Old Road, Chesterfield, S40 2RB**

**W: [www.jpgelectronics.com](http://www.jpgelectronics.com)**



**Retail & Trade Welcome • Free Parking • Google St View Tour: S40 2RB**

**PANEL-POOL®**  
Beta LAYOUT

## Custom Front Panels

Digital printing

Free Design Software

[www.panel-pool.com](http://www.panel-pool.com)

**Beta**  
LAYOUT  
create:electronics

PANEL-POOL® is a registered trademark of Beta LAYOUT GmbH





## MPLAB® Xpress Cloud-based Integrated Development Environment

The image displays the MPLAB Xpress IDE interface. On the left, a 'Project Files' tree shows 'MCC Generated Files' (adc.h, pin\_manager.h, pwm5.h, mtc.h, tmr4.h) and 'Source Files' (adc.c, pin\_manager.c, pwm6.c, mcc.c, tmr4.c, main.c). The main window shows a C code editor with a snippet of code: 

```
void main(void)
{
    // Enable the Global Interrupts
    // Disable the Peripheral Interrupts
    // Disable the Peripheral InterruptDisable();
}
```

 Below the code editor is a 'Hardware Configuration' window showing a logic diagram of a PIC16F18855 microcontroller. The 'Output' window shows a variable 'per\_val' with a value of '<Enter new watch>'. The 'Debug Resources' window shows a tree view of the hardware configuration: LED\_brightness\_control, Device (PIC16F18855), Compiler Toolchain (XC8 (1.35)), Memory, Debug Tool (Simulator / Xpress Board), and Debug Resources (Data BP Used: 1 Free: 999, Program BP Used: 1 Free: 999).

A green PCB board with a PIC16F18855 microcontroller, labeled 'MPLAB Xpress Evaluation Board'.

A red PCB board with a PIC16F18855 microcontroller, labeled 'Curiosity Development Board'.

MPLAB® Xpress  
Evaluation Board

Curiosity  
Development Board

PICKit™ 3



Join now and gain the advantage, go to -  
[MPLABXpress.microchip.com](http://MPLABXpress.microchip.com)



# PROTEUS 8.3

ECAD to MCAD made easy

Data Exchange with  
**STEP/IGES**



AUTODESK. PTC  
SOLIDWORKS

The Proteus Design Suite now includes full support for data exchange with Mechanical CAD packages via the STEP/IGES file formats. This allows you to better visualise your design and helps quickly solve fixtures, fittings and casement problems.

Import 3D STEP/IGES models for your parts and visualise inside the Proteus Design Suite. Export your completed board to Solidworks or other MCAD software.

Visit [www.labcenter.com](http://www.labcenter.com)

Tel: +44 01756753440 E-Mail [info@labcenter.com](mailto:info@labcenter.com)