

**- EPE -  
NEW NAME  
NEW DESIGN!**



# Practical Electronics

The UK's premier electronics and computing maker magazine

## Flowerpot speakers!

A low-cost route to high-quality Hi-Fi

## PIC n' Mix

Software tools for the PIC18F

## Circuit Surgery

Understanding Differential amplifiers


## Ultrabrite LED bike light



**WIN!**  
Microchip  
Explorer 16/32  
Development  
Kit  
**WIN!**

***Don't miss  
our Super  
Summer Sale!***


## Mastering stepper motor drivers

 

## Robot Buggy Ultrasound sensing!



## Meet the Micromite Explore-28

 

## Building the Low-noise theremin PSU



## PLUS!

Cool Beans – Even cooler ping-pong ball lights!  
Net Work – IP security cameras  
Techno Talk – The perils of an enquiring mind...



Sep 2020 £4.99



9 772632 573016

# Introducing a New Generation of AVR<sup>®</sup> Devices

## AVR-DA Flexibility in Design



The Functional Safety Ready AVR-DA family is the new generation of AVR microcontrollers running up to 24 MHz across the full supply voltage range 1.8V to 5.5V featuring intelligent analog and core independent peripherals.


The AVR-DA family uses the latest Core Independent Peripherals and low-power capability to handle real-time control functions in industrial control, home appliance, automotive and Internet of Things (IoT) applications. The Event System and Configurable Custom Logic (CCL) peripherals offer near-zero latency for time-critical functions. Intelligent Analog peripherals like 12-bit differential Analog-to-Digital Converter (ADC), Zero-Cross Detect (ZCD), 10-bit Digital-to-Analog Converter (DAC) and the latest-generation Peripheral Touch Controller (PTC) put the AVR-DA family in the center of sensor interface, system monitoring and human interface applications. 5V operation for increased noise immunity and low-power features ease power supply concerns.

- Product certifications made easier with Functional Safety supporting documentation and development tools.
- Add IoT and connectivity to your application, thanks to the high memory densities and SRAM-to-Flash ratio.
- Design robust and noise-immune applications with built-in safety features and 5V supply.
- Create state-of-the-art capacitive touch interfaces using the latest-generation PTC.



 [www.microchip.com/avr-da](http://www.microchip.com/avr-da)





Made in the UK.

Written in Britain, Australia,  
the US and Ireland.

Read everywhere.

© Electron Publishing Limited 2020

Copyright in all drawings, photographs, articles, technical designs, software and intellectual property published in *Practical Electronics* is fully protected, and reproduction or imitation in whole or in part are expressly forbidden.

The October 2020 issue of *Practical Electronics* will be published on Thursday, 3 September 2020 – see page 72.

## Projects and Circuits

- Ultrabrite LED Pushbike Light** 16  
Design by Daniel Doyle – words by Nicholas Vinen  
Use a tiny (22 × 12mm) high-efficiency LED driver that delivers a constant 1A or 2.2A to make a make a (very!) bright bicycle light, torch or other light source.
- The Micromite Explore-28** by Geoff Graham 24  
Plug-in module with the powerful 28-pin Micromite plus a USB socket for comms and programming – all you need to start with the Micromite in one handy package.
- Three Stepper Motor Drivers** by Allan Linton-Smith 32  
Want to build your own 3D printer or CNC machine? You'll need stepper motor drivers. Here are three of the most common driver modules and how to use them.

## Series, Features and Columns

- The Fox Report** by Barry Fox 8  
A to D: content rescue
- Techno Talk** by Mark Nelson 10  
The perils of an enquiring mind...
- Net Work** by Alan Winstanley 12  
Lights, camera, action! A return to the complex world of IP security cameras.
- Cheap and easy compact speaker enclosures** by Julian Edgar 38  
A novel technique for building enclosures using clay-fibre flowerpots
- Circuit Surgery** by Ian Bell 43  
Differential amplifiers
- Make it with Micromite** by Phil Boyce 48  
Part 20: Ultrasonic obstacle avoidances
- Max's Cool Beans** by Max The Magnificent 53  
Flashing LEDs and drooling engineers – Part 7
- PIC n' Mix** by Mike Hobbett 57  
Part 2: Software tools for the PIC18F
- Audio Out** by Jake Rothman 60  
Low-noise Theremin Power Supply – Part 1

## Regulars and Services

- Wireless for the Warrior** 2
- PE Summer Sale!** 3
- Subscribe to Practical Electronics and save money** 4
- NEW! Practical Electronics back issues DOWNLOADS – great 20-year deal!** 6
- Reader services – Editorial and Advertising Departments** 7
- Editorial** 7  
On yer bike!... It's not over yet, but...
- PE Teach-In 8** 11
- PE Teach-In 9** 14
- Exclusive Microchip reader offer** 15  
Win a Microchip Explorer 16/32 Development Kit
- Practical Electronics – get your back issues here!** 23
- Direct Book Service** 66  
Build your library of carefully chosen technical books
- Practical Electronics PCB Service** 68  
PCBs for Practical Electronics projects
- Teach-In bundle – what a bargain!** 70
- Classified ads and Advertiser index** 71
- Next month! – highlights of our next issue of Practical Electronics** 72



# WIRELESS FOR THE WARRIOR

by LOUIS MEULSTEE

## THE DEFINITIVE TECHNICAL HISTORY OF RADIO COMMUNICATION EQUIPMENT IN THE BRITISH ARMY

The *Wireless for the Warrior* books are a source of reference for the history and development of radio communication equipment used by the British Army from the very early days of wireless up to the 1960s.





The books are very detailed and include circuit diagrams, technical specifications and alignment data, technical development history, complete station lists and vehicle fitting instructions.

*Volume 1* and *Volume 2* cover transmitters and transceivers used between 1932-1948. An era that starts with positive steps taken to formulate and develop a new series of wireless sets that offered great improvements over obsolete World War I pattern equipment. The other end of this

timeframe saw the introduction of VHF FM and hermetically sealed equipment.

*Volume 3* covers army receivers from 1932 to the late 1960s. The book not only describes receivers specifically designed for the British Army, but also the Royal Navy and RAF. Also covered: special receivers, direction finding receivers, Canadian and Australian Army receivers, commercial receivers adopted by the Army, and Army Welfare broadcast receivers.

    *Volume 4* covers clandestine, agent or 'spy' radio equipment, sets which were used by special forces, partisans, resistance, 'stay behind' organisations, Australian Coast Watchers and the diplomatic service. Plus, selected associated power sources, RDF and intercept receivers, bugs and radar beacons.



ORDER YOURS TODAY!

JUST CALL 01202 880299 OR VISIT [www.electronpublishing.com](http://www.electronpublishing.com)



# ***Super Summer Sale!***

## ***Subscribe now and avoid future price rises!***

### **Practical Electronics special offers**

**33% off** all PCBs up to and including those in the December 2019 issue

**25% off** all PE/EPE print back issues up to the December 2019 issue

### **Practical Electronics subscription offer**

Subscribe to PE hard copy for 12-months and receive a **free 12-month back-issue download** of your choice from Volume 28-46 (see page 6).

Subscribe to PE hard copy for 24-months and receive **two free 12-month back-issue downloads** of your choice from Volume 28-46 (see page 6), normal price.

**Existing subscribers** are welcome to renew early for another 12 or 24 months and still receive the offer – your new subscription will simply be added to the end of your existing subscription – **no issues lost by renewing early and you of course avoid future subscription price rises!**

Subscription offers only apply to direct subscriptions via Select Publishing Services, our distributor – not via third-party subscription services.

Payment must be received by close of offer: 30 September 2020




**Don't miss out!**

**Just call 01202 880299 or visit our secure online shop at:  
[www.electronpublishing.com](http://www.electronpublishing.com)**



**- EPE -  
NEW NAME  
NEW DESIGN!**

 

# Practical Electronics

**UK readers **SAVE £1** on every issue**

**NEW subscriptions hotline!**  
**01202 087631**

**Take out a one-year subscription and save £10 over the year.**

**Even better – save £1 per issue if you subscribe for two years – a total saving of £24.**

**Overseas rates represent exceptional value**

- You also:**
- Avoid any cover price increase for the duration of your subscription
  - Get your magazine delivered to your door each month
  - Guarantee a copy, even if the newsagents sell out

- Order by:**
- Phone or post with a cheque, postal order or credit card
  - Or order online at: [www.electronpublishing.com](http://www.electronpublishing.com)



## Practical Electronics

### SUBSCRIPTION PRICES

Subscriptions for delivery direct to any address in:

**UK:** 6-months £26.99, 12-months £49.85, 24-months £94.99

**Europe Airmail:** 6-months £30.99, 12-months £57.99, 24-months £109.99

**Rest Of The World Airmail:** 6-months £37.99, 12-months £70.99, 24-months £135.99

Cheques (in **£ sterling only**) payable to *Practical Electronics* and sent to: Practical Electronics Subscriptions, PO Box 6337, Bournemouth BH1 9EH, United Kingdom


**Tel:** 01202 087631

**Email:** [pesubs@selectps.com](mailto:pesubs@selectps.com)

Also via our online shop at: [www.electronpublishing.com](http://www.electronpublishing.com)

Subscriptions start with the next available issue. We accept MasterCard or Visa.

 (For past issues see the Back Issues page.)



### DIGITAL SUBSCRIPTIONS

Electronic subscriptions are available from £24.99 for 12 months, more details at: [www.electronpublishing.com](http://www.electronpublishing.com)

### SUBSCRIPTION ORDER FORM

- ☐ 6 Months: UK £26.99, Europe £30.99 (Airmail), Rest of the World £37.99 (Airmail)
- ☐ 1 Year: UK £49.85, Europe £57.99 (Airmail), Rest of the World £70.99 (Airmail)
- ☐ 2 Years: UK £94.99, Europe £109.99 (Airmail), Rest of the World £135.99 (Airmail)

**To:** Practical Electronics Subscriptions  
PO Box 6337  
Bournemouth BH1 9EH  
United Kingdom

**Tel:** 01202 087631

**Email:** [pesubs@selectps.com](mailto:pesubs@selectps.com)

**I enclose payment of £ .....**  
(cheque/PO in £ sterling only)  
payable to *Practical Electronics*

☐ Please charge my Visa/Mastercard



My card number is: .....  
Please print clearly, and check that you have the number correct

Card Security Code ..... Valid From Date.....  
(The last 3 digits on or just under the signature strip)

Card Ex. Date .....

Name .....

Address .....

Post code ..... Tel. ....

Email .....

**Subscriptions start with the next available issue.**





# STAY AT HOME!

## AND READ **SILICON CHIP!**

Of course we want you to continue to support Practical Electronics . . . but did you know you can also subscribe to SILICON CHIP – Australia's electronics magazine – direct from the United Kingdom (or anywhere else!)


**And now there's a real choice:**

- (1) A 12 month printed edition subscription (12 issues), delivered right to your mailbox, for \$AU150 per year (that's about £77 / €87 at time of publication)
- (2) A 12 month digital/online edition (exactly the same content as the printed magazine) for \$AU85 (about £44/ €50 at press time) – available to view when printed edition is released in Australia.
- (3) A 12 month combined printed and online subscription – the best of both worlds – read now and have your printed edition available for future reference! That's just \$AU170 for 12 months (about £87/ €98).
- (4) You can order a SILICON CHIP back issue for \$AU10 (about £5 / €6) plus P&P – most recent months still in stock
- (5) Now you can order SILICON CHIP archives on flash drive: a quality metal flash drive containing any five year block of SILICON CHIP – from the first issue back in 1987 until Dec 2019 (see [siliconchip.com.au/shop/digital\\_pdfs](http://siliconchip.com.au/shop/digital_pdfs) for details)

Log onto [www.siliconchip.com.au](http://www.siliconchip.com.au) for much more information!

**You might also be interested in:**

### **Radio, TV & Hobbies on DVD**



Take a trip back in time for the entire Radio, TV and Hobbies magazine, from April 1939 through to March 1965 – ready to enjoy at your leisure, again and again and again. Comes in a protective case – and it's just \$AU62 plus p&p (about £31.60/€36)  
Or you can download the digital edition of Radio, TV & Hobbies: \$AU50 (£25.50 / €29)  
See [siliconchip.com.au/shop/3](http://siliconchip.com.au/shop/3) for other options. And yes, you can order online!

# **SILICON CHIP**

## **Australia's Electronics Magazine**



# DOWNLOAD YOUR PE/EPE BACK ISSUES

**COMPLETE-YEAR** collections – all 12 issues for each year!

**From just £6.95 each**

**VOL 28** – January to December 1999 – **£6.95**

**VOL 29** – January to December 2000 – **£6.95**

**VOL 30** – January to December 2001 – **£6.95**

**VOL 31** – January to December 2002 – **£6.95**

**VOL 32** – January to December 2003 – **£6.95**

**VOL 33** – January to December 2004 – **£6.95**

**VOL 34** – January to December 2005 – **£6.95**

**VOL 35** – January to December 2006 – **£6.95**

**VOL 36** – January to December 2007 – **£6.95**

**VOL 37** – January to December 2008 – **£6.95**

**VOL 38** – January to December 2009 – **£8.95**

**VOL 39** – January to December 2010 – **£8.95**

**VOL 40** – January to December 2011 – **£8.95**

**VOL 41** – January to December 2012 – **£12.95**

**VOL 42** – January to December 2013 – **£12.95**

**VOL 43** – January to December 2014 – **£14.95**

**VOL 44** – January to December 2015 – **£14.95**

**VOL 45** – January to December 2016 – **£16.95**

**VOL 46** – January to December 2017 – **£18.95**

**VOL 47** – January to December 2018 – **£22.95**

**VOL 48** – January to December 2019 – **£24.95**

**FIVE-YEAR** collections – 60 issues!

**From just £14.95 each**

**PE2832:** Jan 99 to Dec 03 – **£14.95**

**PE2933:** Jan 00 to Dec 04 – **£14.95**

**PE3034:** Jan 01 to Dec 05 – **£14.95**

**PE3135:** Jan 02 to Dec 06 – **£14.95**

**PE3236:** Jan 03 to Dec 07 – **£14.95**

**PE3337:** Jan 04 to Dec 08 – **£14.95**

**PE3438:** Jan 05 to Dec 09 – **£19.95**

**PE3539:** Jan 06 to Dec 10 – **£19.95**

**PE3640:** Jan 07 to Dec 11 – **£19.95**

**PE3741:** Jan 08 to Dec 12 – **£19.95**

**PE3842:** Jan 09 to Dec 13 – **£24.95**

**PE3943:** Jan 10 to Dec 14 – **£24.95**

**PE4044:** Jan 11 to Dec 15 – **£29.95**

**PE4145:** Jan 12 to Dec 16 – **£29.95**

**PE4246:** Jan 13 to Dec 17 – **£32.95**

**PE4347:** Jan 14 to Dec 18 – **£34.95**

## 20 YEARS OF PE!

AMAZING BUNDLE OFFER  
Every issue from 1999 – 2018

240 magazines for just

**£49.95**

**PE2832:** Jan 99 to Dec 03  
**PLUS!**

**PE3337:** Jan 04 to Dec 08  
**PLUS!**

**PE3842:** Jan 09 to Dec 13  
**PLUS!**

**PE3447:** Jan 14 to Dec 18

## Do you have the 15-year bundle?

Upgrade to the new 20-year bundle for just £9.95 with: **PE15to20**

Download your collections at: [www.electronpublishing.com](http://www.electronpublishing.com)



### Editorial offices

Practical Electronics  
Electron Publishing Limited  
1 Buckingham Road  
Brighton  
East Sussex BN1 3RA

**Tel** 01273 777619  
**Mob** 07973 518682  
**Fax** 01202 843233  
**Email** [pe@electronpublishing.com](mailto:pe@electronpublishing.com)  
**Web** [www.epemag.com](http://www.epemag.com)

### Advertisement offices

Practical Electronics Adverts  
1 Buckingham Road  
Brighton  
East Sussex BN1 3RA

**Tel** 01273 777619  
**Mob** 07973 518682  
**Email** [pe@electronpublishing.com](mailto:pe@electronpublishing.com)

**Editor** Matt Pulzer  
**General Manager** Louisa Pulzer  
**Digital subscriptions** Stewart Kearn **Tel** 01202 880299  
**Online Editor** Alan Winstanley  
**Web Systems** Kris Thain  
**Publisher** Matt Pulzer

### Print subscriptions

Practical Electronics Subscriptions  
PO Box 6337  
Bournemouth BH1 9EH  
United Kingdom

**Tel** 01202 087631  
**Email** [pesubs@selectps.com](mailto:pesubs@selectps.com)

### Technical enquiries

We regret technical enquiries cannot be answered over the telephone. We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We cannot provide data or answer queries on articles or projects that are more than five years old.

Questions about articles or projects should be sent to the editor by email: [pe@electronpublishing.com](mailto:pe@electronpublishing.com)

### Projects and circuits

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

A number of projects and circuits published in *Practical Electronics* employ voltages that can be lethal. You should not build, test, modify or renovate any item of mains-powered equipment unless you fully understand the safety aspects involved and you use an RCD (GFCI) adaptor.

### Component supplies

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers. We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

### Advertisements

Although the proprietors and staff of *Practical Electronics* take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are bona fide, the magazine and its publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts. The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

### Transmitters/bugs/telephone equipment

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment, as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.

### On yer bike!

Welcome to the September issue of *PE*. There are very few things to recommend a pandemic, but one positive trend has been the rise in cycling as people avoid public transport. Bicycle sales in the UK have shot up, and although currently the days are long and the nights short, a great bike light is still a must-have accessory. (Actually, it's the law after dark, and rightly so.) If you want something with a bit more optical oomph then we have just the project for you: our *Ultrabrite LED Light*.

### It's not over yet, but...

I'm sure there is still a long way to go before we can declare any kind of victory over the current pandemic, but little by little some aspects of life are returning to normality.

In the UK, most retailers that sell *Practical Electronics* are now open and stocking your favourite magazine. However, if your newsagent of choice is not yet open, or you simply prefer to socially isolate for now, then don't forget you can buy *PE* online from us for exactly the same price (£4.99, postage included).

For our overseas readers, delivery is still frustratingly slow, but it is speeding up and the great news for our North American friends is that we are now resuming shipments to US and Canadian stores. So, Barnes & Noble and other retailers will soon be stocking *PE* again.

### Back issue downloads

It's always a slightly nerve-wracking time when a new product is launched on the shop, but I am pleased to report that our new downloads service has worked well and many of you have taken advantage of the new low prices, especially for the older issues. CDs are still available, but the downloads are immediate, cheaper and more secure. A big thank you to Alan Winstanley and Kris Thain who are the behind-the-scenes wizards making the website run smoothly.

Do remember that the downloads service is not just for back issues – we also sell the latest version for immediate download.

### Summer Sale

Last, a reminder that our summer sale is in full swing. If you fancy a nice summer project, then do please see the ad on page 3 outlining the details, and then head over to the online store for some PCB bargains!

Keep well everyone

**Matt Pulzer**

**Publisher**



# The Fox Report

Barry Fox's technology column



## A to D: content rescue

**S**afe bet: everyone has a shoebox (or many) full of old analogue audio tapes and video cassettes. Buried among the drossy taped episodes of long-forgotten soaps, once-new movies that are now regularly shown free on TV and off-air audio cassette dubs of music that are now free on Spotify, there will surely be a few gems – video tapes of family and friends, bootleg audio of long-disbanded bands and off-air time-shifts of TV documentaries that now have historical value.

Anything of real interest or value needs digital dubbing, onto hard disk or memory drive, as soon as possible. Covid-19 lockdown and subsequent restrictions on traditional social activity, such as going to clubs, concerts, theatres and cinemas, has created an unexpected window of unhappy opportunity to get the job done.

Assuming the analogue media has not physically disintegrated, and you can find, borrow or buy from eBay a compatible working player, the question becomes – how to capture the best available quality with the least possible hassle, at minimum cost? Some practical tips, generated from hard-labour trial and error during my enforced lockdown, may be of use. Let's look first at video rescue.

### Capturing analogue video

There are two routes to video capture – analogue and digital.

For the analogue route, plug the SCART, phono or S-Video outputs on the tape player into one of the 'Rescue your VHS tapes' capture dongles which



sell for around £20-£30, and connect by USB lead to a PC. Usually the dongle comes with a disc offering simple PC software to control capture. If there is an option to burn-to-blank DVD, ignore it. DVD is a dying format, and VHS-to-DVD transfer introduces too many opportunities for something to go wrong. Burned DVDs often don't play reliably on all disc players; the discs don't last for ever and will need dubbing off again later as reliable DVD players become as rare as hens' teeth.

So, forget about DVD and the MPEG-2 compression system used for DVD. Opt instead for hard disk or stick

memory with more efficient MP4 (or modern improvements on MP4).

All your video tapes will be Standard Definition and the PC software that comes with basic dongles will be SD. If presented with a resolution option, go for PAL 576/25 (or 30). By and large, anything larger is just wasting bits and storage space on coding noise.

It's probably best to ignore the capture software that comes free with a dongle. It will very likely be overly simple and restrictive, and probably MPEG-2, DVD-specific. The slightly more upmarket commercial programs ArcSoft Showbiz and Hauppauge Capture are simple and easy to use, but my tip is to go for the excellent free Open Source capture program OBS (Open Broadcaster Software): <https://obsproject.com/>

Because OBS offers so many user options, it takes a bit of learning, but the effort is well worth it in the end; and a team of gallant volunteer developers keeps on upgrading OBS.

If you need to edit what you capture, my recommendation is Shotcut, another excellent Open Source program that also requires, but repays, time spent learning to use it: <https://shotcut.org/>

### Games capture boxes


Instead of using a simple SD VHS-to-video capture dongle it is actually far better to use a gameplay capture device 'box', which handles HD video. These



**Extruded enclosures  
standard and heatsink**

[www.hammondmfg.com/1455.htm](http://www.hammondmfg.com/1455.htm)  
[www.hammondmfg.com/1455NHD.htm](http://www.hammondmfg.com/1455NHD.htm)

 **01256 812812**  
**[sales@hammond-electronics.co.uk](mailto:sales@hammond-electronics.co.uk)**



are sold, for instance by Hauppauge, to let computer gamers record their master moves. These device boxes take in analogue Standard or High Definition video and audio (composite or component) from a games console and use custom ICs to deliver a digital bitstream which is sent to a PC by USB. Capture software (Showbiz, OBS or similar) installed on the PC does the rest.

Games capture boxes also take in HDMI digital signals from a console, as long as they are unprotected – ie, not movies which are content copy protected by HDCP.

Games capture boxes will usually also accept SD analogue video signals from a tape deck, digitise them and send the bits to a PC with installed capture software. It's all just bitstreams to the boxes.

(For the sake of completeness, it is possible to buy separate boxes which convert protected HDMI digits to unprotected analogue component video; but that's a whole other story).

My tip, though, is to go the second and 'more digital' route, and get the off-tape analogue video and audio signals into the digital domain as quickly as possible. This is easily done with

a simple SCART-to-HDMI converter, costing less than a tenner online (often direct from China). Use a phono-to-SCART plug or cable from the tape deck to the £10 converter, and a bog-standard HDMI lead from the converter to the gameplay capture device.

The signal from the analogue tape is inherently unprotected, so the HDMI conversion is also unprotected, and the capture box treats it like a gameplay signal – and sends an unprotected bitstream down the USB cable to the PC and any installed capture control software such as OBS. This works well – I've been doing it during lockdown.

### Pricey boxes...

The one fly in the ointment is the cost of gameplay capture box. The better ones cost well over £100. Beware cheaper ones (around £50 plus) which will not successfully connect by USB to a PC; instead they record direct to a USB memory. Often there will be limitations on how large the memory can be (max 32GB) and how it must be formatted. It's not easy to monitor what is being recorded; and very likely the recording will be broken down into 2GB chunks. It then needs stitching



together. Although this can be done with software, such as the excellent Avidemux, available free from several sources, it's more work to be done. Storing a full file, direct to an HDD, is much more convenient: <https://sourceforge.net/projects/avidemux/>

### ...but watch this space!

Salvation on capture box cost may however be at hand, in the shape of low-cost HDMI-to-USB converter dongle sticks from China. I hear great things about them and have one on order for under a tenner. Watch this space for news of what hopefully arrives before Christmas by sea mail.

In the meantime, be aware. As with the SCART-to-HDMI converters, it looks as if many vendors are packaging the same chipset in slightly different casings, at widely varying prices. You may not get more by paying more.



Fluke/Philips PM3092 Oscilloscope  
2+2 Channel 200MHz Delay TB,  
Autoset etc – £250

## STEWART OF READING

17A King Street, Mortimer, near Reading, RG7 3RS

Telephone: 0118 933 1111 Fax: 0118 933 2375

USED ELECTRONIC TEST EQUIPMENT

Check website [www.stewart-of-reading.co.uk](http://www.stewart-of-reading.co.uk)

(ALL PRICES PLUS CARRIAGE & VAT)

Please check availability before ordering or calling in



HP 54600B Oscilloscope  
Analogue/Digital Dual Trace 100MHz  
Only £75, with accessories £125

LAMBDA GENESYS	PSU GEN100-15 100V 15A Boxed As New	£400	Marconi 2305	Modulation Meter	£250
LAMBDA GENESYS	PSU GEN50-30 50V 30A	£400	Marconi 2440	Counter 20GHz	£295
IFR 2025	Signal Generator 9kHz – 2.51GHz Opt 04/11	£900	Marconi 2945/A/B	Communications Test Set Various Options	P O A
IFR 2948B	Communication Service Monitor Opts 03/25 Avionics	P O A	Marconi 2955	Radio Communications Test Set	£595
IFR 6843	Microwave Systems Analyser 10MHz – 20GHz	P O A	Marconi 2955A	Radio Communications Test Set	£725
R&S APN62	Syn Function Generator 1Hz – 260kHz	£295	Marconi 2955B	Radio Communications Test Set	£800
Agilent 8712ET	RF Network Analyser 300kHz – 1300MHz	P O A	Marconi 6200	Microwave Test Set	£1,500
HP8903A/B	Audio Analyser	£750 – £950	Marconi 6200A	Microwave Test Set 10MHz – 20GHz	£1,950
HP8757D	Scaler Network Analyser	P O A	Marconi 6200B	Microwave Test Set	£2,300
HP3325A	Synthesised Function Generator	£195	Marconi 6960B	Power Meter with 6910 sensor	£295
HP3561A	Dynamic Signal Analyser	£650	Tektronix TDS3052B	Oscilloscope 500MHz 2.5GS/s	£1,250
HP6032A	PSU 0-60V 0-50A 1000W	£750	Tektronix TDS3032	Oscilloscope 300MHz 2.5GS/s	£995
HP6622A	PSU 0-20V 4A Twice or 0-50V 2A Twice	£350	Tektronix TDS3012	Oscilloscope 2 Channel 100MHz 1.25GS/s	£450
HP6624A	PSU 4 Outputs	£400	Tektronix 2430A	Oscilloscope Dual Trace 150MHz 100MS/s	£350
HP6632B	PSU 0-20V 0-5A	£195	Tektronix 2465B	Oscilloscope 4 Channel 400MHz	£600
HP6644A	PSU 0-60V 3.5A	£400	Farnell AP60/50	PSU 0-60V 0-50A 1kW Switch Mode	£300
HP6654A	PSU 0-60V 0-9A	£500	Farnell XA35/2T	PSU 0-35V 0-2A Twice Digital	£75
HP8341A	Synthesised Sweep Generator 10MHz – 20GHz	£2,000	Farnell AP100-90	Power Supply 100V 90A	£900
HP83630A	Synthesised Sweeper 10MHz – 26.5 GHz	P O A	Farnell LF1	Sine/Sq Oscillator 10Hz – 1MHz	£45
HP83624A	Synthesised Sweeper 2 – 20GHz	P O A	Racal 1991	Counter/Timer 160MHz 9 Digit	£150
HP8484A	Power Sensor 0.01-18GHz 3nW-10µW	£75	Racal 2101	Counter 20GHz LED	£295
HP8560E	Spectrum Analyser Synthesised 30Hz – 2.9GHz	£1,750	Racal 9300	True RMS Millivoltmeter 5Hz – 20MHz etc	£45
HP8563A	Spectrum Analyser Synthesised 9kHz – 22GHz	£2,250	Racal 9300B	As 9300	£75
HP8566B	Spectrum Analyser 100Hz – 22GHz	£1,200	Solartron 7150/PLUS	6½ Digit DMM True RMS IEEE	£65/£75
HP8662A	RF Generator 10kHz – 1280MHz	£750	Solartron 1253	Gain Phase Analyser 1mHz – 20kHz	£600
Marconi 2022E	Synthesised AM/FM Signal Generator 10kHz – 1.01GHz	£325	Solartron SI 1255	HF Frequency Response Analyser	P O A
Marconi 2024	Synthesised Signal Generator 9kHz – 2.4GHz	£800	Tasakago TM035-2	PSU 0-35V 0-2A 2 Meters	£30
Marconi 2030	Synthesised Signal Generator 10kHz – 1.35GHz	£750	Thurlby PL320QMD	PSU 0-30V 0-2A Twice	£160 – £200
Marconi 2023A	Signal Generator 9kHz – 1.2GHz	£700	Thurlby TG210	Function Generator 0.002-2MHz TTL etc Kenwood Badged	£65



HP/Agilent HP 34401A Digital  
Multimeter 6½ Digit £325 – £375

HP33120A  
HP53131A  
HP53131A  
Audio Precision  
Datron 4708  
Druck DPI 515  
Datron 1081  
ENI 325LA  
Keithley 228  
Time 9818

Function Generator 100 microHz – 15MHz  
Universal Counter 3GHz Boxed unused  
Universal Counter 225MHz  
SYS2712 Audio Analyser – in original box  
Autocal Multifunction Standard  
Pressure Calibrator/Controller  
Autocal Standards Multimeter  
RF Power Amplifier 250kHz – 150MHz 25W 50dB  
Voltage/Current Source  
DC Current & Voltage Calibrator

£350  
£600  
£350  
P O A  
P O A  
£400  
P O A  
P O A  
P O A  
P O A



Marconi 2955B Radio  
Communications Test Set – £800



# The perils of an enquiring mind...

## Techno Talk

Mark Nelson

...and of streaming channels that stop working and smart TVs that lose functionality when they fail to update as expected. But it's not all bad news and this month we have some good tidings regarding lowish-cost gadgets for hands-on electronics constructors. There's plenty to take in, so let's crack on.

**M**any of our character traits are inherited, and ever since birth I have suffered from an over-enquiring mind (from my mother, for what it's worth). I am told that as a toddler I used to scare the living day-lights out of my parents by playing with the aluminium studs that were used to fasten the cuffs of a newly bought shirt. My father would never discard anything that might come in handy (another attribute that I inherited), so they were left lying around. No, I did not try eating the studs, but I did make the technical discovery that these studs were a perfect fit for the round openings in 5A socket outlets that were common in houses in those days. It's a miracle that I did not electrocute myself!

Electrical matters fascinated me at that tender age – and they still do. I always wanted to know how things worked and why our family said 'eye-ther' but other people pronounced the word 'ee-ther' (please don't tell me it doesn't matter!). For me, everything had to be consistent and logical (I know what you're thinking) and easy to understand. Many people are happy to buy their DIY needs at B&Q, but that's not enough for me. I was unable to rest easily until I discovered that the firm's founders were called Richard Block and David Quayle. Enough of the prelude, let's move on now to some practical electronics.

### ROKA – or is it really RoKa?

Almost every reader of this magazine uses ROKA connectors, but possibly without using that name. More likely you call it a DC connector, barrel connector or tip connector (the last because many low-voltage DC power supplies are provided with a dozen or so 'tips' that fit the output cable). Although these low-voltage power connectors are a German design, they are now used all over the world. In the rest of Europe, they are widely called ROKA or RoKa connectors, a

name that comes from the initials of the Robert Karst electronics company in Berlin, which was responsible for either inventing or popularising them.

And popular they are, with at least two dozen different sizes. As Wikipedia laments, many appear quite similar to each other, yet are not quite mechanically or electrically compatible. In addition to a plethora of generic designs of these connectors, there are at least two different national standards – EIAJ in Japan and DIN in Germany, as well as the JSBP connector used on some laptop computers. That's only to be expected, however, if you recall the old saying that runs, 'We favour standardisation fervently; that's precisely why we support so many of them'!

Needless to say, there's not even any agreement on whether the centre pole of these connectors should be positive or negative, although older devices tend to favour a negative centre pin and newer ones are centre-positive. Another rule of thumb is that consumer goods have a positive centre pin, while professional gadgets, test instruments and accessories for electric guitars opt for centre-negative.

### Let's get practical

OK, what do you do when you are given a Sony Walkman to test and it has a barrel connector slenderer than you have ever seen? Other than forking out £30 for a no-name power supply that claims to be fully compatible (even though the photo suggests otherwise), are you stumped? Not now, because you can just head off to Amazon and search for 'Aceyoon DC Barrel Jack Adapter' (<https://amzn.to/2AhIJhY>). This is a 38-piece set of DC power tips in virtually every pattern known to mankind. Each power connector tip can plug into a standard 5.5 × 2.1mm male connector and adapts a power supply to all of the other 38 sizes. The advertising indicates that it is intended primarily for 'road warriors' (do people still use this 1980s expression?)

but of course it is equally useful in the home or workshop. Priced at £12.98, it's hardly expensive and the quality is impressive.


Another handy and affordable gadget I bought recently was a tool for forming wire links and bending component leads (eBay UK item 232645791410). Yes, you can do this work without a jig but if you are populating a large PCB, it helps to use one of these plastic tools to ensure every R and C fits the holes drilled in the board. The price is £6.95 with free postage, and I am sure that the same tool can be found elsewhere on eBay and other websites.

It reminds me of a similar plastic tool that came free with this magazine as a cover gift back in the 1970s or 1980s. I think I still have mine somewhere, but it was designed for those chunky big components that we used half a century ago!

### IoT = Internet of Trouble?

No, it's not just my opinion, nor do I use any IoT gizmos. But it's clear that there's trouble afoot for many people who have either welcomed the Internet of Things into their homes or else are planning to join the smart-home set in the future. That's the clarion warning coming from Scott Helme, a security researcher, entrepreneur and international speaker specialising in hacking and encryption. The problem concerns a specific kind of security certificate (the 'root certificate') that authenticates websites that you or your network connect to. These can expire, leaving you none the wiser, with negative consequences. Some users have found streaming channels no longer working and payment processors having problems too. If you use smart appliances, I encourage you to read his webpage at: <https://bit.ly/pa-sep20-rca> – but if that leaves you as baffled as I am, you can read much more accessible assessments on other webpages at: <https://bit.ly/pe-sep20-ssl> and <https://bit.ly/pe-sep20-reg>
 
# Need a programmed PIC for your Practical Electronics project?



Now available from the Practical Electronics online shop at:  
[www.electronpublishing.com](http://www.electronpublishing.com)



## Teach-In 8 CD-ROM Exploring the Arduino

This CD-ROM version of the exciting and popular *Teach-In 8* series has been designed for electronics enthusiasts who want to get to grips with the inexpensive, immensely popular Arduino microcontroller, as well as coding enthusiasts who want to explore hardware and interfacing. *Teach-In 8* provides a one-stop source of ideas and practical information.

The Arduino offers a remarkably effective platform for developing a huge variety of projects; from operating a set of Christmas tree lights to remotely controlling a robotic vehicle wirelessly or via the Internet. *Teach-In 8* is based around a series of practical projects with plenty of information for customisation. The projects can be combined together in many different ways in order to build more complex systems that can be used to solve a wide variety of home automation and environmental monitoring problems. The series includes topics such as RF technology, wireless networking and remote web access.

### PLUS: PICs and the PICkit 3 – A beginners guide

The CD-ROM also includes a bonus – an extra 12-part series based around the popular PIC microcontroller, explaining how to build PIC-based systems.

### SOFTWARE

The CD-ROM contains the software for both the *Teach-In 8* and PICkit 3 series.



**PRICE**  
**£8.99**

Includes P&P to UK if  
ordered direct from us

**ORDER YOUR COPY TODAY!**  
**JUST CALL 01202 880299 OR VISIT [www.epemag.com](http://www.epemag.com)**



# Net Work

Alan Winstanley

Lights, camera, action! This month, *Net Work* returns to the complex world of IP security cameras.

**B**ack in *Net Work* from the December 2015 issue, I explored the emerging market of IP security cameras that were designed for home network users. After suffering mixed results with several cheap unbranded ones, I chose a UCam 1080p bullet camera. It was a sturdy mid-priced product that offered IP67 protection, infrared, one-way audio, Wi-Fi and Ethernet, along with an SD memory slot. Snapshots and short video clips could be saved to a NAS drive (there was no cloud storage at that time) and the UCam app allowed video to be viewed remotely on a mobile phone, via a wireless hotspot.

## Camera set-up

Using the UCam became quite a learning curve, so this month's *Net Work* outlines a few IP camera practicalities that I stumbled on over the years.

This type of camera needs initialising using an Ethernet cable. Once the Wi-Fi SSID and IP address are configured in the camera, then in theory Ethernet is no longer needed and the camera should operate wirelessly. Despite this, it isn't necessarily a great idea to mount it high up in an inaccessible location (see later). Also, when locating a camera, consider how the sun travels through the day and site the camera to avoid direct sunshine; at night, a camera's IR illuminator will cause dazzle if it's, for example, indoors on a window ledge, because the IR light reflects back off the glass and washes out the video. It's sometimes better to disable IR and rely on ambient street lighting or consider a separate (possibly external) IR illuminator lamp (eBay).

I found that many cameras of this type sprout a clunky power and Ethernet block, with maybe a paltry 12-inch long lead. The connector block might need a 1-inch hole or so to pass through a house wall, possibly needing an SDS drill followed by some sealant or cement. Otherwise, pencil in a weather-proof junction box to house the camera connectors, before routing the wiring indoors. I also plugged the camera's Ethernet port with an RJ45 rubber dust cap (eBay) once setting up was completed.

And of course, the camera requires a DC supply, for which DC extension leads are commonly bought: mains outlets are seldom located where they're needed!

## Network camera practicalities

Looking at some software setup snags, this camera's settings are accessed by logging in with a desktop web browser, which highlighted the next problem: 'Live View' stopped working because popular web browsers stopped supporting the legacy Flash-based viewer, so separate desktop software (supplied) is used instead. This camera's settings menu also configures motion detection zones, but I found that birds or trees blowing in the wind triggered false alarms. The software might offer scheduling and alerts by email or uploading snapshots to a web server, along with the usual arcane network and storage settings. It proved best to give both the camera and the NAS their own static IP addresses. That way, if the router was powered down or reset, the IP camera and NAS would still handshake properly once the network was restored.

My camera has built-in optional storage, although you can still record images to a NAS. One problem is the risk of data loss if the camera is stolen! Many modern camera systems now promise cloud-based storage, but free services might only have a short file retention period. Typically, subscription-based cloud storage is offered (assuming you're satisfied with third-party security) but watch for charges levied for additional cameras.

One risk is that makers will not future-proof apps or software, and products may become crippled at short notice. On 30 June, Belkin pulled the plug on its WeMo NetCam range as its cloud-based video platform was shutting down, leaving 'many users of the WeMo NetCam with a product they can no longer use,' as Belkin helpfully recognised. Also, last November, the US chain Best Buy dropped support for their own-brand Insignia smart device range, leaving owners of their 'smart' appliances (including smart cameras) stranded. This kind of product uncertainty does not endear users to the smart-device sector.

Apart from using Wi-Fi to hook up an IP camera, an Ethernet lead can be used on some (but not all) home cameras. Where Wi-Fi coverage is dodgy, if a mains outlet is available then Homeplug powerline communications (PLC) adaptors such as the Devolo range can conveniently create Wi-Fi access points and/or provide an Ethernet port, by using the ring mains to carry Internet traffic. Devolo has been covered extensively in *Net Work* in the past and there are plenty of used Devolo devices on eBay. A cheap way of implementing PLC networking at home would be to try some second-hand Devolo DLAN 500 units – remember you need to connect one mains 'transmitter' directly to your router, and plug in separate Wi-Fi Add-On Adaptors around the home or outbuildings (up to 300m away). Note the new generation Devolo 'Magic' mesh range (offering up to 2.4 Mbps) is not compatible with these earlier DLAN devices.

In fact, the author installed some extra DLAN 500 repeaters recently for some trials, but after a while it was found that the IP camera had stopped responding for some reason. Checks showed that the NAS had also stopped recording a few weeks earlier! Eventually, it looked like a total camera reset might be needed: that's one good reason not to site such an IP camera too far out of reach – setting it up again would mean hooking it to an Ethernet lead and initialising it all over again. Then the penny dropped: after adding those Devolo DLAN Wi-Fi units, I'd also renamed the Wi-Fi SSIDs,



HeimVision's range is typical of current battery-operated home security cameras.

thereby accidentally cutting off the IP camera's Wi-Fi access in the process! I reset the camera after rigging up a temporary Devolo Ethernet port a few yards away, and the camera burst into life on Wi-Fi once again.

### Network camera innovations

Today, there is more choice than ever and some of the latest user-friendly smart cameras address some of these drawbacks to make installation and operation far simpler. Amazon's Blink XT2 starts at £99 and is typical of the latest wave: it's a compact weatherproof 1080p Wi-Fi camera with two-way audio. Lithium batteries promise up to two-years life (but very much less – reportedly as little as a month – if you use video and audio monitoring extensively, and swapping batteries is fiddly). For indoor use, a micro USB power port allows mains operation (adapter not included). Blink is intended for smaller areas and is Wi-Fi only. It uses a proprietary mains-powered 'sync module' (hub) to broadcast video. Some users complain about time lag, but what it lacks in performance it makes up for in ease of setting up. It's possible to go further and view on an Echo Show LCD or link multiple cameras with the Alexa app as well as using voice control. Furthermore, an Amazon Fire Stick would enable viewing on a TV (as seen on <https://youtu.be/gty7XfUsBf0>). Free limited online storage is included.

Google's Nest Wi-Fi cameras require DC power and are surface-mounted using simple magnetic 'universal joint' hardware (see <https://youtu.be/wG3F8xzhPlo>) so they are not exactly pilfer-proof. It has a speaker and microphone, and three hours of cloud storage is provided free; or choose 'Nest Aware', which costs from £5 a month covering all your Nest cameras. A single Nest Outdoor camera is £179.

### Cameras get a solar boost

A plethora of similar-looking IP cameras is now available, often badged with unrecognised brands so, before investing, it's really useful to see what other users say in product reviews. No consumer IP camera is perfect and whether a product performs well in practice and is well supported can be down to pot-luck. Several branded security cameras stood out, including Reolink's Argus Pro outdoor camera with audio, SD storage, and a self-contained battery topped up by a solar panel. HeimVision's HMD2 also seems well regarded and a solar recharger is available separately. The eufyCam 2C 1080p IP67 wireless camera promises 180-day battery life, anti-theft alarms and Amazon



Simplisafe promises whole-home monitored protection, including a security guard call-out if needed.

Alexa compatibility. Video is encrypted and stored internally on a memory card and technical support seemed to be highly rated.

The US home security firm SimpliSafe has now entered the UK and offers whole-home protection with wireless sensors, glass-break alarms, smoke detectors, flood alarms, panic buttons and smart cameras. Uniquely in this market, SimpliSafe also has a professional monitoring option that can, following confirmation of an incident via cameras, send the police and a security guard to your residential property at a low cost. More details are spelt out on their website at: <https://simplisafe.co.uk>

Doorbell wireless video cameras are also catching on, especially because some 40% of US households have been victims of doorstep package theft or 'porch piracy', according to **Security.org** (YouTube is full of 'porch pirate' entrapment videos featuring booby-trapped parcels). Wireless doorbell cameras include the Google Nest Hello and Amazon's Ring, but there are many others.

### Huawei we go again

After more political wrangling, Britain seems to be on the verge of cutting Huawei adrift. The UK had thus far chosen to 'mitigate' Huawei's involvement in the country's telecoms network through the Huawei Cyber Security Evaluation Centre (HCSEC) Oversight Board. This task force revealed some sloppy coding and security practices and broken assurances that the UK's National Cyber Security Centre (NCSC) still felt were manageable, nonetheless. Further US sanctions on American chip design software and fabricators means that, ongoing, alternative chips might have to be sourced, making it harder to warrant the security of the 5G telecoms

network. At the time of writing, the NCSC was revisiting Britain's relation with Huawei. Meantime, Huawei's plans to build a £400 million opto-electronics research site in Cambridgeshire has received initial approval by the local authority, despite American opposition: Britain's local planning authorities never get involved with politics.

SpaceX continues to lob Starlink satellites into LEO (low-earth orbit), with ten launches totalling nearly 600 satellites so far. The US FCC had questioned whether the network's latency would in fact be low enough (100ms or less, according to them) for it to qualify for the US Government's \$20 billion 'Rural Digital Opportunity' programme intended to bring Internet access to rural districts. The FCC has since softened its approach to allow SpaceX to bid for traffic.

### Boldly going...

SpaceX also launched a second GPS III satellite into orbit for the 'US Space Force', making three satellites in total. These latest-generation GPS satellites have higher accuracy and anti-jamming technology – see: [www.spaceforce.mil](http://www.spaceforce.mil)

Britain has been sidelined by the EU in its Galileo satnav programme, despite being an investor in the past. Earlier this year, in pre-Covid-19 times, the UK trumpeted a hard-to-believe £5bn programme to build its own satnav network, but these ambitions have since been downsized. Instead, the UK has bought a £400 million stake in the bankrupt OneWeb satellite network which may be a fast-track alternative to building a GPS system from scratch – if the technology allows. India's Bharti Global has matched the bid for this LEO Internet service, though reports mentioned nothing about offering GPS.





Anycubic's UV Photon Zero is a low-cost introduction to 3D UV resin printing.

China has polished off its own GPS system with the 35th launch of a Beidou Navigation Satellite at the end of June, in a programme intended to make China self-sufficient (the EU said the same about its own dependence on US GPS, which prompted the EU Galileo programme).

### In other news

Amazon has launched the Echo Auto, an in-car adaptor allowing drivers to access Alexa services while on the road. Powered by a cigar lighter socket or USB port, Echo Auto connects to the car audio via Bluetooth or a 3.5mm lead, and uses the Alexa app on your mobile phone. It has eight microphones and has been optimised to work well over road noise, Amazon says. It's available for £49.99 from Amazon and major retailers.

After killing off its five-year old Dash stick-on hardware buttons that enabled seamless re-ordering of goods, Amazon has ditched their barcode-scanning Dash Wand, a quirky product-ordering gadget that never really caught on. Virtual Dash buttons live on in the Amazon app.

The world's most powerful offshore wind turbine, the 12MW GE Haliade-X (see *Net Work*, January 2020) has been granted a type approval certificate by the global certification body DNV-GL based in Norway. It's a milestone that allows GE to bring the wind turbine from prototype to serial production, says GE.

UV-curing resin printers seem to be catching on, with small 3D printers available for as little as £200. The Anycubic Photon Zero UV Photocuring 3D Printer, for example, is available from

Amazon and prints objects up to 95 × 54 × 150mm. Single-colour UV resin typically costs £41 per litre.

Readers are reminded to be vigilant when receiving SMS PIN numbers for 2FA authentication (described in previous months). It was recently reported that one scammer, described as 'being from a bank's fraud prevention unit and very convincing', knew his victim's account and cellphone number and called to glean from him a 2FA PIN number, after the bank alerted the victim of an attempted hack. Revealing the PIN that way would have enabled the crook to finish off the fraudulent transaction.

PayPal has introduced Honey, a discount voucher 'bot that automatically applies the best promo codes on Internet checkouts. You can install the Honey extension for your browser and it has already saved the author a few valuable pounds shopping on a well-known coffee pod website. Sign up free at: [www.joinhoney.com](http://www.joinhoney.com)

That's all this month – see you in the next issue for more *Net Work*!

The author can be reached at:  
[alan@epemag.net](mailto:alan@epemag.net)

GET THE  
LATEST COPY  
OF OUR  
TEACH-IN SERIES  
AVAILABLE  
NOW!

## Order direct from Electron Publishing

**PRICE £8.99**

(includes P&P to UK if ordered direct from us)



### Teach-In 9 – Get Testing!

This series of articles provides a broad-based introduction to choosing and using a wide range of test gear, how to get the best out of each item and the pitfalls to avoid. It provides hints and tips on using, and – just as importantly – interpreting the results that you get. The series deals with familiar test gear as well as equipment designed for more specialised applications.

The articles have been designed to have the broadest possible appeal and are applicable to all branches of electronics. The series crosses the boundaries of analogue and digital electronics with applications that span the full range of electronics – from a single-stage transistor amplifier to the most sophisticated microcontroller system. There really is something for everyone!

Each part includes a simple but useful practical test gear project that will build into a handy gadget that will either extend the features, ranges and usability of an existing item of test equipment or that will serve as a stand-alone instrument. We've kept the cost of these projects as low as possible, and most of them can be built for less than £10 (including components, enclosure and circuit board).

### FREE COVER-MOUNTED CD-ROM

On the free cover-mounted CD-ROM you will find the software for the *PIC n' Mix* series of articles. Plus the full *Teach-In 2* book – *Using PIC Microcontrollers – A practical introduction* – in PDF format. Also included are Microchip's *MPLAB ICD 4 In-Circuit Debugger User's Guide*; *MPLAB PICKit 4 In-Circuit Debugger Quick Start Guide*; and *MPLAB PICKit4 Debugger User's Guide*.

**ORDER YOUR COPY TODAY JUST CALL  
01202 880299 OR VISIT [www.electronpublishing.com](http://www.electronpublishing.com)**

# Win a Microchip Explorer 16/32 Development Kit

**Practical Electronics** is offering its readers the chance to win a Microchip Explorer 16/32 Development Kit (DM240001-3) – and even if you don't win, receive a 20%-off voucher, plus free shipping for one of these products.

The Explorer 16/32 Development Kit is a flexible, convenient and ready-to-start development, demonstration and testing platform for 16-bit PIC24 MCUs, dsPIC DSCs and 32-bit PIC32 MCUs. It features all the necessary hardware to begin developing and debugging a complete embedded application.

The kit comes with an integrated programmer/debugger and several new features that address the latest embedded systems design needs, as well as providing adaptable and easy-to-start

tools while being backwards compatible to the classic Explorer 16 board.


In addition to the hardware features provided by the board, hardware expansion is possible through the use of PICtail Plus daughter cards and mikroBUS accessory boards. Coupled with the integrated PICkit-On-Board (PKOB), MPLAB ICD 3 In-Circuit Debugger or MPLAB REAL ICE real-time emulation and debug facilities, it enables faster evaluation and prototyping of applications. Included with the Explorer 16/32

Development Kit are:

- Explorer 16/32 development board
- 16-bit high memory, super-set device – PIC24FJ1024GB610 Plug-In-Module (PIM) (MA240023)
- Two USB cables (USB A to Type-C and micro-B cables).

**Worth  
\$110.00  
(approx £87.50)  
each**

## Free-to-enter competition

 

**Microchip**  
Explorer 16/32 Development Kit

### How to enter

For your chance to win a Microchip Explorer 16/32 Development Kit or receive a 20% off voucher, including free shipping, enter your details in the online entry form at:

<https://page.microchip.com/PE-Explorer-Kit.html>

### Closing date

The closing date for this offer is 31 August 2020.

### May 2020 winner

Kemuel Nesbitt

He won a Microchip  
MPLAB ICD 4  
In-Circuit Debugger





# ULTRABRITE LED

# PUSHBIKE LIGHT



This tiny (22 × 12mm) circuit board is a high-efficiency LED driver that delivers a constant 1A or 2.2A. You can use it with a 12V white LED array to make a (very!) bright bicycle light, a torch or another light source. It can be powered from a lithium-ion or LiPo battery pack but there are other options. It also has brightness control and a flashing function. It's a very compact and modern design, for advanced constructors.

**Design by Daniel Doyle – words by Nicholas Vinen**

**T**here are plenty of bicycle lights and LED torches on the market, but there are certain advantages to building your own. You get to choose the battery, so you could use a high-capacity rechargeable lithium-ion or LiPo battery that would last for many hours of use. These are not terribly expensive, and can last for many years if treated well.

You also get to choose the LED(s), so you can use a really efficient one for maximum battery life and brightness.

And you can also tailor the optics to suit your needs. You can build it with a tight, bright beam or a wider beam to improve your visibility to objects not directly in front of you.

You don't necessarily have to use this driver board for a bike light or torch. It could be used for caravan lighting, to light the bed of a utility vehicle or the cargo area of a van, in a shed, or wherever you need a bright light but don't have ready access to mains power. The driver board is tiny, so it can be tucked away just about anywhere. Add an LED and a battery, and away you go.

It has a flashing mode and two reduced brightness options that you can use for longer battery life. You can also build a higher-power version of the circuit to suit more powerful LEDs.

It's a generally useful device. It's also a good way to learn about switchmode power supplies and LED driving.

And while it's designed to drive LEDs, it isn't necessarily limited to only doing that. With a few small changes, this board can be used as a constant current source for a variety of applications.

## Operating principle

This LED driver is a 'buck' step-down DC/DC converter with current regulation. It efficiently reduces the 15-21V battery supply voltage down to around 12V, as required by the LED array. The LED voltage is not regulated directly; rather, the circuit attempts to maintain 1A through the LED array, at whatever voltage is required, from virtually nothing up to the full input voltage.


Fig.1 shows the basic configuration of a buck regulator. Switch S1 is electronically toggled on and off rapidly to control the current through inductor L1. When S1 is on, the current flowing through L1 increases at a rate determined by its inductance and the voltage across it.

Some of this current may flow through the load while the rest charges up capacitor C1. L1's magnetic field also charges up as the current flows.

When S1 switches off, the magnetic field starts to collapse and this forces current to continue to flow into the load and C1, although at a reducing rate.

Since current can no longer flow through S1, it must instead come from the circuit ground and through diode D1, effectively flowing in a loop through D1, L1 and C1/the load, and then back to ground.

It is the energy stored in the magnetic field which makes this an efficient circuit, as the voltage drop across L1 is not dissipated as heat; most of that energy is stored while S1 is switched on, and recovered when it switches off.

 

**Fig.1:** the general configuration of a step-down switching DC/DC converter, also known as a 'buck' converter. When S1 is on, current flows through it and inductor L1 to the load, charging up both capacitor C1 and L1's magnetic field. When S1 switches off, the magnetic field starts to collapse, which forces current to continue to flow. This must come from ground, via D1, which along with the charge in C1, causes the load voltage to drop slowly until S1 switches on again.

By controlling the duty cycle of S1, we can control the current through L1 and thus the average voltage across C1.

### Circuit description

Fig.2 shows the LED driver circuit, including the internal details of the LM3409MY controller. In this case, the switch shown in Fig.1 is actually a MOSFET (Q1).

You should be able to see all the other components from Fig.1 in this circuit, with the addition of a  $0.22\Omega$  current-sense resistor between the supply bypass capacitors and the source of Q1.

Q1 is a P-channel MOSFET, which means that the controller IC can switch it on hard by pulling its gate down to 0V without needing a boosted gate-supply rail. That means if the battery is almost fully discharged, the highest possible LED brightness can still be maintained, as there will be a minimal voltage drop in the circuit (around 0.25V, mostly due to the current-sense resistor).

IC1 is powered from pin 10 ( $V_{IN}$ ) and it has an internal regulator ( $V_{CCREG.}$ ) producing a voltage at pin 9, labelled  $V_{CC}$ . This is a 'negative' regulator which produces a voltage rail that is relative to  $V_{IN}$ , but about 6V lower. The external  $1\mu F$  capacitor filters this rail.

Internally,  $V_{CC}$  is fed to the MOSFET gate driver, and this provides the voltage that the MOSFET gate is pulled down to (via pin 6) to switch it on. This gives the MOSFET a gate-source voltage of  $-6V$ , more than enough for Q1 to be fully in conduction. To switch it off, pin 6 is pulled up to  $V_{IN}$ , so the gate-source voltage is reduced to 0V.

The benefit of this scheme is that it allows  $V_{IN}$  to be higher than it otherwise could be. A typical MOSFET has a maximum gate-source voltage rating of  $\pm 20V$ . If the MOSFET gate were pulled to 0V to switch it on, that would mean that  $V_{IN}$  could not exceed 20V. Our recommended 5-cell Lithium-ion battery has a fully charged voltage of 21V, and the circuit can operate to at least 30V thanks to this internal regulator.

When S1 is on, the current flowing through it and inductor L1 is sensed via the voltage developed across the  $0.22\Omega$  resistor. Both ends of this resistor are connected to a differential amplifier within IC1. The regulated current is determined by the value of the current-sense resistor, and the value connected from the  $I_{ADJ}$  pin (pin 2) to ground, if any.

In this application, no such resistor is fitted. If a resistor is fitted there, it changes the 1.24V reference voltage which controls the voltage divider formed by the internal resistors labelled 'R' (at pin 8) and '5R'.



This photo of a 'naked' bike light really doesn't do the LED justice! It is so bright that you risk temporary vision impairment from looking into it – trust us, that is from experience, so DO NOT do it! You can also see just how small the controller board is from this pic. The LM3904 on this board may get quite warm at higher currents, especially if it's in close proximity to the LED and/or if in a small housing. In this case, a small heatsink is suggested. The battery is a 5-cell, 18.5V, 5000mAh high discharge Li-Po by Turnigy.

## Features and specifications

- Can power a 12V LED array from a 5S (18.5V) lithium-ion/LiPo battery
- Operates from 5-25V (minimum LED operating voltage + 2V)
- Delivers 1A (12W for 12V LED) or 2.2A (26W for 12V LED)
- Can be used with a wide variety of high-brightness LEDs, including 6V and 12V (nominal) types
- Three brightness settings plus flashing mode with pushbutton on/off and mode control
- Low quiescent current when off (around 1mA)
- Under-voltage lockout
- Overheating protection
- High efficiency; typically more than 90%.

With no external resistor, 1.24V appears across the '5R' resistor, meaning that  $0.248V$  ( $1.24V \div 5$ ) appears across the upper 'R' resistor. Therefore, a similar voltage must be developed across the external sense resistor for the current amplifier's output to change polarity. This sets the peak current to 1.13A ( $0.248V \div 0.22\Omega$ ), resulting in an average LED current close to 1A.

IC1 uses a 'controlled off-time' scheme for regulation. With standard PWM, the pulses applied to the gate of Q1 would be at a fixed frequency but with a varying duty cycle. With the controlled off-time scheme, Q1 is switched off for the same time after each pulse; the on-time varies to control the duty cycle. This results in a variable switching frequency.

The advantage of this scheme is that it's easier to stabilise the feedback loop to prevent sub-harmonic oscillation. This avoids the need for external loop-compensation components. The combination of the  $15.8k\Omega$  resistor from the output to pin 4, and the  $560pF$  capacitor from pin 4 to ground, sets the fixed off-time to be very close to  $1\mu s$ . So with a 50% duty cycle, the switching frequency will be around 500kHz.

Diode D1 is a 1.5A schottky diode with an especially low forward voltage of 0.43V at 1.5A, for maximal efficiency.

The resistive divider at pin 1 (UVLO) sets the input supply under-voltage lockout threshold to 5V ( $=1.24V \times [1 + (49.9k\Omega \div 16.5k\Omega)]$ ). The internal switched  $22\mu A$  current source adds 363mV ( $16.5k\Omega \times 22\mu A$ ) of hysteresis, so that the switch-off threshold is 5.363V.

This was chosen to shut down the circuit before the external control circuitry no longer has enough voltage to run, and to allow lower-voltage batteries and LEDs to be used. It is expected that your battery will have built-in over-discharge protection and so will cease supplying current before it is damaged.

If not, you would have to change these divider values to protect your battery. For example, a 5S Li-ion or LiPo battery should not normally be discharged below 3V per cell or 15V total. So you could change the  $49.9k\Omega$  resistor to  $183k\Omega$  ( $16.5k\Omega \times [(15V \div 1.24V) - 1]$ ) ( $180k\Omega$  would do) and the LED drive will automatically shut off when your battery drops below 15V.






 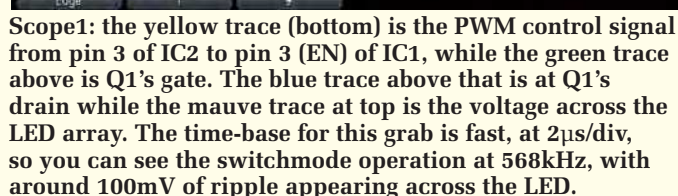
## Control circuitry

The onboard temperature sensor (TS1) has a digital output at pin 5 (T<sub>OVER</sub>) which feeds digital input GP2 (pin 4) on IC2. This pin is driven high if the board gets too hot (over 95°C) and IC2 responds by slowly reducing the LED brightness.

The various modes are selected using external momentary pushbutton S1, which connects between GND and the GP0 digital input (pin 1) of IC2. IC2 has an internal pull-up current to keep this pin high when the button is not pressed. It detects when the button is pressed as that pin is then pulled low.



IC2 and TS1 are powered from a 5V rail developed by low-power regulator REG1. This regulator can withstand input voltages up to 30V (it is the limiting factor in this design), can deliver up to 100mA and has a quiescent current of around 1.9mA. As it is not a micropower regulator, an external power switch is recommended to avoid discharging the battery when the light is not in use.

### Scope grabs

Scope1-Scope4 below show the voltages at four points in the circuit during different phases of operation. See the captions for an explanation of what each trace represents.

**Scope1** Close-up of the switching waveforms, demonstrating how the LED current is regulated. Note how the gate pulses in green all have the same positive width (off-time) while the on-time varies. This is due to switchmode controller IC1 varying the on-time in an attempt to keep the current through the LED at the target level.

**Scope2** Shows how the 200Hz PWM brightness control from IC2 causes the LED driver output to switch on and off rapidly, reducing both the light output and power consumption.

**Scope3** The same effect but on a lower brightness setting, with a duty cycle of around 40%.

**Scope4** Operation of the unit in flashing mode (4Hz), at a much longer time scale, corresponding to a whole second of operation.

### Increasing its current delivery

While the ~1A current delivery of this design can give you a really bright light (around 2100 lumens), it is capable of delivering more than twice that with a few minor changes, for a theoretical output of around 5000 lumens, with the right LED(s)!

Replacing the 0.22 0.75W resistor with a same-size 0.1Ω 2/3W resistor will set the average current to around 2.2A. You also need to make the following two substitutions.

Replace D1 with a 3A schottky diode in the same size package, eg, Comchip CDBA340L-G, Diodes Inc B340LA-13-F, On Semi NRVBA340T3G or Micro Commercial SL34A. Replace inductor L1 with Panasonic ETQ-P5M470YFM, with a current rating of 2.9A and a saturation current of 4.1A, in a package about the same size as the specified DR74-330-R inductor.

Two other possible inductor options which are slightly larger are the Murata DD1217AS-H-330M=P3 and Bourns

SRN8040TA-330M, both 8 × 8mm. They will be a tight fit on the existing footprint, but it should be possible to solder them to the board without modifications. Both have slightly lower current ratings than the Panasonic part though; adequate, but barely so.

### Construction

Fig.3 shows both sides of the assembled board at actual size; it's tiny! The double-sided board is coded 16109191 and measures just 22 × 12mm.

We built our prototype by hand with a regular soldering iron (using a standard chisel tip), so it isn't that difficult, but it definitely requires some skill and patience. IC1 has closely spaced leads (0.5mm apart) while the other parts are not quite so tricky, but are still quite small, so you may need to work under magnification.

The board was designed to be so small to leave as much room as possible to fit the battery in your light housing.

Fig.4(a) shows where the parts go on the top of the board, and it's best to start assembly with this side, specifically, by soldering IC1 in place. As well as having closely spaced leads, this part has a thermal pad on the underside. Ideally, it should be reflow soldered, eg, using a hot-air rework station.


If you have such a station, spread a thin smear of solder paste on all the pads, place the IC in the correct position (ensuring its pin 1 goes towards the nearest corner of the board), then gently heat it with hot air until all the solder reflows. Don't let the hot air dwell too long on one area or you risk burning the PCB or damaging the chip.

The solder under the IC, on the large central pad, is likely to be the last to reflow. But you need to make sure it does, or else you could have hidden short circuits under the chip.


If you don't have a reflow oven or hot air rework station, the PCB pad has been extended slightly past the body of IC1, so that you can still heat the pad directly to solder that thermal pad. You will need a fine-tipped soldering iron to do it this way, though

To hand-solder this chip, add a small amount of solder paste to the middle of the big pad in the middle of its footprint. If you don't have solder paste, spread a thin smear of flux paste over the whole central pad instead. Then locate the pin 1 dot or divot on the IC (using a magnifier) and then rotate it so that it's near the closest corner of the board.

Rotate the whole lot so the that the chip leads are on the left and right sides, then add a tiny bit of solder onto one of the chip's pads (eg, at the upper-right corner if you're right-handed). Heat this solder and gently slide the chip into place.

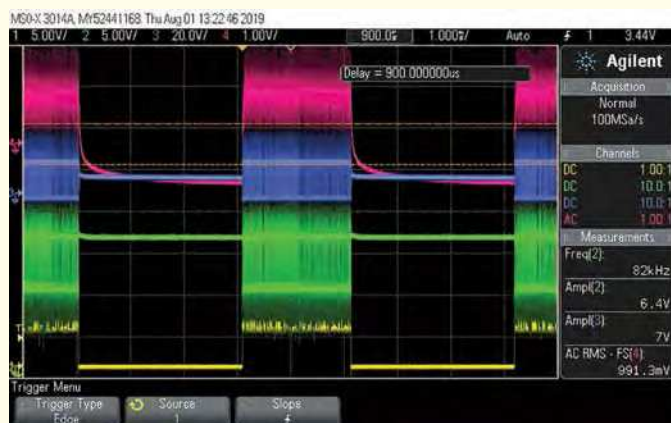

 **Scope3:** this scope grab was taken under the same conditions as Scope2, but now the driver is in low brightness mode, with the PWM duty cycle reduced to around 40%.



**Scope4:** we've now switched the driver into flashing mode and slowed the timebase down again, to 100ms/div, so that you can see the full effect. The flashing frequency is around 4Hz, and the duty cycle is 50%. Other flashing modes involve switching between lower LED brightness (PWM-controlled) and full brightness.



Having removed the heat, check to see whether its pins are properly aligned with the pads on both sides. If not, heat that solder joint and very carefully nudge the IC slightly in the right direction.

We got ours very close on our first attempt (probably close enough) but decided to nudge it a few more times to get the alignment perfect. When you're happy, add flux paste to both sides, then add solder to the diagonally opposite pin before drag-soldering the rest of the pins on that side of the chip.

Return to the other side and solder all the remaining pins, including the one you started with. Bridges are hard to avoid; if you get some, add more flux paste, then use solder wick to suck the excess solder off the pins. When you're finished, check them carefully under magnification. You should have nice looking fillets on all pins, down to the pads on the PCB.

Now add a little extra flux paste to the exposed part of the central pad and feed some solder onto it. Hold the heat on there for a few seconds. If you have solder paste under the chip, it should reflow now. Otherwise, the flux paste under the chip should help suck some solder underneath it (fingers crossed).

If you have a hot air rework station, you can still solder the chip by hand, then re-heat it to reflow solder paste underneath the IC. That's what we did, but again, be very careful to ensure that all the solder paste does melt or you will have trouble later. Also, try not to let the airstream blow the chip off its pads! It helps to keep the airflow rate low.


## Remaining SMDs

With the tricky part out of the way, solder IC2 next. Ideally, it should be pre-programmed (using 1610919A.HEX code available for download from the September 2020 page of the *PE* website). Find its small pin 1 dot and rotate it so that it is facing towards Q1's mounting position. Then use a similar technique as for IC1 to solder it in place. It should be somewhat easier due to having fewer, larger, more widely spaced pins.

Next, fit TS1 and REG1, both of which can only go in one orientation due to the differing number of pins on each side.

Follow with Q1, which has even more widely spaced pins, which can possibly be soldered individually. Ensure its pin 1 dot/divot and chamfered edge go towards the bottom of the board as shown in Fig.3(a).

 The PCB is designed to accept a MOSFET in the SOT-669 package, which has a single large tab in place of pins 5-8, so there is one large pad for these pins. There is no need to



worry therefore if you bridge them; in fact, we suggest you add enough solder on that side of the device to form one, large solder joint, as we did on our prototype.

There's also no need to worry about bridges between pins 1-3 because these all connect to the same point, but you don't want to bridge pins 3 and 4, as pin 4 is the gate. You can use flux paste and solder wick to clean up a bridge between these pins, should it occur.


You can now fit diode D1, with its cathode stripe oriented as shown, followed by the three resistors and three capacitors. Make sure you use the correct values for the two smaller resistors.

## Components on the other side


Now flip the board over. There are just five components to mount on this side of the board, as shown in Fig.3(b). Unfortunately, the board will not sit flat at this stage, so you should find some small plastic shims to place strategically under it so that it won't wobble around as you are soldering these final components.

Start with the two smaller components, making sure that you fit the capacitor in the position closer to the board edge. You can then solder the two larger capacitors in place. It helps to have fine tweezers when doing this, as they are quite close together. As usual, make sure the striped ends are oriented correctly.

 That just leaves the inductor. Spread some flux paste on its pads, then use the usual technique to tack it into place before soldering the opposite lead. Put some heat



 The two sides of the completed PCB are shown here rather significantly oversize, (about twice life size) just so you can see what goes where. The 560pF capacitor, 15.9kΩ resistor, 33µH inductor and the two tantalum capacitors mount on the underside (right) – note the stripes denoting the positive end of the capacitors.



and solder into the joints to make sure the fillets look good on both sides.

### Preparing the LED

You may be able to buy a suitable LED pre-assembled and ready to wire up, but the recommended Cree XHP70 LED generally comes as a bare ‘chip on board’ type LED, which needs to be soldered to a suitable PCB both for electrical connections and to get heat out of it. This is then generally attached to a piece of metal which acts as a heatsink to keep the LED temperature under control.

It’s a good idea to then mount the PCB on the back of this heatsink (with a suitable layer of electrical insulation in between!) so that the PCB can sense the heatsink temperature and reduce the LED brightness if it’s getting too hot.

But we’re getting ahead of ourselves. First, you need to solder the LED to this PCB, which is often in a ‘star’ shape. Note that the XHP70 can be run at 6V or 12V, depending on the configuration of the PCB, so make sure you get a suitable PCB that’s designed to run it at 12V. Otherwise, the LED will require twice as much current for the same brightness.

You can sometimes get the LEDs pre-soldered to the star boards, but we couldn’t find one locally, so we ordered the LED and board separately (from [www.cutter.com.au](http://www.cutter.com.au), but there are plenty of other local/international suppliers).

We then attached the LED to the board. First, we checked the T-shaped marking on the underneath to identify the anodes and cathodes; the bar across the ‘top’ of the T indicates the cathode. This goes towards the side of the star PCB with the negative (–) pads on it.

We then covered all the LED pads (two small rectangles plug a larger Z-shaped pad) with a thin smear of solder paste mixed with some flux paste, placed the LED on top and gently applied heat from a hot air rework station from underneath the board. We did it this way to avoid overheating and damaging the LED lens. Make sure the small pads on the underside of the LED line up with the two small rectangles on the star board.

We managed to heat the star PCB from underneath by clamping it with a hemostat (self-closing tweezers) and then clamping that in a vice, giving us access to the underside of the board without having to hold it. You definitely don’t want to hold an aluminium PCB while heating it to over 200°C! We had to gently nudge the LED using a metal object when the solder reflowed to get it properly centred on its pads. In theory, it should pull itself in due to solder surface tension, but ours got ‘hung up’ on something and needed some help.

### Wiring and testing

The next step is to solder wires to the board for the control pushbutton (S1), battery power and the LED(s). As the board is so small, the wire holes are too, so you aren’t going to be able to solder heavy leads to it. You’ll be keeping the wires fairly short anyway, so medium-duty hookup wire is adequate.

You will probably need to cut away some of the wire strands at the exposed end, so that you can twist the remaining strands together to fit through the holes in the PCB before soldering them. The current will quickly spread out through the other strands in the wire, so this should not cause any problems. But make sure you don’t leave any loose strands that can short to anything else.

Now solder the two LED wires from the board to the ‘+’ and ‘–’ terminals on the LED star, then use screws and thermal paste to attach it to a heatsink. Solder the momentary pushbutton to the end of its wires; its polarity doesn’t matter.

Before powering it up, carefully inspect both sides of the board, looking for short circuits between any of the wire

## Parts list – Ultrabrite LED Driver

- 1 double-sided PCB, code 16109191, 22 × 12mm
- 1 5S Li-ion/LiPo battery or similar, 1Ah+
- 1 5S-capable Li-ion/LiPo battery charger
- 1 2-pin connector to suit battery
- 1 chassis-mount waterproof momentary pushbutton switch (S1) [eg, Altronics S0960/S0961 or Jaycar SP0756]
- 1 12V LED array, eg, Cree XHP70.2 P4 bin (2100 lumens at 1A, 4760 lumens at 2.2A)
- 1 heatsink to suit LED
- 1 lens to suit LED (optional)
- 1 DR74-330-R 33μH 1.4A SMD inductor, 7.2 × 7.2mm (L1)
- 1 waterproof enclosure, large enough for battery and LED(s) short lengths of medium-duty hookup wire or figure-8

### Connector options for battery charging

- 1 waterproof 4-pin chassis-mount socket [Jaycar PS1009+ PS1005 (10A) or Altronics P9444+P9420 (5A)] **or**
- 1 waterproof 6-pin chassis-mount socket [Jaycar PS1003+PS1005 (10A) or Altronics P9446+P9420 (5A)]
- 1 4-pin line plug [Jaycar PP1006 (10A), Altronics P9474 (5A)] **or**
- 1 6-pin line plug [Jaycar PP1000 (10A), Altronics P9476 (5A)]

### Semiconductors

- 1 LM3409MY switchmode LED controller, MSOP-10 (IC1)
- 1 PIC10F202-E/OT 8-bit microcontroller programmed with 1610919A.HEX, SOT-23-6 (IC2)
- 1 TC6502P095VCT temperature switch, SOT-23-5 (TS1)
- 1 LM3480IM3-5.0 high-voltage 5V linear regulator, SOT-23 (REG1)
- 1 Si4447DY 40V 4.5A P-channel MOSFET, SOIC-8 (Q1)
- 1 15MQ040 40V 1.5A schottky diode, DO-214AC (D1)

### Capacitors

- 2 10μF 35V SMD tantalum capacitors, low-ESR, D case [eg, Kemet T495D106K035ATE120]
- 1 1μF 50V X7R SMD ceramic, size 3216/1206
- 2 100nF 50V X7R SMD ceramics, size 1608/0603
- 1 560pF 50V X7R SMD ceramic, size 1608/0603

### Resistors

- (all 1% SMD 1/10W, size 1608/0603 unless otherwise stated)
- 1 49.9kΩ      1 16.5kΩ      1 15.8kΩ
- 1 0.22Ω 1% 0.75W, size 3216/1206 [eg, Susumu KRL1632E-C-R220-F-T1]

solder joints and nearby components, between components or component pins and also to ensure that all pins have good fillets, touching both the pin and the pad.

Magnification and good lighting are critical to successfully inspecting a board populated with tiny SMD components. It’s also a good idea to clean it thoroughly beforehand, using a specialised flux solvent or alcohol (isopropyl, pure ethanol or methylated spirits). Otherwise, flux residue can get in the way of a proper inspection.


Once you’re satisfied that it has been assembled correctly, its time to power it up.

If you have a suitable DC voltage source such as a 15-24V 1A DC plugpack or bench supply, you can now test the unit. Wire up the supply leads and use some electrical tape to make sure they can’t short together, then switch on power. At first, nothing should happen. If your supply has a current meter, you should get a reading of no more than a few milliamps.

If the current reading is significantly more than that, switch off and carefully examine your board and wiring for faults.

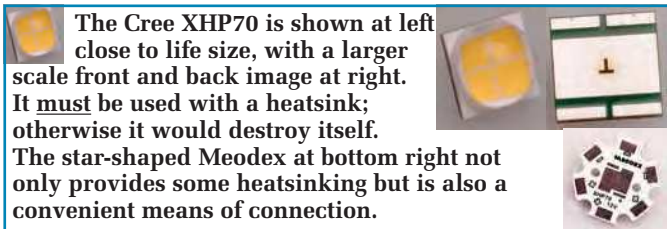Now press the pushbutton, and the LED should come on. Depending on the supply voltage, you should see around





500mA being drawn from the supply; slightly less if its output voltage is significantly above 15V. Brief presses of the button again should change the brightness — cycling between medium, low and off.

Holding it down for a few seconds should switch the LED on at full brightness. If you continue to hold it, the LED should start flashing. Once it's flashing, brief presses of the button will change the flashing mode; hold it down for several more seconds to switch the LED off.

If it doesn't work, most likely you have a soldering problem, or one of the components is in the wrong location or was fitted with the wrong orientation. Carefully inspect the board for problems.

If you don't find any, try adding flux paste to all the small IC leads and re-flow them all, either with a soldering iron that has a clean tip or (even better) a gentle application of hot air. Re-test to see if that fixed it.

Once you're sure it's working, switch off the power, disconnect the test supply and solder the battery connector onto the end of the supply wires. Make sure you get the polarity right (very important!) and use heatshrink tubing to insulate the solder joints. There are several common types of lithium-ion battery connector, so you will need to obtain one that matches your battery (usually from the same source).

We've seen connectors with red/black wire colour coding that's actually the opposite of the supply polarity once it's plugged into the battery. So check yours, and if this is the case, use red and black heatshrink tubing to change the wire colours to avoid mistakes.

### Placing inside your bike light

At the outset, we designed this project 'tiny', so it could fit inside a bike light. However, because every bike light is different, we can't offer much guidance here.

It may be that you have an old dynamo-type bike light set gathering dust in a cupboard; these have been largely superseded by modern lamps which also save your legs somewhat when pedalling up a hill!

But most of these older-style lights had a fair bit of room inside the light itself (because there was no battery). One of these could be worth experimenting with. The battery will need to be mounted in its own case external to the light — though this could be beneficial when it comes to charging.

We should warn you though that many bike lights (especially plastic ones) may not like the heat of the ultrabright LED, so you may need to come up with some arrangement which ensures your bike light doesn't melt.

### Putting it in a case

However, if you need to mount the project in a new case, the following points might help you.

The case should ideally be a waterproof one if you're going to be using it on a bicycle, or anywhere external where it could be in the weather. You will probably have to install a waterproof transparent window so that the LED itself can be mounted inside the box. It can be made from clear plastic and sealed with silicone sealant.

You should also seal around the pushbutton switch to ensure water cannot enter that way. The battery and board should be securely anchored inside the box so that they can't put any strain on the wires.

That just leaves the question of how you charge the battery. You could open the box up and remove the battery to charge it each time it runs low (or just swap it for a fresh one), but that's hardly convenient. To charge the battery without removing it, you will need to fit a waterproof socket to the case and make up a cable with a matching plug to connect to a suitable lithium-ion battery charger.

If you do this, it's vital to choose a connector where you can't accidentally short the pins. That could melt the connector or even damage the battery.

Ideally, multi-cell (series) lithium-ion/LiPo battery packs should be balance charged. In the case of a 5S battery, that requires at least six contacts, two of which will carry the full charging current. But you can get away with the occasional balance charge, so you could compromise by taking the battery out from time to time, and simply fitting a two-pin connector for day-to-day recharges (although some connectors are not available with fewer than four pins).

Another option is to build our April 2017 *Battery Balancer* and mount it inside the case, permanently attached to the battery's balance connector. That way, it will automatically be balanced each time you charge it. It is a relatively small board, so you should not have trouble fitting it, and it draws little current when not active (around 25µA).

We suggest that you use a four-pin chassis-mount socket for regular charging, with the pins wired in pairs for extra current handling, or a six-pin socket for balance charging. Suitable connectors are available from both Jaycar and Altronics; see the parts list for details.

Don't forget to insert the waterproof gasket (if supplied) when putting the lid on your box.

Reproduced by arrangement with  
SILICON CHIP magazine 2020.  
[www.siliconchip.com.au](http://www.siliconchip.com.au)



Having trouble holding the LED in place while you solder it? Here's how we did it: a pair of tweezers held tight in a bench vice, with the LED held firmly at the opposite end! A wooden clothes peg (NOT plastic!) also works well!

## SEPTEMBER 2019

**PROJECTS** • Intelligent Touchscreen Lathe Speed Controller • Twin Dipole Guitar Speaker • Cheap Asian Electronic Modules – Part 19 • Super Digital Sound Effects Module – Part 2 • White Noise Generator

**FEATURES** • Techno Talk • Net Work • Circuit Surgery • Audio Out • Practically Speaking • Make it with Micromite • Max's Cool Beans • Electronic Building Blocks



## OCTOBER 2019

**PROJECTS** • Programmable GPS-synced Frequency Reference – Part 1 • Digital Command Control Programmer for Decoders • Opto-isolated Mains Relay

**FEATURES** • The Fox Report • Techno Talk • Net Work • Using Stepper Motors • Circuit Surgery • Audio Out • Make it with Micromite • Max's Cool Beans • Electronic Building Blocks



## NOVEMBER 2019

**PROJECTS** • Programmable GPS-synced Frequency Reference – Part 2 • Cheap Asian Electronic Modules – Part 20 • Tinnitus & Insomnia Killer • Colour Maximite Computer – Part 1

**FEATURES** • Techno Talk • Net Work • Using Stepper Motors • Circuit Surgery • PIC n' Mix • Audio Out • Make it with Micromite • Max's Cool Beans • Electronic Building Blocks



## DECEMBER 2019

**PROJECTS** • Extremely Sensitive Magnetometer • Useless Box! • Four-channel High-current DC Fan and Pump Controller • Colour Maximite Computer – Part 2

**FEATURES** • The Fox Report • Techno Talk • Net Work • Circuit Surgery • Using Stepper Motors • Audio Out • Make it with Micromite • Max's Cool Beans • Electronic Building Blocks



## JANUARY 2020

**PROJECTS** • Audio DSP – Part 1 • Isolated Serial Link • Four-channel High-current DC Fan and Pump Controller – Part 2 • Colour Maximite Computer – Part 3

**FEATURES** • The Fox Report • Techno Talk • Net Work • PIC n' Mix • Using Stepper Motors • Circuit Surgery • Audio Out • Make it with Micromite • Max's Cool Beans • Electronic Building Blocks



## FEBRUARY 2020

**PROJECTS** • Audio DSP – Part 2 • Motion-Triggered 12V Switch • USB Keyboard and Mouse Adaptor for Micros • Using Cheap Asian Electronic Modules – Part 21 • Colour Maximite Computer – Part 4

**FEATURES** • The Fox Report • Techno Talk • Net Work • Practically Speaking • Using Stepper Motors • Circuit Surgery • Audio Out • Make it with Micromite • Max's Cool Beans • Electronic Building Blocks



## MARCH 2020

**PROJECTS** • Diode Curve Plotter • Audio DSP – Part 3 • Steam Train Whistle / Diesel Horn Sound Generator • Using Cheap Asian Electronic Modules – Part 22

**FEATURES** • The Fox Report • Techno Talk • Net Work • PIC n' Mix • Circuit Surgery • Audio Out • Make it with Micromite • Visual programming with XOD • Max's Cool Beans • Electronic Building Blocks



## APRIL 2020

**PROJECTS** • Ultra-low-distortion Preamplifier with Tone Controls – Part 1 • iCEstick – Part 1 • Flip-dot Display

**FEATURES** • Techno Talk • Net Work • Practically Speaking • Circuit Surgery • Audio Out • Make it with Micromite • Max's Cool Beans • Visual programming with XOD



## MAY 2020

**PROJECTS** • 433MHz Wireless Data Range Extender • Bridge-mode Audio Amplifier Adaptor • iCEstick – Part 2 • Ultra-low-distortion Preamplifier with Tone Controls – Part 2

**FEATURES** • The Fox Report • Techno Talk • Net Work • PIC n' Mix • Circuit Surgery • Audio Out • Make it with Micromite • Max's Cool Beans • Visual programming with XOD



## JUNE 2020

**PROJECTS** • AM/FM/CW Scanning HF/VHF RF Signal Generator – Part 1 • Low-cost 3.5-inch touchscreen for the Arduino or Micromite • Ultra-low-distortion Preamplifier with Tone Controls – Part 3

**FEATURES** • Techno Talk • Net Work • Practically Speaking • Circuit Surgery • Audio Out • Make it with Micromite • Max's Cool Beans



## JULY 2020

**PROJECTS** • Speech Synthesiser with the Raspberry Pi Zero • AD584 Precision Voltage References • AM/FM/CW Scanning HF/VHF RF Signal Generator – Part 2 • High-current Solid-state 12V Battery Isolator

**FEATURES** • Techno Talk • Net Work • PIC n' Mix • Circuit Surgery • Audio Out • Make it with Micromite • Max's Cool Beans • Electronic Building Blocks



## AUGUST 2020

**PROJECTS** • Micromite LCD Backpack V3 • Steering Wheel Audio Button to Infrared Adaptor • Junk Mail Repeller • Class-D Stereo Plus Subwoofer Amplifier

**FEATURES** • The Fox Report • Techno Talk • Net Work • Circuit Surgery • Audio Out • Make it with Micromite • Practically Speaking • Max's Cool Beans • Electronic Building Blocks



## BACK ISSUES – ONLY £5.95

£5.95 per issue for UK incl p&p ■ £9.95 Europe Air Mail ■ £11.95 ROW Air Mail

We can supply back issues of PE/EPE by post.

We stock magazines back to 2006, except for the following:

2006 Jan, Feb, Mar, Apr, May, Jul  
2007 Jun, Jul, Aug  
2008 Aug, Nov, Dec  
2009 Jan, Mar, Apr  
2010 May, Jun, Jul, Aug, Oct, Nov  
2011 Jan  
2014 Jan  
2018 Jan, Nov, Dec  
2019 Jan, Feb, May, June

Issues from Jan 1999 are available on CD-ROM / DVD-ROM

If we do not have a paper version of a particular issue, then a PDF can be supplied for the same price – your email address must be included on your order.

Please make sure all components are still available before commencing any project from a back-dated issue.

## ORDER FORM – BACK ISSUES

☐ Back issues required (month / year) .....

Name .....

Address .....

.....Tel: .....

Email .....

☐ I enclose cheque/PO to the value of £ .....

☐ Please charge my Visa/Mastercard £ .....



Card No. ....

Valid From ..... Card Expiry Date .....


Card Security Code ..... (Last three digits on or under the signature strip)

SEND TO: **Practical Electronics, Wimborne Publishing Ltd**  
113 Lynwood Drive, Merley, Wimborne, Dorset BH21 1UU.  
Tel: 01202 880299 Fax: 01202 843233.  
Email: [stewart.earn@wimborne.co.uk](mailto:stewart.earn@wimborne.co.uk) On-line Shop: [www.epemag.com](http://www.epemag.com)

Payments must be in £ sterling – cheque drawn on a UK bank. All items are normally posted within seven days of receipt of order. Send a copy of this form, or order by letter / online if you do not wish to cut your issue.



# THE MICROMITE EXPLORE-28

 

<http://geoffg.net>

The 28-pin Micromite has been used in many of our projects, and with good reason. It is a low-cost, powerful microcontroller which allows you to create advanced devices with minimal effort. Now the *Explore-28* will make your life even easier. It's a small plug-in module with the same powerful PIC plus a USB socket for comms and programming, giving you everything you need to get started with the Micromite in one handy package.

**T**he Micromite is a high performance 32-bit microcontroller which can be programmed in a friendly BASIC programming language.

It has a lot of built-in capabilities, including a variety of communications protocols (I<sup>2</sup>C, SPI, serial...), the ability to easily interface to many devices (LCD screens, GPS modules, temperature sensors...). And it's really easy to learn how to use it.

To start with the Micromite, you just need a programmed chip, which you can then plug into a breadboard.

This is not hard to do, but there is a bit of fiddling about to be done before you can start programming the chip. Many readers would prefer a pre-assembled module that can be immediately put to use.

That is the essence of the *Explore-28*. You can plug it into a USB port on your laptop and in a few minutes, have a simple program up and running.

For readers who read the short introductory series *Meet the Mighty Micromite* (February to April 2017) and now follow the *Make it with Micromite* series (from February 2019), the *Explore-28* combines the 28-pin Micromite Mk2 with the *Microbridge* interface (May 2018).

Another way to think about it is that it is a bit like the *Micromite LCD Backpack V2* (May 2018) but without the LCD, and in a much smaller package.

The whole module is only a little bit larger than a 28-pin DIP IC package but it packs a lot of hardware, including:

- A 28-pin Micromite pre-programmed with the latest MMBasic interpreter.
- A USB-to-serial interface, which allows you to plug the *Explore-28* into your computer and immediately start programming.

- A PIC32 programmer, so that you can update the BASIC interpreter whenever a new version is released.
  - A power supply with a 4-16V input range and the ability to supply up to 150mA at 3.3V (plus 5V, when powered from USB) for external circuitry.
- This means that if you purchase a pre-assembled *Explore-28* module, you can immediately start experimenting with it. You do not need to source the microcontroller, program the firmware or setup a breadboard. It is a fully assembled and ready-to-go package.

It is interesting to compare the *Explore-28* to the Commodore 64 from 1982, which also came with a built-in BASIC interpreter and was the most popular computer in the 1980s. Many millions were sold worldwide, for around US \$600 each.

The *Explore-28* is fifty times faster, with much more memory and costs about US \$20. While they clearly have different end uses, this still illustrates how far modern semiconductor technology has progressed.

The *Explore-28* printed circuit board and concept was developed by two Micromite enthusiasts in New Zealand:

Graeme Rixon and Robert Rozee. It can be purchased as a kit of parts or as a completely assembled module from [micromite.org](http://micromite.org) or Graeme's website – see the last page of this article for details.

Graeme Rixon also offers a full construction pack, which you can download from his website. This includes the PCB Gerber files, parts list and firmware.

So, you can get your own PCBs made and build your *Explore-28* modules from scratch if you wish.

## Connections

The *Explore-28* has the same 'form factor' as the Arduino Nano, which means that breakout boards designed for the Nano will suit the *Explore-28*. But the two are quite different in a programming sense; the Micromite is vastly more powerful and is programmed in BASIC, not C/C++.

The pin-out of the *Explore-28* is shown in Fig.1. Essentially, it mimics the pins on the 28-pin DIP version of the Micromite, except pin 20 which is not present. The module also includes two extra pins at the bottom, labelled +5V, which can be used to feed power in or out.

## Explore-28 features

- Complete microcontroller module with USB interface and power supply
- Programmed in BASIC, with 60KB program space and 50KB RAM for variables
- 19 I/O pins with 10 capable of being used as analogue inputs
- Supports communications protocols including async serial, I<sup>2</sup>C, SPI and Dallas OneWire
- Support for special devices such as temperature sensors, keypads, IR remote controls
- Full support for touch-sensitive LCD panels up to 3.6-inch (9.2cm) diagonal
- Embedded controller features such as sleep, control over clock speed and watchdog timer
- Built-in PIC32 programmer for updating the firmware
- Runs from 4-16V @ 50mA
- Compact size: 40mm long, 19mm wide and 8mm tall (without header pins)





# The Mighty Micromite

The Micromite is based on the Microchip PIC32, which is a high-performance 32-bit microcontroller. While this chip as supplied is powerful, it is not that easy to write programs for it (the manuals run to over a thousand pages!) and the standard programming languages used on it are assembler, C or C++. These languages and the programming software are complex and require experience to use properly.

For the average hobbyist, the Micromite firmware makes programming much easier. It's loaded into the Flash memory of the PIC32 and turns the chip into a Micromite. The Micromite firmware insulates you from the complexities of the underlying silicon, while still allowing you to use its features.

To program the Micromite, you use the BASIC programming language, which is designed to be easy for beginners and allows you to get started almost immediately.

## The BASIC language

The following is an elementary introduction to Micromite programming. We published a comprehensive three-part series on using the Micromite in the February to April 2017 issues, so refer to those articles for more detailed instruction. Plus of course the ongoing Make it with Micromite series.

The Micromite version of BASIC is called MMBasic (short for MicroMite BASIC) which is loosely based on the Microsoft BASIC interpreter that was popular years ago. 'Interpreted' means that the firmware reads through your program line-by-line, executing each command as it finds them.

BASIC (an acronym for **B**eginner's **A**ll-purpose **S**ymbolic **I**nstruction **C**ode) was initially developed by Dartmouth College in the US for teaching programming, and therefore emphasises ease of use. BASIC is also a powerful language, and it became popular in the 1980s and 90s with the introduction of small computers such as the Commodore 64 and Apple II. These days, it is still used in some large commercial data systems (usually running Pick Basic).

BASIC program execution starts at the top of the program and continues until it runs off the bottom or hits an `END` command. Generally, there is one command per line, although you can have more if you wish, each separated by the colon (`:`) character.

A command can be something like `PRINT` which will output some text to the console, `PIN()` which will set the state of an output pin, or `SERVO` which will control a servo motor.

Decisions within the program are made using the `IF...THEN` command. So, for example, your program can include something like:

```
IF t > 30 THEN PRINT "too high"
```

Your program can also run commands in loops. For example, the following will display the numbers from one to ten:

```
FOR nbr = 1 to 10
  PRINT nbr
NEXT nbr
```

## Micromite input/output

The Micromite is intended to be a controller that can be embedded in something like a burglar alarm or process controller. In this type of role, its ability to use the I/O pins to control external devices is critical.

An I/O pin refers to the physical pin on the Micromite chip. On the Explore-28, these are routed to pin headers on the edge of the module, with the same numbering.

So, when you refer to a pin number in your program, that is both the physical pin on the chip and the pin header number.

In MMBasic, you configure an I/O pin on the chip using the `SETPIN` command – it defines the pin as a digital input, digital output or analogue input. For example, if pin 2 on the chip has been defined as an analogue input, the function `PIN(2)` will read the voltage on pin number 2; eg:

```
PRINT PIN(2) would create a simple voltmeter.
```

To read the state of a pin configured as a digital input, you use the same function, but in that case, it will return zero for a low voltage and one for voltage high. You can set the output level of a pin configured as a digital output by assigning a value to `PIN()`. For example, this will set the output on pin 24 to a logic high (3.3V):

```
PIN(24) = 1
```

There are many other things that you can do with the Micromite's I/O pins, including measuring frequency, timing, generating square waves and more.

## Special device support

A great feature of the Micromite is that it has built-in support for many external devices like temperature and humidity sensors, keypads, real-time clocks and servos. For example, using the `IR` command, you can receive commands from an infrared remote control.

This is easy to do, and it adds flair (and utility) to your project when you can control it by pressing a button on a remote control.

As another example, you can connect a low-cost ultrasonic distance sensor to the Micromite and with one function, read the distance to an object in centimetres.

Measuring temperature and humidity is just as easy; MMBasic will query the sensor for you and return the temperature in degrees Celsius and humidity in %RH.

Perhaps the most outstanding feature of the Micromite is its ability to control a touch-sensitive LCD panel. The Micromite can display text and graphics and respond to touch inputs on the panel's face.

## Communications protocols

There are many modules and chips that you can buy to measure anything from air quality to acceleration. These all send their data via some communication protocol, usually serial, and the Micromite supports four main protocols:

- Asynchronous serial, which is used by computers, lab equipment and GPS modules.
- I<sup>2</sup>C, which is used by gas sensors, real-time clocks and many other chips.
- SPI, which is used, for example, by accelerometers, memory chips and electronic compasses.
- Dallas One-Wire, which is mostly used for temperature sensors.

GPS modules are particularly valuable; they're cheap (£8-20) and give you your precise location, altitude, speed, heading and the exact time.

Using the Micromite's serial interface, it is easy to retrieve this information and they open up a world of exciting projects that can be built.

Micromite will return the result of dividing 1 by 7, then display the command prompt again.

This is called 'command mode' and it allows you to try out most BASIC commands at the command prompt. It is handy for testing commands while you are learning the language.

Note that when you type something on the console or the Micromite sends some data to your PC, the LED marked

'MODE' (LED2) will briefly flash to indicate that data is being sent over the virtual serial port.

The tactile pushbutton near the LEDs (switch S1) is used to put the *Microbridge* into its programming mode (more about that later).

A handy feature of the *Microbridge* is that you can reset the chip by sending a break signal over the virtual serial interface. In Tera Term, this is done

by pressing `ALT-B`, and this has the same effect as cycling the power to the Micromite.

## Programming example

We mentioned how easy it is to get started with the *Explore-28*, so here is a short tutorial to illustrate that point. For a beginner, the best method of entering a program into the Micromite is to use the Micromite's built-in full-screen editor.

This is fully documented in the *Micromite User Manual*, but to get started, all you need to know is that the arrow keys on your keyboard will move the cursor around the text and the back-space key will delete the character before the cursor.

At the command prompt, type `EDIT` followed by the `Enter` key. This will take you into the Micromite's editor. Then, enter this short program:

```
SETPIN 15, DOUT
DO
  PIN(15) = 1
  PAUSE 500
  PIN(15) = 0
  PAUSE 500
LOOP
```

To save this program, press the `F1` key or `CTRL-Q` (which does the same thing). This will return you to the command prompt. Then, to run the program, type `RUN` and press `Enter`.

This program toggles the voltage on pin 15 of the *Explore-28* from zero to 3.3V and then back again every second, and continues doing it forever. You can test this by probing pin 15 with a voltmeter, and you should see the voltage jumping up and down at 1Hz.

While the program is running, you will not see the command prompt in the terminal emulator. This is because the Micromite is now busy, but you can regain control by pressing `CTRL-C`.

This is the break key and it will interrupt any running program and return control to the command prompt, so that you can edit the program or enter other commands.

## Circuit description

The circuit of the *Explore-28* is shown in Fig.4. As you can see, it isn't terribly complex. It consists of three main components: IC1, the 28-pin PIC32 microcontroller (the Micromite); IC2, the PIC16F1455 (*Microbridge*) which provides the USB interface; and a voltage regulator to provide the 3.3V supply (REG1).

The PIC32 used for the Micromite (IC1) is in a 28-pin surface-mounting package, with most of its pins going directly to the header pins on the edge of the board (CON1-CON3). The 10µF capacitor on pin 20 is critical and must be a high-quality multilayer ceramic type. It is used to stabilise the chip's internal 1.8V regulator, and if it is missing or the wrong type is used, the Micromite will not work.

The only Micromite pins which do not go directly to a corresponding pin on CON1-CON3 are: pin 11, the serial data out line, which goes via a 1.5kΩ resistor in order to protect IC1 if an

external device attempts to drive it above +3.3V or below 0V (eg, a raw RS-232 signal); and pin 20 (VCAP), as this micro pin is already connected to the required capacitor.

Several of the micro's pins also connect to the *Microbridge* (IC2), to allow the *Microbridge* to reprogram the chip and for its USB/serial function. As mentioned earlier, the *Microbridge* chip has two functions; it acts as a USB-to-serial bridge and as a PIC32 programmer.

On power-up, it starts in the USB-to-serial bridge mode, with the MODE LED (LED2) off, except for flickering when there is serial activity. Serial data is transmitted from pin 6, which connects to the receive data pin (pin 12) on IC1.


Similarly, the Micromite's transmit pin (pin 11) connects to receive (pin 5) on the *Microbridge* chip.

A second 1.5kΩ resistor between the TX pin of IC2 (pin 6) and the RX pin of IC1 (in 12) protects IC2 in case external circuitry tries to send data to the Micromite while the *Microbridge* is active.

A 10kΩ pull-up resistor from 3.3V to pin 11 of IC1 prevents glitches on the serial port when the Micromite is reset. Another 10kΩ pull-up resistor on pin 1 ( $\overline{\text{MCLR}}$ ) prevents spurious resets of the chip.

The tactile switch on pin 4 of IC2 is used to place the *Microbridge* into its PIC32 programming mode. In this mode, the MODE LED (LED2) lights up, and the *Microbridge* chip uses pin 7 to reset the PIC32 and pins 2 and 3 to drive its programming interface.

 In normal operation, these pins are in a high-impedance state, so the corresponding I/O pins on the Micromite can be used for other purposes.



**The *Explore-28* is just a little larger than the original 28-pin Micromite in a standard dual inline plastic (DIP) package. But it has many more features, including a USB-to-serial interface, onboard PIC32 programmer and a 3.3V regulator.**

## Parts list – Micromite Explore-28

- 1 four-layer PCB coded 07108191, 39 × 18.5mm
- 1 15-pin male header, 2.54mm pitch (CON1)
- 1 6-pin and 8-pin male header, 2.54mm pitch (CON2, CON3) (optional)
- 1 mini type-B SMD USB socket (CON4) [Altronics P1308, element14 2300434]
- 1 mini SMD tactile pushbutton switch (S1) [element14 1629616]

### Semiconductors

- 1 PIC32MX170F256B-50I/SO microcontroller programmed with MMBasic, SOIC-28 (IC1)
- 1 PIC16F1455-I/SL microcontroller programmed for Microbridge, SOIC-14 (IC2)
- 1 MCP1703A-3302E/DB low-dropout 3.3V regulator, SOT-223 (REG1)
- 2 red SMD LEDs, 2012/0805-size (LED1, LED2)

### Capacitors (all SMD 2012/0805 ceramic)

- 1 10µF 6.3V X5R
- 2 4.7µF 16V X5R
- 2 100nF 50V X7R

### Resistors (all 1% SMD 2012/0805)

- 2 10kΩ (Code 103)
- 4 1.5kΩ (Code 152)
- 1 10Ω (Code 100)

The power supply is based on a low-dropout linear regulator (REG1; Microchip MCP1703) with a fixed output of 3.3V.

This powers both the *Microbridge* chip (IC2) and the Micromite (IC1) and as mentioned, is also made available on pin 13 of CON1 for external circuitry to use. The MCP1703 can source up to 250mA, with about 50mA of that being used by the *Microbridge* and the Micromite.

Besides the critical 10µF capacitor described above, there are two 100nF bypass capacitors for the 3.3V supplies of IC1 and IC2, plus 4.7µF input bypassing and output filtering ceramic capacitors for REG1.

### PIC32 programmer

We mentioned above that the *Microbridge* chip can act as a PIC32 programmer for loading firmware updates into the Micromite (IC1).

You essentially get this feature for free, which is handy, as previously you needed to purchase a separate PIC32 programmer to take advantage of new releases of the Micromite firmware.

If you purchased the *Explore-28* as a fully assembled module or a kit,



The Windows version does not need to be installed; you can copy

Generally, the firmware is contained in a .zip file, along with the Micro-mite manuals, so you need to unzip its contents and locate the firmware file (it has a .hex extension). Then, copy this file to the same folder as the **pic32prog** program.

To program this file into the Micromite chip, run **pic32prog** with the following arguments:

Here, `xx` is the COM port number and `yyyy.hex` is the name of the firmware file. The COM port number is the same as that allocated by Windows when the

After the programming operation, the MODE LED will switch off, the *Microbridge* will revert to operating as a USB-

Updating the Micromite's firmware will reset any options set and completely erase the BASIC program memory. So make sure that you make a copy of the program stored on the Micromite before starting the upgrade.

We have often covered soldering surface mounted components before, and

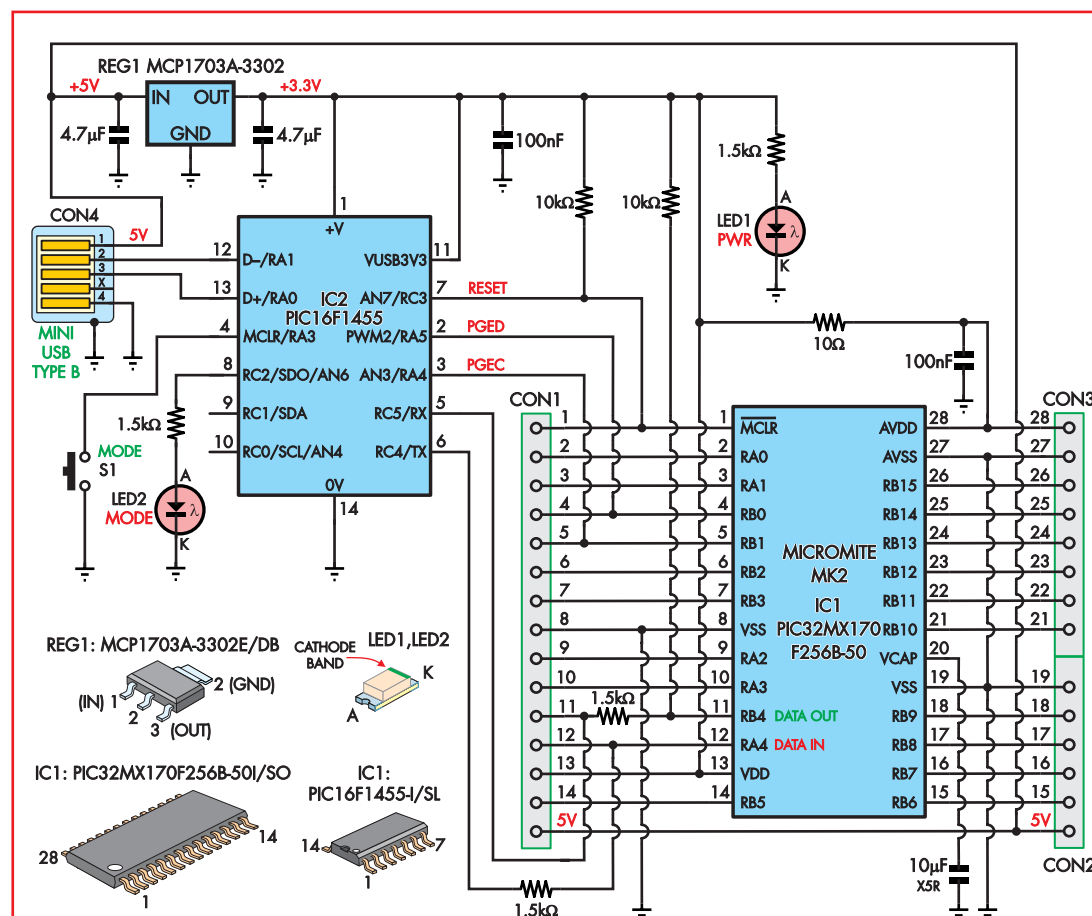


Fig. 4: the circuit of the *Explore-28* module is elegant in its simplicity. IC1 is the PIC32 which runs MMBasic; IC2 is the Microbridge which provides a USB serial port and the ability to reprogram IC1; and REG1 is a low-dropout regulator which provides both ICs with a 3.3V supply rail, derived from USB 5V or a source of 4-16V DC fed in via CON1 and/or CON2.

using them is nothing to be feared. The secret is to use plenty of flux paste and keep only a small amount of solder on the soldering iron's tip. The flux makes the solder flow smoothly around the joint while using only a minimal amount of solder means that you will avoid solder bridges and blobs.

The PCB used for the *Explore-28* is a four-layer board, coded 07108191, measures 39 × 18.5mm, and has components mounted on both sides. It is available from the *PE PCB Service*.

The overlay diagrams, Figs.6(a) and (b), show where the components are mounted, along with top and bottom layer tracks.

We haven't shown the two inner layers because that would make the diagrams hard to read. The outer layer tracks shown are used for signal routing, while the two inner layers consist of a ground plane and a power (+3.3V) plane.

These cover most of the board and only have holes where vias pass between the top and bottom layers.

Other vias are used to connect these planes to component pins.

While Fig.6 shows where all the components need to be mounted, the silk screen printing on the board will also guide you during assembly.

It's best to solder the SMD components on the bottom side first (the side with IC2 and REG1), then add the components to the top side, and finish with the pin headers.

Before soldering IC2, if you haven't purchased a pre-programmed kit, you need to program it with the *Microbridge* firmware. This can be downloaded from the *PE* website or from:

```
Administrator: C:\Windows\system32\cmd.exe

C:\>pic32prog -d ascii:con9 Micromite_5.2.hex
Programmer for Microchip PIC32 microcontrollers, Version 2.0.220
Copyright: (C) 2011-2015 Serge Vakulenko
(ascii ICSP coded by Robert Rozee)

Adapter: . OK! OK2 - ascii ICSP v1N
Processor: MK170F256B
Flash memory: 256 kbytes
Boot memory: 3 kbytes
Data: 259244 bytes
Erase: (100ns) done
Loading PE: 1 2 3 4 (LDR) 5 6 7a (PE) 7b 8 u030f
Program flash: ##### done
Program boot: ##### done
Verify flash: ##### done
Verify boot: ##### done
Program rate: 5255 bytes per second

total TDI/TMS pairs sent = 3682539 pairs
total TDO bits received = 949824 bits
total ascii codes sent = 1176948
total ascii codes recvd = 326254
maximum continuous write = 452 chars
O/S serial writes = 110284
O/S serial reads (data) = 29666
O/S serial reads (sync) = 10
XferFastData count = 58199
10ms delays (E/X/R) = 10/0/0
elapsed programming time = 0m 50s

C:\>_
```

Fig.5: the typical output from pic32prog after it has programmed a new version of the MMBasic firmware into the Micromite using the Microbridge. The whole operation is straight forward and takes less than a minute.

<http://geoffg.net/microbridge.html> (scroll to the bottom of the page).

You will also need a narrow SOIC programming socket to do this, so unless you have one, you're better off acquiring a programmed chip.

You do not need to program the PIC32 microcontroller used for the Micromite because the *Microbridge* will do that for you when you have finished construction.

Solder IC2 on the bottom side of the board first, taking care that its pin 1 dot is oriented towards the nearby empty square pads, as shown in Fig.6.

If you bridge two pins with solder, clean up the bridge by applying a little flux paste and then solder wick.

Follow with REG1, which can only go in one way around. It's best to apply a little flux paste to the large pad first, then solder the three smaller pins before finishing with the large tab. You may need to turn your iron up to get a good solder joint on the tab.

Now add the seven resistors and five capacitors to the bottom side, being careful not get any of the different values mixed up.

Flip the board over and then solder the USB socket. Make sure its five signal pins line up correctly with the pads (aided by the two plastic posts going into holes on the board), then solder those signal pins and ensure there are no bridges between them.


 


Fig.6: use these same-size photos and PCB overlay diagrams (top and bottom view) as a guide to assembling the *Explore-28*. Because the Micromite *Explore-28* is so small, we've also prepared the twice-life-size diagrams at right to make life a little easier! As mentioned in the text, it's easiest to populate the bottom side first (with IC2 and REG1) since these components are all similar heights, so the board should still sit relatively flat while you solder the remaining components on the top side. If you're having trouble getting it to sit flat, try plugging a pair of 15-pin headers into a breadboard and then resting the PCB on top.

 



The *Explore-28* is designed to plug into a standard (solderless) breadboard for easy prototyping. Using the pre-assembled module, you can plug it into a USB port on your laptop, and in a few minutes have a simple program running.

If there are bridges, apply some flux paste and clean them up using solder wick. Then solder the four large mounting tabs, to hold the socket firmly to the board.

With that done, you can continue with soldering IC1; again, watch its orientation – pin 1 goes at the opposite end from the USB socket.

Then fit LED1 and LED2, with their cathodes (generally indicated with a green stripe or dot) towards the 'K' shown in Fig.6 (shown on the PCB itself as white squares). But note that while most LEDs have a green dot or stripe

to indicate the cathode, we've seen LEDs where it indicates the anode.

So to be extra safe (and avoid a lot of fiddly rotating of components later), it's best to probe each end of the LEDs with a multimeter set on diode-test mode.

When they light up, the red probe is on the anode and the black probe on the cathode.

Finish up by soldering pushbutton S1 in place, followed by the headers, fitted to the underside of the board as shown.

### Testing

To test the completed *Explore-28*, simply connect it to a USB port on your computer and program the latest firmware into the Micromite as described above (if your Micromite chip wasn't already programmed).

Then check that you can get the MMBasic command prompt via a terminal emulator. If you can, it means that everything is working perfectly.

If you do not see the virtual serial port created by the *Microbridge* on your computer, the first thing to check is that the voltage regulator is producing 3.3V (measure between pins 13 and 8).

If this is OK, then the *Microbridge* chip is probably at fault, with the most likely causes being poor soldering or an incorrectly programmed chip.

If you can connect via the USB-to-serial interface but you do not see the

## Where to buy the Explore-28... ... parts, kits and modules

- A full kit, major parts or a complete pre-assembled module is available from the dedicated UK Micromite store at: <https://micromite.org/>

- Also visit the Rictech Ltd website for a downloadable construction pack with PCB and firmware: [www.rictech.nz/micromite-products](http://www.rictech.nz/micromite-products)

Micromite's prompt, you should check that the Micromite was programmed correctly, that the capacitor on pin 20 is of the correct type and, of course, that your soldering is good.

A handy check is the current drawn by the completed module. This is normally about 36mA.

You would need to connect an ammeter between a 4-16V DC supply and the bottom row of pins on the board to measure this.

If it is closer to 15mA, the Micromite chip is not running correctly, while a current draw of less than 5mA points to a problem with the voltage regulator.

So, there you have it. The *Explore-28* is an easy-to-use microcontroller module that you can use as the brains of your next project. It is a fun electronic building block to play with and an excellent way of learning to program in the BASIC programming language.

Reproduced by arrangement with  
SILICON CHIP magazine 2020.  
[www.siliconchip.com.au](http://www.siliconchip.com.au)

## Micromite Resources

Latest firmware versions, manuals and tutorials: ..... <http://geoffg.net>  
'Getting Started with the Micromite' and 'Micromite User Manual': ..... <http://geoffg.net/micromite.html#Downloads>  
The Back Shed forum, where many knowledgeable users can help newcomers:.... [www.thebackshed.com/forum/Microcontrollers](http://www.thebackshed.com/forum/Microcontrollers)

### Microbridge Resources

Firmware for the Microbridge (PIC16F1455) in the Explore-28: ..... <http://geoffg.net/microbridge.html#Downloads>  
pic32prog, used to program new firmware into the Micromite (Windows):..... <http://geoffg.net/microbridge.html#Downloads>  
P32P, a user-friendly GUI interface for pic32prog.exe (Windows): .... [www.thebackshed.com/docregister/ViewDoc.asp?DocID=21](http://www.thebackshed.com/docregister/ViewDoc.asp?DocID=21)

### Terminal Emulators

Tera Term, the standard terminal emulator used with the Micromite: ..... <http://tera-term.en.lo4d.com/>  
GFXterm, a terminal emulator designed specifically for use with the Micromite. It works with the Micromite's built-in editor and supports a set of graphics extensions: ..... [www.thebackshed.com/docregister/ViewDoc.asp?DocID=22](http://www.thebackshed.com/docregister/ViewDoc.asp?DocID=22)  
MMEdit, a complete IDE (Integrated Development Environment) specifically designed for the Micromite. It includes advanced features such as colour-coded text, formatting, download and run, and more: ..... [www.c-com.com.au/MMedit.htm](http://www.c-com.com.au/MMedit.htm)

# You can now download any issue of Practical Electronics since 1999.

## Cheap. Easy. Instant.

# www.electronpublishing.com



ESR Electronic Components Ltd 

**All of our stock is RoHS compliant and CE approved. Visit our well stocked shop for all of your requirements or order on-line.**

**We can help and advise with your enquiry, from design to construction.**

3D Printing • Cable • CCTV • Connectors • Components • Enclosures • Fans • Fuses • Hardware • Lamps • LED's • Leads • Loudspeakers • Panel Meters • PCB Production • Power Supplies • Relays • Resistors • Semiconductors • Soldering Irons • Switches • Test Equipment • Transformers and so much more...


**Monday to Friday 08:30 - 17.00, Saturday 08:30 - 15:30**



**Station Road  
Cullercoats  
North Shields  
Tyne & Wear  
NE30 4PQ**


**Tel: 0191 2514363 sales@esr.co.uk www.esr.co.uk**

## Tag-Connect

 

**JTAG Connector Plugs Directly into PCB!!**

**No Header! No Brainer!**

 

Our patented range of Plug-of-Nails™ spring-pin cables plug directly into a tiny footprint of pads and locating holes in your PCB, eliminating the need for a mating header. **Save Cost & Space on Every PCB!!**

Solutions for: PIC • dsPIC • ARM • MSP430 • Atmel • Generic JTAG • Altera Xilinx • BDM • C2000 • SPY-BI-WIRE • SPI / IIC • Altium Mini-HDMI • & More


**www.PlugOfNails.com**

Tag-Connector footprints as small as 0.02 sq. inch (0.13 sq cm)


 
# Three Stepper Motor Drivers

Want to build your own 3D printer or CNC machine? You'll need multiple stepper motors to control it, and a way to drive them. Or maybe you have some stepper motors from old printers or disc drives and want to reuse them. Here are three of the most common stepper motor driver modules and how to use them.



**T**his article assumes you understand the basics of how stepper motors work. If you want an introduction to this type of motor then read Paul Cooper's excellent *Using Stepper Motors* series in the October 2019 to February 2020 issues.

Our first driver module is also the largest, at  $60 \times 55 \times 28\text{mm}$ , including the finned heatsink for the driver IC. It's based on the ST Microelectronics L298N dual H-bridge driver chip and is currently available on eBay for around £3 to £4.50 (at the time of writing see item 182636983939). If you don't mind waiting up to a month for delivery, then AliExpress sell this item for nearly half the eBay price.

The 'N' on the end of the chip version signifies that it's in a 15-pin Multiwatt Power package, intended to be mounted vertically on a heatsink. ST Micro also make a similar version (L298HN) intended to be mounted horizontally, and a version in a Power-SO20 SMD package (L298P).

Fig.1 shows a simplified block diagram of what's inside the L298. It has two full H-bridge drivers (using bipolar power transistors) and so can drive both stator windings of a standard two-phase bipolar hybrid stepper motor.

Each bridge has an enable input and two logic control inputs, and both bridges have their negative supply

connections brought out separately, to allow for an external current-sensing resistor (RSA and RSB, shown in red).

The L298 can operate from supply voltages from 6-46V and can handle up to 2A per bridge. The inputs are TTL compatible. This makes it the most rugged of the driver ICs we're looking at here, especially when it's fitted to that  $23 \times 25 \times 15\text{mm}$  finned heatsink.

Fig.2 shows the full circuit of the L298N-based driver module. In addition to the L298N chip itself (IC1), there's regulator REG1, which provides a 5V supply for the logic circuitry from the stator supply voltage  $V_{MS}$ , if no separate 5V supply is available. REG1 is enabled simply by leaving the jumper shunt in place on the '5V\_EN' header.

There are also eight MDDM7 fast-switching silicon diodes to ensure that all four outputs of IC1 are protected from damage due to back-EMF spikes from the motor stator windings, at the end of each current pulse.

The upper diodes prevent the outputs from swinging more positive than one diode forward-voltage drop above the supply voltage ( $V_{MS}$ ), while the lower diodes prevent them from swinging below ground by more than one diode forward drop.

Note that there are no current-sensing resistors fitted between the Sense<sub>A</sub>

(pin 1) and Sense<sub>B</sub> (pin 15) pins of IC1 and ground. Instead, these pins are brought out to the two pairs of header pins (CSA and CSB) at the right-hand end of the 6x2 pin DIL header, just below IC1 in Fig.2.

This allows you to connect in current-sensing resistors if you wish, or just short both pins to ground (by leaving the jumper shunts in place) if you do not need current monitoring.

The other four pairs of header pins (U1-U4) allow you to disconnect the four 10kΩ pull-up resistors between the control inputs of IC1 and +5V. Four of the five indicator LEDs (LEDs1-4) show when each of the four logic inputs is high, while the fifth (LED5) is a 5V power-on indicator.

This module is quite flexible but it does have one significant shortcoming: it is purely a dual H-bridge stepper driver, lacking any built-in indexing controller.

ST Micro make a matching controller chip for use with the L298, called the L297. This can control the L298 for full- or half-stepping, wave microstepping and clockwise or anti-clockwise rotation. It can also sense the voltages across the current sensing resistors CSA and CSB, and use PWM to control and regulate the stator winding currents. However, the L297 chip costs around £10 – two to


 


Fig.1 (right): block diagram of the L298N IC, which is shown as part of the module above, attached to the heatsink.

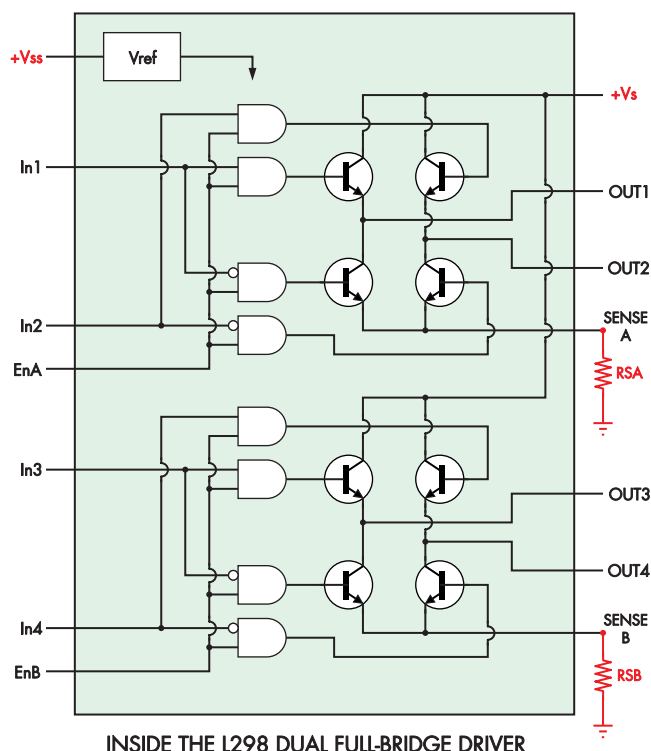

three times the price of the L298 module itself. Instead of using an L297 controller chip, you can use software running in your Arduino, Micromite or some other micro. Developing this can be a bit of a challenge but it is by no means impossible.

By the way, the L298N module isn't restricted to driving a stepper motor. It can also be used to drive a pair of conventional brushed DC motors – one from each of the two H-bridges.

All you need to do is feed one input of each bridge with a PWM (pulse-width modulated) pulse stream. You could drive one input for clockwise rotation and the other for anticlockwise rotation.

#### DRV8825-based module

The next module is much smaller and combines a stepper motor controller and driver, both within the Texas Instruments DRV8825 chip. The mod-

ule measures just 20 × 15 × 16mm, including the stick-on heatsink; and is currently available from eBay suppliers for around £1.25 each (at the time of writing, see item 392867154045).

The DRV8825 chip packs a lot into a 28-pin SSOP (SMD) package, as you can see from the internal block diagram in Fig.3.

There are two full H-bridge drivers, labelled MOTOR DRIVER A and MOTOR DRIVER B. These use N-channel

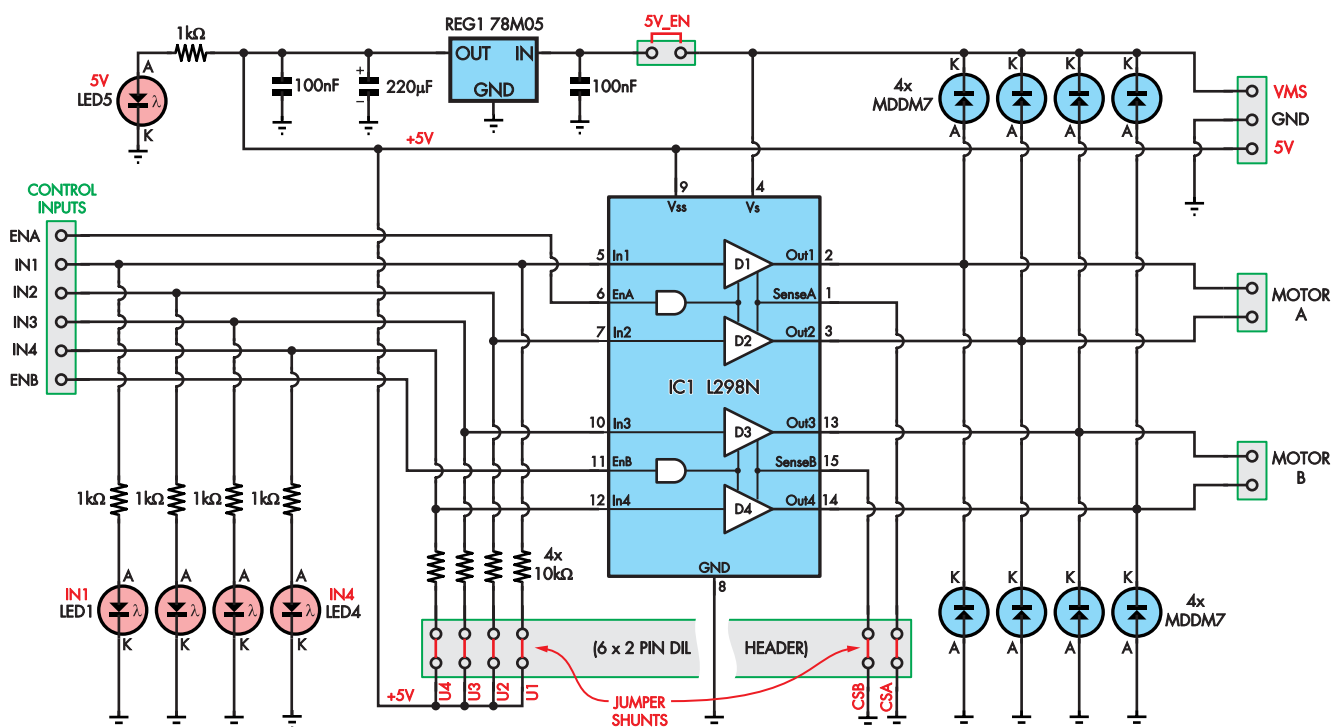


Fig.2: complete circuit diagram of the L298N-based stepper driver module. CSA and CSB can be fitted with two current-sensing resistors if needed, otherwise they can just be shorted to ground.



Internal feedback from the  $I_{\text{SENA}}$  and  $I_{\text{SENB}}$  pins allows the PWM circuitry to regulate the motor winding currents at the same time. The chip supports fast, slow or mixed current decay modes.

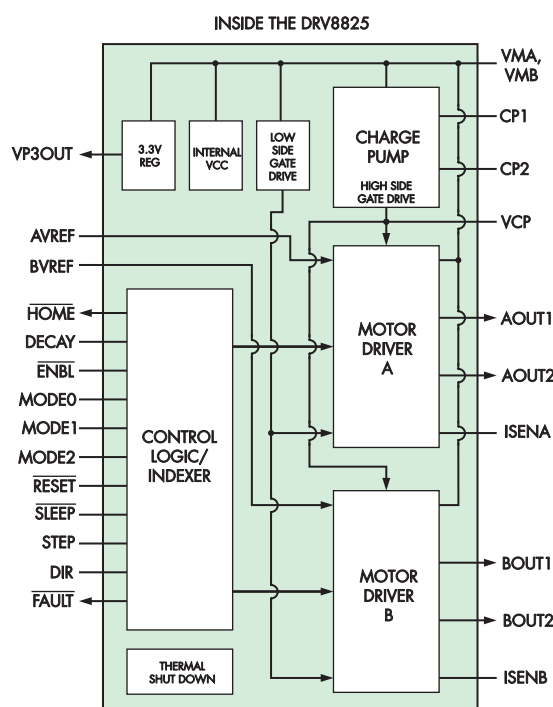


Fig.4 shows the full circuit of the DRV8825-based stepper driver module, and there's little in it apart from the DRV8825 chip (IC1).

The DRV8825 data sheet advises that there is an op amp with a gain of five in the feedback circuit from the  $I_{\text{SEN A}}$  and  $I_{\text{SEN B}}$  pins, so the relationship between the maximum motor winding current, the sensing resistor values and the  $V_{\text{REF}}$  voltage (set by VR1) is straightforward:

$$I_{MAX} = V_{REF} \div (5 \times R_{SENSE})$$

As you can see, despite its tiny size, the DRV8825 has a surprising range of capabilities, including a very flexible built-in indexing controller to


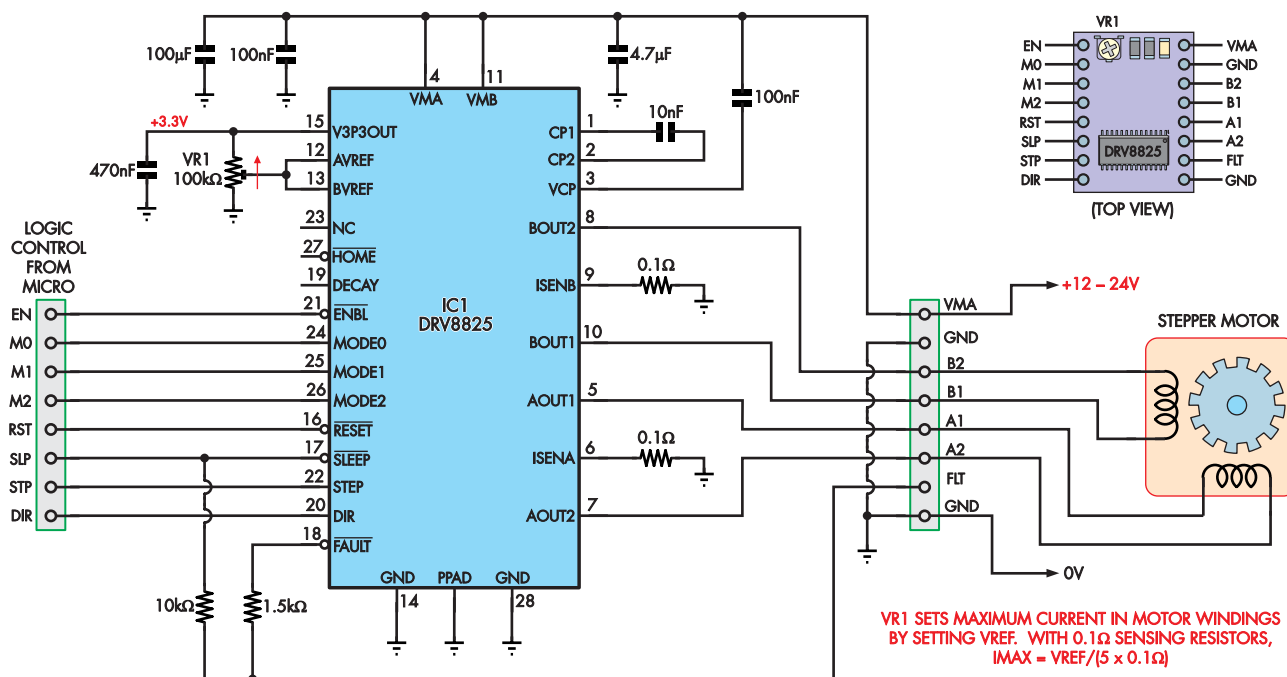
 


Fig.4: complete circuit diagram of the DRV8825-based stepper driver/controller module. While this circuit is less complex than the L298N-based module shown in Fig.2, it doubles as a controller and driver instead of only being a driver.

 

The DRV8825 (left) and TB6612FNG-based module (right) shown slightly enlarged. Note the stick-on heatsink for the DRV8825, which would likely be required when driving large stepper motors with windings that pull 1A or more.

simplify controlling a stepper motor from a micro.

### TB6612FNG driver module

The third stepper motor driver module is based on the Toshiba TB6612FNG chip. It's slightly larger than the DRV8825-based module, measuring only 20.5 × 20.5 × 11mm, including headers. It's available from suppliers on eBay for around £2.40 each – at the time of writing see item 254645741337.

Fig.5 shows a simplified block diagram of what's inside the TB6612FNG, which comes in a 24-pin SSOP SMD package. It's basically a pair of H-bridge drivers, each driven from a control logic block. So in many ways, it's rather like the L298N, except that the H-bridges use LDMOS power transistors rather than bipolar power transistors.

The TB6612FNG is rated to operate at a maximum motor supply volt-

age (VM) of 15V, and to deliver output currents of up to 1.2A average or 3.2A peak, for each channel. But it also needs a logic circuit supply voltage ( $V_{CC}$ ) of between 2.7V and 5.5V, and there is no on-chip regulator to derive this from the motor supply. So this must be supplied externally.

Note that although the ground connection of each H-bridge is brought out to a pair of device pins (3 and 4, 9 and 10), these pins are all linked together inside the device.

You therefore can't individually monitor or control bridge currents. You'd have to use a single resistor, and it would develop a voltage corresponding to a vector sum of the two bridge currents.

By the way, like the L298N, the TB6612FNG does not include any indexing/control circuitry ahead of the control logic. So it too needs external indexing hardware or software

to drive a stepper motor.

On the other hand, it's suitable for driving a pair of brush-type DC motors, using PWM input signals to control motor speed and the  $A_{IN1}/A_{IN2}$  and  $B_{IN1}/B_{IN2}$  signals to determine rotation.

Fig.6 shows the actual circuit of the TB6612FNG based driver module, and clearly, there is very little in it apart from the main chip itself (IC1).

There are just three bypass capacitors on the supply lines and two 8-pin SIL headers (CON1 and CON2) to make the input and output connections. It couldn't be much simpler.

### Trying them out

Since the driving schemes of the L298N and TB6612FNG are quite similar, we've decided to concentrate on demonstrating how to use the L298N and DRV8825-based modules. And we're going to demonstrate driving


 


Fig.5 (left): block diagram of the TB6612FNG driver IC.

Fig.6 (above): complete circuit diagram of the TB6612FNG-based module which is only a driver module and does not have any control circuitry.

 

## Low-cost stepper motors currently available

Currently, there are quite a few new stepper motors available via eBay and other online sources.

Here's a sample of those we found in the standard NEMA sizes, together with their price range:

**NEMA 11** from around £9-£30 each depending on specification

**NEMA 17** £7.50 each or five for £26

**NEMA 23** around £25 each

There were also many small non-NEMA steppers available at much lower prices.

For example, a 28BYJ-48 5V unipolar stepper motor bundled with a ULN2003 driver module was around £3 each or £12 for a pack of five.

one from an Arduino and one from a Micromite.

You should not have difficulty adapting our examples to different combinations of the modules and controllers if it turns out that you'd prefer to use some other pairing.

First, let's start by driving the L298N-based module from an Arduino. While this module lacks its own indexing controller, the Arduino IDE comes with a library called 'Stepper' which has functions to perform indexing. That makes hooking up controller chips like the L298N (or the TB6612FNG) quite easy.

Fig.7 shows how we connected the L298N module to an Arduino Uno and a typical bipolar stepper motor. The

connections between the Uno and the module inputs are the defaults for the Stepper library, so it's important to follow these carefully.

The stepper motor windings are each connected to either the MOTOR A or MOTOR B output terminals, while the  $V_{MS}$  and GND terminals are connected to the motor power supply.

All the jumper shunts are left in place on the module.

Also, note that the module's centre GND pin needs to be connected to one of the GND pins of the Arduino. That's because there is no other connection between the two GNDs, and the control signals would otherwise not work correctly.

The Arduino IDE Stepper library comes with some example sketches written by Tom Igoe. We adapted one of these to make it easier for our readers. It's called **SCStepper\_oneRevolution.ino** and you can download it from the September 2020 page of the *PE* website. It directs the stepper motor to rotate in one direction by a full revolution, then reverse and rotate back by a full revolution.

The number of steps required for a full revolution needs to be added to the sketch before you run it. The correct figure for many motors is 200, so that is the default.

If you find this sketch interesting, you'll find another three sketches in the 'Examples' folder of the Stepper library folder on your PC (if you have installed the Arduino IDE). These will all work with the setup shown in Fig.7, performing different functions.

### Microstepping with the Micromite

We decided to drive the DRV8825-based module with a Micromite because its

inbuilt indexer made it a little easier to program 'from scratch'.

Fig.8 shows how we connected the module between the Micromite and a bipolar stepper. The main STP and DIR inputs of the module are driven from pins 10 and 9 of the Micromite, with the  $\overline{SLP}$  and  $\overline{RST}$  inputs both driven from pin 16.

Similarly, the ENBL input is driven from pin 22, while the M0, M1 and M2 mode control inputs are driven from pins 21, 18 and 17 respectively.

On the output side, the motor windings are connected to the A1, A2, B1 and B2 pins, while the motor supply is connected to the  $V_{MA}$  (+12V) and GND pins. The two GND pins are also connected together, and on to a GND pin on the Micromite. This is done to ensure that both the module and the Micromite have a common ground.

An electrolytic capacitor of at least 100µF must be connected between the  $V_{MA}$  and GND pins of the module, as shown in Fig.8.

This is to provide a low impedance reservoir from which the module's H-bridges can draw current pulses – without any impedance from inductance in the power leads.

The USB-UART bridge module at top centre in Fig.8 is to program the Micromite from your PC, as well as to provide the Micromite with 5V DC.

Note that while the DRV8825 module comes with a tiny (9 × 9 × 5mm) finned heatsink which can be attached to the top of the DRV8825 chip using an adhesive patch, it is unnecessary when driving a small stepper motor from a 12V supply. Presumably, it would be required if the module is driving a reasonably large stepper motor with windings drawing over 1A from a 24V supply.


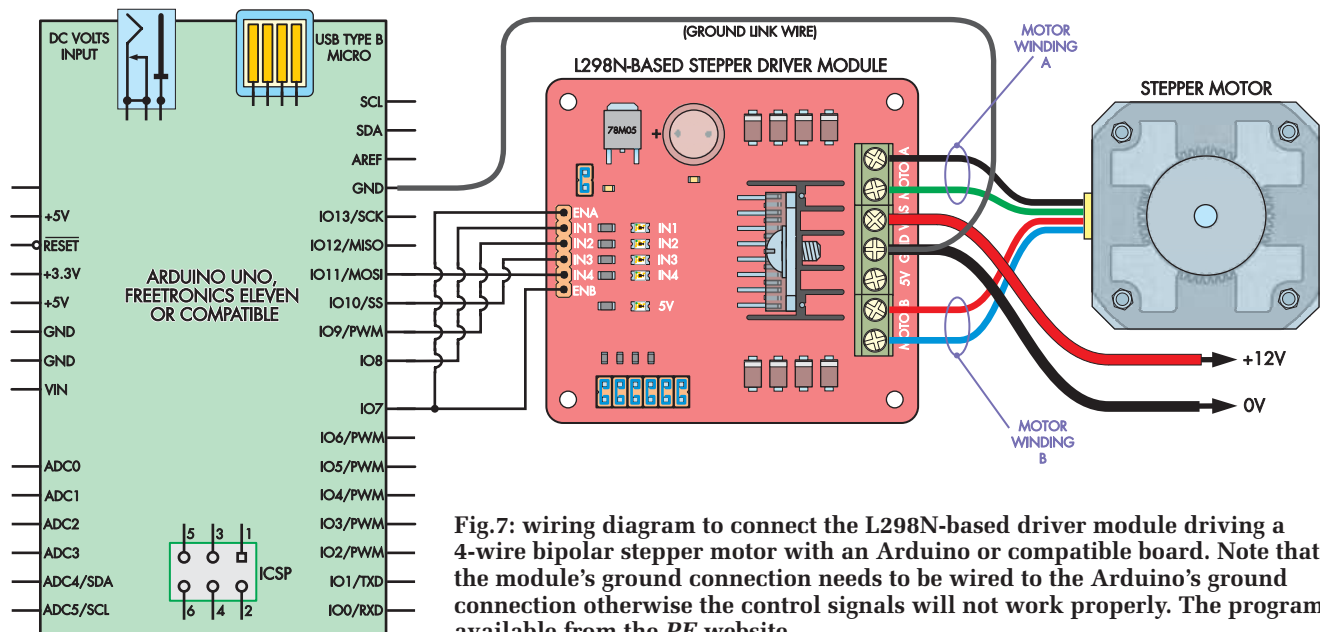


Fig.7: wiring diagram to connect the L298N-based driver module driving a 4-wire bipolar stepper motor with an Arduino or compatible board. Note that the module's ground connection needs to be wired to the Arduino's ground connection otherwise the control signals will not work properly. The program is available from the *PE* website.

 

The three screengrabs of the example microstepping program for the DRV8825 running on a Micromite. From left to right there is the main menu at power-up, the SET FUNCT sub menu (which determine how the drive pulses should be sent) and then the SET MODE sub menu (which is used to select the stepping mode).

In our test, the winding current was only about 330mA and even without the extra heatsink, the DRV8825 became only barely warm. The module PCB provides copper patches on both sides under the chip, linked by an array of vias. So it already has a useful amount of heatsinking.

After studying TI's datasheet and application notes, I was able to write a Micromite program to control a stepper via the DRV8825 module.

This program is named **DRV8825 stepper driving program.bas** and you can download it from the September 2020 page of the *PE* website.

When loaded onto a Micromite with *LCD Backpack*, at power-up it will present you with the main screen with six touch buttons, shown in Screen 1. The buttons are labelled SET FUNCT, SET MODE, < DIR, DIR >, START and STOP. Pressing SET FUNCT loads the SELECT FUNCTION screen shown in Screen 2. This lets you choose from one of five functions:

- SINGLE** Send a single step pulse each time
- CONTIN** Send a large number of step pulses)
- 1/2 REV** Send pulses for a half revolution of the motor)
- FULL REV** Send pulses for a full revolution)
- FWD-REV** Send pulses for one full revolution in one direction, followed by pulses to make the motor return in the opposite direction to its original position).

The sixth button on this screen is labelled RETURN, allowing you to get back to the main screen without changing the existing selection.

If you press the SET MODE button on the main screen, you'll be presented with the SELECT STEPPING MODE screen shown in Screen 3. This allows you to select one of the six stepping modes provided by the DRV8825: FULL STEP, HALF STEP, 1/4 STEP, 1/8 STEP, 1/16 STEP or 1/32 STEP.

Touching any one of these buttons selects the desired mode and switches you back to the main screen.

The two red buttons on the main screen are used to select the direction of motor rotation. And touching the START button at lower left should result in the motor performing the selected function, using steps of the mode you've selected. The STOP button allows you to stop the motor at any time.

This program demonstrates a fair number of possibilities when it comes to using the Micromite to control a stepper motor using the DRV8825 module.

Some useful links on each of the modules are listed below:

[www.st.com/en/motor-drivers/1298](http://www.st.com/en/motor-drivers/1298)  
[www.ti.com/product/DRV8825](http://www.ti.com/product/DRV8825)  
[siliconchip.com.au/link/aama](http://siliconchip.com.au/link/aama)

Reproduced by arrangement with  
*SILICON CHIP* magazine 2020.  
[www.siliconchip.com.au](http://www.siliconchip.com.au)

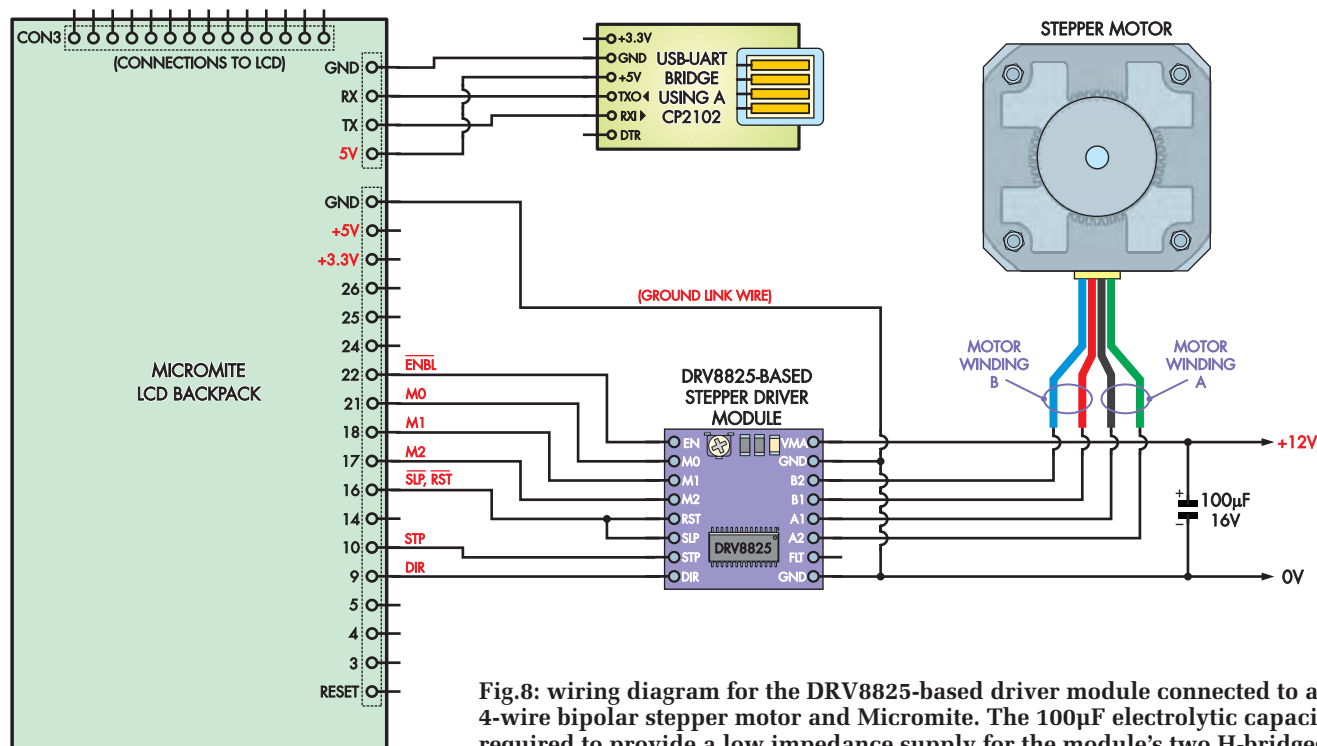


Fig.8: wiring diagram for the DRV8825-based driver module connected to a 4-wire bipolar stepper motor and Micromite. The 100µF electrolytic capacitor is required to provide a low impedance supply for the module's two H-bridges.



# Cheap and easy compact speaker enclosures

by Julian Edgar



Want to build speaker enclosures but put off by the woodwork involved? Julian Edgar describes a novel technique using clay-fibre flowerpots. They look stunning – and sound excellent, too.

**S**peaker building is great fun, but one of the greatest challenges in home Hi-Fi speaker construction is making the enclosures. Typically, speaker enclosures are constructed from veneered or plastic-coated particle board, and to develop good-looking and stiff enclosures usually requires access to some pretty serious woodworking machinery. A different approach is to base the enclosure design around flat-pack furniture – but when taking that route, the expense quickly adds up.

However, the enclosure design covered here takes a completely different approach – you could say, a radically different approach! Rather than make a rectangular enclosure from composite board, this approach uses clay-fibre flowerpots (planters) that are glued together. Constructing the compact enclosures takes hours rather than days, and the cost can also be quite low. Fascinatingly, this method of enclosure design also has major benefits to the sound that's developed.

First, let's go back to the beginning – how did such an unusual approach come about?

## Beginnings

Near where I live, there is a small-scale manufacturer of very expensive, esoteric speaker enclosures. The enclosures are spherical and are hand-made from concrete. The outer surfaces are polished or painted, and the enclosures sit on avant-garde sheet metal stands.

I wandered in one day to experience the sound. On the one hand I was impressed – the music sounded incredibly open and spacious – and on the other, underwhelmed. What I was most underwhelmed by was the price. The cost of the speakers was way out of my budget, and so I started thinking about building my own.



The constructor of the concrete enclosures uses custom moulds in which the concrete is cast. On my visit, he told me of the years of development that had gone into the technique, and how he'd had plenty of failures along the way. For a one-off pair of enclosures, the time and effort in my making moulds would be horrendous, so I wondered – was there another way of achieving a similar outcome?

That's when I discovered the joys of flowerpots!

## The enclosures

The enclosures shown here use ordinary flowerpots, also called 'planters',

but crucially they are made from clay-fibre (also often listed as 'fibre-clay', 'fibreclay' or similar). This material uses a mixture of traditional clay and fibre – the latter is apparently a waste product from pulp mills. Acoustically, it is relatively dead (the pots don't ring when tapped) and can be worked and cut with normal tools – more on this in a moment.

## Pot shape – not just spheres

The pots I use are hemi-spherical – that is, when two are glued together, they form a sphere. However, depending on the shape of the pots that you start with, you can have all sorts

of shapes. For example, if you glue together two pots having extended sides, you will end up with more of a prolate spheroid. (Yes, I had to look that one up – it means an elongated sphere.)

The curved walls of the enclosures provide excellent stiffness, reduce internal standing-wave reflection, and potentially have some advantages in reducing diffraction effects (there are no front enclosure edges).

Although the precise shape is not critical, do use circular ones, not the box-shaped ones, which are weaker, heavier and lack the acoustical advantages of pots with continuous rotational symmetry.

While I haven't done so, it may also be possible to glue a flat piece of particle board within the mouth of an elongated pot and mount the speaker driver on that. (This would still massively reduce the amount of work needed to be done over building a conventional enclosure.)

### Flowerpot selection

When selecting appropriate pots, you first need to consider the internal volume required for your design. For example, does your final enclosure design need to have a volume of 15 litres – or 30 litres? Using off-the-shelf flowerpots, you obviously won't be able to have an infinite variety of internal volumes available, but if the sound is to be good, you'll need an internal volume that is close to the required design spec.

Second, ensure that the flat surface (the one on which the pot normally sits) is large enough in diameter to take the main bass driver (the woofer). In a two-way system, I mount the tweeter externally, but if you want the tweeter to be in the same panel as the woofer, the flat part of the pot will need to be larger. In ported designs, I use the rear flat area of the enclosure for the port.

Finally, the quality of clay-fibre flowerpots varies considerably, so ensure that you have solid examples.

(And where to source the pots? Just wander along to your nearest large garden supplies store. Looking online, Homebase has a wide variety of clay-fibre pots.)

In addition to the clay-fibre pots, you will also need:

- Water clean-up industrial adhesive
- Polyester fibre internal damping material (I use low-cost quilt wadding)
- Acoustic components (drivers, crossovers, terminal blocks, ports)
- Basic tools, including an electric drill and an electric jigsaw. An angle grinder is useful and hastens the work, but you could use a hand file instead.

### How to construct your enclosures

The accompanying photo panels and captions give you the main construction details. There is room for considerable innovation and personalisation, so stick to the basic techniques, but don't be afraid to add your own design flourishes.



Fig.1. (above) The first step is to buy a pair of the bowls. At the time of writing, these bowls were available in 28cm, 34cm, 40cm and 51cm diameters, and in black or white finishes. The one used here is 34cm (external) diameter with a black finish. Two glued together give a 16-litre internal volume. (The ear defenders give a sense of scale and are a reminder to wear PPE when using power tools or working on a dust-generating job!)



Fig.2. (above right) Here is the as-bought bowl turned upside-down. While it isn't super clear in this pic, the bowl rests on 'feet' which are formed into the bowl. To gain a flat surface, these feet need to be ground off.

Fig.3. (opposite) A normal metal grinding disc mounted in an angle grinder does a good job of removing the 'feet'. Again, it's a dusty job and so it's best done outside with the operator wearing goggles, hearing protection and a dust mask.







Fig.4. Here's the view with the base smoothed. To get it as flat as possible, follow-up the grinder with the use of a belt sander, or moderately coarse sandpaper and a sanding block.



Fig.5. The next step is to mark the cut-out required for the driver. Be careful in sizing this hole – too small and there will be the need for lots of further grinding; too large and you will not get the driver to seal in the hole. Note the pot drainage hole.



Fig.6. The hole for the driver can be cut out with an electric jigsaw – this pic shows the piece that's been removed. Use a coarse wood-cutting blade – and expect to get only a few holes out of the blade before it is blunt. Don't go like a bull in a china shop – you can crack the bowl if you push too hard.



Fig.7. Here is the hole immediately after the jigsawing had been done. It's difficult in the clay-fibre mix to follow the line accurately (there are small pebbles in the material too), so it's better to err on the side of undersize rather than oversize. The hole can then be ground back to the line by carefully using the angle grinder or a half-round file.



Fig.8. It's hard to see, but the arrow points to one of the speaker mounting holes that has been drilled. If you have a masonry drill bit, you could use that (not with a hammer drill!) but these holes were drilled with a normal HSS (high-speed steel) bit. Drill the holes sufficiently large that machine screws can be inserted – nyloc nuts and washers will go on the inside of the bowl.



Fig.9. Use silicone sealant under the edge of the speaker frame. This is important because despite smoothing with the grinder and sandpaper, the mounting surface is likely to not be perfectly flat. You don't want air leaks around the edge of the driver.

# – Flowerpot speaker acoustic design –

The complete acoustic design of loudspeaker systems is well beyond this article – however, here are some tips.

The most critical component to get right in terms of enclosure sizing is the woofer. Woofers are available with Thiele-Small specifications, and there are free online calculators into which these specs can be plugged. The software will quickly show you the required enclosure volume, and whether it is better that it be sealed or ported. (And in ported designs, the software will also show you the required diameter and length of the port.)

Note that the easiest way of measuring the internal volume of the pot is to fill it with sand, measuring the required volume of the sand with a measuring jug. (If using two pots, obviously double this volume.)

## Thiele parameters

If you would like to measure the Thiele-Small specs of the driver yourself (perhaps you have an unknown

driver for which the specs are not available) I recommend Woofer Tester 2, a combination hardware/software package that connects to a PC and allows quick and easy driver testing and enclosure modelling. I reviewed this package in the May 2017 issue of *EPE/PE*.

However, probably the easiest (and potentially cheapest) way of sourcing decent drivers, crossovers and an enclosure design, is to buy a good quality second-hand pair of speakers close to the enclosure volume you are chasing. If the particle board cabinets are a bit knocked around, you can pay very little for such speakers. You then just transfer everything (woofer, tweeter, crossover, port and terminal block) into the flowerpot enclosure. With the added wadding and usually acoustically better enclosure, the sound is very likely to be improved over the original – and of course, the speakers will look stunning.

In the enclosure design you can see here, I used Alpine SPR-17S 6.5-inch

Type R Component Splits – these are sold for use in cars. This set comprises nominal 6.5-inch woofers with cast alloy frames, 1-inch dome tweeters, and full crossovers (not just capacitors).

The bass drivers lend themselves to compact ported enclosures, and the crossovers have variable tweeter attenuation so you can tweak the high-end response as you wish. The drivers also have plenty of power handling and, since in ported enclosures their efficiency is fairly high, lots of sound volume is available. At the opposite end of the spectrum, they also still sound good with only a few watts powering them.

The enclosures have an internal volume of 16 litres and are tuned to 49Hz, with a port 50mm in diameter and 118mm long. The tweeter is mounted below the main enclosure, and the crossover and port are mounted on the rear.

The sound of the finished speakers is outstanding – especially in their transparency and their ability for the vocalist to be ‘with you in the room’.



Fig.10. The driver installed in the hole. Note the use of washers and nyloc nuts on the speaker mounting screws. Tighten these when the sealant is yet to set – but be careful not to over-tighten or you could crack the bowl.

Fig.11. With the driver installed, it's time to tackle the other bowl. The other bowl, its ‘feet’ already ground off, needs a hole made for the port tube. I found the easiest way to do this was to use the jigsaw to cut a series of radial slots like this, with the pieces then broken off by the careful use of pliers. The hole was then filed to final shape. The hole doesn't have to be perfect – the industrial glue used to secure the port in place will fill any small gaps. (Don't use an expensive holesaw to make this opening – the teeth will soon be blunt and the holesaw ruined.)



Fig.12. The port tube needs to be the correct diameter and length to match the enclosure design. PVC pipe is cheap and easy. This port is 50mm in diameter and 118mm long.



Fig.13. The port glued into place. For this task, and also gluing the bowl halves together, I used water clean-up Liquid Nails. Note that this glue was also used to seal the ‘water drainage hole’ provided in the original bowl.





Fig.14. Now is also the time to feed the cable through a hole drilled in the bowl, and seal it with further glue. Either solder the wires to the woofer's terminals or equip the cable with push-on terminals to make this connection. I chose to mount the crossover on the rear of the enclosure, but it could also be mounted inside.



Fig.15. This photo shows two steps. The first is that polyester quilt wadding has been placed around the inside of the lower bowl. Ensure that there is enough projecting upwards from the lower bowl so that when the two bowls are glued together, the wadding covers the inside surfaces of the upper bowl as well. Also ensure the rear of the driver and the port are not blocked by the wadding. The second step is to glue the two halves together. Use a generous amount of glue around the rim of the lower bowl. The upper bowl is then carefully lowered over the lower bowl, ensuring the wadding goes inside the upper bowl as it is lowered. (This job is best done by two people.)

Fig.16. The bowls are pushed together and then a wet finger used to smear the glue around the join, ensuring that the gap is filled. A damp cloth is then used to carefully remove the surplus glue. (The glue must be of the water clean-up type!) Note the chalk witness line (arrowed) that shows the correct alignment of the bowls as they are joined. This line is made earlier when the best rotational fit is found – because their lips aren't dead-flat, the bowls fit together better in some orientations than others.



Fig.17. The tweeter is mounted below the main enclosure. I could have run the tweeter cable within the square tube, but in normal use the cable is not as visible as it is here. The physical position of the tweeter makes a substantial difference to the sound – it must be as far forward as the main driver.



Fig.18. (above) The next step is to mount the crossovers on the rear 'flat'. The crossover was glued into position just below the port.



Fig.19. (right) The stand shown here was made from square tube. You can make any type of stand you wish – but the speaker must be off the ground to work at its best. (Also, when you are buying the pots, check out the available pot stands!)

# Circuit Surgery

Regular clinic by Ian Bell

## Differential amplifiers

**R**ecently, on EEWab's forum, Robinson-Constantin Chera posted a question asking about simulating an amplifier circuit, writing: 'I need to implement the following circuit [Fig.1] in LTspice but I don't know what  $V_{CM}$ ,  $V_g$ ,  $V_{CC}$  and  $C$  infinite are... Can you help me with the symbols for it?'

This is a basic operational amplifier (op amp) type circuit; or more specifically, the initial gain stages of an op amp without the power-amplifying output stage. The circuit is typical of those designed for implementation as integrated circuits (ICs), where transistors are used wherever possible and resistors are kept to a minimum. The amplifier only uses one resistor (R2) the other resistor in the schematic (R1) is a load and the capacitor ( $C_\infty$ ) is also part of the load. Circuits like this can look like an impossible mass of transistors if you are not familiar with the various building blocks which are used – so Fig.2 highlights the various sections.

The following outlines the circuit's structure (also refer to Fig.2) – if the terminology here is not all familiar, don't worry because we will explain its operation in more detail later. The amplifier has two stages. The first stage

comprises a differential amplifier formed by Q1 and Q2, biased by the current source formed by Q6 and Q7, and connected to an active load formed by Q3 and Q4. Q6 and Q7 form a current mirror, with Q6 providing the reference for Q7 to deliver the bias current to the differential amplifier. The second stage is a common-emitter amplifier using Q5, for which Q8 is an active load. Q8 is a current source to provide bias and act as a high resistance load; like Q7 its reference is provided by Q6.

We discussed the common-emitter amplifier with active loads in a recent *Circuit Surgery* article (PE, December 2019) so we will focus on the differential amplifier in this article.

### Spicing up the circuit

Robinson-Constantin posted a couple of LTspice schematics on the forum and received feedback. We will not look at those specifically, but will discuss some general issues about setting up this (and similar circuits) for simulation. The schematic in Fig.1 is a typical 'textbook' circuit (we will refer to it as such, although of course the source may be a web page). The aim of such circuits is often to explain operating

principles, and some things may be left out to simplify the explanation or focus on a particular aspect, which may lead to problems with simulation. Textbook circuits may be idealised to facilitate a discussion of key points without getting bogged down in complexities.

SPICE can simulate highly idealised circuits, but the assumptions may not match reality, particularly with active devices such as transistors, which again, may cause problems. This will be more likely if 'real' transistors are used in the simulations (models of actual devices), as Robinson-Constantin did. Default models match NPN and PNP transistor characteristics, which is unlikely with real device models – the circuit may 'unbalance' and fail – typically one or more transistors may get stuck in saturation. Similar issues were discussed in the December 2019 article on active loads. Even the default transistor models may not give the desired results without some tweaking to match what is implied by any assumptions.

Before worrying about these things, you need to set up the schematic – copying the basic schematic from the textbook is probably straightforward, but you may need to add components

 


Fig.1. Robinson-Constantin Chera's amplifier circuit.

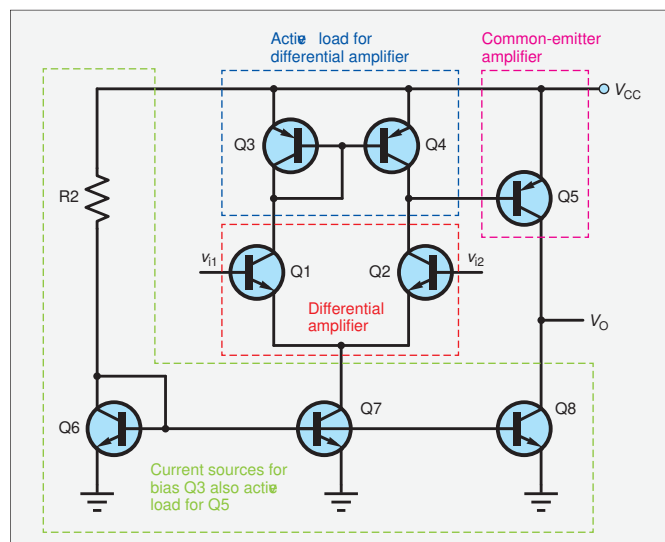


Fig.2. The circuit in Fig.1 with the various building blocks identified.



to account for the input signals, power supplies and loads. Robinson-Constantin asks about  $V_{CM}$ ,  $V_g$  and  $V_{CC}$  – these are the inputs signal ( $V_{CM}$ ,  $v_g$ ) and supply ( $V_{CC}$ ). The value of  $V_{CC}$  was not specified in the original post, but later 10V was used.

It is often a good idea to simulate circuits with a load, even if the value is idealised (eg, to a very large value) while the basic operation is confirmed. Changing the load's value will provide insight to the circuit's performance. In Fig.1, R1 is the load and  $C_\infty$  is a coupling capacitor which is chosen to have a much lower impedance than R1 at the frequencies of interest. If this condition is met then the specific value is generally not very important in a simulation.

In textbooks, supplies are often just labelled (eg,  $V_{CC}$  in Fig.1), but for a simulation you will need to put voltage sources on the schematic to account for each power supply – in this case there is only one, but split supplies are common, and some circuits have multiple supply voltages.

## Differential signals

The circuit in Fig.1 is a differential amplifier, so it has two inputs and we can use two voltage sources in the simulation to set up the input signal. Differential signals are carried on two wires, so the signal of interest – the signal we want to amplify – is the voltage between the two wires. For example, this could be 1mV, but the individual voltages could be -0.5mV and +0.5mV or 1.9995V and 2.0005V, or an infinite number of other possibilities. The voltage difference does not completely describe the situation, we also need to specify the average value of the two voltages, called the common-mode voltage, which is 0V and 2V respectively in the two examples.

In Fig.1 the common-mode voltage is applied to the two inputs with two equal  $V_{CM}$  DC voltage sources. Having established the common-mode voltage, the wanted signal – the difference – can be applied using a signal voltage source on one of the inputs. Exactly the same setup can be used in the simulation, but actually only one SPICE voltage source needs to be used per input because one can be set to be DC at  $V_{CM}$  and the other to be a sine wave source of amplitude  $v_g$  with a DC offset of  $V_{CM}$ . Alternatively, we can use two DC-plus-sine sources with 180°-out-of-phase sinewaves of the same frequency and half the amplitude of the desired differential input signal.

Differential-input circuits such as op amps can only operate over a limited range of common-mode voltages, and the circuit in Fig.1 is no exception. We must use a suitable value and 0V might seem like a simple option, but

it will not work for Fig.1. Unlike many basic op amp examples, which use a split positive and negative supply with 0V in the middle, the circuit in Fig.1 operates on a single supply, so  $V_{CM} = 0V$  would switch off the transistors in the amplifier – it would not work. We need  $V_{CM}$  to be about half the supply voltage for optimal operation. Similarly, we need to set a suitable value for  $v_g$ , which we will discuss later.

## Current sources

As indicated above, in ICs, circuits based on transistors are typically more economical and provide better performance than using resistors. Basic transistor amplifiers use resistors (for example, a potential divider connected to the base) to set the operating point – the current flowing in the transistor with no signal present. Instead of using resistors, the operating point can be set by using a circuit which sets up a constant current, equal to the operating point current, into the transistor. During operation the transistor's total current will vary around this point as the signal changes, just as it does with resistor-based biasing.

The circuit in Fig.1 uses a basic current source – a two-transistor current mirror, as shown in Fig.3, where the transistors have been labelled to match their role in Fig.1. The base-emitter voltages ( $V_{BE}$ ) of the two transistors are exactly equal because they are connected directly together, so if the transistors are identical, and have the same environmental conditions (in particular their temperatures are equal), then the currents in both devices, which are controlled by  $V_{BE}$ , must be equal. It follows that two currents  $I_{in}$  and  $I_{copy}$  in Fig.3 are *almost* equal. They are not exactly equal because some of  $I_{in}$  is diverted to provide the base currents, but this is typically a very small proportion (typically 1/50 to 1/100 or less), so values are very close. If we apply a current ( $I_{in}$ ) to Q1 we get the same current flowing in Q2, thus the circuit can copy, or 'mirror', a current from one part of a circuit to another.

 


Fig.3. The basic matched-transistor current mirror.

Transistors with identical characteristics and environment are referred to as 'matched'. They are often used in IC designs, where designers can use layout techniques to ensure the transistors are closely matched. For discrete designs, matched transistors in a single package are available.

In the circuit in Fig.3, Q6 is 'diode connected' – the base and collector are shorted so the transistor acts as a diode (the base-emitter junction). It is easy to establish a fixed current in Q6 by connecting the collector to a fixed voltage via a resistor – exactly as in Fig.1, where the collector of Q6 is connected to the supply via R2. This will fix the  $V_{BE}$  of Q6 and Q7 and cause a fixed current to flow in Q7 ( $I_{out}$ ). Thus, Q7 acts like a constant-current source with one end connected to ground.

As just discussed, Q6 and R2 provides the reference  $V_{BE}$  to set the current in Q7. Within reason, we can connect more transistors in the same way and get further copies of the reference current in Q6. This is done in the circuit in Fig.1 – Q8 provides a second copy of the reference current. Transistors can only be added 'within reason' because each diverts more base current from the reference and makes it more difficult to ensure they are all matched.

## Differential amplifier

When investigating a circuit with multiple blocks it can be useful to simulate individual sections. The circuit for an LTspice simulation of just a basic differential amplifier is shown in Fig.4, this uses resistors instead of an active load to make it simpler (R1 and R2 in Fig.4 instead of Q3 and Q4 in Fig.1). Similarly, the bias is provided by an ideal current source rather than the circuit implementation in Fig.1. The circuit uses a  $\pm 15V$  split power supply (V3 and V4, to provide an illustration of this in LTspice, in contrast to the signal supply of Fig.1 (LTspice version shown later). The supply lines are VCC and  $-V_{EE}$  (labelled as nVEE). The input signal has 0V common mode as this is the middle point of the split supply.

The circuit in Fig.4 uses a custom transistor model (myNPN) based on the default LTspice NPN model. Only two parameters are changed the saturation current (IS) and the Forward Early voltage (VAF). The default is  $IS = 1.0 \times 10^{-16}A$ , but using  $1.0 \times 10^{-14}A$  brings the value closer to typical signal transistors. The key effect is to scale the base-emitter voltage to emitter current relationship, shifting the  $V_{BE}$  for a given collector current. We will look at Early voltage later.

Notice the symmetry of the differential amplifier – it is key to its operation

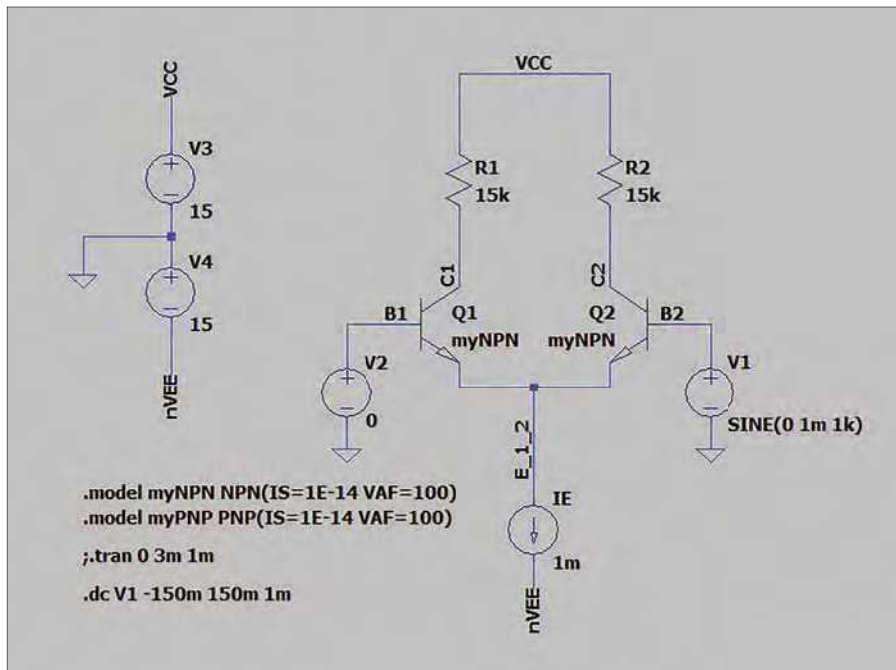


Fig.4- Basic differential amplifier LTspice schematic.

– to achieve it the two transistors must be matched. It has two inputs (B1 and B2 on Fig.4) and two outputs (C1 and C2, also on Fig.4). Small differences in the input voltages cause relatively large changes in the output voltages, also in a differential manner (ie, as one output voltage increases, the other will decrease by the same amount). We can, however, choose to use only one output ('single-ended' output). Key points to understanding the circuit's operation are: first, a transistor's collector and emitter currents are very sensitive to changes in base voltage; and second, the emitters are connected to a constant-current source (IE).

The constant-current source means that the sum of the two emitter currents must

always be equal to IE. If the two base voltages are equal, and the transistors are exactly the same then it follows that IE will split equally between the two transistors; that is, they will draw the same base current, and their collector currents will be equal. Since the two collector resistors are equal the voltages dropped across them will also be equal (assuming there is no output current). If the two input voltages change together (a common-mode input signal) then the symmetry will not be disturbed, IE will still split equally between the two transistors. At first, though, it may seem that changing the input voltage must change the collector and emitter currents, but it does not have to because the emitter voltage is free to change,

whereas IE is fixed by virtue of the constant-current source.

The lack of response to common-mode inputs helps makes the design of very high-gain DC amplifiers possible. If the temperature of a single-transistor amplifier changes then the bias currents and voltages shift. In capacitively coupled (ie, AC) circuits this does not matter because the temperature changes are slow and are below the cut-off frequency due to the coupling capacitor. However, if there is no capacitive coupling then any changes in voltages due to temperature (or other forms of 'drift') are effectively indistinguishable from required low-frequency signals and will be amplified. If the temperature of a properly matched differential pair changes, however, both transistors are affected equally and there is no change in the output (the drift is a common-mode signal). The worst place to get drift is in the first stage, as the error is amplified by all subsequent stages; thus, having a differential pair as the first stage is a good way of reducing overall drift.

If we change the (still equal) input voltages by a large amount, then the circuit will cease to function as just described. For example, if we take the input voltages down to near the  $-V_{EE}$  rail then the current source may no longer function properly. This would determine the amplifier's common-mode input range.

The high sensitivity of the transistor's collector and emitter currents to base voltage comes into play when we make the voltages at the two inputs slightly different. This breaks the symmetry and causes a larger proportion of IE to flow in one transistor than in another. For example, if we increase VB1 slightly and decrease VB2 by the same amount then a greater proportion of IE will flow in Q1 than Q2. This will cause the voltage drop across R1 to be larger than that across R2, so VC1 will be lower than VC2. In op amp terminology, if we take a single-ended output from C2 then VB2 will act as the inverting input and VB1 as the non-inverting input.

## DC Sweep

It is useful to look at the relationship between the input voltage difference ( $V_{B2} - V_{B1}$ ) and voltages at the two collectors over a range of DC values for the input. We can plot this using a DC sweep simulation in LTspice. To do this, select the DC sweep simulation command, select the source as V1, set sweep type to linear and select the range (start and stop voltages) and the increment value. The simulator will calculate DC voltages in the circuit for all values of the selected source starting at the start

 


Fig.5. Plot of output voltages at the collectors vs input voltage difference (voltage between the bases) for the circuit in Fig.4.



 


Fig.6. Plot of differential input voltage (VB2 – VB1) and differential output voltage (VC2 – VC1) for the circuit in Fig.4.

voltage, stepping by the increment until the stop voltage is reached. Stepping V1 by 1mV from –150mV to +150mV and plotting the voltages at C1 and C2 produces the result shown in Fig.5.

Fig.5 shows that differences over a few tens of mV result in most of IE flowing in one or other of the two transistors. Over a large input difference range the response of the circuit is exponential, but in the range of a few mV difference between the inputs the change in the output voltage is near-enough directly proportional to the input difference (the central part of the curves in Fig.5 are straight). So, we have a linear differential amplifier for small input voltage differences.

The voltage gain of the circuit in Fig.4 (difference-in to difference-out) is given

by  $g_m R_C$  where  $R_C$  is the collector resistor value (equal to both R1 and R2).  $g_m$  is the transconductance gain of the transistor – the ratio of collector signal current (output) to base-emitter signal voltage (input). People are generally more familiar with  $\beta$  (or  $h_{fe}$ ) as the transistor gain – this is the current gain, but using transconductance is often more convenient when we are dealing with a voltage input.

We often assume that  $\beta$  is fixed at 100 if we do not have more specific information, and indeed the default transistor model in LTspice uses this value.  $g_m$  is more complex in that it varies with bias current, so we can't assume a fixed value. Specifically,  $g_m = I_{CQ}/V_T$  where  $I_{CQ}$  is the bias or quiescent collector current and  $V_T$  is the 'thermal

voltage', a term which occurs in many semiconductor equations.  $V_T$  varies with temperature but is about 26mV at 27°C – a commonly used default value in rough calculations (27°C is also LTspice's default temperature). For the circuit in Fig.4,  $I_C$  is  $I_E/2 = 0.5\text{mA}$ , so  $g_m = 0.0005/0.026 = 19.2\text{mS}$  ( $g_m$  is current/voltage which is 1/resistance, which is measured in siemens, symbol S). The gain is therefore  $0.0192 \times 15,000 = 288$ . Knowledge of the expected gain and the linear input range indicated by Fig.5 informs the choice of input signal amplitude for a transient simulation. 1mV is used in Fig.4. The result is shown in Fig.6 – the output amplitude is 270mV, so the gain (270) is close to our rough calculation. Fig.6 shows a plot of voltage differences – note the syntax for the waveform  $V(X, Y)$  is the voltage at X measured from Y. Such plots can be obtained by right-clicking on wire X and selecting 'Mark Reference' from the menu, then clicking on Y.

The  $g_m$  equation shows that the choice of bias current from the current source influences the gain of the circuit. Running the circuit at a higher bias current provides more gain but has other effects too. Power consumption will be higher at higher bias currents and a transistor's base-emitter resistance is dependent on bias current. Increasing operating currents result in a proportional decrease in base-emitter resistance and hence reduced differential input resistance. This will need to be considered in a real design but will not affect the simulations discussed here as the inputs are driven by ideal voltage sources.

### Active load

The gain of the circuit in Fig.4 can be increased by increasing the collector resistors as well as increasing the bias current; however, this also has its limiting factors. The output voltage with no signal present is  $V_{CC} - R_C I_E/2$ , the supply minus the voltage dropped by the resistor with the bias current flowing through it. Increasing  $R_C$  reduces this voltage, but it cannot go much below 0V or Q1 and Q2 will start to saturate (the emitters are at  $-V_{BE}$ ). This limits the maximum  $R_C$  at a given bias current. Increasing  $V_{CC}$  could compensate, but this is likely to be constrained by the requirements of other

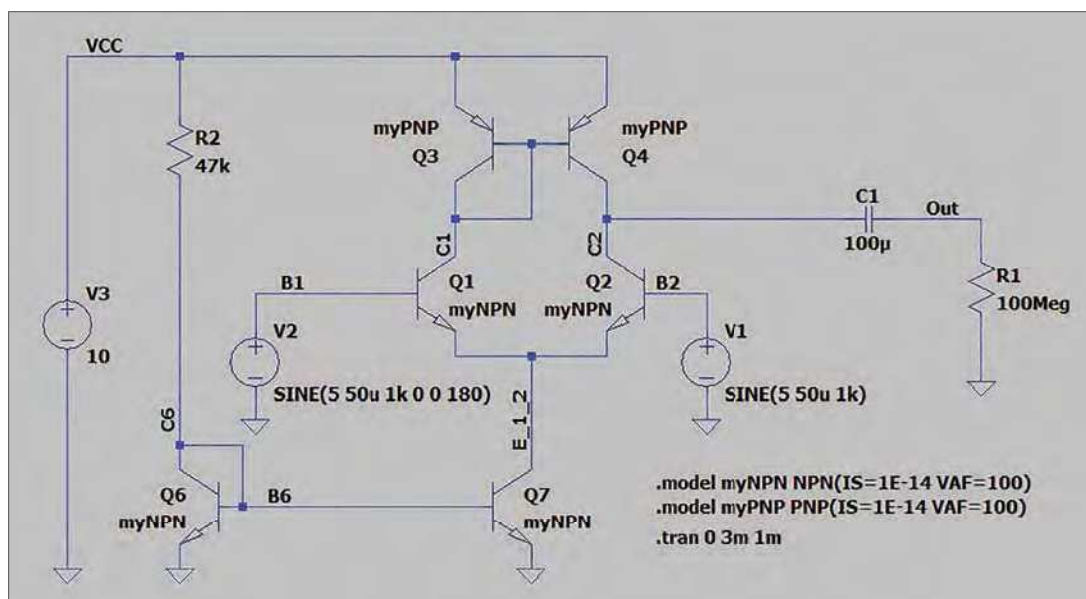


Fig.7. LTspice schematic for the first stage of the circuit in Fig.1.

 


Fig.8. Plot of differential input voltage (VB2 – VB1) and output voltage (Vout) for the circuit in Fig.7.

circuitry, and realistically cannot be very large. The solution is to use an active load, as in the circuit in Fig.1, which has Q3 and Q4 in place of the collector resistors. Active loads allow bias currents to be set to any reasonable level while presenting an effective resistance value equal to the transistor's output resistance, which can be as high as megaohms.

Q3 and Q4 in Fig.1 form a current mirror like that in Fig.3, except using PNP transistors. Recall the discussion on the symmetry of the differential amplifier. If we assume that the current mirror is ideal, then with no differential signal present (equal base voltages for Q1 and Q2) the circuit's balance is preserved. Q1's and Q2's collector currents are both  $I_E/2$ . Q1's collector current acts as the reference for the mirror and is copied from Q3 to Q4 where it exactly matches Q2's collector current. However, if we apply a voltage difference, then Q1's current copied to Q4 will not match the current in Q2. We cannot have two different currents in the same wire, so what happens? The answer is that the transistors are not perfect current sources and have some resistance between collector and emitter, referred to as their output resistance ( $r_o$ ). The difference between Q4's and Q2's collector currents will flow in their output resistances. The resistances of the two transistors are in parallel as far as this difference current is concerned, so the effective value is the parallel combination of Q2's and Q4's output resistance, which is  $r_o/2$ , assuming they are matched.

Comparing this with the gain formula for the circuit in Fig.1 indicates a

possible gain of  $g_m r_o/2$  but the current delivered to the output is twice that of the circuit in Fig.4 because the current from Q1 is mirrored to the output (at C2), doubling the potential differential gain to  $g_m r_o$ . However, although the differential amplifier with active load is symmetrical in current terms, the diode-connected transistor Q3 presents a low resistance, so the voltage signal at C1 in Fig.1 is small. Therefore, we use the single-ended output from C2, which provides half the gain compared to differential output (if it were available), so the gain is  $g_m r_o/2$ .

### Early voltage

The value of a transistor's output resistance depends on a parameter called the Early voltage ( $V_A$ ); specifically,  $r_o = V_A/I_{CQ}$  where  $I_{CQ}$  is the collector bias current. This is like the  $g_m$  and base-emitter resistance discussed earlier in being dependent on bias current. The default value for  $V_A$  in calculations is typically 100V, but for the default transistor models in LTspice it is infinite, so simulation results will not match expectations unless this is changed. Therefore, the Early voltage (VAF parameter) has been set to 100 in the simulations used here. The value of  $r_o$  for the circuit in Fig.4 is  $100/0.0005 = 200k\Omega$ , which does not have much effect in parallel with  $R_C$  of  $15k\Omega$ , but including it gives the gain as 268, which is closer to the simulation.

Finally, we get to the simulation of the input stage of Fig.1. The LTspice schematic is shown in Fig.7. Here we have somewhat arbitrarily chosen a

current of  $200\mu A$  for the mirror reference ( $100\mu A$  bias each for Q1 and Q2), R2 is set using  $(V_{CC} - V_{BE})/I_{ref} = (10 - 0.6)/200\mu A = 47k\Omega$ . With this bias current we get  $g_m = 100\mu A/0.026 = 3.85mS$  and  $r_o = 100/100\mu A = 1M\Omega$ , so the gain is  $1M\Omega \times 3.85mS/2 = 1923$ . Simulation results are shown in Fig.8. The simulated gain is about 1970.

The gain of the circuit in Fig.7 is strongly dependent on the load resistance – driving a low resistance will dramatically reduce the gain. This is why an extremely high load resistance was used here. The output resistance is around  $500k\Omega$ , so setting R1 to this value will half the output voltage. The second stage in Fig.1 presents quite a low resistance load to the differential amplifier, so the gain from the input to Q2's collector in circuit in Fig.1 will be much lower than the circuit in Fig.7. However, the second stage can add significant gain, so overall the circuit can have a higher gain than with just the single stage. Despite this, it can be argued that the circuit in Fig.1 wastes much of the potential gain from the differential amplifier, and many op amp designs use circuits with a much higher input resistance for the circuit directly after the differential stage.

### Simulation files

Most, but not every month, LTspice is used to support descriptions and analysis in *Circuit Surgery*. The examples and files are available for download from the PE website.



# Make it with Micromite

Phil Boyce – hands on with the mighty PIC-powered, BASIC microcontroller

## Part 20: Ultrasonic obstacle avoidance

 


Fig.39. By adding an ultrasonic distance module, the *MRB* can be programmed to avoid crashing into objects.

**W**e now come to the last part of our *Micromite Robot Buggy (MRB)* mini series. The objective this month is to enable it to roam autonomously without crashing into anything, which means it will need to have some form of obstacle avoidance mechanism. So, this month we are going to show you how to implement this feature by using a low-cost ultrasonic distance sensor mounted on the front of the *MRB* (see Fig.39). This will require us to make a simple hardware modification to the TFT module that we originally assembled back in *Part 15*. For our *MRB* program code to interface with the ultrasonic distance sensor, we will use the Micromite *DISTANCE* command. As usual, MMBASIC greatly

simplifies everything for us; in this case, the *DISTANCE* command communicates directly with the ultrasonic sensor, returning a numeric value that represents the distance (in centimetres (cm)) to an object positioned in front of it.

We will start this month by working through the hardware modification to the TFT module, and then we will test that it works correctly by writing a five-line demo program that incorporates the *DISTANCE* command. This demo program will perform the function of a basic, yet highly accurate *Digital Tape Measure* – a great little project in its own right. We will then take this demo program and modify it slightly so that it forms the basis of our *MRB* obstacle avoidance code.

### Concept of obstacle avoidance

The ultrasonic (US) distance sensor hardware, along with the MMBASIC *DISTANCE* software command, enables our program code to measure the distance (in cm) to any object that is in front of the *MRB*. By continually measuring the distance value while the robot is moving forward, the *MRB* program code can be made to automatically ‘apply the brakes’ should the distance value fall below a certain threshold value.

### Micromite code

The code in this article is available for download from the *PE* website.

 


Fig.40. The low-cost Ultrasonic distance module used in the MRB has just four pins. Two pins supply 5V power, and the other two pins connect directly to Micromite I/O pins.

For example, consider setting a threshold value in the *MRB* code to 10cm. Whenever the distance measured is greater than this 10cm threshold, then the *MRB* can be allowed to continue to move forward without the risk of hitting anything. However, as soon as the measured distance falls below the 10cm threshold, then the program code can be written to automatically stop the *MRB* from moving forward, and hence prevent it from crashing into an object.

This distance-measuring method of obstacle avoidance is much better than implementing some fancy form of front-mounted mechanical ‘bumper-switch’ (as used in some other mobile robots). Implementing the bumper-switch method means that the robot has to actually crash into an object first in order to apply the brakes. For this reason, we consider the bumper-switch method as *collision detection* rather than *obstacle avoidance*.

### The HC-SR04 module

The US distance sensor module that we are using here is the readily available HC-SR04. It comprises a US transmitter, and a US receiver, along with just a few support components. It has four pins presented on a 0.1-inch header (see Fig.40). Two pins supply the required 5V power, and there are two control pins. The control pin marked ‘TRIG’ is an input trigger, and the ‘ECHO’ control pin is an output. The module operates as follows: when a pulse is sent to the TRIG input pin from an external device (in this case from the Micromite) the US transmitter sends out a short pulse of US waves. The US receiver then waits for a short period of time to see if it can detect these US waves being reflected (ie, bounced) off an object directly in front of it. If it sees a reflection, then the ECHO output pin sends out a pulse to an external device (the Micromite).


 
 


Fig.41. A small piece of stripboard acts as a mini-riser board. This allows the US module to have an unobstructed view over the animated LED eyes.

 

The time between the transmission of the US wave and the reception of any reflected waves (the time between sending a TRIG pulse and receiving the ECHO pulse) will infer the distance to the object – much like the way radar operates using electromagnetic waves. The Micromite performs all of the timing calculations from within firmware (whenever the `DISTANCE` command is used) and conveniently returns a calculated distance as a numeric value – more on this later.

### Circuit diagram

The circuit connections for adding obstacle avoidance to the *MRB* is also shown in Fig.40. As always, it is just a matter of connecting the external hardware (ie, the US distance sensor) to the relevant power pins and Micromite I/O pins. It really could not be any simpler as there are only four physical connections required. Out of the four connections, only two are required to be connected to I/O pins on the Micromite. Checking which Micromite



pins are still available for use on the *MRB*, we only have pins 17 and 18 that are currently unassigned to anything – therefore we will use these two I/O pins. Hence the four connections that need to be made are:

- Vcc connected to 5V (the 5V pin is physically to the right of Micromite pin 15)
- TRIG connected to Micromite pin 17
- ECHO connected to Micromite pin 18
- GND connected to 0V (which conveniently is on Micromite pin 19).

All four of the US distance sensor module pins can be brought together into a 4-way header on the TFT module; however, we will need to make a slight modification to the TFT stripboard first. We must also ensure that the US distance module is physically mounted in such a way that it can face forwards on our *MRB* without being impeded by the animated eyes (if installed). This we can do by adding a new mini-riser board (see Fig.41).

### Modifications to the TFT module

The assembly of the TFT module was discussed in *Part 15* (*PE*, April 2020). Referring back to Fig.5 from that article, you can see that the Micromite pins that are required for the US module (pins 17, 18, and 19) were not included in the header (J2) that ultimately plugs into the *MKC*. Therefore, the main modification to the TFT module requires the addition of these three downward-facing pins into J2. The stripboard layout from *Part 15* is recreated here in Fig.42, and it has been updated to show the required US modifications in red. As can be seen, in addition to the three pins for J2, there are seven track cuts, four wire links to insert, and also the soldering of a new mini-riser board via a 4-way right-angle header pin (see Fig.41).

Begin by making the seven track cuts on the *MRB* TFT module; ensure you follow the usual practice of marking out first, then checking the positions at least twice. Once the cuts are made, do a quick visual check to ensure that no copper swarf is bridging across neighbouring tracks.

Next, insert the three downward-facing pins into the plastic housing of J2 into positions V15, V16 and V17. These three new pins will ultimately be inserted into the *MRB* daughterboard, so do check that their length matches the existing downward-facing pins that are on the TFT module.

Next, install the four jumper links, as shown in Fig.42; again, make sure you check for and remove any accidental solder bridges with neighbouring tracks.

### Mini-riser board

The mini-riser board is built from a small piece of stripboard 4-tracks wide, by 10-holes long (high), as shown in Fig.41. To this we need to solder a 4-way socket (that the US distance module plugs into), and a 4-way right-angle pin header (to solder the mini-riser board directly to the TFT module). Note that there are no track cuts or wire links needed on the mini-riser board.

Begin by cutting out the required size stripboard and solder the 4-way socket and the 4-way right-angle connector as shown in the various photos in Fig.41. Perform a visual check and ensure you remove any solder bridges between neighbouring tracks. Last, carefully solder the mini-riser board to the TFT module into positions A11-A14 (highlighted in red in Fig.42).

It is now time to mount the modified TFT module (complete with the new mini-riser board) onto the *MRB* daughterboard. Insert the US distance sensor into the 4-way socket, ensuring the US transmitter and receiver units are facing forwards. Plug in all relevant modules so that the *MRB* can be powered

up as usual. We will now load a simple test program to check that the US distance sensor is working correctly.

### Testing the US distance sensor

Begin by downloading the file **MRB\_DigitalTapeMeasure.txt**, and then install it onto your *MRB* in the usual manner. On running the program, you should see the TFT screen clear to a blue screen with a thin green border. In the centre of the screen there should be a number (displayed in white). This number represents the distance being measured by the US sensor.

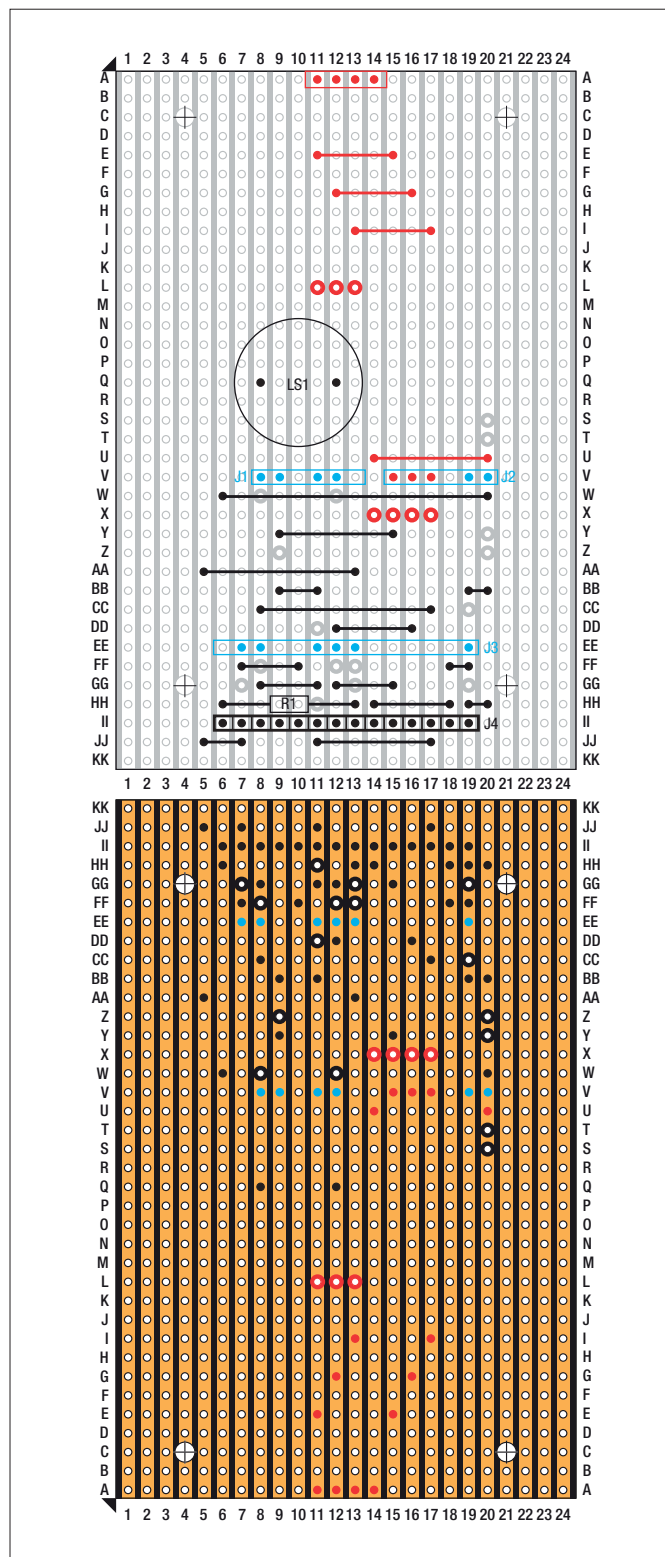


Fig.42. The original *MRB* TFT module from Part 15. The required US modifications are highlighted in red.



Fig.43. Side view of the completed *Micromite Robot Buggy*.

If the number displayed is -2, then the Micromite is not seeing the US sensor correctly. If this happens, first check the US sensor is inserted correctly into the 4-way socket. If this is fine, then you will need to carefully check that all modifications made to the TFT module match Fig.42.

Once you observe a number on the screen other than -2, then position your hand in front of the US module so that the US waves can bounce off it (or use a book). Now move your hand back and forth in front of the US sensor and you should see that the number displayed on the TFT changes – increasing in value as you move your hand away from the sensor, and reducing in value as you move your hand towards the sensor. If this appears to work, then point your robot towards a nearby wall and you should see the number remain reasonably static. Now use a tape measure to measure the actual distance between the US sensor and the wall – you should find the displayed number on the TFT is within a couple of centimetres of what you measured. If not, then you may need to slightly alter the angle of the US sensor so that it is pointing at right-angles to the wall.

If all is working as described above, point the *MRB* towards various other flat objects and check the accuracy of the distance shown on the TFT. Note that any object made from a soft material (such as a cushion or an item of clothing) may not be able to reflect the US waves and hence will not be detected; therefore, ensure you use relatively solid objects for this test, and you should find that your *MRB* is now operating as an accurate digital tape measure.

### The DISTANCE command

Press `Ctrl_C` to stop the program running, and type `EDIT` so that you can take a look at the code. The Main Program comprises of just five lines of code, as follows:

```
DO
  d=DISTANCE (17,18)
  TEXT ..... , ...STR$ (INT (d) ) ... , .....
  PAUSE 100
LOOP
```

As you saw when you ran the **DigitalTapeMeasure** program, the above code continually displays the measured distance on the TFT screen. The code is just a simple `DO...LOOP`

with the magic happening in the line: `d=DISTANCE (17,18)`. The format of the `DISTANCE` command requires two values to be passed – these are the pin numbers that connect to the `TRIG` pin and the `ECHO` pin respectively. The `MMBASIC` Firmware will then automatically send a pulse to the `TRIG` pin (output), and will wait for a reflection pulse on the `ECHO` pin (input). The time taken to see any reflected pulse is then converted into a numeric value that represents the true distance (in cm).


In the above code, this numeric value is loaded into variable `d`. Note that the `DISTANCE` command automatically configures the two Micromite pins to the relevant I/O state – in other words, there is no need to use the `SETPIN` command to configure pins 17 and 18.

The second line of code in the `DO...LOOP` uses the `TEXT`, `STR$ (...)` and `INT` commands to display the integer value of `d` on the TFT (effectively the integer value drops any decimal places making an easier-to-read display).

Finally, the `PAUSE` command is included in the `DO...LOOP` to prevent the `TRIG` pulse from being generated too soon after the previous measurement was triggered.




## PoKeys Connect, Control

 

- USB
- Ethernet
- Web server
- Modbus
- CNC (Mach3/4)
- IO
- PWM
- Encoders
- LCD
- Analog inputs
- Compact PLC

## Stepper motor drivers Drive

 

- up to 256 microsteps
- 50 V / 6 A
- USB configuration
- Isolated
- up to 32 microsteps
- 30 V / 2.5 A

## PoScope Mega1+ PoScope Mega50 Measure



- up to 50MS/s
- resolution up to 12bit
- Lowest power consumption
- Smallest and lightest
- 7 in 1: Oscilloscope, FFT, X/Y, Recorder, Logic Analyzer, Protocol decoder, Signal generator

Scrolling further down the code into the subroutines section, you will see that there are quite a few lines of code, each containing many numbers. These numbers are part of what is known as a 'CFunction'. This topic is well beyond the scope of this series; however, in essence, they contain the code that adds the `DISTANCE` command into MMBASIC. For more information, refer to the [Distance.pdf](#) file (available for download from the September 2020 page of the *PE* website)

So, in summary, to measure the distance of an object from the sensor, and to then load the result into a variable, you simply use the command syntax: `variable = DISTANCE(TRIG_pin_number, ECHO_pin_number)`

### Adding obstacle avoidance to the MRB

We will now modify the code from last month ([MRB\\_IR\\_Control.txt](#)) to include obstacle avoidance. Currently, if you run the [MRB\\_IR\\_Control](#) program and press the blue arrow button on the 44-button IR transmitter, then the *MRB* will move forward at the set speed. The *MRB* will continue moving forward until you either:

- Stop it
- Select turn (to the left or right)
- Or the *MRB* hits an object (in which case there is a chance the motors can be damaged by being put under too much stress).

Now download [MRB\\_IR\\_Control\\_with\\_ObstacleAvoidance.txt](#) (available from the September 2020 page of the *PE* website) and install it on your *MRB*. RUN the program and point your *MRB* towards a wall. Then press the 'Forwards' button on your IR remote and observe what happens. If all is well, your *MRB* will automatically stop short of the wall with a notification on the TFT screen, as well as an animated eye effect being displayed. However, you may feel more comfortable to be on standby just in case it does not stop!

This version of the program simply monitors the measured US distance whenever the *MRB* is moving forward. If this value is below a threshold distance, the *MRB* is made to stop (as discussed at the start of this article). As well as stopping the motors, we also call an animated eye-effect subroutine, as well as displaying a warning message on the TFT screen.

As usual, the Micromite's program code is commented throughout, so do take a look and have a go at altering the stopping distance (and see how close you can get it to stop in front of objects before there is a collision).

The code to do all of the above-mentioned features should be reasonably familiar to you by now, but if not, then please read the comments included in the code to help you understand how it all works.

### Allowing the MRB to explore by itself

Finally, this month we will run one more program that you should then use as a basis to write your own robot code. Download [MRB\\_Self\\_Explore.txt](#) from the September 2020 page of the *PE* website and install it on your *MRB*. This program will allow your *MRB* to roam freely without crashing into large objects. The IR transmitter is used only for two things: to start exploring (press the blue forward arrow button) and for the emergency stop (press any other button on the IR transmitter).

RUN the program and press the blue forward arrow button. This will make your *MRB* move and it will appear to go off and roam around by itself. Any time you feel it necessary to apply the emergency brakes, simply press any other button on the IR remote – this may be necessary if the *MRB* has run into a small undetected object.

The point of this program is really for it to be the basis for you to create your own *MRB* functionality. By now you know how to write code to:

- Move the *MRB*
- Avoid the *MRB* hitting objects
- Draw and animate the eye images
- Make beeping sounds (and play simple tunes)
- Write to the colour TFT touch screen
- Control via an IR remote control (or from your Terminal program via Bluetooth).

The design concept of the *MRB* was to bring together many of the topics that we covered in the *Make it with Micromite* series.

Do please have a go at writing your own *MRB* program code. Start simple, and continually add new features. Any time you feel you're struggling then simply drop me an email and I will gladly help you out.

### Next month

That's enough *Robot Buggy* for now – but we may return to it. In the next issue we will move on to a brand new topic: Micromite UART communication. Until then, have fun, and please do stay safe!

Questions? Please email Phil at: [contactus@micromite.org](mailto:contactus@micromite.org)



## Flashing LEDs and drooling engineers – Part 7

**W**ell hello there! How nice it is to see you again. It probably won't surprise you to hear that things have been progressing apace here at Maxfield Manor with regard to my  $12 \times 12$  ping-pong ball array. I should perhaps warn you that we will be leaping from topic to topic with the agility of young mountain goats in this column, so please take a moment to make sure you're wearing appropriate clothing before we proceed further.

### Blinded by the light

Let's commence by reminding ourselves that each of our pixels (ping-pong balls) contains a tricolour LED called a NeoPixel. Furthermore, each NeoPixel contains red, green, and blue sub-pixels, each of which can be driven with 256 different levels from 0 (0x00 in hexadecimal = 0% = fully off) to 255 (0xFF in hexadecimal = 100% = fully on).

I don't know about you, but whenever I'm working on a project like this, questions pop into my mind and I realise that there are all sorts of things I don't know. For example, suppose we were to light up one of our pixels 100% red. Now suppose we were to light up an adjacent pixel with 100% green and 100% blue, resulting in cyan. Does this mean that the cyan pixel is twice as bright as the red pixel? In turn, does this mean that we should really light the green and blue sub-pixels at 50% (128 in decimal = 0x80 in hexadecimal) so as to achieve the same brightness as the red pixel?

Similarly, if we were to take another pixel that's adjacent to our original red pixel and light all three sub-pixels to generate white, does this mean that we should really set the red, green, and blue sub-pixels to 33% (85 in decimal = 0x55 in hexadecimal) in order to achieve the same brightness as the red pixel?

I thought it might be a good idea to test things out. As you may recall from my previous column (*PE*, August 2020), our NeoPixels are connected together as a single string numbered from 1 to 144 (there's also a sacrificial pixel 0, which we're using as a voltage-level converter, but this plays no part in the visible portion of the display).

We're considering our array to be an (X,Y) matrix with both X (horizontal) and Y (vertical) positions numbered from 0 to



That's what I call a pixel array... and the shirt's not bad either!

11, and with pixel (0,0) in the bottom left-hand corner. Also, we created a simple function called `GetNeoNum()`, which accepts X and Y values as arguments and returns the number of the corresponding NeoPixel in the string.

As a first test of this brightness/contrast conundrum, I created a simple sketch (program) that fills the outer pixels with 100% white and an inner  $4 \times 4$  square of pixels with 100% red (Fig.1a). Then we drop the surrounding white to 33%. Next, the sketch fills the outer pixels with 100% red and the inner square with 100% white (Fig.1b). Once again, we subsequently drop the white to 33%. We then cycle back to perform the whole sequence over and over again. If you wish, you can download this sketch and peruse and ponder it at your leisure (it's file **CB-Aug20-01.txt** – available for download, along with the other three files discussed in this column, on the September 2020 page of the *PE* website). For your delectation and delight, I've also created a short video showing all of this in action (<https://bit.ly/2OG9lgg>).

As an aside, you may recall from an earlier column (*PE*, July 2020) that the creators of Adafruit's NeoPixel library provided two ways for us to specify the colour of a pixel. Let's suppose our string is called `Neos` and that we want to set the colour associated with pixel 42 to have red, green, and blue colour components of 128, 0, and 255, respectively (these would be 0x80, 0x00, and 0xFF in hexadecimal). If we wish, we can specify the colours individually using a statement like:

```
Neos.setPixelColor(42, 128, 0, 255)
```

Or:

```
Neos.setPixelColor(42, 0x80, 0x00, 0xFF)
```

 


Fig.1. First contrast test.



As an alternative we can specify all three colours together as a single numerical value using a statement like:

```
Neos.setPixelColor(42, 8388863)
```

where the number is specified in decimal, or:

```
Neos.setPixelColor(42, 0x8000FF)
```

with the number specified in hexadecimal. Using a single numerical value in hexadecimal makes our lives a lot easier, so that's what we'll do. This explains why you will see the colour definitions in my sketches looking something like the following:

```
#define COLOR_WHITE 0xFFFFFU
#define COLOR_BLACK 0x00000U
#define COLOR_RED   0xFF000U
#define COLOR_GREEN 0x00FF0U
#define COLOR_BLUE   0x0000FFU
```

Note that adding 'U' (or 'u') characters on the end of these values informs the compiler to regard them as being unsigned (see this month's *Tips and Tricks* column for more discussions on the difference between signed and unsigned values). Most of the time this won't be necessary, but every now and then...

Next, I started to wonder if my  $4 \times 4$  centre square was a tad small (16 pixels) in comparison to the surrounding area (128 pixels), so I decided to increase its size to  $6 \times 6$ . Fortunately, due to the way I created my original program, all I had to do to generate the new version was to change two definitions: `XY_CENTER_MIN` was changed from 4 to 3, while `XY_CENTER_MAX` was changed from 7 to 8. Once again, you can download this sketch (**CB-Aug20-02.txt**). And, once again, I've created a short video showing all of this in action (<https://bit.ly/2OG9lgg>).

Personally, I think the 33% white looks a bit washed out. My conclusion is that, if we were trying to use our array to represent images or to play extremely low-resolution videos, then we would probably vary the intensity of each sub-pixel to balance everything out. By comparison, in the case of our simple effects, we probably want to make everything as bright as possible, which – happily – is my default position anyway.

## Feeling random?

To give our effects an 'organic' feel, we're going to be using the C/C++ `random()` function, which accepts two arguments and returns a random result as follows:

```
result = random(min, max);
```

The `min` argument is optional. If this value is not specified, it will default to 0. This value is also *inclusive*, which means it may appear in the result. By comparison, the `max` argument is required and (for all sorts of reasons we won't go

into here) it's also *exclusive*, which means it won't appear in the result. Another way to look at this is to observe that when this function is called it will return a result between `min` and `(max - 1)`.

## A bit of a drip

For our first series of effects, we're going to imagine that our array is lying flat on the floor and that occasional drips of water – virtual raindrops, if you will – are randomly falling from the sky. Whenever a virtual drip lands on one of our pixels (ping-pong balls), that pixel will light up bright white for a short period of time.

You may find it advantageous to download the sketch associated with this effect (file **CB-Aug20-03.txt**) and reference it in conjunction with these discussions.

As you will see, we declare two integer global variables called `OldX` and `OldY`, which we will use to keep track of the (X,Y) coordinates of the last pixel that was lit up. We initialise both of these variables with random values between 0 and 11 in our `setup()` function.

Most of this sketch is self-explanatory. The interesting part is where we generate the (X,Y) coordinates associated with a new drip as follows (the +1s associated with the maximum values are there to offset the fact that, as we just discussed, the `random()` function treats its maximum argument as being exclusive):

```
do
{
    newX = random(MIN_X, (MAX_X + 1));
    newY = random(MIN_Y, (MAX_Y + 1));
} while (condition);
```

This loop will be executed at least one time, and it will keep on executing until its `condition` is met (ie, returns `true`). But what condition should we use? One alternative would be to say:

```
((OldX == newX) && (OldY == newY))
```

In this case, the loop will keep on executing until the new pixel is different from the old pixel, but there's nothing to prevent the new pixel from being horizontally or vertically adjacent to the old pixel.

Personally, I prefer a tad more differentiation, so I opted to swap the `&&` (logical AND) operator for the `||` (logical OR) operator and use:

```
((OldX == newX) || (OldY == newY))
```

This means the new pixel cannot be on the same row or column as the old pixel.

The only other things to note about this sketch are that we also use the `random()` function to vary the duration of the flashes associated with each of the drips and the gaps between drips. Also, the last thing we do at the end of each cycle is set the values of `OldX` and `OldY` to be the values of `newX` and `newY`, respectively. This means that the pixel we just flashed will be considered to be our old pixel the next time we pass through the loop. Do you even need to ask?! Yes, of course I've carefully crafted a video showing all of this in action (see: <https://bit.ly/2OG9lgg>).

## Do you believe in colour fairies?

When I was a little kid, I had a book that described how the red, yellow, and blue colour fairies spent the night repainting everything, which explained why all of the colours looked so bright and fresh each morning.

 


Fig.2. Subtractive and additive primary colours.

 


Fig.3. The colour wheel we will be using in our experiments.

This all made perfect sense to me, especially since I knew from school that the fairies could generate other colours by working together: red and yellow made orange, red and blue made purple, yellow and blue made green, and so forth.

Later, my teacher explained that red (R), yellow (Y), and blue (B) were primary colours. What she didn't say was that this was just one possible set of primaries, because the term 'primary colours' simply refers to a small collection of three or more colours that can be combined to form a range of additional hues, shades, tints and tones. For example, printers use cyan (C), magenta (M), and yellow (Y) inks as their primary colours. Furthermore, although it's possible to mix cyan, magenta, and yellow to form black, printers typically use a special black pigment. We use the letter K to represent this pigment because B could be confused with blue. This explains why we use the term CMYK when we're talking about printer ink.

Now, the thing about inks, paints and pigments is that they are subtractive in nature. One way to think about this is that we start with a white background illuminated with white light. The white background reflects all of the frequencies in the white light. When we start to add our colours, each colour absorbs (subtracts) some of the frequencies from the white light (Fig.2a). Furthermore, when inks, paints, or pigments are mixed together, they each absorb different frequencies. Basically, what we see is what's left over; that is, what isn't absorbed. When all of the colours are mixed together, they absorb all of the frequencies leaving us with nothing to see (ie, black).

By comparison, light is additive. The set of primary light colours with which we are most familiar are red (R), green (G), and blue (B). One way to think about this is that we start with a black room and add our primary light sources. Red and green add together to form yellow, red and blue add to form magenta, and green and blue add to form cyan. When they are all combined, red, green, and blue are perceived as white.

### Technicolor drips

The reason for our interest in primary colours is that the next version of our drip program is going to illuminate our pixels with randomly selected colours. Since we have red, green, and blue subpixels, each of which can be assigned values from 0 to 255, we have the potential for  $256 \times 256 \times 256 = 16,777,216$  ( $2^{24}$ ) different hues, shades, tints and tones.





# CRICKLEWOOD ELECTRONICS

Established 1981

**Your best bet since MAPLIN**

**Chock-a-Block with Stock**

Visit: [www.cricklewoodelectronics.com](http://www.cricklewoodelectronics.com)

Or phone our friendly knowledgeable staff on **020 8452 0161**

**Components • Audio • Video • Connectors • Cables**  
**Arduino • Test Equipment etc, etc**



Visit our Shop, Call or Buy online at:  
[www.cricklewoodelectronics.com](http://www.cricklewoodelectronics.com)

**020 8452 0161**

Visit our shop at:  
40-42 Cricklewood Broadway  
London NW2 3ET

Of course, some of these little rascals are going to be dim and lacklustre but – from our experiments in contrast at the beginning of this column – we know that we want our colours to be as bright and shiny as they can be. One way to represent colours is to use a colour wheel (Fig.3).

As we see, our three primary colours (red green and blue) can be combined to form three secondary colours (yellow, cyan, and magenta) and six tertiary colours (with more exotic names: flush orange, chartreuse, spring green, azure, electric indigo, and rose).

These 12 colours are the ones we will use in our sketch, which you can download if you wish ([CB-Aug20-04.txt](#)). If you compare this sketch to our previous version, you will observe that the only difference is that – as opposed to lighting our pixels with white – for each virtual drip we now use the `random()` function to select one of our 12 colour options. Once again, I've created a video showing all of this in action (<https://bit.ly/2OG9lgg>).

### Next time

I must admit that I do like the coloured drips featured in our last sketch, but simply turning our pixels hard on and hard off is not very subtle and lacks a little *je ne sais quoi*. One way in which we can add a *souçon* of sophistication is by fading the colour up, holding it steady, and then fading it back down again, so this is what we'll do in my next column. Until then, have a good one!

Cool bean Max Maxfield (Hawaiian shirt, on the right) is emperor of all he surveys at [CliveMaxfield.com](http://CliveMaxfield.com) – the go-to site for the latest and greatest in technological geekdom.

Comments or questions? Email Max at: [max@CliveMaxfield.com](mailto:max@CliveMaxfield.com)





In my previous tips and tricks column (PE August 2020), we noted that when people are first introduced to the C/C++ programming languages, one of the first data types to which they are introduced is the `int`, which stands for ‘integer’. We also noted that we may decide to declare our integers as being signed or unsigned:

```
signed    int John;
unsigned int Jane;
```

A signed `int` can be used to represent both positive and negative values, while an unsigned `int` can be used to represent only positive values. Interestingly enough, the C/C++ standards don’t explicitly define the size of an `int`. All they say is that an `int` should be a minimum of two bytes (16 bits). In the case of an Arduino Uno with its 8-bit data bus, the size of an `int` is indeed two bytes; in other computers it can be two bytes, four bytes, or more.

A 2-byte (16-bit) variable can be used to represent  $2^{16} = 65,536$  different patterns of 0s and 1s. In the case of a signed `int`, these patterns can be used to represent both negative and positive values in the range  $-32,768$  to  $+32,767$ . By comparison, in the case of an unsigned `int`, these patterns can be used to represent only positive values in the range 0 to 65,535.

## Hey, short stuff!

There are also short and long flavours of the `int`:

```
signed    short int Fred;
signed    long  int Bert;
unsigned short int Mary;
unsigned long  int Beth;
```

In the same way we assume a number like 42 to be positive without explicitly writing it as  $+42$ , the compiler will assume that an unqualified `int` is signed, which means we may omit the signed part of the declaration if we wish:

```
int        John;
short int Fred;
long  int Bert;
```

Similarly, if we declare something as being of type `short` or `long`, the compiler will happily assume that we are talking about integer values, so we may also omit the `int` part if we wish:

```
int    John;
short Fred;
long  Bert;
```

The C/C++ specifications state that the minimum size of a short `int` is two bytes (16 bits), while the minimum size of a long `int` is four bytes (32 bits).

## Fixing the width

It can be a tad disconcerting when one first discovers that the size of the different types of integers can vary from one machine to another. The reason behind this is to allow the compiler to make use of its knowledge of the targeted processor’s internal architecture to use optimal data sizes for that particular machine.

Things aren’t too bad if you are a hobbyist writing code for only one processor. However, depending on the size of the numbers you are trying to represent, problems may arise if you try to port your code from a machine that supports four-byte integers to one

whose integers are only two bytes in size, for example. In order to get around this, we can use the fixed-width integer types that have been available since the v11 release of C++; for example:

```
int8_t  Cuthbert; // Unequivocally 8 bits (one byte)
uint8_t Clarence; // Indubitably 8 bits (one byte)
```

There are also 16-bit (`int16_t` and `uint16_t`), 32-bit (`int32_t` and `uint32_t`), and 64-bit (`int64_t` and `uint64_t`) equivalents of these fixed-width types.

## A dangerous thing

‘A little knowledge is a dangerous thing,’ as the old saying goes. Suppose you are writing a program for an Arduino Uno and you know that the counter you are using to control a `for()` loop will only ever count up to 100. In this case, would you be better off using an `int8_t` (8 bits) rather than an `int` (16 bits), thereby saving a byte (8 bits) in memory? For example:

```
for (int8_t i = 0; i < 100; i++)
{
    // Do something cunning here
}
```

Generally speaking, the answer is ‘no’. The problem is that using a smaller variable in order to save memory may negatively impact the performance of your program. Unless you are intimately familiar with the workings of your compiler and the internal architecture of your processor, you are best advised to use an `int` and let the compiler use its detailed knowledge of the processor’s architecture to make optimal decisions for you.

Having said this, if you do have specific requirements, then by all means use the appropriate fixed-width types. In the case of the programs for my 12 × 12 ping-pong ball array project, for example, you will observe that I declare all of my colour values as being of type `uint32_t` (ie, unsigned 32-bit integers). The equivalent would be an unsigned `long` in the case of the Arduino Uno, but I prefer to be explicit in the case of these declarations.

## But wait, there’s more!

I come from the days where every memory location and every clock cycle were considered to be precious commodities. Computer magazines used to have columns of cunning tricks for doing things like swapping the upper and lower four bits in a byte in the least number of clock cycles or using the smallest number of instructions or consuming the least amount of memory.

Some designers of embedded systems are pushing the boundaries of the processors they’ve been instructed to use. In this case, they may decide to use the *minimum width* and *fastest minimum width* types that have been supported by C since 1999 (known as C99-compliant compilers); for example:

```
int8_t Bob;           // Fixed width signed
                       // 8-bit integer
int_least8_t Dan;     // Minimum width signed
                       // 8-bit integer
int_fast8_t Sam;      // Fastest minimum width
                       // signed 8-bit integer
```

Of course, there are unsigned versions of these types, along with 16-, 32-, and 64-bit variants, but I’d advise holding off on using these little scamps until you are 100% sure you are aware of any and all implications.

# PIC n' Mix

Mike Hibbett's column for PIC project enlightenment and related topics

## Part 2: Software tools for the PIC18F

**S**eptember 2020 marks the 15th anniversary of my start as a writer for the magazine. Back in 2005, articles were submitted by paper copy months in advance, followed by many iterations, all requiring that alterations still fitted within the same layout. 'If you take five letters out, add five letters in' was standard practice. 15 years later we rework articles through email but there are still many iterations to create our published output. In 15 years, editorial processes have changed, but I still recognise and remember the magazine I read as a child in the 1970s, and the authors who I was fortunate enough to work with since becoming an author. It's with great fondness I remember John Becker, my former technical editor, who was both my professional liaison with the magazine and my hero from the 1970s.

### Tools for the job

So, onto this month's article, where we look at the software tools available for developing programs on Microchip PIC processors.

In the July issue we covered how we selected the PIC18F47K42 (in a 40-pin DIL package) to form the basis of our PIC18 'Experimenter' board. We chose the PIC18F47K42 through a long selection process – there are around 17,000 Microchip processors to choose from – because it offers a broad range of peripherals, in an easy-to-work-with package. It has not been used in projects within the magazine before, which makes it an interesting candidate. There has been no particular reason why it has not been used before – authors tend to stick with older processors they are familiar with – but the PIC18F47K42 offers a wide range of peripherals and lots of memory, which will make it adaptable for many different projects.

Before we delve into the hardware aspects of any designs based on this processor, we need to get the software development environment installed, and a level of familiarity established. This is true whether you are a hobbyist or a professional

developer; having a complete development environment and being comfortable using it can make a huge difference to how easy it is to build a project, quickly.

### PIC vs Arduino

Developing software for the PIC processor is very different to platforms such as the Arduino, which comes with over a hundred libraries and example applications. Microchip focus on providing a few key low-level driver libraries, and just a handful of example applications. Their low-level documentation for the processor is excellent however, so writing any new driver libraries is possible, and allows you to fine tune your software to match your application's needs, and the capabilities of the processor. It does, however, require that you understand more about what is going inside the processor. That's fine – it's the reason why we experiment with PIC processors, to learn more about what is going on. If this learning opportunity does not interest you and you only want to get a project up and running as quickly as possible, then an Arduino development system would be more appropriate. The benefit of learning more about the processor itself is that it will provide you with many more options to solving a design challenge, and with more complex designs, enable you to create a solution that would not be possible on a simple Arduino platform.

### MPLAB X IDE

Developing software requires a number of different tools. At a minimum, you need the following:

- Text editor
- Compiler
- Driver libraries
- Programmer/debugger
- Programming interface

To pull all these requirements together Microchip have created an Integrated Development Environment (IDE) called MPLAB X, which combines the code editor, programmer and debugger capabilities into a single application. The IDE is really a framework application that allows other PC programs to be configured, run and the results viewed all within the same application. It's possible to run the compiler, see a list of error messages from that compiler in an IDE window, that when you click the mouse on them will cause the offending line of code to come up in the editor window. Using MPLAB X is not a hard-and-fast requirement; you could edit your programs using your favourite editor, then compile the program in a command shell. However, Microchip's IDE simply makes the process easier and quicker to perform.

In addition to MPLAB X we will also need a compiler. This is a standalone application that will convert our programs, written in text files in the 'C' programming language, into the



Fig.1. Microchip debuggers (l-r): PICKit 4, Snap, PICKit 3. We strongly recommend the PICKit 4, but the PICKit 3 is also a good choice. The Snap, however, is too limited for this project series.



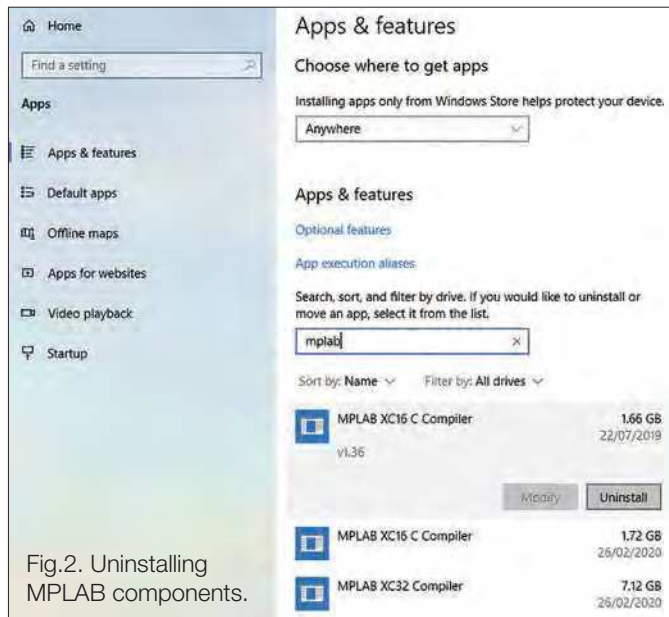


Fig.2. Uninstalling MPLAB components.

binary format that the processor understands. Microchip provide three different compilers for the different PIC families:

- MPLAB XC8: all 8-bit PIC devices, from the PIC10F to the largest PIC18F
- MPLAB XC16: all 16-bit PIC devices, PIC24, dsPIC33
- MPLAB XC32: all 32-bit PIC devices, such as the PIC32

These have to be download separately to MPLAB X but are very easy to install.

The programmer and debugger capabilities are pre-built into MPLAB X and do not require a separate download.

With the above components you have the minimum software necessary to start developing programs. However, one further download provides a set of goodies – example drivers and sample applications – that will make our life easier, especially if we are using UART, I<sup>2</sup>C or SPI communications. Confusingly, Microchip provide three different software packs to fulfil this, called MLA, Harmony and MCC.

MLA is the old and now deprecated ‘Microchip Libraries for Applications’, which has been replaced by MCC, ‘Microchip Code Configurator’. MCC is used with 8-bit devices, such as the PIC18F family. Harmony is a similar pack of libraries, but targeted to 32-bit devices, so of no interest to us today. We will be installing MCC and will be making frequent use of it.

In summary, our installation process will be MPLAB X, the XC8 compiler, followed by MCC. If you plan to use a 16-bit or 32-bit processor in the future, feel free to install those two compilers too, as they can co-exist with no issue. MPLAB X is smart enough to choose the correct compiler for your project, as we will show later.

Last, but not least, Microchip have helpfully made these tools available not only for Windows, but also Linux and macOS PCs.

### ...and the cost?

The great news is that the MPLAB X IDE and the MCC libraries are free – however, the situation is a little more complicated with the compiler programs. They are provided for free, but you can pay to unlock commercial/professional features. The professional versions provide additional optimisations in the translation to a code binary, and this can result in a 20-30% improvement in code space use compared to the ‘free’ version of the compiler. There may also be some reductions in the amount of RAM used. In our opinion, for hobbyists, these improvements do not justify a fairly expensive purchase of a professional compiler licence. The ‘free’ version is not crippled in any way; all compiler features are available – the difference is in the optimisations the

compiler performs to reduce code size. This would be important if you were building a large number of products and would like to use smaller, cheaper versions of a microcontroller. For hobbyists, we can simply purchase the device with larger memory that costs perhaps 50p more. To reiterate, you are not missing out on features by avoiding an expensive purchase.

### Programming interface

Microchip processors require a small piece of hardware, called a ‘debugger’, to transfer programs to a device. The tool of choice is the PICkit 4 from Microchip, which costs around £55. The previous generation debugger, the PICkit 3, can also support the processor we are using and is cheap secondhand on eBay (from £12). Clones of the PICkit 3 can be purchased on eBay for as little as £15, but we strongly recommend using the official device. We will focus on using the PICkit 4 in this and future articles. It’s a solid product that should last for years – we have never had a Microchip debugger fail on us in 25 years, the only issue is that every decade or so new processors become available that require a programmer update, but you will be required to update your programmer only if you want to use those new ICs.

There is a lower-cost debugger available from Microchip called the ‘Snap’, which costs around £18. It can program the PIC18F47K42 but has limited features, comes as just a bare PCB and in our opinion is just too basic for our plans. You can see these three debuggers in Fig.1.

On a historical note, our first emulator for the PIC16 series of processors cost around £900 back in 1995!

The debugger is connected to the PC via a USB cable (supplied with the debugger.) Five signals connect the debugger to your target PCB via an 8 pin 0.1-inch pitch header socket. Hook-up wires can be used to make the connection, but we prefer to fit an 8-pin header strip to our boards and plug the debugger in directly – we will provide an 8-pin header strip on our experimenter board.

### Installation preparation

In the following sections we describe the setup for PCs running the Windows OS, as this is the most common setup. The installation process for other operating systems will be similar – check online for exact details if you are using Linux or macOS operating systems.

Before we install the latest versions of the software (Microchip update their software tools frequently) we will want to remove any previous versions. Your creations will not be deleted by these steps, just the very large IDE and compiler install files, which can add up to many gigabytes of disk space. If you do not have Microchip tools installed you can skip to the ‘Installation’ section below.

To remove earlier versions, first click on the ‘Start’ button, then type ‘Add’, and select ‘Add or Remove programs’. From the drop-down list that appears, as shown in Fig.2, type ‘mplab’ in the search box to filter just the Microchip software components. Now *remove* all ‘Microchip’ installed features. You will have to do these one at a time. Left click on an item in the list, then click the ‘Uninstall’ button. Follow the instructions, and when done, repeat for all the other entries. We had about a dozen entries for multiple old versions of the toolchain, so this bit of spring-cleaning freed up over 10GB of disk space.

### Installation

We start by installing the latest version of MPLAB X IDE, which at the time of writing is version v5.40. In your browser, go to: <https://www.microchip.com/mplab/mplab-x-ide> and scroll down to the ‘Downloads’ tab. Click on the text ‘MPLAB X IDE v5.40’ to start the download. Don’t worry if the version has been updated, changes are likely to be minimal. Microchip make regular updates to their software tools (typically when new processors



Fig.3. The MPLAB X main window.

are added, but also for bug fixes and improvements.) MPLAB has been in development and maintained for many years.

Once downloaded, double click the file to start the installation process. Other than clicking to accept the software licence terms, accept all defaults. We recommend that you do not change the installation folder as this will make installing the compiler and MCC libraries difficult.

Close to the end of installation a Windows Security pop-up will be displayed. Click 'Install' to install the hardware drivers for the debugger tool. At the end of installation, a Setup pop-up appears; *untick* the three checkboxes – we will perform these steps manually. Click 'Finish' to complete the installation.

Now for the compiler; in your browser, go to: <https://www.microchip.com/mplab/compilers>. and scroll down until you see the 'Compiler Downloads' tab. Click on that, and then click on 'MPLAB® XC8 Compiler v2.20'. Again, this version may have been updated by the time you get to it, so it may be v2.21 or similar. This is fine; compiler updates rarely impact users of the tool, and just provide minor bug fixes. Again, once downloaded, double-click on the file to start installation. Other than clicking to accept the software licence terms, accept all defaults. The installation process will update MPLAB so that it 'knows' a compiler has been installed.

We can now start MPLAB X IDE by double-clicking on the newly created desktop icon, or by clicking on the Windows 'Start' icon and typing 'mplab x'. Be careful at this point – the MPLAB X IDE installation process installs another useful application, a programmer utility, that is amusingly called MPLAB X IPE. Given this differs by only a few pixels on the screen, it's easy to click on the wrong one. We ended up deleting the desktop icon for IPE by right-clicking on the desktop icon and selecting 'Delete'. This removes the short-cut icon from the desktop, but leaves the program installed and ready to launch from the Windows Start menu.

If you've previously installed MPLAB you will be presented with a pop-up box asking whether you would like to import old settings from the previous installation. We recommend you do not do this – we want to start with a clean sheet. So click 'No' if presented with that message.

You may get a warning from your virus protection software that ***mplab\_ide64.exe*** is attempting to access the network. Go ahead and click 'Allow access', as we trust Microchip, and this feature enables MPLAB to check for updates to software automatically.

You should now see the main IDE window, as shown in Fig.3. Two windows are opened on start-up, 'Start Page' and 'MPLAB X Store'. Go ahead and close these windows by clicking the 'x' on the right-hand side of the tabs.

## Adding MCC

Our final installation step is to bring in MCC – the drivers that we can add to our projects. MCC is not just a set of source files, it's a complete GUI (graphical user interface) that helps simplify the process. Confusingly, there are several ways to install MCC; we will do it within MPLAB X itself, as the IDE has a 'plug-in' tool already built in.

Click on the 'Tools' menu option, followed by 'Plugins' (*not* 'Plugins Download').

Click on 'Available Plugins' and scroll down until you see 'MPLAB Code Configurator'. Click the check-box, then click on the 'Install' icon at the bottom of the window, as shown in Fig.4. Click 'Next', then accept the licence agreement, and click 'Next' to start the installation process. MPLAB X will now download MCC and install it; so this may take a minute or two. At the end, MPLAB X will need to restart, so just click 'Finish'. MPLAB X will restart automatically after a few seconds and complete the installation process. We are now ready to create our first project.

If you have a PICkit 4 debugger, go ahead and plug that in now. The front of the device should illuminate blue once connected.

In MPLAB X IDE, click on the 'File' menu option, followed by 'New Project...'. In the 'Categories' section of the pop-up window leave 'Microchip Embedded' highlighted and click on 'Standalone Project' followed by 'Next'. In the highlighted 'Device:' field, type in the name of our processor, 'PIC18F47K42'. If you have a PICkit 4 plugged in then select it from the 'Tool:' drop-down list. Click 'Next'. We can select the compiler we will be using; XC8. This should be shown in this list, so click on that and then click 'Next'.

Finally, we have to give our project a name (type 'test') and specify where this project will live on your PC's disk. This directory will hold your project settings and all the source files you create. For now, it is an empty project and we shall leave MPLAB X at this point and return to it once we have completed our hardware design.

## Coming up next

In the next article we will start the design of our experiment-er PCB. Our intent is to make clear the thought process going into the design of the board and explore the capabilities of the processor. We will be focusing on *using* the processor rather than diving into the details of internal processor peripherals. We are going to cover: GPS location reporting, digital compass, various display technologies, speech output, PC connection via USB, Wi-Fi communication, interfacing with Amazon Alexa, Servo motor control, analogue input.

Some are more ambitious than others, but it will be a fun journey and we hope you will join in. The PCB will be available from our usual suppliers, and full PCB Gerber and design files available should you wish to etch your own, although as a double-sided design this might be challenging.



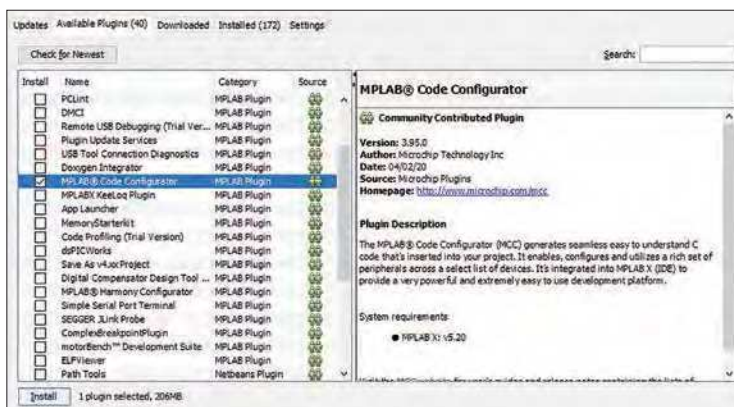
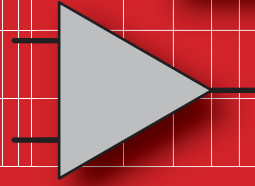


Fig.4. MCC installation via MPLAB X.

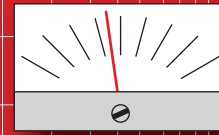

# AUDIO OUT

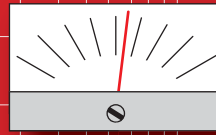

By Jake Rothman

## Low-noise Theremin Power Supply – Part 2

**L**ast month, we discussed the importance of a low-noise power supply for sensitive audio applications, such as a Theremin. This month, we will move on from theory and actually build one. In fact, we will offer not just one, but four circuits based around the same flexible PCB, supplying different voltage outputs.

### Basic design

For linear power supplies we have to factor in all the losses, as shown in Fig.15:

- Headroom required by the regulators, (the minimum difference between the input and output voltages is around 2V for the LM317 used here).
- Regulation figure or the voltage droop of the transformer at the expected load current.
- Total forward voltage drop ( $V_f$ ) of the rectifier diodes (1.4V for silicon or 0.5V for Schottky devices).
- Minimum input voltage at the bottom of the ripple waveform. This can be minimised by fitting the biggest smoothing capacitors (C10/13) physically possible in a small PSU, typically 1000 to 2200 $\mu$ F.

Since it is a bridge-rectifier/capacitor circuit, the output voltage is theoretically equal to the peak AC ( $\times 1.4$  the RMS input voltage), which gives us a useful boost. However, there is no such thing as free energy, this comes from a corresponding rise in the current drawn. All these factors limit the real-world current that can be drawn to around 120mA if the regulated voltages are set to around 9V and 15V. At least we won't need any heatsinks on the regulators at this level. This circuit is thus ideal for powering the Theremin or other sensitive circuits and we also have an isolated 15V supply for the audio amplifier, which avoids interaction between the two sections.

### PCB layout

Getting low hum on the output is dependant on the PCB track layout. It is very important to ensure the charging pulses from the rectifiers to the smoothing capacitors do not get superimposed on the output. This can easily be achieved by making sure the two lines from the rectifier go directly to the smoothing capacitor pins with no other connections along these

 


Fig.16. PCB tracks from the rectifier to the smoothing capacitors. These have nasty pulses on them due to charging currents. Nothing else must be connected or 100Hz noise will result. Note the following on the above PCB: the track jumps from D3 to C10 on the other side of the board. (Red is the positive (+) line and the black dotted is the negative line (-))

tracks. The lines to the regulators then have to be taken directly from the capacitor pins. This practice is called 'nodding' or 'starring'. The two paths on the PCB are shown in Fig.16. There is no provision for the Zobel network on the PCB, since the components are rather large and the Theremin works fine without it. If you do want one, it will have to be hard-wired to the board, possibly using a small board as shown in Fig.31. Note that only one Zobel network will be needed for dual rails, since the two windings are well-coupled magnetically via the transformer.

### Regulators

The low noise of the LM317 voltage regulator has been recognised for years by the audio community. In the 1980s it was expensive, now it is a cheap commodity component. It has lower noise because it uses a band-gap voltage reference rather than a Zener diode. The reference can also be decoupled with an external capacitor, which knocks the noise down by a further factor of 10. A classic example of a band-gap reference is the difference between silicon and germanium diode junctions being set to 0.43V by adjusting the currents flowing through them. The 0.43V is the point of maximum temperature stability. In the case of the LM317, the band-gap is made from

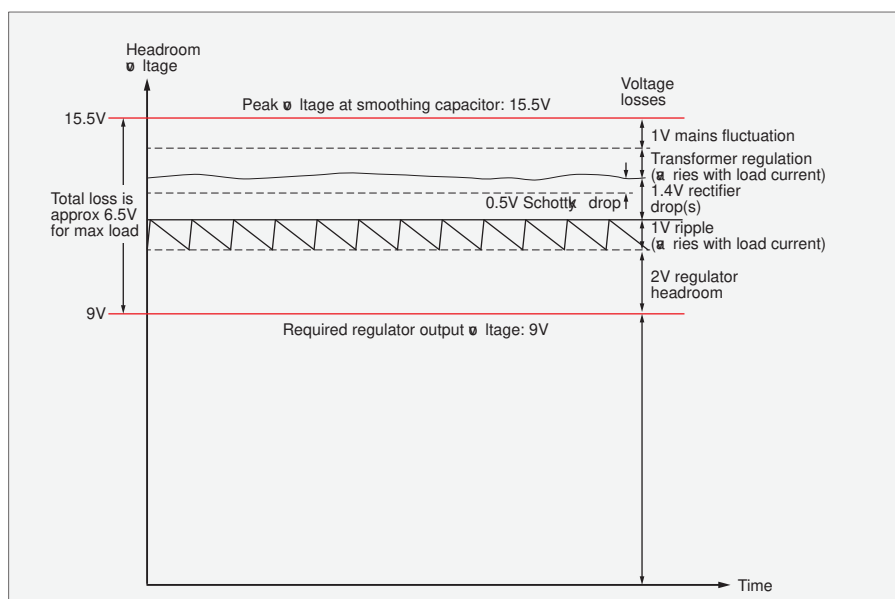


Fig.15. Taking account of the cumulative losses in linear power supply design.

 


Fig.17. Basic LM317 voltage regulator circuit. A relatively low-resistance voltage-setting divider reduces variations due to variations in the regulators quiescent current that flows out of the adjust pin.

two dissimilar silicon junctions giving a reference of 1.25V using one of the late Bob Widlar's unique circuits. (He's worth looking up on Wikipedia). By scaling this voltage using a resistor network, any desired voltage from 1.2 to around 32V can be obtained, as shown in the basic circuit in Fig.17. The equation is basically the gain of a non-inverting op-amp multiplied by the 1.25V voltage reference:

$$V_{out} = 1.25[1 + (R2/R1)]$$

R1 is usually 120Ω to 240Ω; note that 120Ω uses more current, but gives a more predictable voltage.

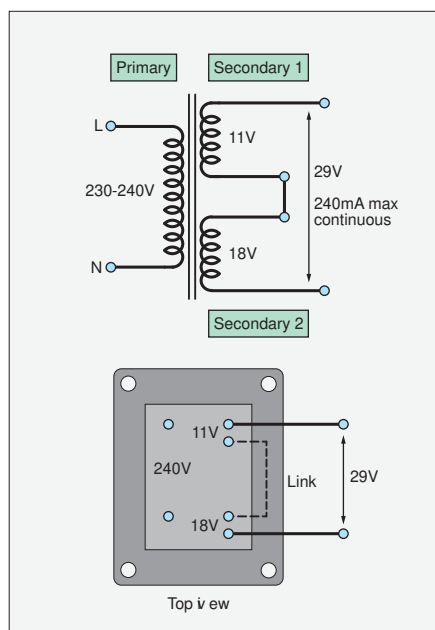


Fig.18. The transformer secondaries can be connected in series if needed to get a single-rail higher voltage supply up to 30V.

 


Fig.19. A suitable internal fuse holder – this is insulated so you can't get a shock off it. It must be placed in the live wire.

If you want an on-line calculator then <https://circuitdigest.com/calculators/lm317-resistor-voltage-calculator> is good. Note the overall tolerance of the set voltage of the LM317 is about 10%, so a bit of resistor tweaking may be needed. Make the calculated R2 value a bit bigger than required, and then put resistors in parallel with R2 to tweak its output down to create the required voltage.

Here's a list of some typical voltages and the associated value of R2 (R1 = 120Ω):

5V	360Ω
6V	453Ω E96
7.5V	600Ω
9V	750Ω
12V	1kΩ
15V	1.3kΩ
18V	1.6kΩ
22V	2kΩ
24V	2.2kΩ
25V	2.32kΩ E96
28V	2.55kΩ E96
30V	2.7kΩ (33kΩ in parallel with 3kΩ)

Some values are from the E96 series. These are inexpensive now, about 3p from Mouser; eg. Part no. MFR-25FBF52-2K32.

Above 15V, the transformer windings will have to be put in series (see Fig.18) unless the current drawn is very low. (With Schottky diodes and around 30mA load it is possible to get 18V.)

## Protection

### Over-current

The LM317 has a short-circuit current limit of 1.5A, assuming a massive heat sink. This is so high that it's useless, something else usually blows up first. Here we will have to use a fuse in series with the primary. A low value (250mA) time-delay is about right. Don't just rely on the 13A

fuse in the mains plug. This can be wired as shown in Fig.19 or you can use a panel-mounted holder.

### Thermal

A 127°C or 105°C non-resetting thermal cut-out is placed in series with the primary to guard against the transformer overheating. Its physical placement against the earthed laminations is shown in Fig.20. If it trips it has to be replaced.

### Over-voltage

The absolute maximum input voltage to the LM317 is 37V. If the secondaries are connected in series (Fig.24), the off-load voltage can breach this so replace the standard protection diodes with Zeners.

## Components

The devices are not hard to source – see the transformer notes below and in Part 1. Explain versions. This list is for the +9V/+15V version. there are some changes for the +30V version marked with an asterisk, '\*'.

### Resistors

R1	1kΩ 5% 0.5W
R3, R5	120Ω 1% 0.25W

 


Fig.20. Location of the thermal cut-out; vital if you use a plastic or wooden case.





Fig.21. The output cable of DC power supplies is often the polarised figure-of-eight type, typically cheap speaker cable. Note the rubber grommet.

R2, R4 See above table for required values (use 0.25W, 1%)  
 R2a\* 33k $\Omega$   
 Rz 2.2 $\Omega$ , 0.25W, 5% (optional Zobel)

#### Capacitors

C1 10nF ceramic, 5mm X7R  
 C2-C9 100nF ceramic, 5mm X7R  
 C10 2200 $\mu$ F 25V (\*1000 $\mu$ F, 50V)  
 C11,12 100 $\mu$ F 25V (\*35V)  
 C13 2200 $\mu$ F 25V (\*1000 $\mu$ F, 50V)  
 C14,15 100 $\mu$ F 25V  
 Cz 4.7 $\mu$ F, 63V any non-polarised type (optional Zobel)

Note: the electrolytic capacitors determine the life expectancy of linear power supplies, so use long-life types (> 2000 hours at 105°C) such as those by Nichicon, Kemet and Panasonic. They don't need to be low equivalent series resistance (ESR) types (see capacitor 'tuning' later). All electrolytics used are radial.

#### Semiconductors

IC1,2 LM317T positive adjustable voltage regulator  
 D1-D8 SB40 1A 40V Schottky rectifiers (used where low voltage drop is required. If 1.4V can be accommodated then use 1N4002. For lower noise use UF4002)  
 D9-D12 1N4001 (\*22V BZY61, 1.3W zener)

#### Miscellaneous

- Fuse holder, Camden Boss single fused terminal block (Rapid 21-0740 with T250mA 20mm fuse)
- IEC connector (Rapid Bulgin 51-4336 or Chinese 23-0100)
- Rubber boot (Cliff Rapid 23-0350)
- M3  $\times$  40mm fixing screws (Rapid 51-3341)
- Die-cast box, 115  $\times$  90  $\times$  55mm Eddy-stone. Hammond 120  $\times$  100  $\times$  60mm Rapid 30-7070.
- Thermal cut-out SetFuse X1 (Rapid 26-0940 (127°C) or 26-0900 (105°C))
- TO220 clip-on heatsink
- Rubber grommet for enclosure cables exit hole (Rapid 04-0202)

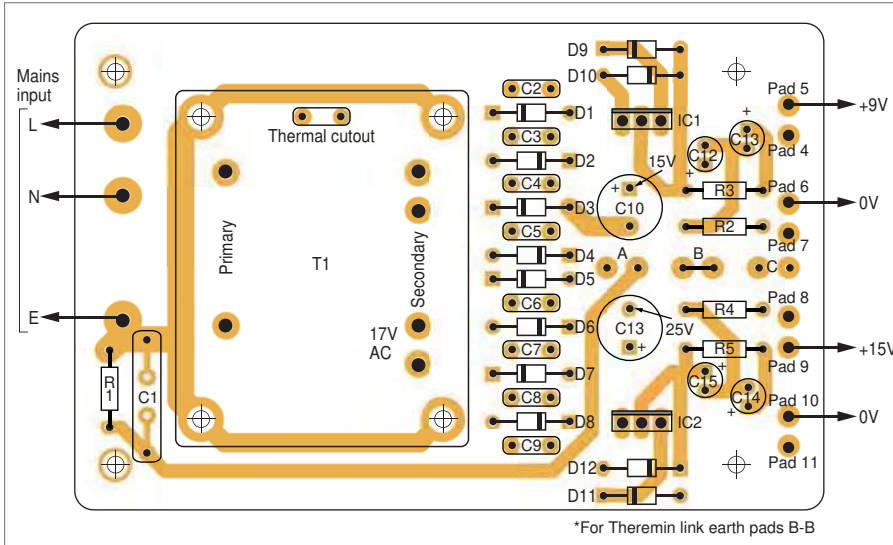


Fig.23. Standard low-noise Theremin +9/+15V power supply for the circuit in Fig.22. Note earth link B is linked.

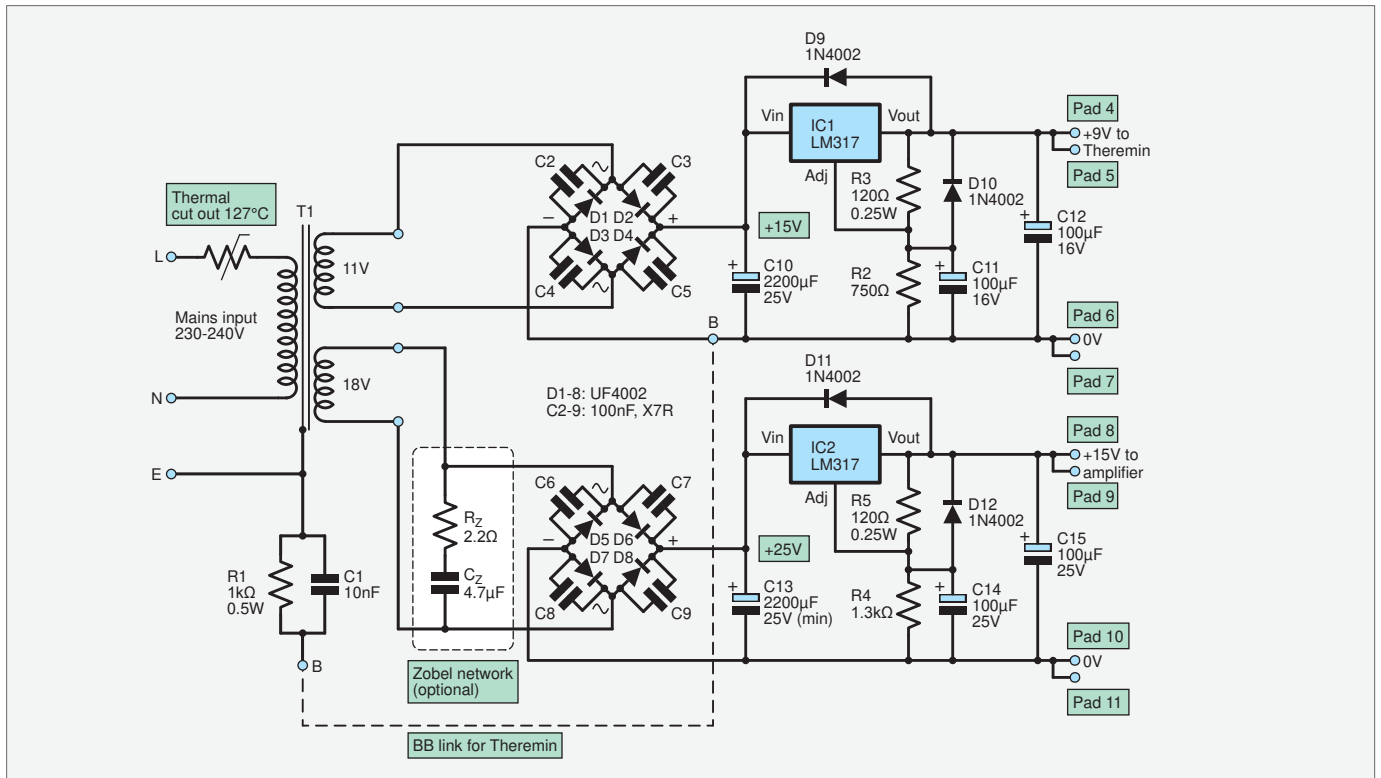


Fig.22. Full circuit diagram of the power supply with the Zobel add-ons in red. +9V and + 15 dual power supply for Theremin. By changing the links and values of R2 and R4 to 1k $\Omega$  this can be made into a  $\pm$ 12V supply for op amp circuits (see Fig.27).

 


Fig.24. Single 30V rail designs for discrete pre-amplifier circuits. Note that the secondaries are in series and it's worth putting a heatsink on the regulator.

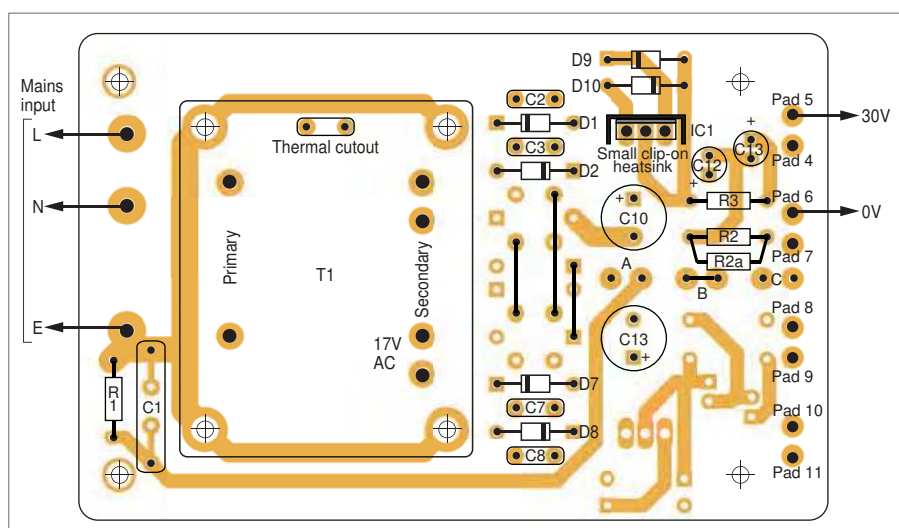


Fig.25. Low-noise, single-rail +30V power supply. Very handy for single-rail preamplifiers using discrete circuitry. Note the three links to the left of C10/13.

### Transformer and PCB

These can be obtained from the *PE PCB Service*. Other parts are available from the author.

[jacob.rothman@hotmail.com](mailto:jacob.rothman@hotmail.com)  
01597 829102

### Power supply connectors

The mains input socket is pretty much standard, thanks to the IEC (International Electrical Commission). However, for the output connectors, prepare to enter a standardisation minefield, it's complete chaos. You can use screw terminals, 4-pin male XLR sockets, terminal blocks or one of the huge range of so-called DC connectors with an outer and centre pin.

One so-called 'standard' in the audio industry for guitar pedals is a 2.1mm DC connector wired centre pin negative. Another 'standard' is polarised cable. Normally, figure-of-eight thin speaker cable is used with the rib or printed line denoting positive. This can be seen coming out of the protective rubber grommet in Fig.21.

### Variations

There are four variants of the power supply using the same board. This was originally designed for the *PE Theremin*, but with simple variations can be used to power a multitude of audio circuits.

- 1) **+9V and +15V dual-rail** – this is the 'standard dual-rail power supply shown in Fig.22 It is designed to power a Theremin and its associated amplifier driving the speaker. If the amplifier is not used, then the 15V power supply can be omitted and the circuit simply becomes a low-noise +9V supply.
- 2) **Single-rail +30V** – higher voltage design for discrete pre-amps and single rail op amp circuitry, as shown in Fig.24
- 3) **±12V general-purpose dual-rail** – ideal for low-power op amp applications such as pre-amps and musical synthesisers. Shown in Fig.27.
- 4) **Positive-earth -9V** – designed for germanium circuits, such as Tonebender fuzz pedals and old 1960s radios, typically

those made by Roberts and Bush. This is a nice little extra I thought up after the Theremin supply was designed, built and finished. We haven't got space to cover it this month, so it will be described in the next column.

### Links on the PCB

On the PCB overlay there are three link positions A, B and C, as shown in Fig.23 These are needed to connect the power supply DC ground or 0V to the ground lifted (by R1 and C1) mains earth connection. Link A connects the 0V of the 17V AC secondary winding power supply rail to mains earth. Link B connects the mains earth to the 11V-AC-fed power supply rail 0V line. Link C connects the positive of the 17V fed supply to the 0V of the 11V fed supply. This is used to make centre-tapped dual rail supplies.

Note that when using the Theremin +9/+15V power supply the mains earth is connected to the 0V of the 9V supply. This is because the Theremin needs a stable earth reference – more so than the amplifier.

### Capacitor 'tuning'

Since voltage regulators are a negative-feedback control system with a falling open-loop gain at high frequencies, the reduction in output impedance becomes less effective at high frequencies. This means the output impedance of linear voltage regulators is slightly inductive. This can cause a resonant noise peak with the output capacitor (C12) if it is a low ESR (around 0.1Ω) type. National Semiconductor application engineer Robert Pease showed in his book *Troubleshooting Analogue Circuits*, that a bit of loss in the output capacitor was necessary. An ESR of 0.6Ω to 3Ω was needed to avoid noise peaks. (To see the noise



Fig.26. Basic board before final voltage setting resistors R2 and R4 are added. Note the blue snubber capacitors across the rectifiers.



Fig.27. 12-0-12V low-noise supply uses the 18V winding on the transformer for the positive rail. This is because most synthesisers use more current on the plus rail.

The adjust pin filtering capacitor (C11/14) can have a quite high ESR before it be-

9V

To scope

Load resistor

470Ω

BC337

2.2kΩ

Signal generator  
2V pk pk 100Hz  
Square wave

Output

0V

Connect across output of power supply

Fig.28. Low-noise, dual-rail 12-0-12V power supply. A useful general-purpose supply – handy for op amp circuits. Note the link from Pad 4 to Pad 11, and the A link.

Making C12 a large value, say 470μF, will swamp this noise problem, but then another problem emerges in that a lower frequency ringing of a few cycles (around 80mV pk-pk) can occur if the regulator load is switched on and off. This is because too big a capacitor across the output reduces the open-loop gain of the whole system, causing ringing as the negative-feedback loop seeks to correct its self in a sluggish manner, then overshooting. This effect is proportional to load current. Again, a damping resistance in series with the capacitor can reduce this problem.

The way to test for poor dynamic load response is to put a 'scope probe set to AC on the output and dab a load on and off. A better way, is to electronically switch the load on and off with a transistor, such as the circuit shown in Fig.28. By driving the transistor with a square wave from a signal generator at around 100Hz the sweep of the 'scope can be synchronised to get a good view.

Practical Electronics | September | 2020

 


Fig.30. Stages in cutting the hole for mains IEC socket in die-cast box (top to bottom):  
a) Mark out area to be removed and cut down the two vertical sides with hack saw.  
b) Grip 'tab' firmly with pliers  
c) Snap off 'tab' with pliers.  
d) Position the socket to mark out the screw holes.

to 22 $\mu$ F works fine – see Fig.29. A polymer SAL capacitor works effectively as well. A diode (D10,D12) is used to protect the regulator adjust pin from discharge on turn off or output shorting. In the current-limited tantalum circuit, a 1N4148 is sufficient. If no resistor is used, a 1N4001 is needed, as previously specified.

## Construction

Although it's tempting just to solder the transformer to the PCB, that's not strong

enough mechanically; it needs to be bolted down. I've had pieces of equipment where the transformer has sheared off the PCB when dropped. It's not good having a lump of steel loose inside the box! Remember to employ the standard electronic construction technique of soldering after bolting, to prevent the soldered joints being strained. A suggested mounting arrangement is shown in Fig.1, *Part 1*, where 3mm bolts are used. The core is also earthed by the bolts, essential to ensure safe operation of the thermal cut-out. Incidentally, it's a good idea to use a smear of heatsink compound to aid thermal coupling between the thermal cut-out and the transformer core. This should be pressed firmly against the core prior to soldering. (see Fig.20). Remember to solder it quickly, otherwise it may overheat and go open-circuit!

## Testing

The first thing to do is to make it safe to turn on. There is mains voltage on the board; if you are not scared of it, you should be. I always tape over exposed tracks and insulate terminals with silicon rubber sleeves. I also put a rubber boot over the mains input connector. Check there is earthing continuity from the earth pin on the plug to metal box. If there is no continuity you could be electrocuted.

When turning on, listen for any buzzing noises from a stressed transformer or odd cracks and hisses from incorrectly inserted electrolytic capacitors swelling up. I know it sounds paranoid, but I've been on the receiving end of exploding electrolytic capacitors from inexperienced students, so I insist on them wearing glasses. If it passes this test, switch off and feel for any hot components. If okay, switch on again and measure the output voltage. Next, put on a suitable load resistor to give the maximum current draw required. This will normally be a big high-wattage type and will get hot. For example, if you are making a 12V power supply and need a 100mA output, then use a 120 $\Omega$  2W resistor. Finally, while loaded, check components for excessive heating. Note, it may take about 30 minutes for the transformer to reach its full running temperature. At this point it's worth checking the electrical noise level.

## On the case

Electronics belongs in metal boxes. They provide electrical safety when earthed, electromagnetic fields are screened, heat can get out without ventilation holes, they can't catch fire and they don't fall apart after two years. After a good 30 years life they can then be effectively recycled, like all metals. Steel is more effective than aluminium alloys at reducing magnetic fields, but it is harder to drill and it can buzz mechanically if the transformer is too close to any of the panels.



Fig.31. Interior of power supply – the small board on the side is the Zobel – the 'wacky circuit' from *Part 1*.



Fig.32. A view of the 30V board; note the links on the diode section and the regulator heatsink.

## Socket mounting

The round DC connectors are relatively easy to mount with a 12.5mm (half-inch) hole. It should really have an anti-rotation flat on it but this needs a £400 metal punch set-up. It can be quite difficult cutting a rectangular hole in a metal box for the IEC socket. However, here's a little technician's trick I've used over the years to make it easier. It works very quickly with die-cast boxes, which although they are expensive, have always been the best choice for hand-built electronics. The stages involved are shown in Fig.30. The interior of the case is shown in Fig.31. The 30V board is shown in Fig.32.

I have loads of these power supplies in my studio and they are not humming along nicely like the wall-warts used to.

## Next month

In the next issue we will finish this power supply project with a handy positive-earth –9V variant.



# DIRECT BOOK SERVICE

## Teach-In 2017

### Introducing the BBC micro:bit



#### PYTHON CODING ON THE BBC MICRO:BIT

Jim Gatenby


Python is the leading programming language, easy to learn and widely used by professional programmers. This book uses MicroPython, a version of Python adapted for the BBC Micro:bit.

Among the many topics covered are: main features of the BBC micro:bit including a simulation in a web browser screen; various levels of programming languages; Mu Editor for writing, saving and retrieving programs, with sample programs and practice exercises; REPL, an interactive program for quickly testing lines of code; scrolling messages, creating and animating images on the micro:bit's LEDs; playing and creating music, sounds and synthesized speech; using the on-board accelerometer to detect movement of the micro:bit on three axes; glossary of computing terms.

This book is written using plain English, avoids technical jargon wherever possible and covers many of the coding instructions and methods which are common to most programming languages. It should be helpful to beginners of any age, whether planning a career in computing or writing code as an enjoyable hobby.

118 Pages

Order code PYTH MBIT £7.99

 

#### GETTING STARTED WITH THE BBC MICRO:BIT

Mike Tooley

Not just an educational resource for teaching youngsters coding, the BBC micro:bit is a tiny low cost, low-profile ARM-based single-board computer. The board measures 43mm x 52mm but despite its diminutive footprint it has all the features of a fully fledged microcontroller together with a simple LED matrix display, two buttons, an accelerometer and a magnetometer.

Mike Tooley's book will show you how the micro:bit can be used in a wide range of applications from simple domestic gadgets to more complex control systems such as those used for lighting, central heating and security applications. Using Microsoft Code Blocks, the book provides a progressive introduction to coding as well as interfacing with sensors and transducers.

Each chapter concludes with a simple practical project that puts into practice what the reader has learned. The featured projects include an electronic direction finder, frost alarm, reaction tester, battery checker, thermostatic controller and a passive infrared (PIR) security alarm.

No previous coding experience is assumed, making this book ideal for complete beginners as well as those with some previous knowledge. Self-test questions are provided at the end of each chapter, together with answers at the end of the book. So whatever your starting point, this book will take you further along the road to developing and coding your own real-world applications.

108 Pages

Order code BBC MBIT £7.99

## THEORY AND REFERENCE

#### PRACTICAL ELECTRONICS HANDBOOK – 6th Ed

Ian Sinclair

440 pages

Order code NE21 £33.99

#### STARTING ELECTRONICS – 4th Ed

Keith Brindley

296 pages

Order code ELSEV100 £18.99

#### ELECTRONIC CIRCUITS – FUNDAMENTALS & APPLICATIONS – Updated version

Mike Tooley

400 pages

Order code TF43 £32.99

#### FUNDAMENTAL ELECTRICAL AND ELECTRONIC PRINCIPLES – 3rd Ed

C.R. Robertson

368 pages

Order code TF47 £21.99

#### A BEGINNER'S GUIDE TO TTL DIGITAL ICs

Robert Penfold

142 pages

OUT OF PRINT BP332 £5.45

#### UNDERSTANDING ELECTRONIC CONTROL SYSTEMS

Owen Bishop

228 pages

Order code NE35 £36.99

The books listed here have been selected by the *Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door.

FOR A FULL DESCRIPTION OF THESE BOOKS AND CD-ROMS SEE THE SHOP ON OUR WEBSITE

[www.electronpublishing.com](http://www.electronpublishing.com)

All prices include UK postage

## MICROPROCESSORS

#### INTERFACING PIC MICROCONTROLLERS – 2nd Ed

Martin Bates

298 pages

Order code NE48 £34.99

#### PROGRAMMING 16-BIT PIC MICROCONTROLLERS IN C – LEARNING TO FLY THE PIC24

Lucio Di Jasio (Application Segments Manager, Microchip, USA)

496 pages + CD-ROM

Order code NE45 £38.00

#### INTRODUCTION TO MICROPROCESSORS AND MICROCONTROLLERS – 2nd Ed

John Crisp

222 pages

Order code NE31 £29.99

#### THE PIC MICROCONTROLLER YOUR PERSONAL INTRODUCTORY COURSE – 3rd Ed

John Morton

270 pages

Order code NE36 £25.00

#### PIC IN PRACTICE – 2nd Ed

David W. Smith

308 pages

Order code NE39 £24.99

#### MICROCONTROLLER COOKBOOK

Mike James

240 pages

Order code NE26 £36.99

## BOOK ORDERING DETAILS

All prices include UK postage.

For postage, add £3 per book to Europe, £4 for rest of the world per book.

CD-ROM prices include VAT and/or postage to anywhere in the world.

Send a cheque, (£ sterling only) made payable to: **Practical Electronics** or credit card details (Visa or Mastercard) to:

**Electron Publishing Limited,**  
113 Lynwood Drive, Wimborne, Dorset BH21 1UU

Books are normally sent within seven days of receipt of order.

Please check price (see latest issue of *Practical Electronics* or website) before ordering from old lists.

For a full description of these books please see the shop on our website.

Tel: 01202 880299 – Email: [shop@electronpublishing.com](mailto:shop@electronpublishing.com)

Order from our online shop at: [www.electronpublishing.com](http://www.electronpublishing.com)



## ARDUINO

### ARDUINO FOR DUMMIES

John Nussey

Arduino is no ordinary circuit board. Whether you're an artist, a designer, a programmer, or a hobbyist, Arduino lets you learn about and play with electronics. You'll discover how to build a variety of circuits that can sense or control real-world objects, prototype your own product, and even create interactive artwork. This handy guide is exactly what you need to build your own Arduino project – what you make is up to you!

- **Learn by doing** – start building circuits and programming your Arduino with a few easy examples – right away!
- **Easy does it** – work through Arduino sketches line by line, and learn how they work and how to write your own.
- **Solder on!** – don't know a soldering iron from a curling iron? No problem! You'll learn the basics and be prototyping in no time.
- **Kitted out** – discover new and interesting hardware to turn your Arduino into anything from a mobile phone to a Geiger counter.
- **Become an Arduino savant** – find out about functions, arrays, libraries, shields and other tools that let you take your Arduino project to the next level
- **Get social** – teach your Arduino to communicate with software running on a computer to link the physical world with the virtual world

438 Pages **Order code ARDDUM01** £19.99

### EXPLORING ARDUINO

Jeremy Blum

Arduino can take you anywhere. This book is the roadmap. Exploring Arduino shows how to use the world's most popular microcontroller to create cool, practical, artistic and educational projects. Through lessons in electrical engineering, programming and human-computer interaction, this book walks you through specific, increasingly complex projects, all the while providing best practices that you can apply to your own projects once you've mastered these. You'll acquire valuable skills – and have a whole lot of fun.

- **Explore** the features of commonly used Arduino boards
- **Use** Arduino to control simple tasks or complex electronics
- **Learn** principles of system design, programming and electrical engineering
- **Discover** code snippets, best practices and system schematics you can apply to your original projects
- **Master** skills you can use for engineering endeavours in other fields and with different platforms

357 Pages **Order code EXPARD01** £26.99

## BOOK ORDER FORM

Full name: .....

Address: .....

.....

..... Post code: ..... Telephone No: .....

Email: .....

☐ I enclose cheque/PO payable to Practical Electronics for £ .....

☐ Please charge my card £ ..... Card expiry date.....

Card Number .....

Valid From Date ..... Card Security Code ..... (The last three digits on or just below the signature strip)

Please send book order codes: .....

.....

.....

Please continue on separate sheet of paper if necessary

## COMPUTING AND ROBOTICS

### NEWNES INTERFACING COMPANION

Tony Fischer-Cripps

295 pages **Order code NE38** £41.00

### HOW TO BUILD A COMPUTER MADE EASY

Robert Penfold

120 pages **Order code BP707** £8.49

### EASY PC CASE MODDING

Robert Penfold

192 pages + CD-ROM **Order code BP542** £8.99

### FREE DOWNLOADS TO PEP-UP AND PROTECT YOUR PC

Robert Penfold

128 pages **Order code BP722** £7.99

### WINDOWS XP EXPLAINED

N. Kantaris and P.R.M. Oliver

264 pages **Order code BP514** £7.99

### THE INTERNET – TWEAKS, TIPS AND TRICKS

Robert Penfold

128 pages **Order code BP721** £7.99

### eBAY – TWEAKS, TIPS AND TRICKS

Robert Penfold

128 pages **Order code BP716** £7.50

### AN INTRODUCTION TO eBAY FOR THE OLDER GENERATION

Cherry Nixon

120 pages **Order code BP709** £8.49

### HOW TO FIX YOUR PC PROBLEMS

Robert Penfold

128 pages **Order code BP705** £8.49

### AN INTRODUCTION TO WINDOWS VISTA

P.R.M. Oliver and N. Kantaris

120 pages **Order code BP703** £8.49

### WINDOWS 8.1 EXPLAINED

180 Pages

**Order code BP747** £10.99

### AN INTRODUCTION TO THE NEXUS 7

118 Pages

**Order code BP744** £8.99

### COMPUTING FOR THE OLDER GENERATION

Jim Gatenby

308 pages **Order code BP601** £8.99

### ANDROIDS, ROBOTS AND ANIMATRONICS

Second Edition – John Iovine

224 pages **Order code MGH1** £16.99

### ROBOT BUILDERS COOKBOOK

Owen Bishop

366 pages **Order code NE46** £26.00

### INTRODUCING ROBOTICS WITH LEGO MINDSTORMS

Robert Penfold

288 pages + **Order code BP901** £14.99

### MORE ADVANCED ROBOTICS WITH LEGO MINDSTORMS

Robert Penfold

298 pages **Order code BP902** £14.99

### HOW TO FIX YOUR PC PROBLEMS

Robert Penfold

128 pages **Order code BP705** £8.49

### WINDOWS 7 – TWEAKS, TIPS AND TRICKS

Andrew Edney

120 pages **Order code BP708** £8.49

### GETTING STARTED IN COMPUTING FOR THE OLDER GENERATION

Jim Gatenby

120 pages **Order code BP704** £8.49

### WINDOWS 8.1 EXPLAINED

Noel Kantaris

180 Pages **Order code BP747** £10.99

### COMPUTING WITH A LAPTOP FOR THE OLDER GENERATION

Robert Penfold

120 pages **Order code BP702** £8.49

### AN INTRODUCTION TO EXCEL SPREADSHEETS

Jim Gatenby

18 pages **Order code BP701** £8.49

### KINDLE FIRE HDX EXPLAINED

118 Pages

**Order code BP743** £8.99

## THE BASIC SOLDERING GUIDE

**LEARN TO SOLDER SUCCESSFULLY!**

**ALAN WINSTANLEY**

The No.1 resource for learning all the basic aspects of electronics soldering by hand.

With more than 80 high quality colour photographs, this book explains the correct choice of soldering irons, solder, fluxes and tools. The techniques of how to solder and desolder electronic components are then explained in a clear, friendly and non-technical fashion so you'll be soldering successfully in next to no time! The book also includes sections on reflow soldering and desoldering techniques, potential hazards, useful resources and a very useful troubleshooting guide.

Also ideal for those approaching electronics from other industries, the *Basic Soldering Guide Handbook* is the best resource of its type, and thanks to its excellent colour photography and crystal clear text, the art of soldering can now be learned by everyone!

86 Pages

**Order code AW1** £9.99



**VISIT OUR WEBSITE FOR MORE BOOKS AND FAST, EASY ONLINE ORDERING: [www.electronpublishing.com](http://www.electronpublishing.com)**



# Practical Electronics PCB SERVICE

PROJECT	CODE	PRICE	PROJECT	CODE	PRICE
<b>SEPTEMBER 2020</b>			<b>OCTOBER 2019</b>		
PE Theremin PSU .....	AO-0920-01	£5.95	Programmable GPS-synced Frequency Reference .....	04107181	£11.50
PE Theremin PSU transformer .....	AO-0920-02	£7.95	Digital Command Control Programmer for Decoders .....	09107181	£8.75
Micromite Explore-28 .....	07108191	£5.95	Opto-isolated Mains Relay (main board) .....	10107181	£11.50
Ultrabrite LED Driver .....	16109191	£5.95	Opto-isolated Mains Relay (2 × terminal extension board)...	10107182	
<b>AUGUST 2020</b>			<b>AUGUST 2019</b>		
Micromite LCD BackPack V3 .....	07106191	£7.95	Brainwave Monitor .....	25108181	£12.90
Steering Wheel Audio Button to Infrared Adaptor .....	05105191	£7.95	Super Digital Sound Effects Module .....	01107181	£5.60
<b>JULY 2020</b>			Watchdog Alarm .....	03107181	£8.00
AM/FM/CW Scanning HF/VHF RF Signal Generator .....	04106191	£11.95	PE Theremin (three boards: pitch, volume, VCA) .....	PETX0819	£19.50
Speech Synthesiser with the Raspberry Pi Zero .....	01106191	£5.95	PE Theremin component pack (see p.56, August 2019) ...	PETY0819	£15.00
PE Mini-organ PCB .....	AO-0720-01	£14.95	<b>JULY 2019</b>		
PE Mini-organ selected parts .....	AO-0720-02	£8.95	Full-wave 10A Universal Motor Speed Controller .....	10102181	£12.90
High-current Solid-state 12V Battery Isolator – control .....	05106191	£6.95	Recurring Event Reminder .....	19107181	£8.00
High-current Solid-state 12V Battery Isolator FET (2oz) ...	05106192	£9.95	Temperature Switch Mk2 .....	05105181	£10.45
<b>JUNE 2020</b>			<b>JUNE 2019</b>		
Arduino breakout board – 3.5-inch LCD Display .....	24111181	£6.95	Arduino-based LC Meter .....	04106181	£8.00
Six-input Audio Selector main board .....	01110191	10.95	USB Flexitimer .....	19106181	£10.45
Six-input Audio Selector switch panel board .....	01110192		<b>MAY 2019</b>		
<b>MAY 2020</b>			2x 12V Battery Balancer .....	14106181	£5.60
Ultra-low-distortion Preamplifier Input Selector .....	01111112	11.25	Deluxe Frequency Switch .....	05104181	£10.45
Ultra-low-distortion Preamplifier pushbutton Input Selector .....	01111113		USB Port Protector .....	07105181	£5.60
Universal Regulator .....	18103111	7.95	<b>APRIL 2019</b>		
433MHz Wireless Data Repeater .....	15004191	8.50	Heater Controller .....	10104181	£14.00
Bridge-mode Adaptor for Amplifier .....	01105191	7.95	<b>MARCH 2019</b>		
iCEstick VGA Terminal .....	02103191	4.95	10-LED Bargraph Main Board .....	04101181	£11.25
Analogue noise with tilt control .....	AO-0520-01	7.95	+Processing Board .....	04101182	£8.60
Audio Spectrum Analyser .....	PM-0520-01	8.95	<b>FEBRUARY 2019</b>		
<b>APRIL 2020</b>			1.5kW Induction Motor Speed Controller .....	10105122	£35.00
Flip-dot Display black coil board .....	19111181		<b>NOVEMBER 2018</b>		
Flip-dot Display black pixels .....	19111182	£14.95	Super-7 AM Radio Receiver .....	06111171	£27.50
Flip-dot Display black frame .....	19111183		<b>OCTOBER 2018</b>		
Flip-dot Display green driver board .....	19111184		6GHz+ Touchscreen Frequency Counter .....	04110171	£12.88
<b>MARCH 2020</b>			Two 230VAC MainsTimers .....	10108161	£12.88
Diode Curve Plotter .....	04112181	£10.95		10108162	
Steam Train Whistle / Diesel Horn Sound Generator .....	09106181	£8.50	<b>SEPTEMBER 2018</b>		
Universal Passive Crossover (one off) .....	UPC0320	£12.50	3-Way Active Crossover .....	01108171	£22.60
Crossover component set for Wavecor speaker (one off) .....	WAVXO (see website)		Ultra-low-voltage Mini LED Flasher .....	16110161	£5.60
<b>FEBRUARY 2020</b>			<b>AUGUST 2018</b>		
Motion-Sensing 12V Power Switch .....	05102191	£5.95	Universal Temperature Alarm .....	03105161	£7.05
USB Keyboard / Mouse Adaptor .....	24311181	£8.50	Power Supply For Battery-Operated Valve Radios .....	18108171	
DSP Active Crossover (ADC) .....	01106191			18108172	£27.50
DSP Active Crossover (DAC) ×2 .....	01106192			18108173	
DSP Active Crossover (CPU) .....	01106193	£29.95		18108174	
DSP Active Crossover (Power/routing) .....	01106194		<b>JULY 2018</b>		
DSP Active Crossover (Front panel) .....	01106195		Touchscreen Appliance Energy Meter – Part 1 .....	04116061	£17.75
DSP Active Crossover (LCD) .....	01106196		Automotive Sensor Modifier .....	05111161	£12.88
<b>JANUARY 2020</b>			<b>JUNE 2018</b>		
Isolated Serial Link .....	24107181	£8.50	High Performance 10-Octave Stereo Graphic Equaliser ...	01105171	£15.30
<b>DECEMBER 2019</b>			<b>MAY 2018</b>		
Extremely Sensitive Magnetometer .....	04101011	£16.75	High Performance RF Prescaler .....	04112162	£10.45
Four-channel High-current DC Fan and Pump Controller ...	05108181	£8.75	Micromite BackPack V2 .....	07104171	£10.45
Useless Box .....	08111181	£11.50	Microbridge .....	24104171	£5.60
<b>NOVEMBER 2019</b>					
Tinnitus & Insomnia Killer (Jaycar case – see text) .....	01110181	£8.75			
Tinnitus & Insomnia Killer (Altronics case – see text) .....	01110182	£8.75			

PCBs for most recent *PE/EPE* constructional projects are available. From the July 2013 issue onwards, PCBs with eight-digit codes have silk screen overlays and, where applicable, are double-sided, have plated-through holes, and solder mask. They are similar to photos in the project articles. Earlier PCBs are likely to be more basic and may not include silk screen overlay, be single-sided, lack plated-through holes and solder mask.

Always check price and availability in the latest issue or online. A large number of older boards are listed for ordering on our website.

**In most cases we do not supply kits or components for our projects. For older projects it is important to check the availability of all components before purchasing PCBs.**

Back issues of articles are available – see Back Issues page for details.





# ETI BUNDLE (1) Teach-In 3, 4 and 5 – all on CD-ROM – only £18.95

## ELECTRONICS TEACH-IN 3 – CD-ROM

Mike & Richard Tooley


The three sections of the *Teach-In 3* CD-ROM cover a huge range of subjects that will interest everyone involved in electronics – from newcomers to the hobby and students to experienced constructors and professionals.

The first section (80 pages) is dedicated to *Circuit Surgery*, EPE/PE's regular clinic dealing with readers' queries on circuit design problems – from voltage regulation to using SPICE circuit simulation software.

The second section – *Practically Speaking* – covers hands-on aspects of electronics construction. Again, a whole range of subjects, from soldering to avoiding problems with static electricity and identifying components is covered. Finally, our collection of *Ingenuity Unlimited* circuits provides over 40 circuit designs submitted by readers.

The CD-ROM also contains the complete *Electronics Teach-In 1* book, which provides a broad-based introduction to electronics in PDF form, plus interactive quizzes to test your knowledge and TINA circuit simulation software (a limited version – plus a specially written TINA Tutorial).

 The *Teach-In 1* series covers everything from electric current through to microprocessors and microcontrollers, and each part includes demonstration circuits to build on breadboards or to simulate on your PC.



## ELECTRONICS TEACH-IN 5 – CD-ROM

JUMP START

Mike & Richard Tooley

15 design and build circuit projects for newcomers or those following courses in school and colleges.

The projects are: ■ Moisture Detector ■ Quiz Machine ■ Battery Voltage Checker ■ Solar-Powered Charger ■ Versatile Theft Alarm ■ Spooky Circuits ■ Frost Alarm ■ Mini Christmas Lights ■ iPod Speaker ■ Logic Probe ■ DC Motor Controller ■ Egg Timer ■ Signal Injector Probe ■ Simple Radio Receiver ■ Temperature Alarm.

## PLUS

*PIC'n' Mix* – starting out with the popular range of PIC microcontrollers and *Practically Speaking* – tips and techniques for project construction.

The CD-ROM also contains:

- Complete *Teach-In 2* book, a practical introduction to PIC microprocessors
- MikroElektronika, Microchip and L-Tek PoScope software.




## ELECTRONICS TEACH-IN 4 – CD-ROM A BROAD-BASED INTRODUCTION TO ELECTRONICS

Mike & Richard Tooley

The *Teach-In 4* CD-ROM covers three of the most important electronics units that are currently studied in many schools and colleges. These include, Edexcel BTEC level 2 awards and the electronics units of the Diploma in Engineering, Level 2.

The CD-ROM also contains the full *Modern Electronics Manual*, worth £29.95. The *Manual* contains over 800 pages of electronics theory, projects, data, assembly instructions and web links.

 A package of exceptional value that will appeal to anyone interested in learning about electronics – hobbyists, students or professionals.



Three Teach-ins for the great price of  
£18.95

PLUS you also get the contents of the  
free CD-ROM from each issue...

... so that's another TWO Teach-Ins and  
The Full Modern Electronics Manual!

What a Bargain!!

# ETI BUNDLE (2) Teach-In 6, 7 and 8 – all on CD-ROM – only £18.95

## ELECTRONICS TEACH-IN 6 – CD-ROM A COMPREHENSIVE GUIDE TO RASPBERRY PI

Mike & Richard Tooley

*Teach-In 6* contains an exciting series of articles that provides a complete introduction to the Raspberry Pi, the low cost computer that has taken the education and computing world by storm.

This latest book in our *Teach-In* series will appeal to electronics enthusiasts and computer buffs who want to get to grips with the Raspberry Pi.

*Teach-In 6* is for anyone searching for ideas to use their Pi, or who has an idea for a project but doesn't know how to turn it into reality. This book will prove invaluable for anyone fascinated by the revolutionary Pi. It covers:

- Pi programming
- Pi hardware
- Pi communications
- Pi Projects
- Pi Class
- Python Quickstart
- Pi World
- ...and much more!

The *Teach-In 6* CD-ROM also contains all the necessary software for the series, so that readers and circuit designers can get started quickly and easily with the projects and ideas covered.



## ELECTRONICS TEACH-IN 7 – CD-ROM DISCRETE LINEAR CIRCUIT DESIGN

Mike & Richard Tooley

*Teach-In 7* is a complete introduction to the design of analogue electronic circuits. It is ideal for everyone interested in electronics as a hobby and for those studying technology at schools and colleges. The CD-ROM also contains all the circuit software for the course, plus demo CAD software for use with the *Teach-In* series.

- Discrete Linear Circuit Design
- Understand linear circuit design
- Learn with 'TINA' – modern CAD software
- Design simple, but elegant circuits
- Five projects to build:
  - i) Pre-amp
  - ii) Headphone Amp
  - iii) Tone Control
  - iv) VU-meter
  - v) High Performance Audio Power Amp.

## PLUS

*Audio Out* – an analogue expert's take on specialist circuits

*Practically Speaking* – the techniques of project building.



## ELECTRONICS TEACH-IN 8 – CD-ROM INTRODUCING THE ARDUINO

Mike & Richard Tooley

**Hardware:** learn about components and circuits

**Programming:** powerful integrated development system

**Microcontrollers:** understand control operations

**Communications:** connect to PCs and other Arduinos.

*Teach-In 8* is an exciting series designed for electronics enthusiasts who want to get to grips with the inexpensive, popular Arduino microcontroller, as well as coding enthusiasts who want to explore hardware and interfacing. It will provide a one-stop source of ideas and practical information.

The Arduino offers a truly effective platform for developing a huge variety of projects; from operating a set of Christmas tree lights to remotely controlling a robotic vehicle through wireless or the Internet.

*Teach-In 8* is based around a series of practical projects with plenty of information for customisation.

This book also includes *PIC n' Mix*: 'PICs and the PICkit 3 – A Beginners guide' by Mike O'Keefe and *Circuit Surgery* by Ian Bell – 'State Machines part 1 and 2'.

The CD-ROM includes the files for:


- *Teach-In 8*
- Microchip MPLAB IDE XC8 8-bit compiler
- PICkit 3 User Guide
- Lab-Nation Smartscope software.



ORDER YOUR BUNDLE TODAY!

JUST CALL 01202 880299 – OR VISIT [www.electronpublishing.com](http://www.electronpublishing.com)

# CLASSIFIED ADVERTISING

 

# Practical Electronics

If you want your advertisements to be seen by the largest readership at the most economical price then our classified page offers excellent value. The rate for semi-display space is £10 (+VAT) per centimetre high, with a minimum height of 2.5cm. All semi-display adverts have a width of 5.5cm. The prepaid rate for classified adverts is 40p (+VAT) per word (minimum 12 words).

Cheques are made payable to 'Practical Electronics'. **VAT must be added.** Advertisements with remittance should be sent to: Practical Electronics, 113 Lynwood Drive, Wimborne, Dorset, BH21 1UU.

Tel 01202 880299 Email: [stewart.kearn@wimborne.co.uk](mailto:stewart.kearn@wimborne.co.uk)

For rates and further information on display and classified advertising please contact our Advertisement Manager, Stewart Kearn – see below.

**Practical Electronics reaches more UK readers than any other UK monthly hobby electronics magazine. Our sales figures prove it.**

**We have been the leading monthly magazine in this market for the last twenty-seven years.**

## BOWOOD ELECTRONICS LTD

*Suppliers of Electronic Components*

[www.bowood-electronics.co.uk](http://www.bowood-electronics.co.uk)

Unit 10, Boythorpe Business Park, Dock Walk, Chesterfield, Derbyshire S40 2QR. Sales: 01246 200 222

Send large letter stamp for Catalogue

## MISCELLANEOUS

**VALVES AND ALLIED COMPONENTS IN STOCK.** Phone for free list. Valves, books and magazines wanted. Geoff Davies (Radio), tel. 01788 574774.

**PIC DEVELOPMENT KITS, DTMF kits** and modules, CTCSS Encoder and Decoder/Display kits. Visit [www.cstech.co.uk](http://www.cstech.co.uk)

## Electrical Industries Charity (EIC)

We help people working in the electrical, electronics and energy community as well as their family members and retirees.

We use workplace programmes that give the industry access to financial grants and a comprehensive range of free and confidential services.

[www.electricalcharity.org](http://www.electricalcharity.org)



## COAST ELECTRONICS

BREAKOUTS-COMPONENTS-  
CONTRACT DESIGN-3D PRINTER PARTS-  
MUSICAL-MICROCONTROLLERS

[WWW.COASTELECTRONICS.CO.UK](http://WWW.COASTELECTRONICS.CO.UK)

**Andrew Kenny – Qualified Patent Agent**  
EPO UKIPO USPTO

**Circuits Electric Machinery Mechatronics**

Web: [www.akennypatentm.com](http://www.akennypatentm.com)

Email: [Enquiries@akennypatentm.com](mailto:Enquiries@akennypatentm.com)

Tel: 0789 606 9725

# ADVERTISING INDEX

CRICKLEWOOD ELECTRONICS .....	55
ESR ELECTRONIC COMPONENTS.....	31
HAMMOND ELECTRONICS Ltd .....	8
JPG ELECTRONICS .....	72
MICROCHIP .....	Cover (ii)
PEAK ELECTRONIC DESIGN.....	Cover (iv)
POLABS D.O.O.....	52
SILICON CHIP .....	5
STEWART OF READING.....	9
TAG-CONNECT .....	31

## Advertisement offices

Electron Publishing Ltd  
113 Lynwood Drive  
Merley  
Wimborne,  
Dorset BH21 1UU

**Tel** 01202 880299

**Fax** 01202 843233

**Email** [pe@electronpublishing.com](mailto:pe@electronpublishing.com)

**Web** [www.electronpublishing.com](http://www.electronpublishing.com)

For editorial contact details see page 7.



# Next Month – in the October issue

## High Power – 45V/8A Variable Linear Supply

This adjustable bench supply can deliver heaps of power – up to 360W in total – making it ideal for the test bench or just general-purpose use. It can operate as a voltage or current source at 0–45V and 0–8A. An entirely linear, analogue design, it's fan-cooled with automatic fan-speed control, short-circuit/overload protection and thermal self-protection.

## Arduino-Based Digital Audio Millivoltmeter

If your hobby or business involves audio – at any level – you really must have an audio millivoltmeter in your test gear arsenal. Once you've used one, you'll wonder how you managed without it. It's useful for setting up and calibrating audio systems, doing performance measurements and troubleshooting audio equipment, and much more.

## Precision Audio Signal Amplifier

You can never have too much test equipment. Even if it is pretty specialised; even if you only need it once every blue moon, there will come a time when you do need it. This one fits the bill perfectly: you're not going to need it every day, but when you do, you'll thank your good sense that you do have one on hand!

## Practically Speaking

Next month, Mike Hibbett looks at laser cutters – what are they, how do you use them and where do they fit in project-based electronics.

## PLUS!

All your favourite regular columns from *Audio Out*, *Cool Beans* and *Circuit Surgery*, to *Electronic Building Blocks*, *PIC n' Mix* and *Net Work*.



**On sale 3 September 2020**

Content may be subject to change

## WELCOME TO JPG ELECTRONICS

**Selling Electronics in Chesterfield for 29 Years**

**Open Monday to Friday 9am to 5:30pm  
And Saturday 9:30am to 5pm**

- Aerials, Satellite Dishes & LCD Brackets
- Audio Adaptors, Connectors & Leads
- BT, Broadband, Network & USB Leads
- Computer Memory, Hard Drives & Parts
- DJ Equipment, Lighting & Supplies
- Extensive Electronic Components
  - ICs, Project Boxes, Relays & Resistors
- Raspberry Pi & Arduino Products
- Replacement Laptop Power Supplies
- Batteries, Fuses, Glue, Tools & Lots more...



**T: 01246 211 202**

**E: [sales@jpgelectronics.com](mailto:sales@jpgelectronics.com)**

**JPG Electronics, Shaw's Row,  
Old Road, Chesterfield, S40 2RB**

**W: [www.jpgelectronics.com](http://www.jpgelectronics.com)**



**Retail & Trade Welcome • Free Parking • Google St View Tour: S40 2RB**

## NEW subscriptions hotline!

# Practical Electronics

We have changed the way we sell and renew subscriptions. We now use 'Select Publisher Services' for all print subscriptions – to start a new subscription or renew an existing one you have three choices:

1. Call our NEW print subscription hotline: 01202 087631, or email: [pesubs@selectps.com](mailto:pesubs@selectps.com)
2. Visit our shop at: [www.electronpublishing.com](http://www.electronpublishing.com)
3. Send a cheque (payable to: 'Practical Electronics') with your details to:

Practical Electronics Subscriptions, PO Box 6337,  
Bournemouth BH1 9EH, United Kingdom

Remember, we print the date of the last issue of your current subscription in a box on the address sheet that comes with your copy.

Digital subscribers, please call 01202 880299 or visit: [www.electronpublishing.com](http://www.electronpublishing.com)

Published on approximately the first Thursday of each month by Electron Publishing Limited, 1 Buckingham Road, Brighton, East Sussex BN1 3RA. Printed in England by Acorn Web Offset Ltd., Normanton WF6 1TW. Distributed by Seymour, 86 Newman St., London W1T 3EX. Subscriptions UK: £26.99 (6 months); £49.85 (12 months); £94.99 (2 years). EUROPE: airmail service, £30.99 (6 months); £57.99 (12 months); £109.99 (2 years). REST OF THE WORLD: airmail service, £37.99 (6 months); £70.99 (12 months); £135.99 (2 years). Payments payable to 'Practical Electronics', Practical Electronics Subscriptions, PO Box 6337, Bournemouth BH1 9EH, United Kingdom. Email: [pesubs@selectps.com](mailto:pesubs@selectps.com). PRACTICAL ELECTRONICS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# Did you know our online shop now sells the current issue of *PE* for £4.99 inc. p&p?



You read that right! We now sell the current issue of your favourite electronics magazine for exactly the same price as in the High Street, but we deliver it straight to your door – and for UK addresses we pay the postage. No need to journey into town to queue outside the newsagent. Just go to our website, set up an account in 30 seconds, order your magazine and we'll do the rest.

## [www.electronpublishing.com](http://www.electronpublishing.com)



## ZEN50 Zener Diode Analyser (inc. LEDs, TVSs etc)

### Popular product!

The **Atlas ZEN** (model ZEN50) is ideal for testing Zeners, VDRs, transient suppressors, LED strings and many other components.

- Measure Zener Voltage (from 0.00 up to 50.00V!)
- Measure Slope Resistance.
- Selectable test current: 2mA, 5mA, 10mA and 15mA.
- Very low duty cycle to minimise temperature rise.
- Continuous measurements.
- Single AAA battery (included) with very long battery life.
- Gold plated croc clips included.
- Can measure forward voltage of LEDs and LED strings too.



~~£46.50~~ **£39.53**  
~~£36.75+VAT~~ with discount!

## LCR45 LCR and Impedance Meter with Auto and Manual modes

### Advanced firmware!

The powerful LCR45 meter that not only identifies and measures your passive components (Inductors, Capacitors and Resistors) but also measures complex impedance, magnitude of impedance with phase and admittance too! Auto and Manual test modes allow you to specify the test frequency and component type.

- Continuous fluid measurements.
- Improved measurement resolution: (<0.2μH, <0.2pF).
- Test frequencies: DC, 1kHz, 15kHz, 200kHz.
- Measure the true impedance of speakers and more.
- Great for hobbyists and professionals.



~~£91.50~~ **£77.78**  
~~£76.25+VAT~~ with discount!

## DCA55 Semiconductor Analyser - Identify your semi's

### Now with backlit display and AAA battery!

Connect any way round to identify the type of component and the pinout! Also measures many parameters including transistor gain, base-emitter voltages, MOSFET thresholds, LED voltages etc. Complete with a comprehensive illustrated user guide. Includes an Alkaline battery so you're ready to go straight away.

- Transistors (including NPN/PNP, darlington, Si & Ge).
- Measure hFE, V<sub>BE</sub> and leakage.
- Diodes and LEDs. Measure V<sub>F</sub>.
- MOSFETs. Measure V<sub>GS(th)</sub>.
- Gold plated hook probes.
- Long battery life.
- Free technical support for life.
- Comprehensive instruction book.
- 2 year warranty.



~~£52.50~~ **£44.63**  
~~£43.75+VAT~~ with discount!

## ESR70 Equivalent Series Resistance and Capacitance Meter

### Now with backlit display and AAA battery!

The new improved ESR70 is great for identifying capacitors (especially electrolytics) that are suffering from high ESR. ESR is a great indicator of capacitor condition, especially in applications demanding high ripple currents such as reservoir capacitors, SMPSUs, motor capacitors etc. Includes Alkaline AAA battery and a very comprehensive user guide. The ESR70 will even perform a controlled discharge of your caps!



~~£84.00~~ **£71.40**  
~~£70.00+VAT~~ with discount!

It's only possible to show summary specifications here. Please ask if you'd like detailed data. Further information is also available on our website. Product price refunded if you're not happy.